

# ASIC-FPGA Chip Design

Electrical Engineering Department

Sharif University of Technology

## Assignment #4, 2018

1- Consider the following code describing a combinational logic:

```
module DUT (A, B, C, S, out);  
  input A, B, C;  
  input [2:0] S;  
  output reg out;  
  always @(*)  
  begin  
    if (S[0])  
      out = A;  
    else if (S[1])  
      out = B;  
    else if (S[2])  
      out = C;  
  end  
endmodule
```

- a. Draw the synthesized circuit out of the above code. What is the possible problem with this design?
- b. Proposed two solutions to resolve this problem along with their synthesized circuits.
- c. Implement the modified design in part (b) using tri-state buffers without using multiplexers. Show your architecture and RTL code.

- 2- I: In the following partial code, *count* becomes 1 at time 10. Write values of *a* and *b* between time 0 and 40. Assume *a*=0 and *b*=0 as their initial value.

```

always begin
wait (count)
#10 a = a + 1;
end

always begin
@ (count)
#10 b = b + 1;
end

```


| Time | Count | a | b |
|------|-------|---|---|
| 00   | 0     |   |   |
| 10   | 1     |   |   |
| 20   | 1     |   |   |
| 30   | 1     |   |   |
| 40   | 1     |   |   |

- II: Rewrite the following code fragment using blocking statements but without using fork:

```

fork begin
#5 a = b;
#12 c = d;
end

```

 

- 3- Consider the following variables in a system:

- I. A : a signed number with (16,7)
- II. B : an unsigned number with (12,5)
- III. C : a signed number with (6,1),

where (n,m) represents a 2's complement n-bit number with m bits for the fractional part. Write a Verilog code that implements the following function

$$D = A + B.C,$$

where D is a signed number with the highest possible resolution.

4- Consider the following recursive filter:

$$Y(n) = X(n) + aY(n-1)$$

- a) Write a Verilog code to implement this filter. (A complete module that is synthesizable)
- b) Show its corresponding architecture.
- c) What is the critical path of the above architecture?
- d) Come up with an architecture that implements the above filter with twice as much throughput.
- e) Can we decrease the critical path with the simple pipelining technique? Why?
- f) The pipelining technique can be applied to the above architecture with a minor modification to the above architecture. Show how to do it on the architecture to reduce the critical path and show the final pipelined design. (Hint: write the above equation for a few consecutive iterations).

5- Design an architecture that sorts four 10-bit inputs. For each of the following flavors find

- I. The architecture
  - II. Critical path of the design
  - III. Number of clock cycles it takes to perform sorting
  - IV. Throughput of the design
  - V. Number of comparisons
- a. A zero-latency architecture
  - b. A high-throughput architecture that outputs a sorted list every clock cycle
  - c. Write the RTL code of the design in part b