
ASIC/FPGA Chip Design

Power Dissipation

Mahdi Shabany

Department of Electrical Engineering
Sharif University of technology



Outline

- Introduction
- Dynamic Power Dissipation
- Static Power Dissipation



Outline

- Introduction
- Dynamic Power Dissipation
- Static Power Dissipation




Why Power Matters?

- Packaging costs
- Power supply rail design
- Chip and system cooling costs
- Noise immunity and system reliability
- Battery life (in portable systems)
- Environmental concerns



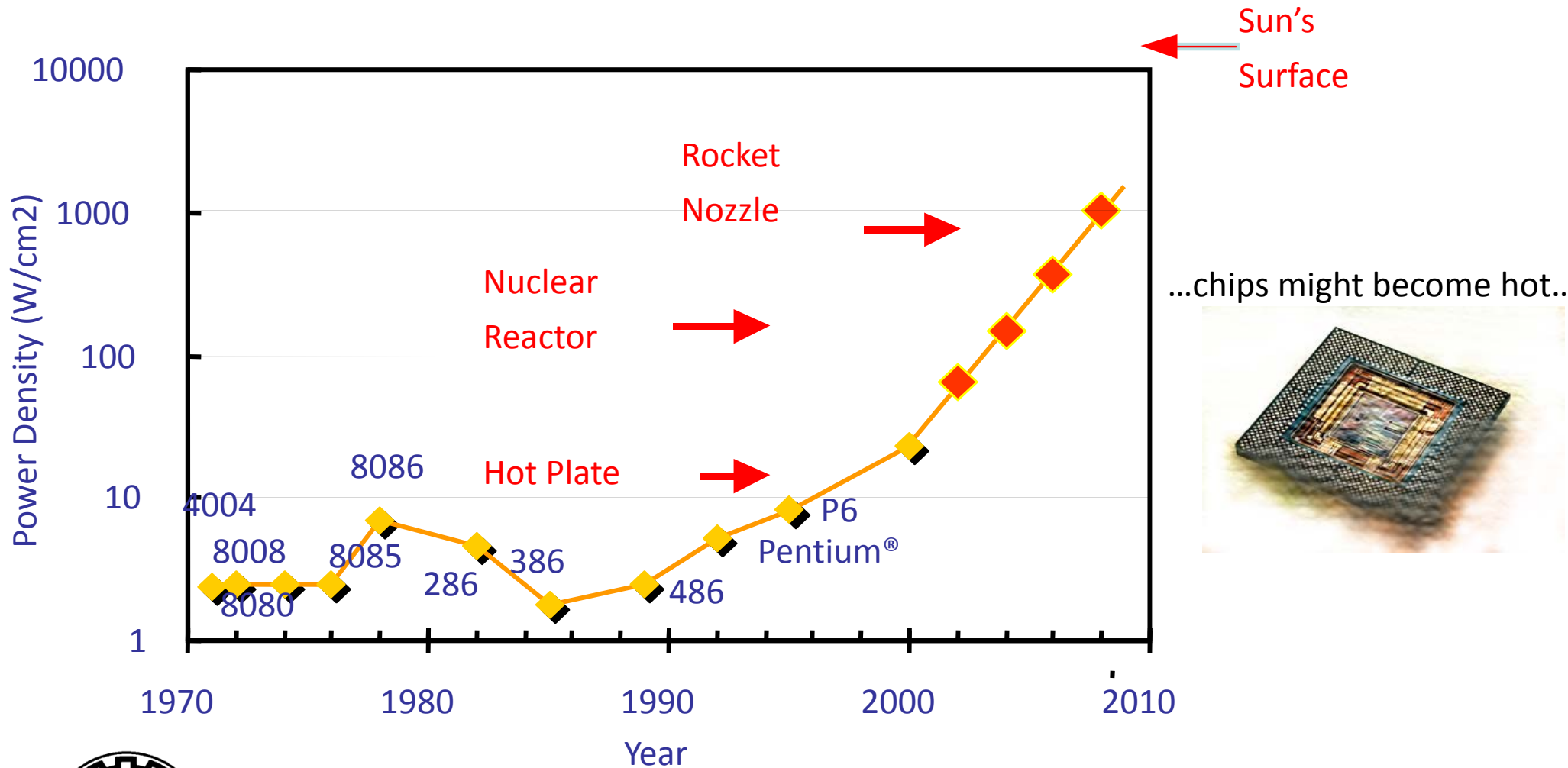
Why worry about power? Chip Power Density



Why worry about power? Standby Power

Year	2002	2005	2008	2011	2014
Power supply V_{dd} (V)	1.5	1.2	0.9	0.7	0.6
Threshold V_T (V)	0.4	0.4	0.35	0.3	0.25

 - Drain leakage will increase as V_T decreases to maintain noise margins and meet frequency demands, leading to excessive battery draining standby power consumption.





Power and Energy Figures of Merit

- ❑ Power consumption in Watts
 - Determines battery life in hours
- ❑ Peak power
 - Determines power ground wiring designs
 - Sets packaging limits
 - Impacts signal noise margin and reliability analysis
- ❑ Energy efficiency in Joules
 - Rate at which power is consumed over time
- ❑ Energy = power * delay
 - Joules = Watts * seconds
 - Lower energy number means less power to perform a computation at the same frequency

**Power is the rate at which energy is delivered or exchanged;
Power dissipation is the rate at which energy is taken from the
source and converted into heat**



Power vs. Energy

  

Power and Energy

Power is drawn from a voltage source attached to the V_{DD} pin(s) of a chip.

Instantaneous Power:

$$P(t) = I(t)V(t)$$

Energy:

$$E = \int_0^T P(t)dt$$

Average Power:

$$P_{\text{avg}} = \frac{E}{T} = \frac{1}{T} \int_0^T P(t)dt$$



Power in Circuit Elements


$$P_{VDD}(t) = I_{DD}(t)V_{DD}$$



$$P_R(t) = \frac{V_R^2(t)}{R} = I_R^2(t)R$$


 
$$\begin{aligned} E_C &= \int_0^{\infty} I(t)V(t)dt = \int_0^{\infty} C \frac{dV}{dt} V(t)dt \\ &= C \int_0^{V_C} V(t)dV = \frac{1}{2} CV_C^2 \end{aligned}$$



Power Dissipation

- ❑ **Power:** Due to the current flowing from supply to ground


$$P = I_D V_{DD}$$

- ❑ **Power Dissipation:**

- **Dynamic Power :** Occurs only when the gate switches
 - Charging/discharging of load capacitances
 - Short-circuit power during switching (when both NMOS and PMOS are ON)
- **Static Power:** Due to the presence of a path in the gate b/w the power supply & GND
 - In CMOS, when circuit is quiescent (no switching) one of the transistors is OFF thus ideally no current flows through an OFF transistor so no current b/w VDD and GND thus zero static power



Power Dissipation

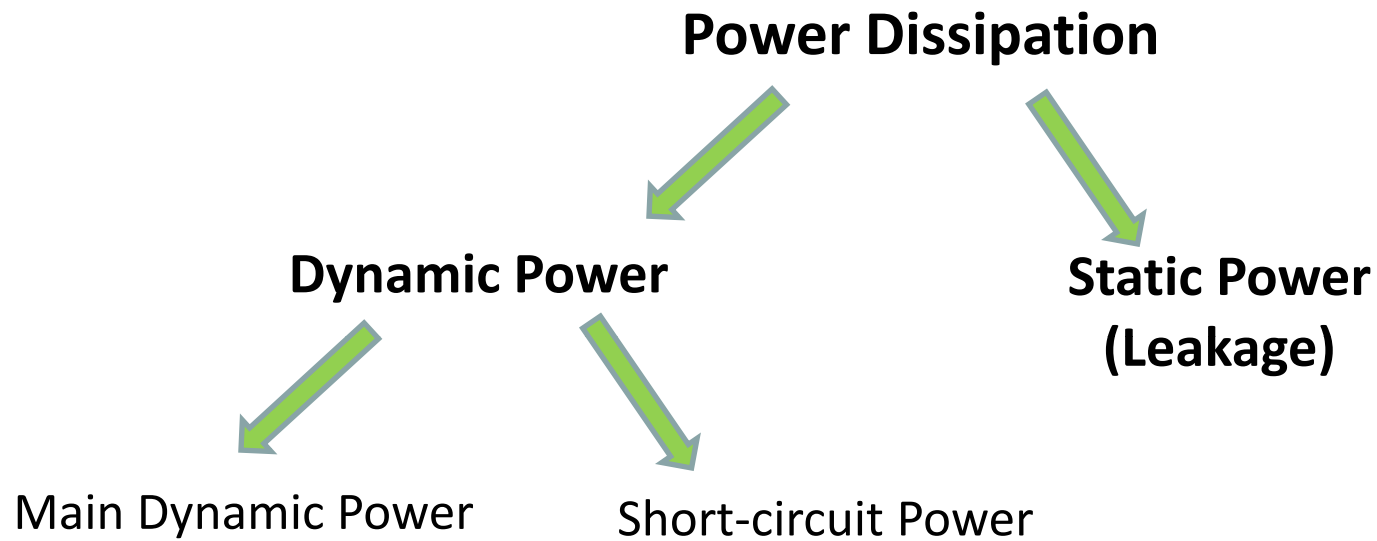

CMOS Total Energy & Power Equations

$$E = C_L V_{DD}^2 \alpha_{0 \rightarrow 1} + \alpha_{sc} V_{DD}^2 C_L + V_{DD} I_{static}$$

$$f_{0 \rightarrow 1} = \alpha_{0 \rightarrow 1} * f_{clk}$$

$$P = C_L V_{DD}^2 f_{0 \rightarrow 1} + \alpha_{sc} V_{DD}^2 C_L f_{clk} + V_{DD} I_{static}$$

Dynamic Power

(~90% today and decreasing relatively)

Short-circuit Power

(~8% today and decreasing absolutely)

Static Power

(~2% today and increasing)




Outline

- Introduction
- **Dynamic Power Dissipation**
- Static Power Dissipation




Power Dissipation

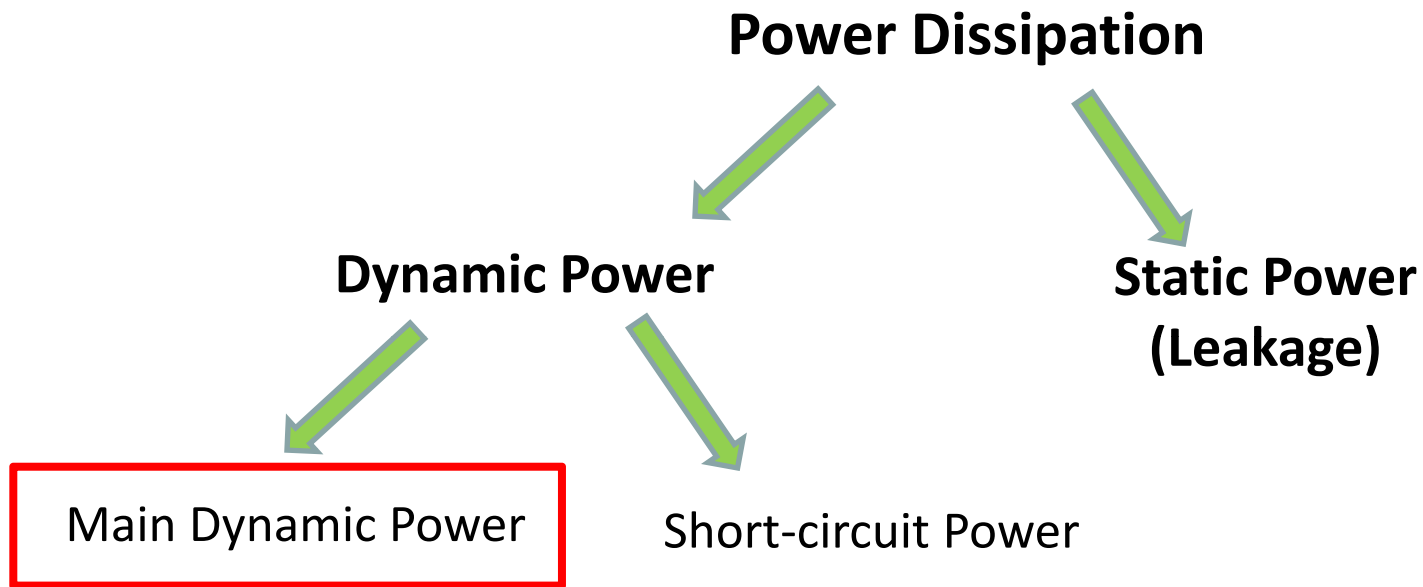

Power Dissipation: Main Dynamic Power

- Due to the charging/discharging the load capacitances
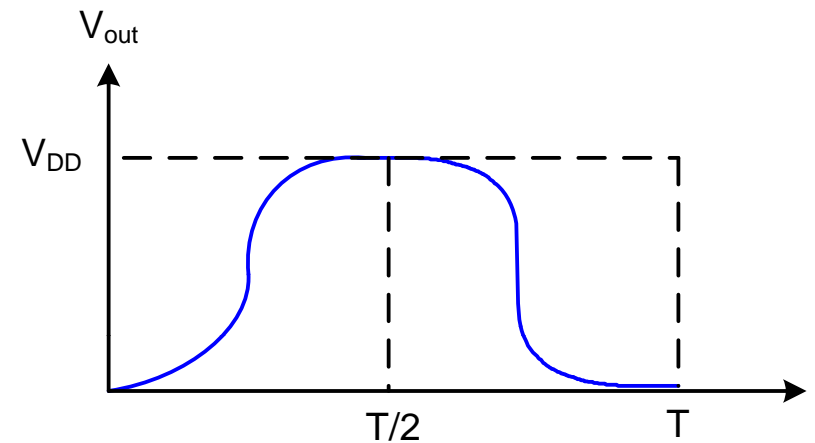
$$P_{avg} = \frac{1}{T} \int_0^T v(t)i(t)dt$$



$$P_{avg} = \frac{1}{T} \left[\int_0^{T/2} (V_{out}) C_L \frac{dV_{out}}{dt} dt + \int_{T/2}^T V_{out} (-C_L \frac{dV_{out}}{dt}) dt \right]$$

$$\Rightarrow P_{avg} = \frac{1}{T} \left[\left(\frac{V_{out}^2}{2} C_L \right)_{0}^{T/2} - \left(\frac{V_{out}^2}{2} C_L \right)_{T/2}^T \right] = \frac{1}{T} V_{DD}^2 C_L = C_L V_{DD}^2 f_{clk}$$



Power Dissipation: Dynamic Power

Average Dynamic Power:

- Linearly dependent to f_{clk} (Clock frequency)
- Independent of the transistor sizing

Considering the utilization factor:

$$P_{\text{avg}} = \alpha C_L V_{\text{DD}}^2 f_{\text{clk}} \quad \alpha : \text{Activity Factor}$$

In general, a chip with higher area burns more power unless its utilization factor is lower

Power Delay Product: (dissipated as heat in transistors)

$$\text{PDP} = C_L V_{\text{DD}}^2$$



Charging a Capacitor

□ When the gate output rises

- Energy stored in capacitor is

$$E_C = \frac{1}{2} C_L V_{DD}^2$$

- But energy drawn from the supply is


$$E_{V_{DD}} = \int_0^{\infty} I(t) V_{DD} dt = \int_0^{\infty} C_L \frac{dV}{dt} V_{DD} dt$$

$$= C_L V_{DD} \int_0^{V_{DD}} dV = C_L V_{DD}^2$$


- Half the energy from V_{DD} is dissipated in the PMOS transistor as heat, other half stored in the capacitor

□ When the gate output falls

 - Energy in capacitor is dumped to GND
- Dissipated as heat in the NMOS transistor



Dynamic Power Consumption

 

$$\text{Energy/transition} = C_L * V_{DD}^2 * \alpha_{0 \rightarrow 1}$$

$$P_{\text{dyn}} = \text{Energy/transition} * f = C_L * V_{DD}^2 * \alpha_{0 \rightarrow 1} * f$$

$$P_{\text{dyn}} = C_{\text{eff}} * V_{DD}^2 * f \quad \text{where } C_{\text{eff}} = \alpha_{0 \rightarrow 1} C_L$$

- Not a function of transistor sizes!
- Data dependent - a function of switching activity!



Lowering Dynamic Power

Capacitance:
Function of fan-out, wire
length, transistor sizes

Supply Voltage:
Has been dropping with
successive generations

$$P_{\text{dyn}} = C_L V_{\text{DD}}^2 \alpha_{0 \rightarrow 1} f$$

Activity factor:
How often, on average, do wires
switch?

Clock frequency:
Increasing...



Lowering Dynamic Power

□ Try to minimize:

➤ Activity factor

➤ Capacitance

➤ Supply voltage

➤ Frequency

$$P_{\text{dyn}} = C_L V_{\text{DD}}^2 \alpha_{0 \rightarrow 1} f$$



Lowering Dynamic Power – Activity Factor

□ Probability that output is “zero” in one cycle and will be “one” in the next cycle

$$\alpha_{0 \rightarrow 1} = P_0 P_1 = \frac{N_0}{2^N} \frac{N_1}{2^N} = \frac{N_0(2^N - N_0)}{2^{2N}}$$

➤ where

N_0 : Number of zero entries in the output column of the function truth table

N_1 : Number of one entries in the output column of the function truth table


❖ **Example:** A 2-input NOR

$$\alpha_{0 \rightarrow 1} = \frac{3(4 - 3)}{2^4} = \frac{3}{16} \Rightarrow P_{\text{avg}} = \frac{3}{16} C_L V_{DD}^2 f_{\text{clk}}$$



 
Example

- ❑ A 4-input AND is built out of two levels of gates
- ❑ Estimate the activity factor at each node if the inputs have $P = 0.5$



Lowering Dynamic Power: Clock Gating

 - ❑ The best way to reduce the activity is to turn off the clock to registers in unused blocks
 - Saves clock activity ($\alpha = 1$)
 - Eliminates all switching activity in the block
 - Requires determining if block will be used



Lowering Dynamic Power: Capacitance

❑ Gate capacitance

- Fewer stages of logic
- Small gate sizes

❑ Wire capacitance

- Good floorplanning to keep communicating blocks close to each other
- Drive long wires with inverters or buffers rather than complex gates




Lowering Dynamic Power: Voltage / Frequency

❑ Run each block at the lowest possible voltage and frequency that meets performance requirements


❑ Voltage Domains

 - Provide separate supplies to different blocks
- Level converters required when crossing from low to high V_{DD} domains



❑ Dynamic Voltage Scaling

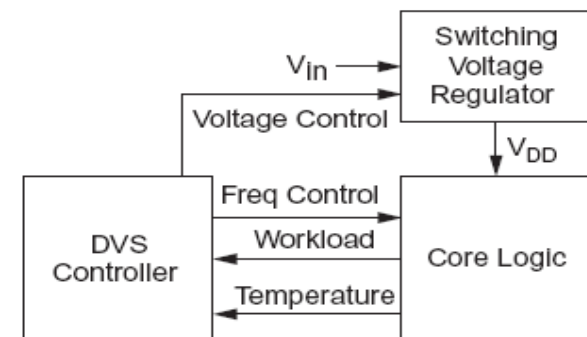- Adjust V_{DD} and f according to workload



Power Dissipation: Dynamic Power

□ In a digital CMOS circuit:

$$t_p \cdot I_{\text{sat}} = C\Delta V$$

$$t_p \cdot K(V_{\text{DD}} - V_t)^2 = C\Delta V \Rightarrow t_p \propto \frac{CV_{\text{DD}}}{(V_{\text{DD}} - V_t)^2} \Rightarrow f_{\text{max}} \propto \frac{(V_{\text{DD}} - V_t)^2}{V_{\text{DD}}} \propto V_{\text{DD}}$$

□ Therefore, it can be shown that

$$P_{\text{avg}} \propto CV_{\text{DD}}^2 f \propto V_{\text{DD}}^3$$

$$\Rightarrow V_{\text{DD}} \uparrow \Rightarrow \text{delay} \downarrow \Rightarrow \text{Power} \uparrow$$

Throughput can be compromised for power



PDP and EDP

□ **Power-delay product (PDP)** = $P_{av} * t_p = C_L V_{DD}^2$


- PDP is the average energy consumed per switching event (Watts * sec = Joule)
- Lower power design could simply be a slower design
- For a given structure the PDP may be made arbitrarily low by reducing the supply voltage that comes at the expense of performance.

□ **Energy-delay product (EDP)** = $PDP * t_p = P_{av} * t_p^2$

- EDP is the average energy consumed multiplied by the computation time required
- Takes into account that one can trade increased delay for lower energy/operation (e.g., via supply voltage scaling that increases delay, but decreases energy consumption)



PDP and EDP

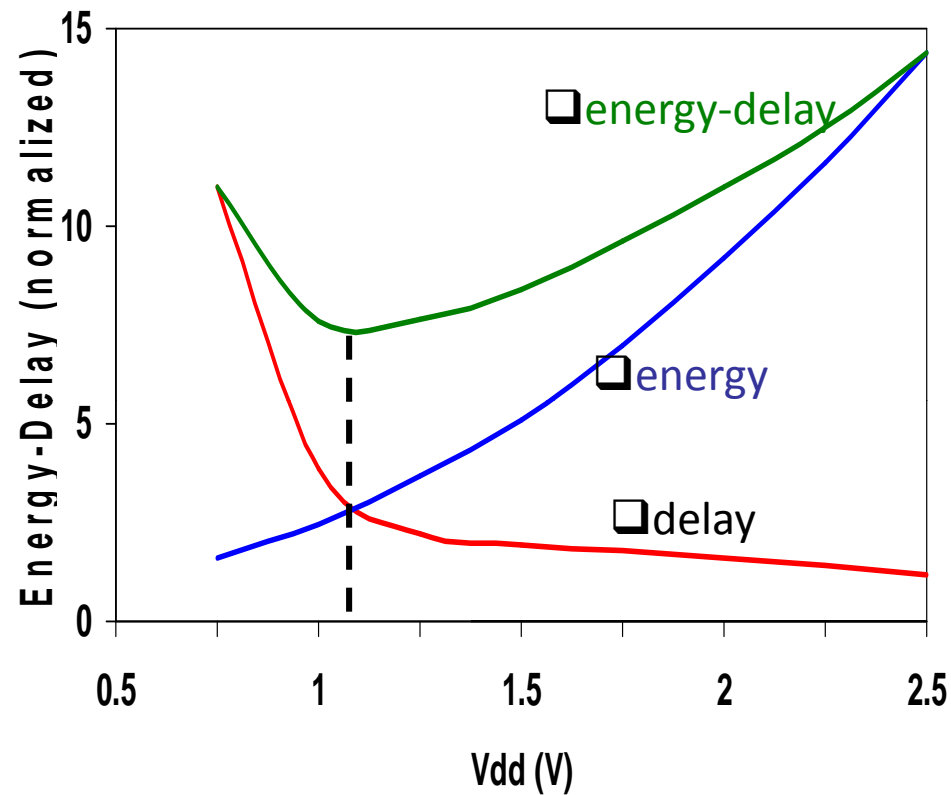


Rule-of-thumb:
$$V_{DD}^{Opt} = \frac{3}{2} \left(V_t + \frac{V_{DS}^{Sat}}{2} \right)$$




Understanding Tradeoffs

□ Which design is the “best” (fastest, coolest, both) ?

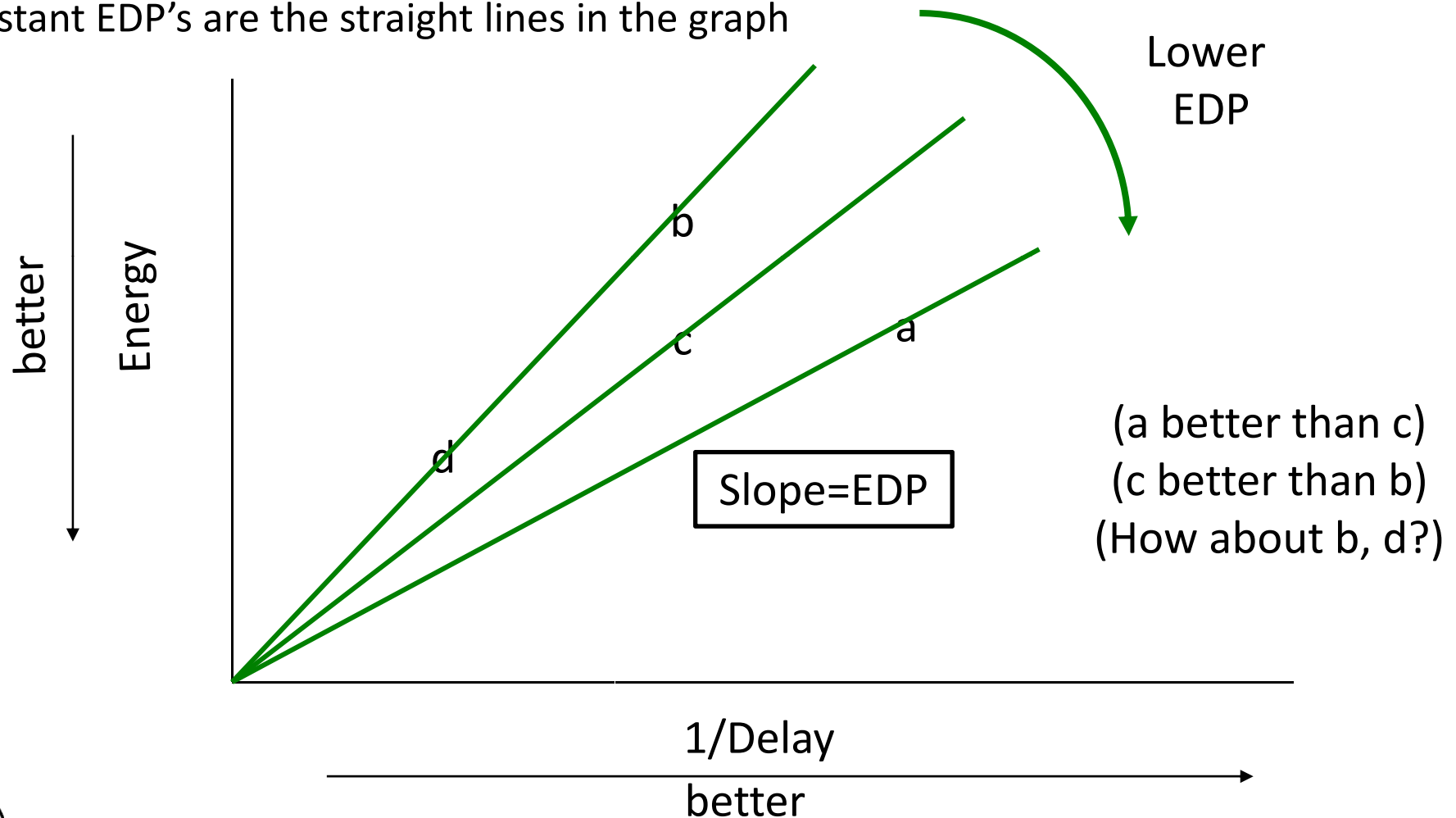➤ Constant EDP's are the straight lines in the graph





Power Dissipation

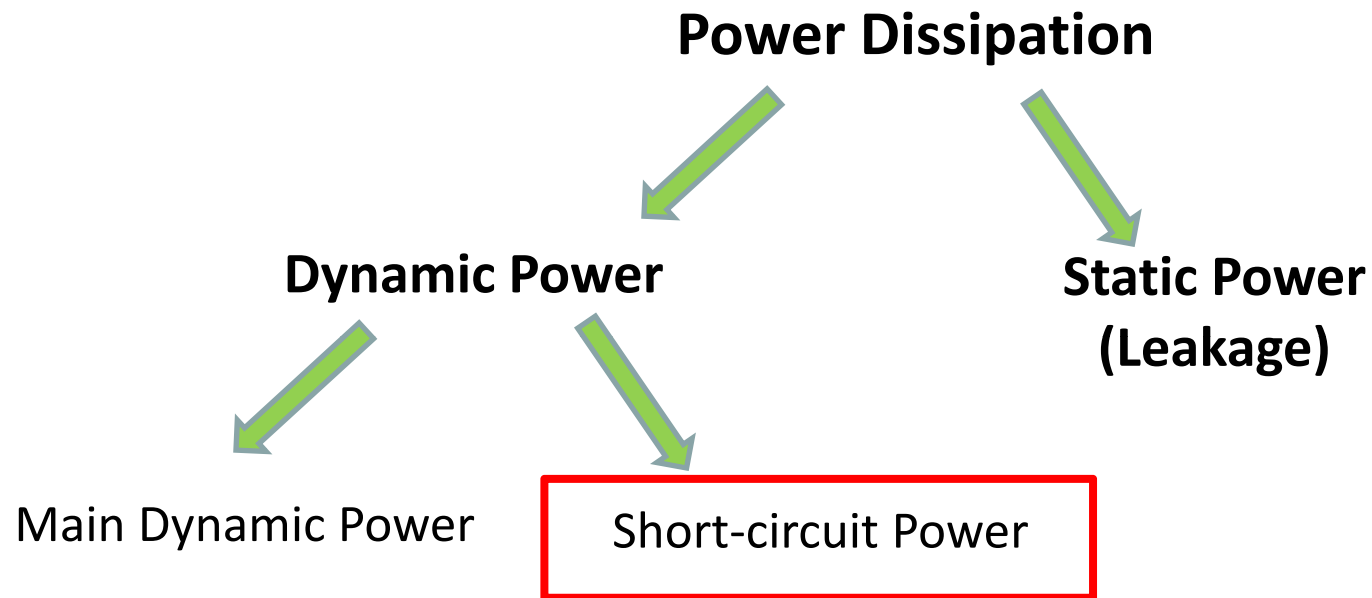

Short Circuit Power Consumption

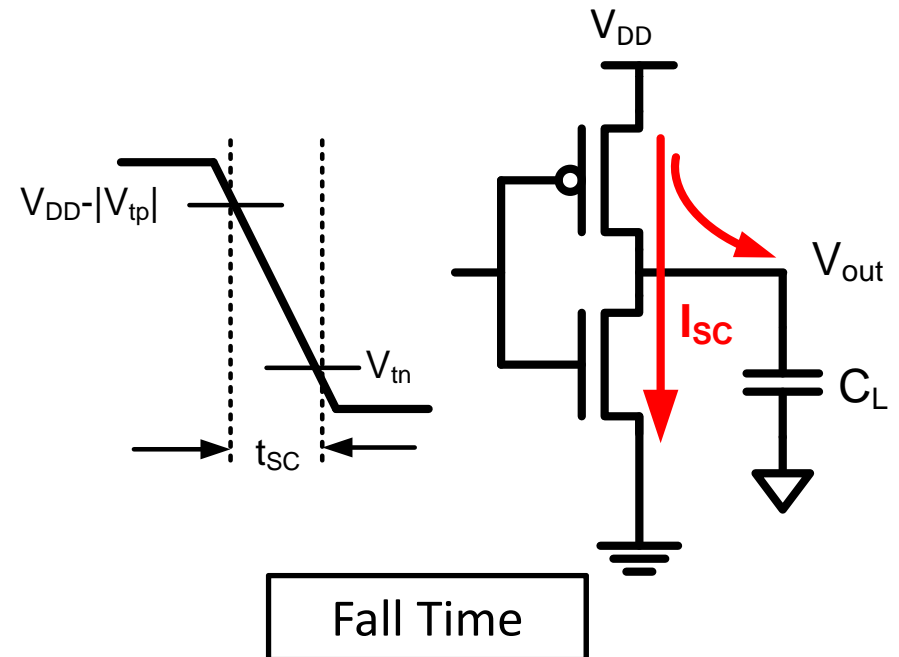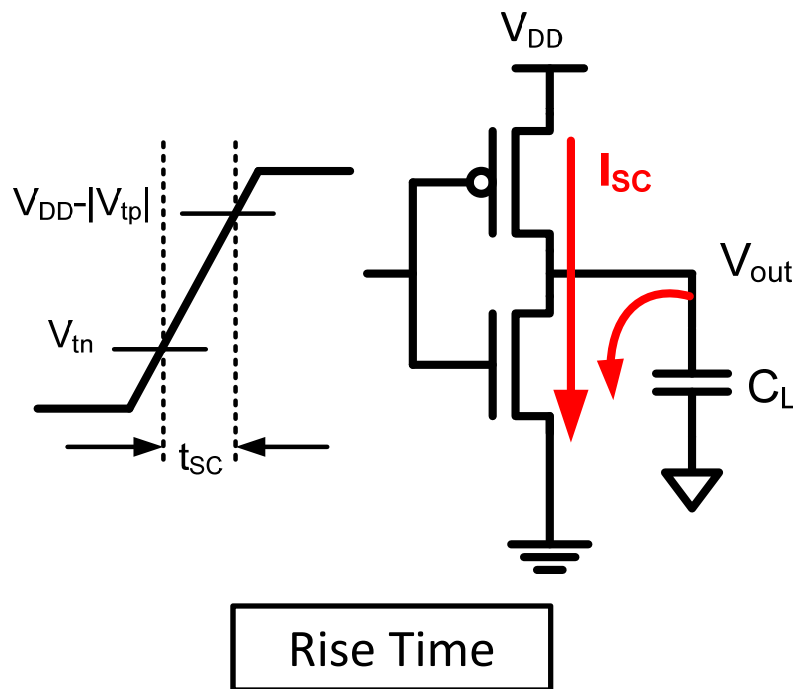□ Finite slope of the input signal causes a direct current path between V_{DD} and GND for a short period of time during switching when both the NMOS and PMOS transistors are conducting.



Short Circuit Currents Determinates

$$t_{sc} = t_{sc}^r + t_{sc}^f$$

$$I = C \frac{dv}{dt} \Rightarrow t_{sc} I_{sc,avg} = C_{sc} V_{DD}$$

$$I_{sc} = \frac{t_{sc} \cdot I_{sc,avg}}{T}$$

Peak and duration of I_{sc} both increase as the input slope decreases

$$P_{sc} = I_{sc} V_{DD} = t_{sc} I_{sc,avg} V_{DD} f$$

$$\Rightarrow P_{sc} = C_{sc} V_{DD}^2 f = \alpha_{sc} C_L V_{DD}^2 f$$

$$\Rightarrow E_{sc} = C_{sc} V_{DD}^2 = \alpha_{sc} C_L V_{DD}^2$$



Short Circuit Currents Determinates

$$P_{sc} = \alpha_{sc} C_L V_{DD}^2 f$$


$$E_{sc} = \alpha_{sc} C_L V_{DD}^2$$

□ I_{peak} determined by

- Saturation current of the P and N transistors, which depend on their sizes, process technology, temperature, etc.
- Strong function of the ratio between input and output slopes
 - Function of C_L



Impact of C_L on I_{sc}

 


Large capacitive load



Output fall time significantly larger than input rise time.

 □ As the source-drain voltage of the PMOS is approximately 0 during transition, the device shuts off without ever delivering any current, so I_{sc} is close to zero.



Small capacitive load




Output fall time substantially smaller than the input rise time.

□ Drain-source voltage of PMOS equals VDD for most of the transition period, giving maximum I_{sc}



I_{peak} as a Function of C_L

 


When load capacitance is small, I_{peak} is large.

Short circuit dissipation is minimized by matching the rise/fall times of the input and output signals - slope engineering.



P_{sc} as a Function of Rise/Fall Times

 

When load capacitance is small ($t_{sin}/t_{sout} > 2$ for $V_{DD} > 2\text{V}$) the power is dominated by P_{sc}

If $V_{DD} < V_{Tn} + |V_{Tp}|$ then P_{sc} is eliminated since both devices are never ON at the same time.

- ❑ For large capacitance values, all the power dissipation is devoted to charging and discharging the load capacitance.
- ❑ When the rise/fall times of inputs and outputs are equalized, most power dissipation is associated with dynamic power and only a minor fraction (<10%) is devoted to P_{sc} .



Dynamic Power Example

- ❑ 1 billion transistor chip
 - 50M logic transistors
 - Average width: $12 L_{\min}$
 - Activity factor = 0.1
 - 950M memory transistors
 - Average width: $4 L_{\min}$
 - Activity factor = 0.02
 - 1.0 V 25 nm process
 - $C = 1 \text{ fF/mm (gate)} + 0.8 \text{ fF/mm (diffusion)}$
- ❑ Estimate dynamic power consumption @ 1 GHz. Neglect wire capacitance and short-circuit current.



Dynamic Power Example

$$C_{\text{logic}} = (50 \times 10^6)(12\lambda)(0.025 \mu\text{m} / \lambda)(1.8 \text{ fF} / \mu\text{m}) = 27 \text{ nF}$$

$$C_{\text{mem}} = (950 \times 10^6)(4\lambda)(0.025 \mu\text{m} / \lambda)(1.8 \text{ fF} / \mu\text{m}) = 171 \text{ nF}$$

$$P_{\text{dynamic}} = [0.1C_{\text{logic}} + 0.02C_{\text{mem}}](1.0)^2(1.0 \text{ GHz}) = 6.1 \text{ W}$$




Outline

- Introduction
- Dynamic Power Dissipation
- Static Power Dissipation



Power Dissipation

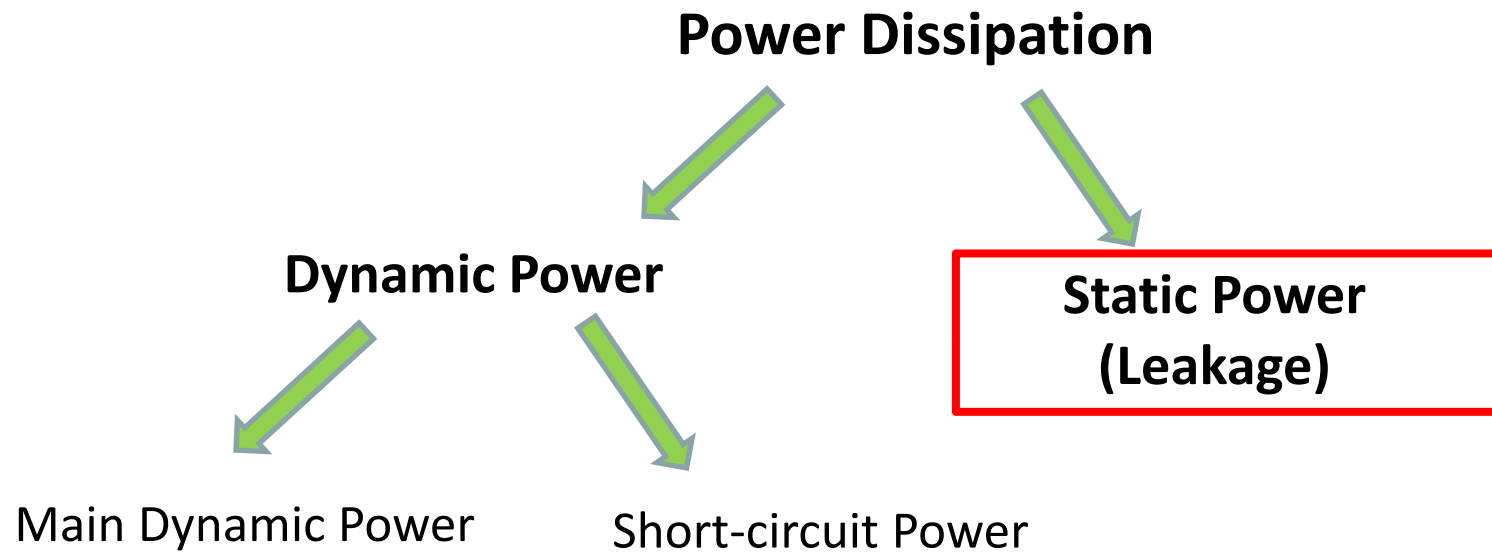

Power Dissipation: Static Power

- ❑ Non-ideal Effects: small leakage current flows through the OFF transistor (I_{static})

$$P_{\text{static}} = \frac{1}{T} \int_0^T i_{\text{static}} V_{\text{DD}} dt = I_{\text{static}} V_{\text{DD}}$$

- ❑ Sources of Leakage:


- **Sub-threshold Conduction:** Exponentially increases as V_T scales down
- **Tunneling through the gate oxide:** Exponentially increases as oxide thickness decreases
 - (Important for 130nm and smaller technologies)
- **Leakage through reverse-biased diodes**

Static power dissipation an issue in deep sub-micron processes




Power Dissipation: Static (Leakage) Power

 - ❑ Sub-threshold current is the dominant factor.
- ❑ All increase exponentially with temperature!



Leakage as a Function of V_T

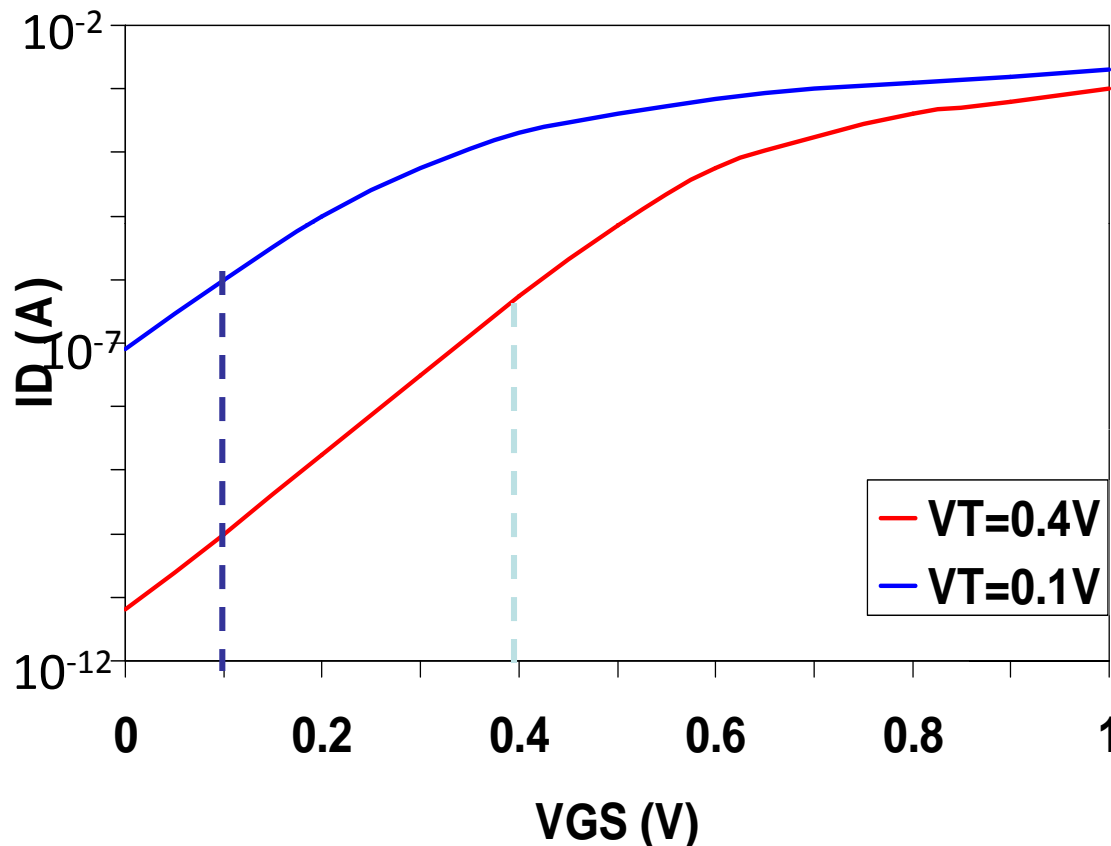- Continued scaling of supply voltage and the subsequent scaling of threshold voltage will make sub-threshold conduction a dominate component of power dissipation.



An 90mV/decade V_T roll-off - so each 255mV increase in V_T gives 3 orders of magnitude reduction in leakage (but adversely affects performance)




TSMC Processes Leakage and V_T

	CL018 G	CL018 LP	CL018 ULP	CL018 HS	CL015 HS	CL013 HS
V_{dd}	1.8 V	1.8 V	1.8 V	2 V	1.5 V	1.2 V
T_{ox} (effective)	42 Å	42 Å	42 Å	42 Å	29 Å	24 Å
L_{gate}	0.16 μm	0.16 μm	0.18 μm	0.13 μm	0.11 μm	0.08 μm
I_{DSat} (n/p) ($\mu A/\mu m$)	600/260	500/180	320/130	780/360	860/370	920/400
I_{off} (leakage) ($\rho A/\mu m$)	20	1.60	0.15	300	1,800	13,000
V_{Tn}	0.42 V	0.63 V	0.73 V	0.40 V	0.29 V	0.25 V
FET Perf. (GHz)	30	22	14	43	52	80

(G: generic, LP: low power, ULP: ultra low power, HS: high speed)



Exponential Increase in Leakage Currents

 

Leakage Control

- ❑ Leakage and delay trade off
 - Aim for low leakage in sleep and low delay in active mode
- ❑ To reduce leakage:
 - Increase V_t : *multiple V_t*
 - Use low V_t only in critical circuits
 - Increase V_s : *stack effect*
 - *Input vector control* in sleep
 - Decrease V_b
 - *Reverse body bias* in sleep
 - Or forward body bias in active mode



Gate Leakage

- ❑ Extremely strong function of t_{ox} and V_{gs}
 - Negligible for older processes
 - Approaches sub-threshold leakage at 65 nm and below in some processes
- ❑ An order of magnitude less for PMOS than NMOS
- ❑ Control leakage in the process using $t_{ox} > 10.5 \text{ \AA}$
 - High-k gate dielectrics help
 - Some processes provide multiple t_{ox}
 - e.g. thicker oxide for 3.3 V I/O transistors
- ❑ Control leakage in circuits by limiting V_{DD}



Static Power Example

- ❑ Revisit power estimation for 1 billion transistor chip
- ❑ Estimate static power consumption
 - Subthreshold leakage
 - Normal V_t : 100 nA/mm
 - High V_t : 10 nA/mm
 - High V_t used in all memories and in 95% of logic gates
 - Gate leakage 5 nA/mm
 - Junction leakage negligible



Solution

$$W_{\text{normal-}V_t} = (50 \times 10^6)(12\lambda)(0.025 \mu\text{m} / \lambda)(0.05) = 0.75 \times 10^6 \mu\text{m}$$

$$W_{\text{high-}V_t} = \left[(50 \times 10^6)(12\lambda)(0.95) + (950 \times 10^6)(4\lambda) \right] (0.025 \mu\text{m} / \lambda) = 109.25 \times 10^6 \mu\text{m}$$

$$I_{\text{sub}} = \left[W_{\text{normal-}V_t} \times 100 \text{ nA}/\mu\text{m} + W_{\text{high-}V_t} \times 10 \text{ nA}/\mu\text{m} \right] / 2 = 584 \text{ mA}$$

$$I_{\text{gate}} = \left[(W_{\text{normal-}V_t} + W_{\text{high-}V_t}) \times 5 \text{ nA}/\mu\text{m} \right] / 2 = 275 \text{ mA}$$

$$P_{\text{static}} = (584 \text{ mA} + 275 \text{ mA})(1.0 \text{ V}) = 859 \text{ mW}$$



Review: Designing Fast CMOS Gates

- ❑ Transistor sizing
 - MOS closest to the output is smallest of series MOS transistors
- ❑ Transistor ordering
 - put latest arriving signal closest to the output
- ❑ Logic structure reordering
 - replace large fan-in gates with smaller fan-in gate network
- ❑ Apply “logical effort”
- ❑ Buffer (inverter) insertion
 - separate large fan-in from large C_L with buffers
 - uses buffers so there are no more than four TGs in series

