

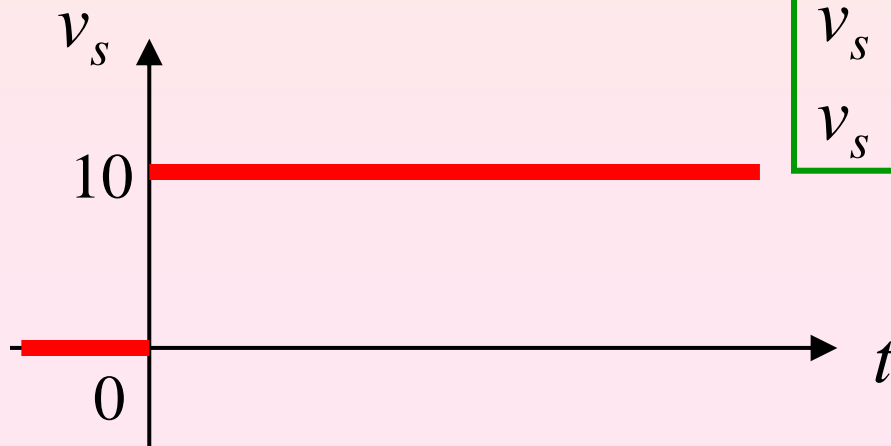
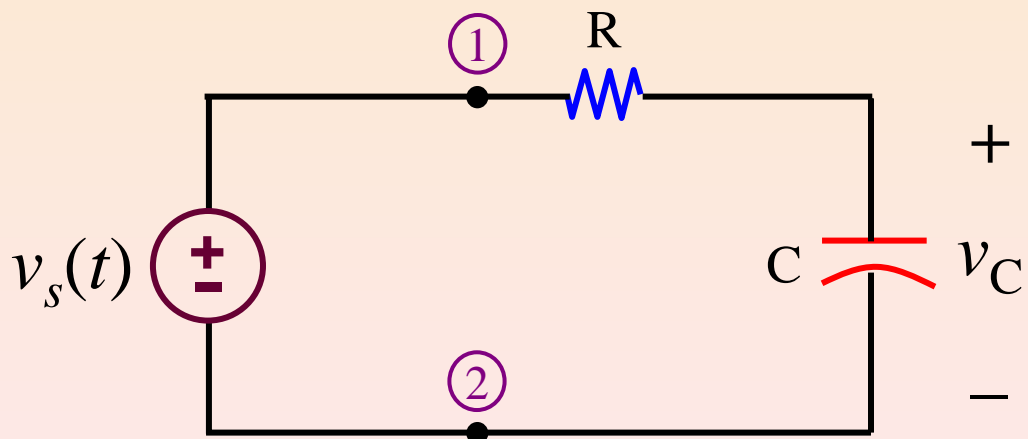


## Two Equivalent Representations

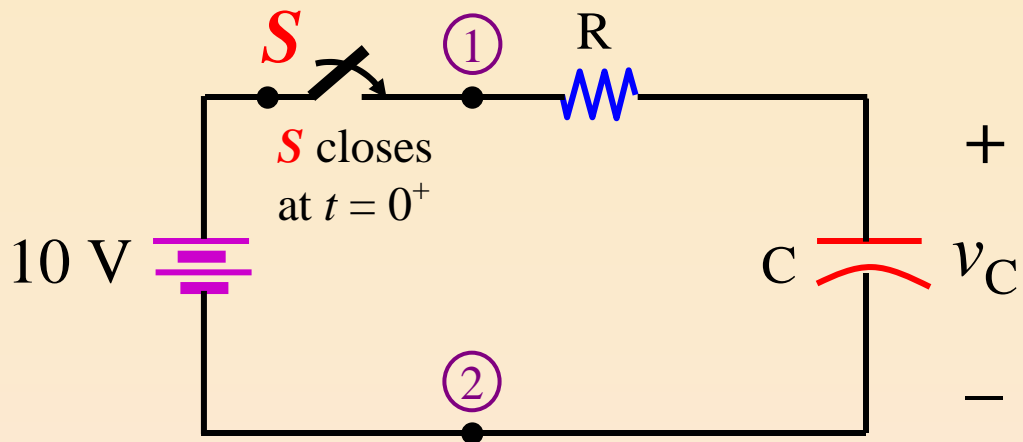

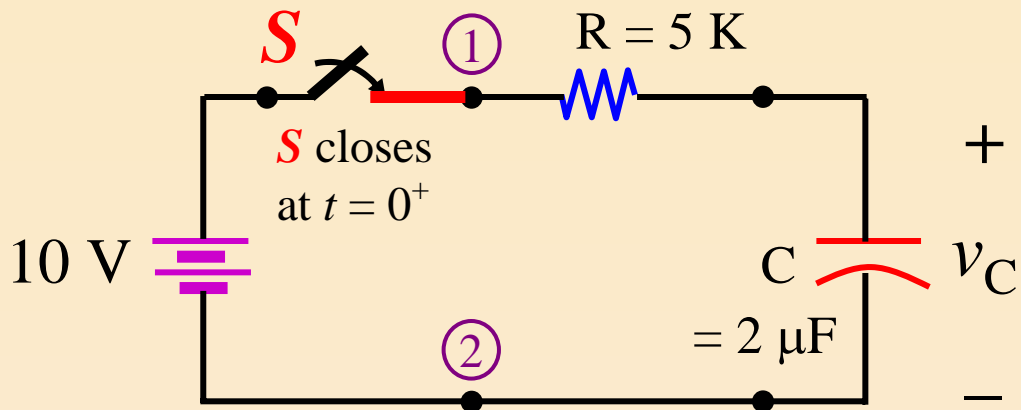
$$\begin{aligned} v_s(0^-) &= 0 \\ v_s(0^+) &= 10 \end{aligned}$$




Step 1

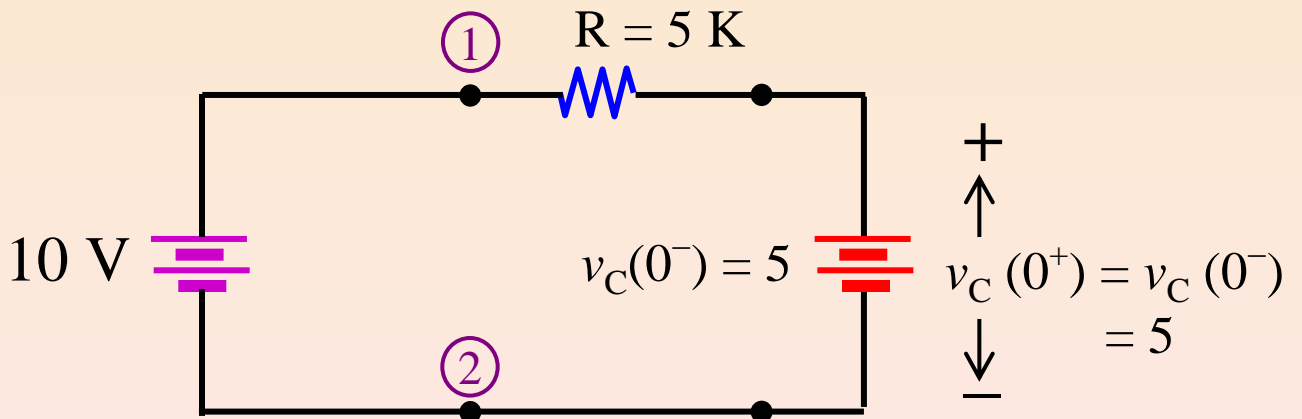Find  $v_C(0^+)$ : Replace  $C$  by battery with voltage =  $v_C(0^-)$ , then calculate  $v_C(0^+)$ .



Step 2

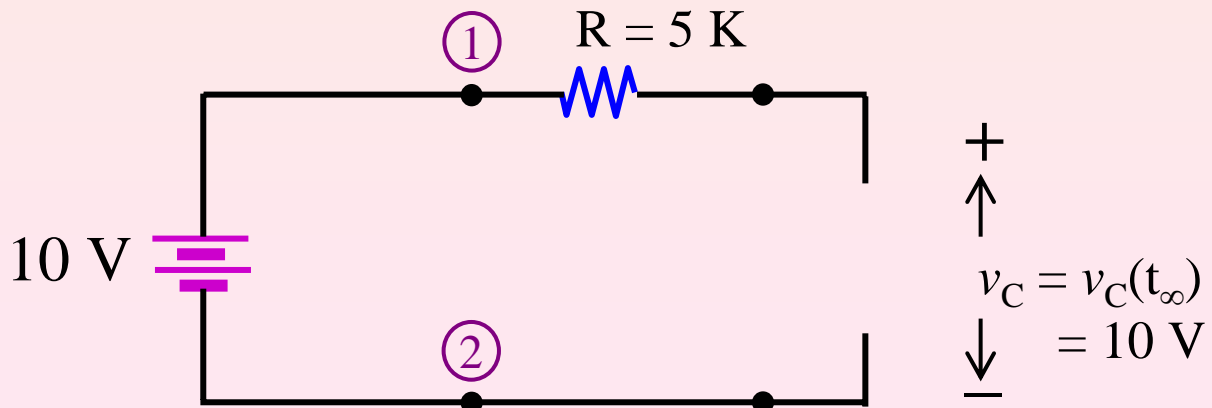Find  $v_C(t_\infty)$ : Replace  $C$  by *open* circuit, then calculate  $v_C = v_C(t_\infty)$ .



Step 3


Calculate the *time constant*

$$\tau = R C$$

## Fundamental Behavior of 1st-order Circuits


The *voltage*  $v_{jk}(t)$  between any pair of nodes  $\textcircled{j}$  and  $\textcircled{k}$ , and the *current*  $i_o(t)$  at any terminal of any *linear resistive circuit* is always an *exponential waveform*, except for the trivial circuit consisting of a *current source* (resp., *voltage source*) connected across a capacitor (resp., inductor), whose solution is a linear “*ramp*” function.

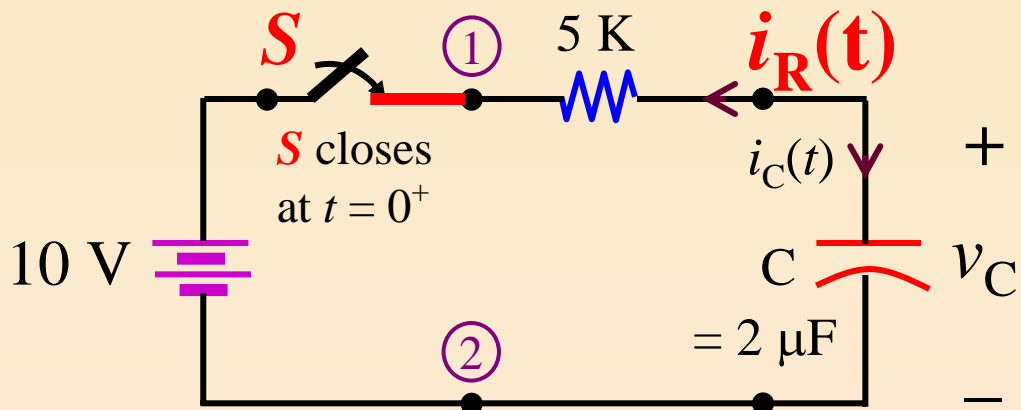Problem : Calculate  $i_R(t)$  under the same setting.



Step 1

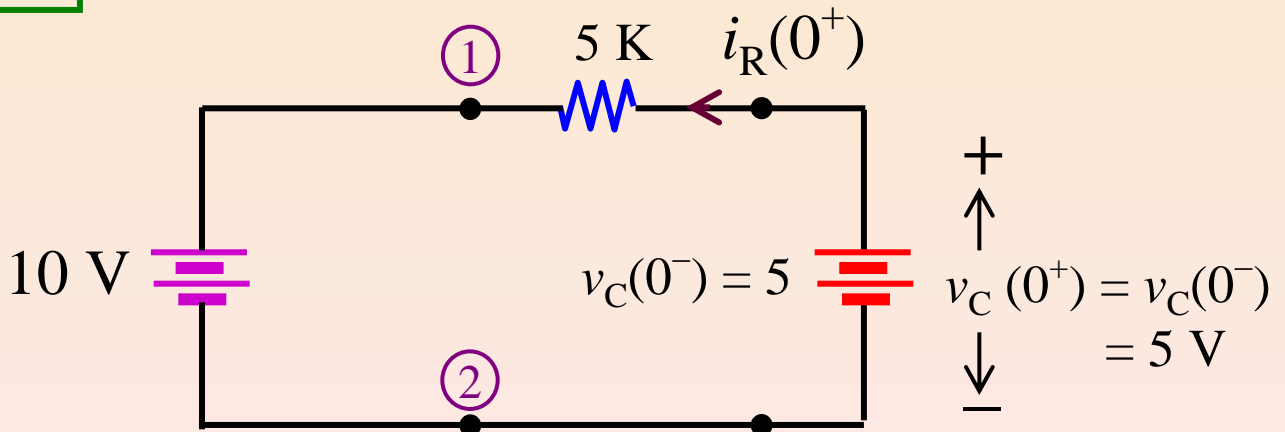Calculate  $i_R(0^+)$  : Replace  $C$  by a 5 V battery :




Calculate :

$$i_R(0^+) = \frac{5 - 10}{5 \text{ K}} = -1 \text{ mA}$$

Step 2

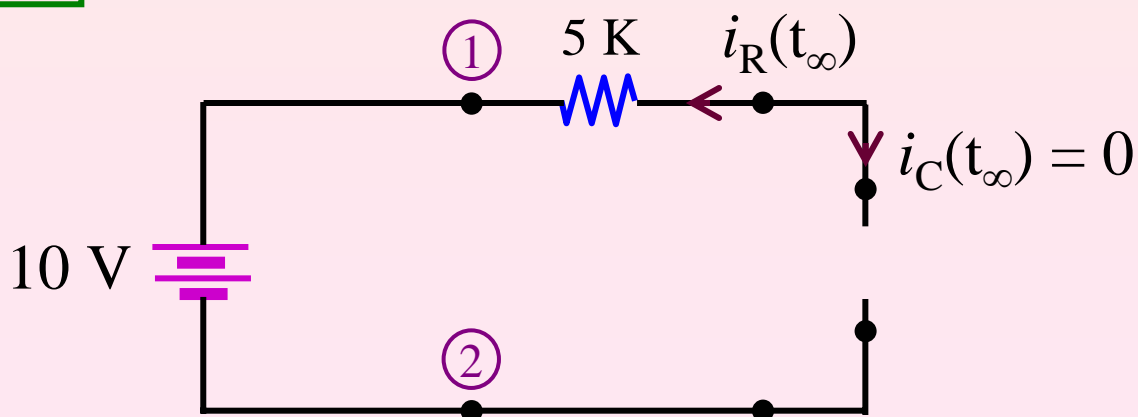Calculate  $i_R(t_\infty)$  : Replace  $C$  by *open* circuit :





Calculate :

$$i_R(t_\infty) = 0$$

**Step 3**

Calculate time constant

$$\tau = R C = (5 \times 10^3) (2 \times 10^{-6}) = 10 \text{ ms}$$

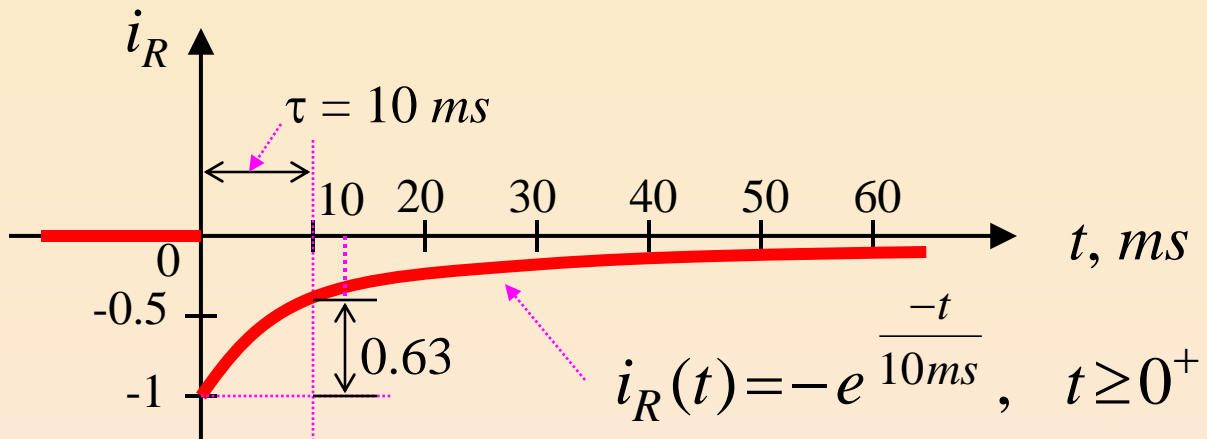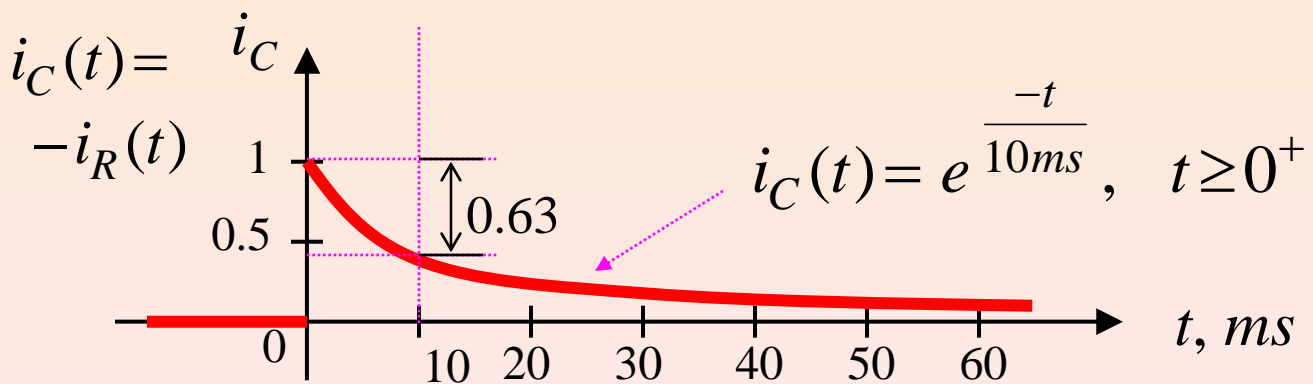
**Verification of solution**

$$\begin{aligned}
 v_C(t) &= v_C(0^-) + \frac{1}{C} \int_{0^+}^t e^{-\frac{t}{10 \times 10^{-3}}} dt \\
 &= 5 + \frac{1}{2 \times 10^{-3}} \int_{0^+}^t e^{-\frac{t}{10 \times 10^{-3}}} dt \\
 &= 5 + \left[ -5 e^{-\frac{t}{10 \times 10^{-3}}} + 5 \right] \\
 &= 10 - 5 e^{-\frac{t}{10 \times 10^{-3}}}, \quad t \geq 0^+
 \end{aligned}$$

**Step 3**

Calculate time constant

$$\tau = R C = (5 \times 10^3) (2 \times 10^{-6}) = 10 \text{ ms}$$

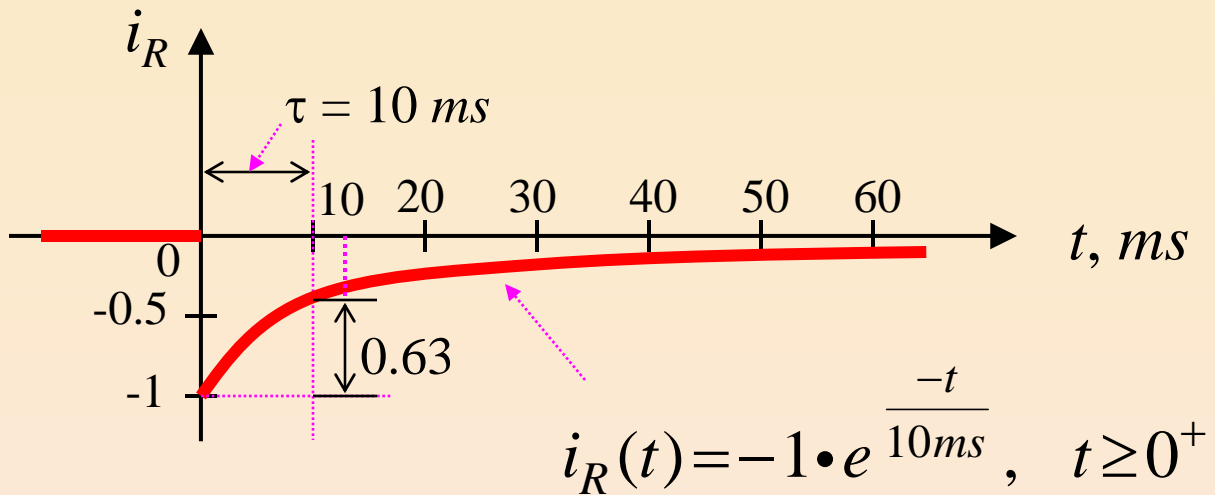**Verification**

Let us calculate :

$$i_C(t) = -i_R(t) = e^{-\frac{t}{10\text{ms}}}$$


$$v_C(t) = v_C(0^-) + \frac{1}{C} \int_{0^+}^t i_C(\tau) d\tau$$

$$= 5 + \frac{1}{2 \times 10^{-3}} \int_{0^+}^t e^{-\frac{\tau}{10 \times 10^{-3}}} d\tau$$

$$= 5 + \left[ -5 e^{-\frac{\tau}{10 \times 10^{-3}}} + 5 \right]$$

$$= 10 - 5 e^{-\frac{t}{\tau}}, t \geq 0^+$$

## Finding Solutions by Inspection

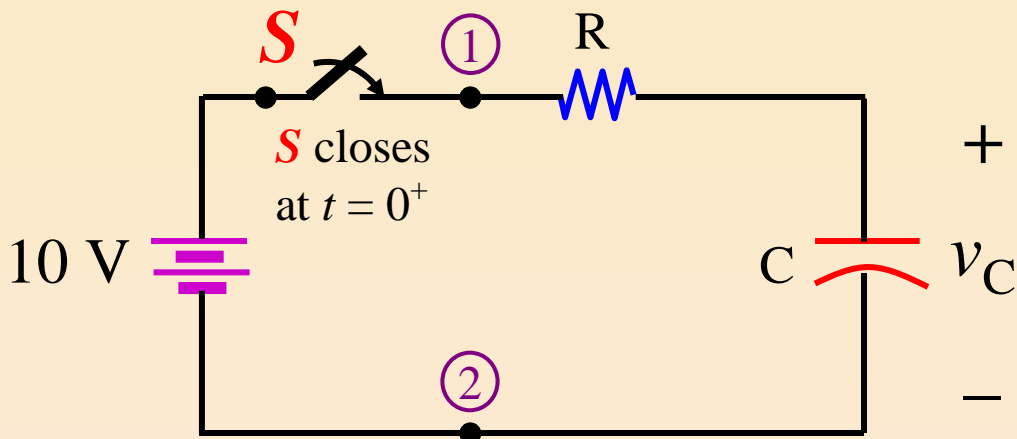


### Problem

Assume  $v_C(0^-) = 5 \text{ V}$ , where  $t = 0^-$  denotes the time just before switch  $S$  made contact with resistor  $R$ .

Sketch  $v_C(t)$  for  $t \geq 0^+$ , where  $t = 0^+$  denotes the instant switch  $S$  made contact with resistor  $R$ .


**Solution**  $v_C(0^+) = v_C(0^-) = 5 \text{ V}$ ,  $v_C(t_\infty) = 10 \text{ V}$
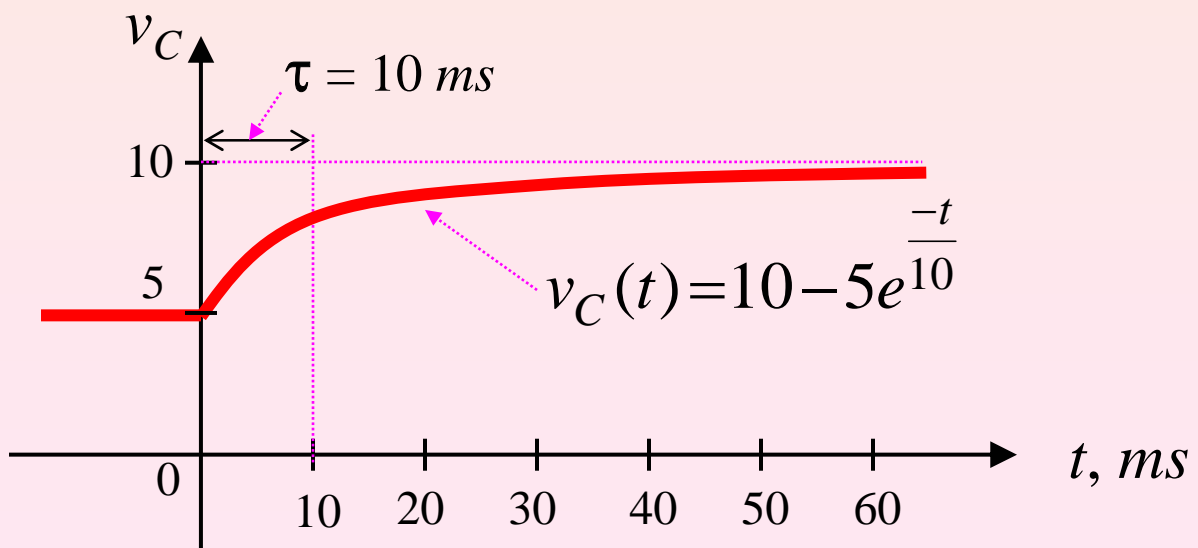
$$\tau = R C = 5(10^3) [2(10^{-6})] = 10 \text{ ms}$$



Calculate:  $v_C(t) = 10 - 5e^{-\frac{t}{10}}$ ,  $t \geq 0^+$

## How to Find $v_C(t_\infty)$ ?

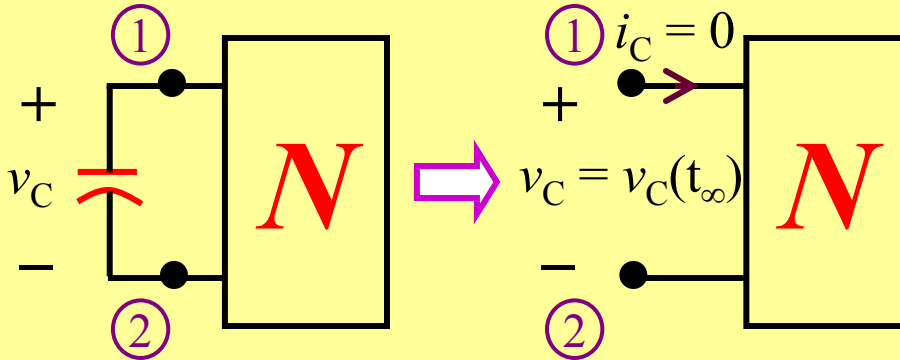

Step 1 :

*Open capacitor*


Step 2 :

Calculate :  $v_C|_{\text{Open capacitor}}$

Then

$$v_C(t_\infty) = v_C |_{\text{Open capacitor}}$$

## How to Find $i_L(t_\infty)$ ?

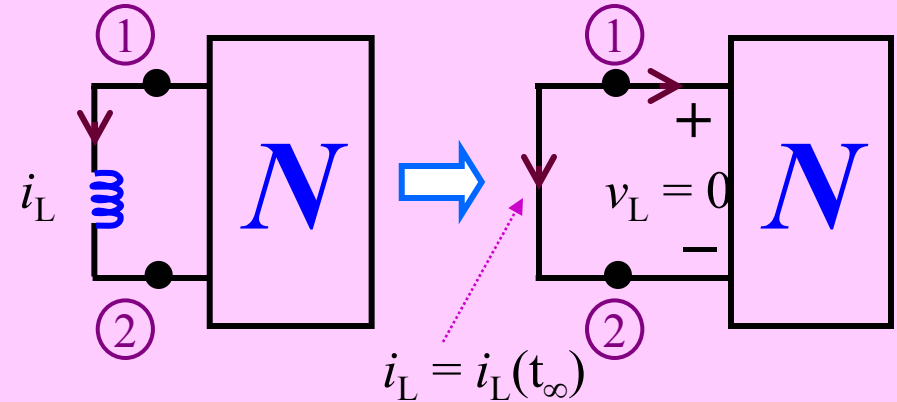

Step 1 :

*Short capacitor*

Step 2 :


Calculate :  $i_L|_{\text{Short inductor}}$

Then

$$i_L(t_\infty) = i_L |_{\text{Short inductor}}$$



How to Find  $v_c(t_o^+)$  ?

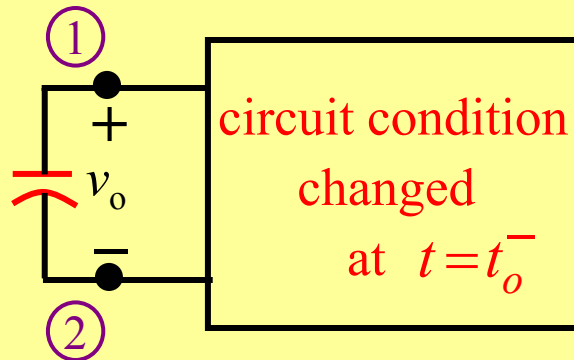


Step 1 :

Calculate :  $v_C(t_o^-)$

Step 2 :

$$v_C(t_o^+) = v_C(t_o^-)$$

How to Find  $i_L(t_o^+)$  ?

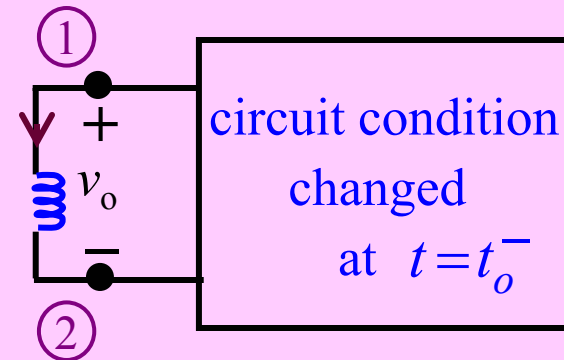


Step 1 :

Calculate :  $i_L(t_o^-)$

Step 2 :

$$i_L(t_o^+) = i_L(t_o^-)$$

How to Find  $\tau = R C$  ?

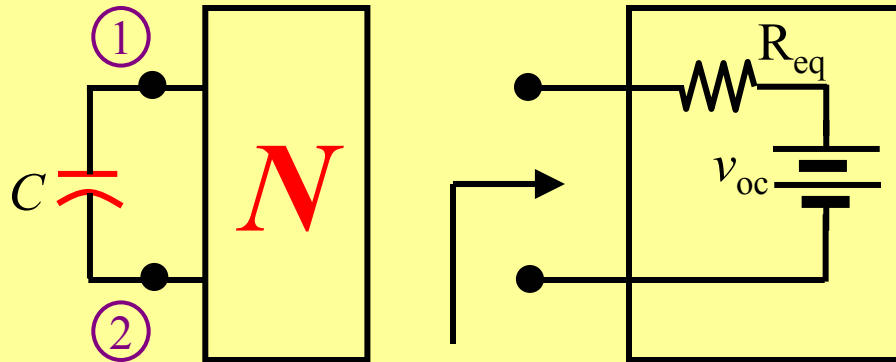

Thevenin  
equivalent circuit


Step 1 :

Find *Thevenin* equivalent  
circuit of N.

Step 2 :

$$\tau = R_{eq} C$$

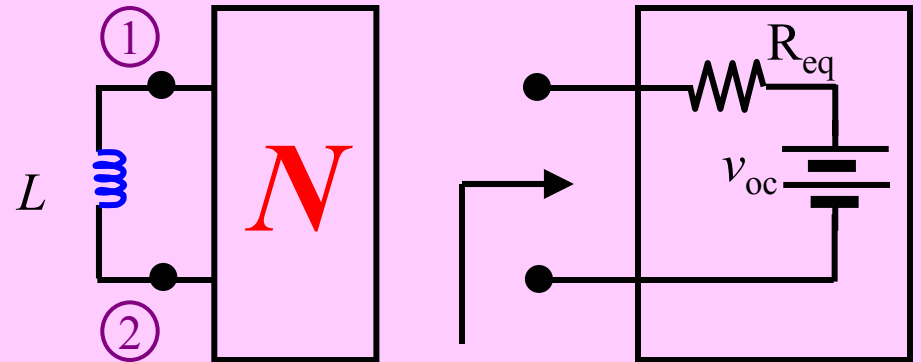How to Find  $\tau = G L = \frac{L}{R}$  ?



Thevenin  
equivalent circuit

Step 1 :

Find *Thevenin (or Norton)*  
equivalent circuit of N.


Step 2 :

$$\tau = \frac{L}{R_{eq}}$$


# Substitution Theorem

Let  $N$  be a circuit made of a nonlinear resistive one-port  $N_R$  terminated in an arbitrary one-port  $N_L$ , as shown in Fig. (a).

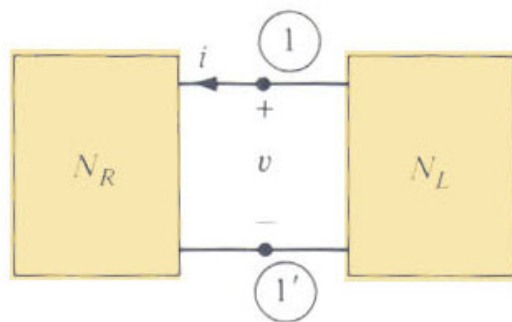
1. If  $N$  has a *unique* solution  $v = \hat{v}(t)$  for all  $t$ , then  $N_L$  may be substituted by a voltage source  $\hat{v}(t)$  without affecting the branch voltage and branch current solution inside  $N_R$ , provided the substituted circuit  $N_v$  in Fig. (b) has a *unique* solution for all  $t$ .
2. If  $N$  has a *unique* solution  $i = \hat{i}(t)$  for all  $t$ , then  $N_L$  may be substituted by a current source  $\hat{i}(t)$  without affecting the branch voltage and branch current solution inside  $N_R$ , provided the substituted circuit  $N_i$  in Fig. (c) has a *unique* solution for all  $t$ .



(a) Circuit  $N$

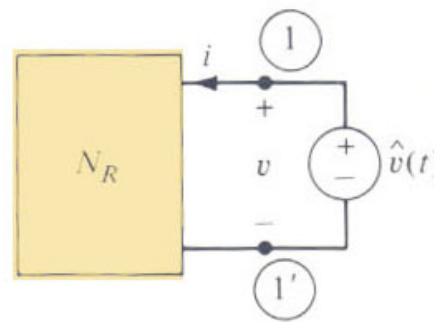

(b)

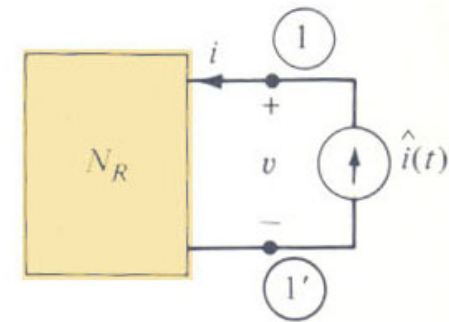

(c)

(a) Circuit  $N$ . (b) Substituted circuit  $N_v$ . (c) Substituted circuit  $N_i$ .