

MMIC Design and Technology

Active Devices

Instructor: Dr. Ali Medi

MESFET Operation

$$I_{ds} = qN_d(h-a)wv$$

$$v = \mu E$$

$$E = \frac{V_{ds}}{s}$$

$$a = \left(\frac{2\epsilon_0\epsilon_r(V_{bi} - V_{gs})}{qN_d} \right)^{\frac{1}{2}}$$

$$g_m = \left. \frac{\partial I_{ds}}{\partial V_{gs}} \right|_{V_{ds} = \text{Const}}$$

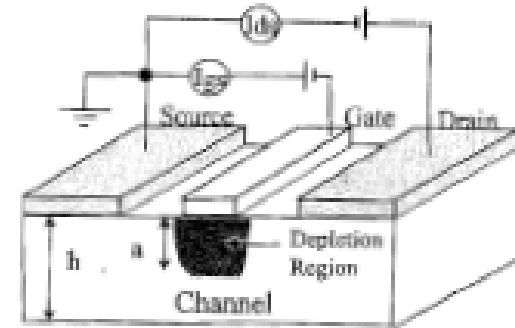


Figure 2.31 Schematic of a MESFET

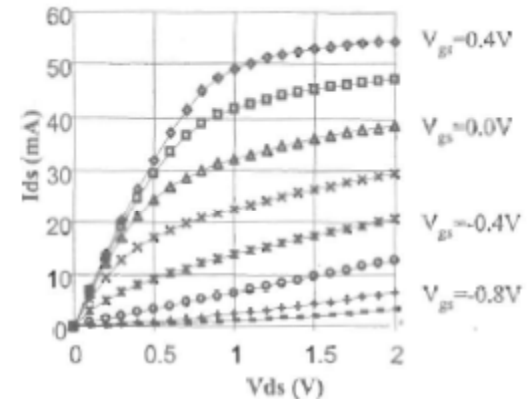


Figure 2.33 Output characteristics of a MESFET

MESFET Equivalent Circuit

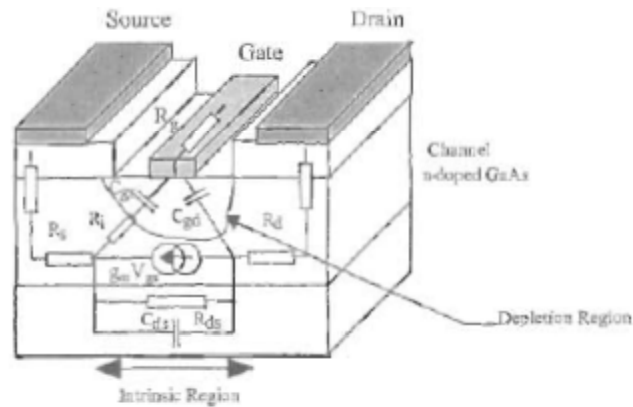


Figure 2.34 Cross-section of MESFET with superimposed lumped-element equivalent circuit

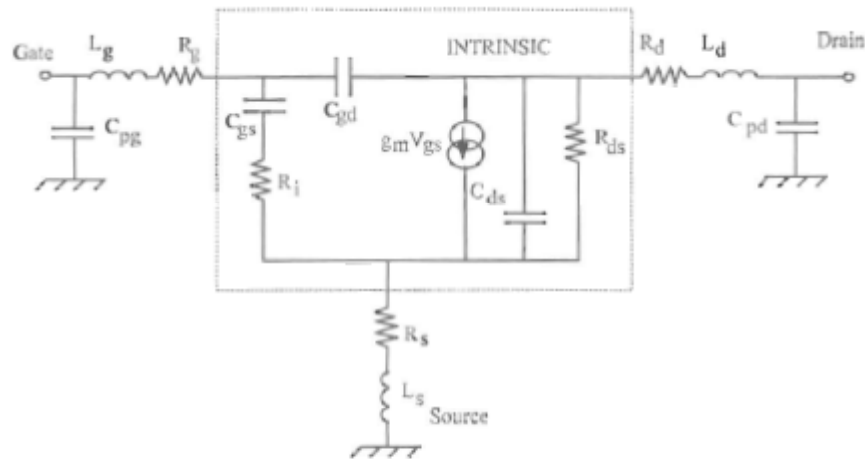


Figure 2.35 Lumped-element equivalent circuit of a MESFET

$$g_m = \left. \frac{\partial I_{ds}}{\partial V_{gs}} \right|_{V_{ds} = \text{Const}}$$

Frequency

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

Cut off Frequency where $I_{ds} = I_{gs}$

$$f_T = \frac{v_{eff}}{2\pi L_g}$$

For High frequency
Increase effective velocity
and reduce gate lengths

$$f_T = \frac{g_m}{2\pi \left[(C_{gs} + C_{gd}) \left(1 + \frac{R_s + R_d}{R_{ds}} \right) + g_m C_{gd} (R_s + R_d) \right]}$$

And minimize resistance

HEMT and pHEMT

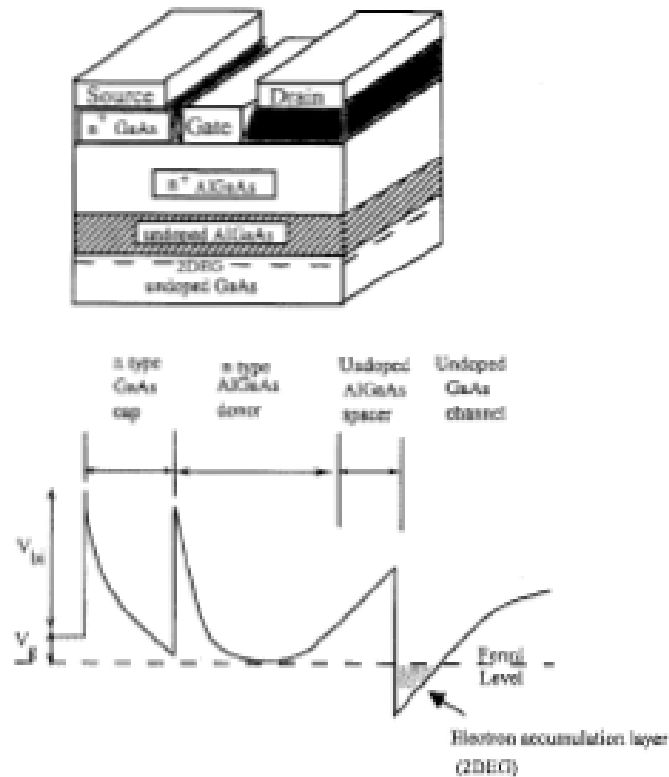


Figure 2.37 Cross-section of AlGaAs/GaAs HEMT and its conduction band diagram

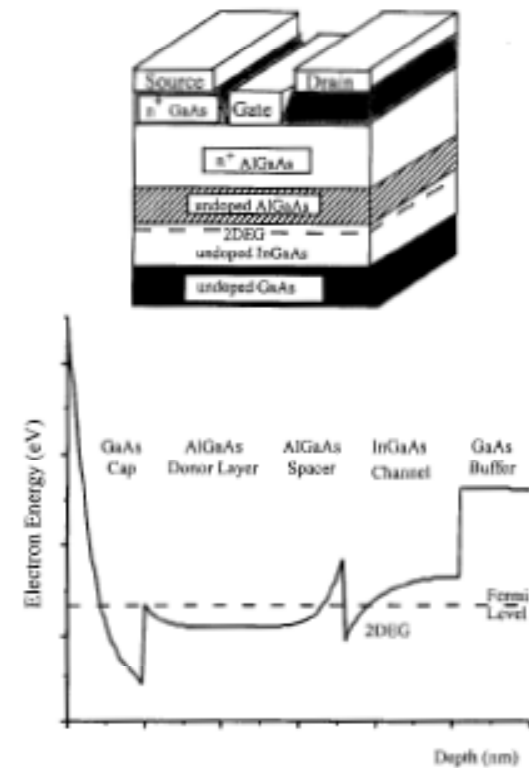


Figure 2.39 Cross-section of a GaAs pHEMT grown on a GaAs substrate and its conduction band diagram


Data file for actual device

```
! FILENAME: N67300.S2P VERSION: 1.0
! NEC PART NUMBER: NE67300 DATE: 4/83
! BIAS CONDITIONS: VDS=3V, IDS=10mA
! NOTE : GATE AND DRAIN BOND WIRES ARE DE-EMBEDDED.
! NOTE : SOURCE BOND WIRE EFFECTS ARE INCLUDED. Ltotal = 0.07 nH
! (4 EACH 0.7 mil DIAMETER GOLD WIRES APPROXIMATELY 0.015" LONG).
```


```
# GHZ S MA R 50
```

2	0.95	-26	3.79	161	0.04	79	0.59	-13
4	0.89	-50	3.26	141	0.06	66	0.58	-24
6	0.82	-70	2.83	126	0.08	56	0.54	-33
8	0.78	-88	2.55	114	0.09	51	0.5	-42
10	0.73	-102	2.21	104	0.1	48	0.47	-48
12	0.71	-114	2.16	93	0.1	43	0.45	-55
14	0.71	-122	2.11	90	0.11	44	0.47	-62
16	0.67	-128	1.92	76	0.11	43	0.49	-64
18	0.66	-140	1.81	63	0.11	40	0.52	-70
f1	ReS11	ImS11	ReS21	ImS21	ReS12	ImS12	ReS22	ImS22

S11 on Smith Chart

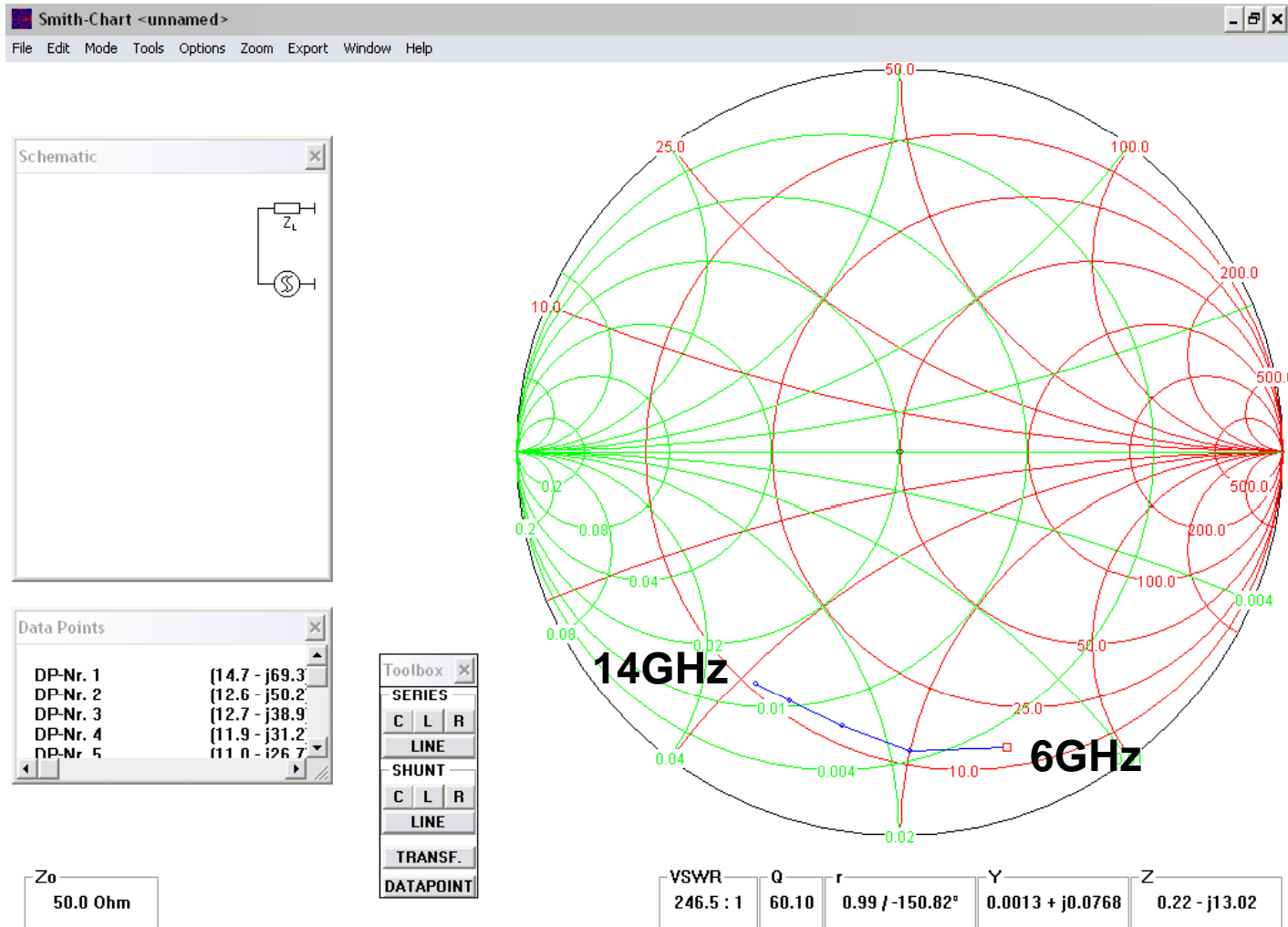

S21 and S12

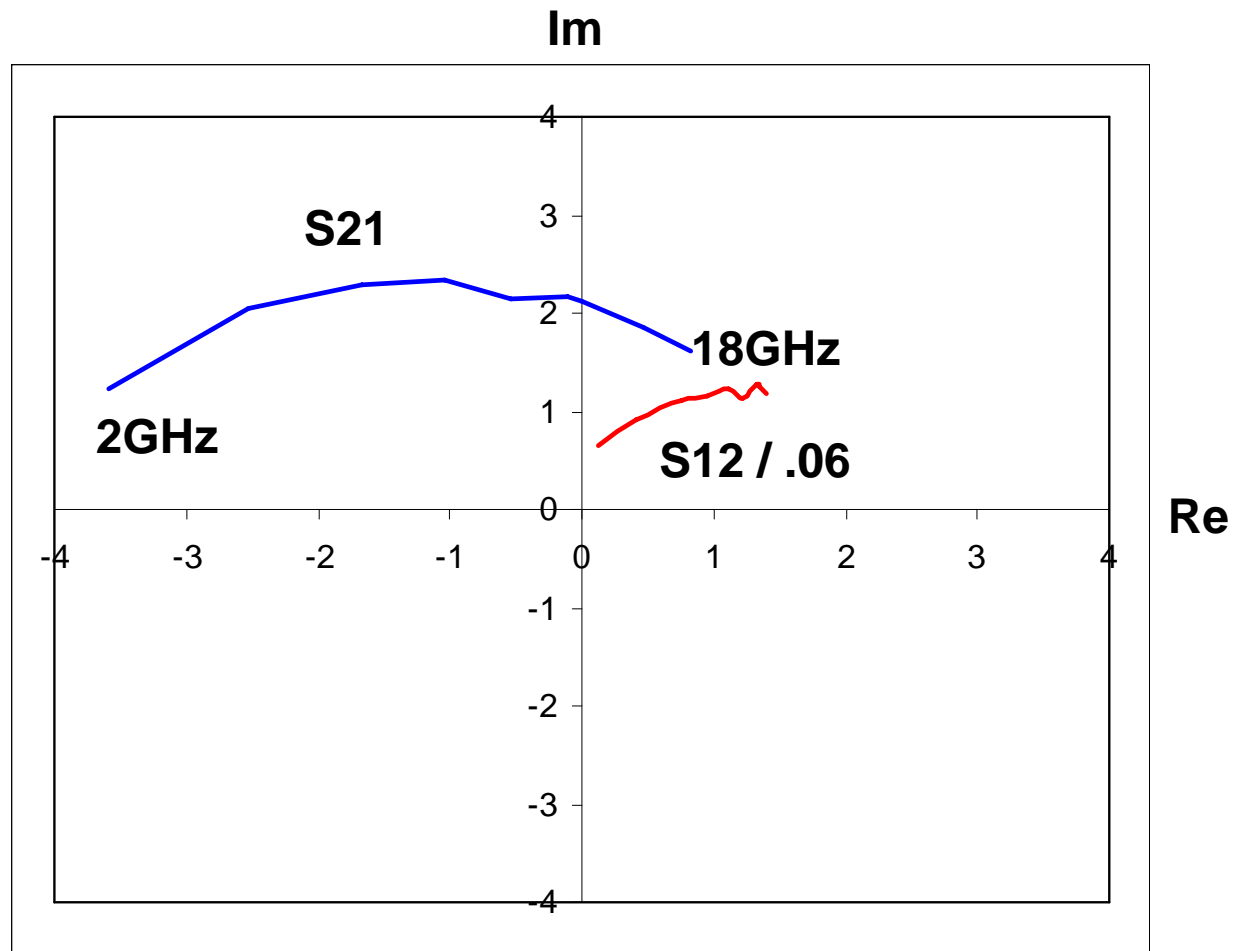


FET Example

Production Process




TQTRx
MESFET Foundry Service

GFET
300 um
Vds=3V
50% Idss

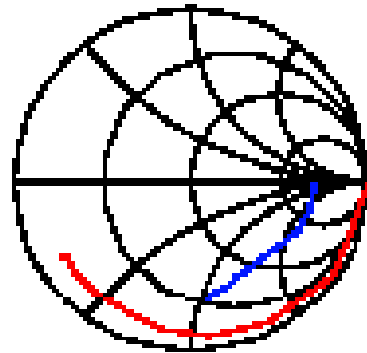

811
822

Freq (0.1GHz to 28.1GHz)

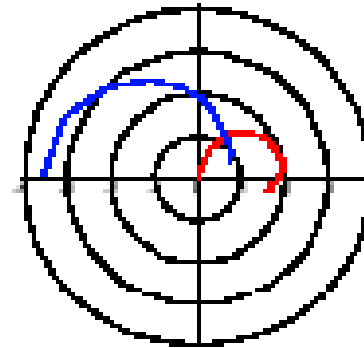


812 / .05
821

Input Reflection Coefficient

- S_{11} is reflection coefficient only when port 2 is terminated in a matched load
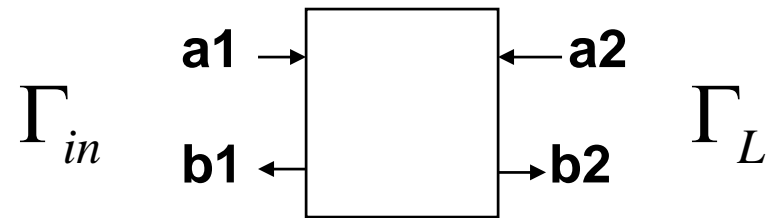
$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$




$$\Gamma_{in} = \frac{b_1}{a_1} = S_{11} + \frac{S_{21}S_{12}\Gamma_L}{1 - S_{22}\Gamma_L} = S_{11} \text{ when } S_{12} = 0$$

Output Reflection Coefficient

- S_{22} is reflection coefficient only when port 1 is terminated in a matched load
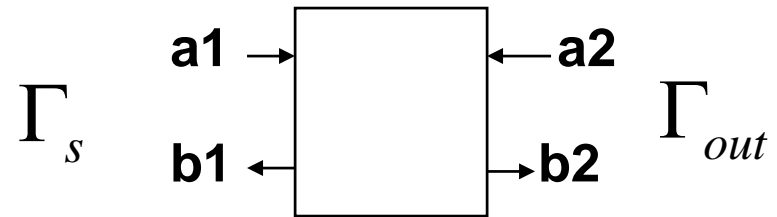
$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$



$$\Gamma_{out} = \frac{b_2}{a_2} = S_{22} + \frac{S_{21}S_{12}\Gamma_s}{1 - S_{11}\Gamma_s} \quad = S_{22} \text{ when } S_{12} = 0$$

Stability

- Transistor is unstable when $|\Gamma_{in}| > 1$

$$\Gamma_{in} = \frac{b_1}{a_1} = S_{11} + \frac{S_{21}S_{12}\Gamma_L}{1 - S_{22}\Gamma_L}$$

Boundary Condition for Stability

$$\left| S_{11} + \frac{S_{21}S_{12}\Gamma_L}{1 - S_{22}\Gamma_L} \right| = 1$$

Stability

- Transistor is unstable when $|\Gamma_{out}| > 1$

$$\Gamma_{out} = \frac{b_2}{a_2} = S_{22} + \frac{S_{21}S_{12}\Gamma_s}{1 - S_{11}\Gamma_s}$$

Boundary Condition for Stability

$$\left| S_{22} + \frac{S_{21}S_{12}\Gamma_s}{1 - S_{22}\Gamma_s} \right| = 1$$

Stability Circles on Smith Chart

- Load or Source stability circle is the locus of points in the Γ_L or Γ_s plane, for which Γ_{in} or $\Gamma_{out} = 1$. If the center of the smith chart is enclosed by the stability circle then all points inside the circle are stable. If the center is not enclosed then all points inside the circle are unstable.

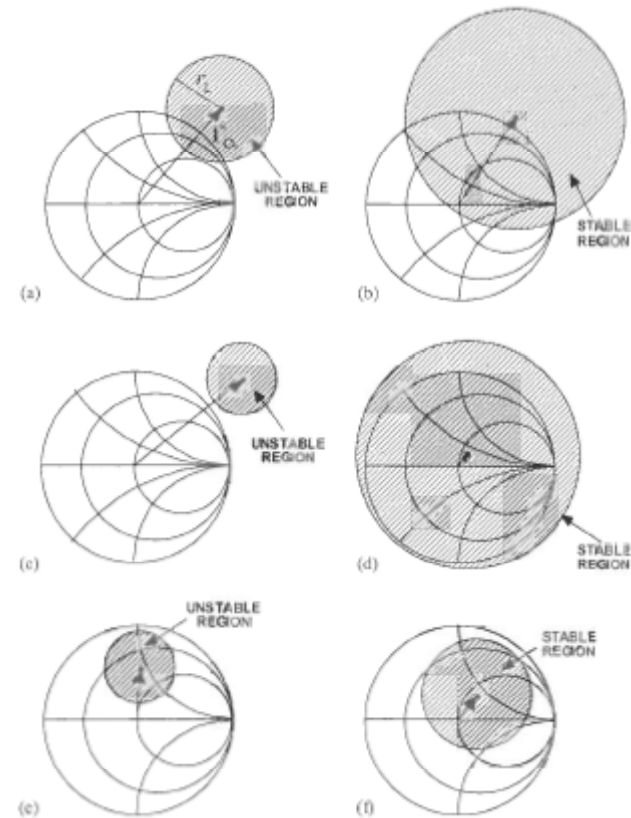


Figure 5.2 Stability circles on the Smith chart: (a) stability circle partially inside the Smith chart, (b) partially inside and encircling the 50 Ω point, (c) completely outside, (d) completely encircling the Smith chart, (e) completely inside but not encircling the 50 Ω point and (f) completely inside and encircling the 50 Ω point

Unconditional Stability

- If all of the smith chart is in a stable region then the transistor is said to be unconditionally stable.
 - Γ_{in} or $\Gamma_{out} < 1$ for all values of Γ_L or Γ_S

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{12}S_{21}|}$$

Unconditionally Stable for $K > 1$

$$\Delta = S_{11}S_{22} - S_{12}S_{21}$$