

MATHEMATICAL QUESTIONS

Question 1

If the two networks shown in each of Figs. 1 and 2 are equivalent, specify values for L_a , L_b , and L_c . For each equivalent circuit, show that L_a , L_b , and L_c can be non-negative by a proper choice of n

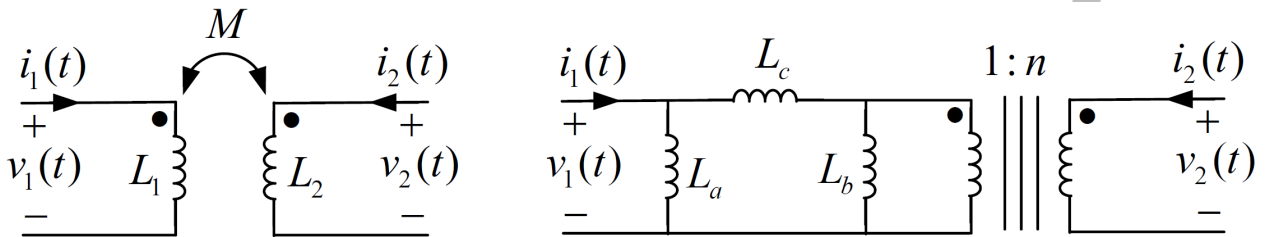


Figure 1: A pair of coupled inductors and its π equivalent circuit.

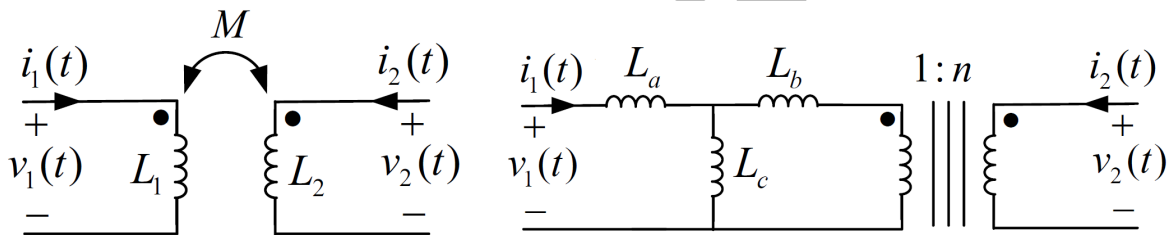


Figure 2: A pair of coupled inductors and its T equivalent circuit.

Question 2

Find the frequency response $H(j\omega) = \frac{V_o(j\omega)}{V_s(j\omega)}$ of the double-tuned circuit shown in Fig. 3.

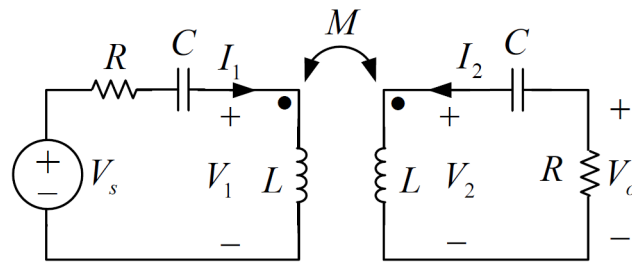


Figure 3: Double-tuned circuit.

Question 3

For the circuit of Fig. 4, find the input impedance Z_{in} seen from the source terminals.

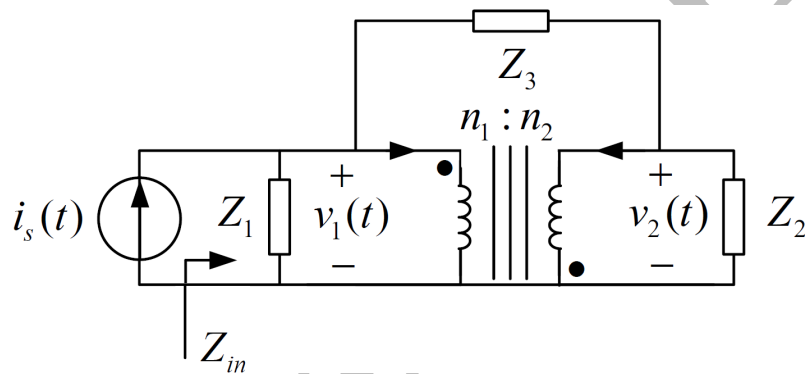


Figure 4: A circuit for which the input impedance is required.

Question 4

Calculate I_x and V_2 as labeled in Fig. 5.

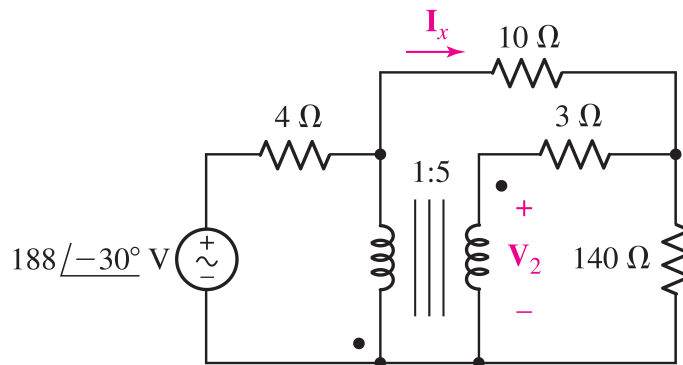


Figure 5: A simple circuit having an ideal transformer.

Question 5

With respect to the circuit depicted in Fig. 6,

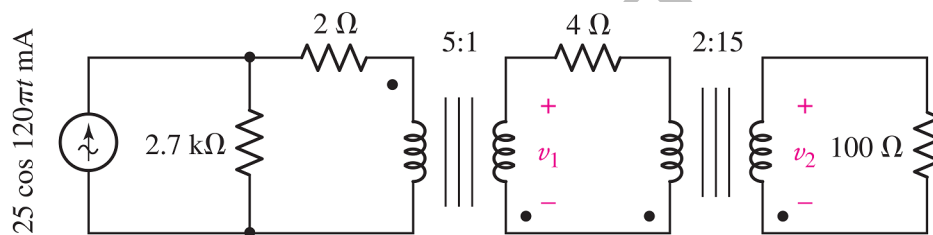


Figure 6: A circuit with two ideal transformers.

(a) Calculate the voltages v_1 and v_2 .

(b) Compute the average power delivered to each resistor.

SOFTWARE QUESTIONS

Question 6

A real transformer is usually modeled as the circuit of Fig. 6, where L_p is the primary leakage inductance, R_p is the primary copper loss, R_c is the core losses due to eddy currents and hysteresis, L_m is the magnetization inductance, L_s is the secondary leakage inductance, and R_s is the secondary copper loss. Use CircuitLab, which is an online circuit simulation platform, to investigate the impact of L_p , R_p , R_c , L_m , L_s , and R_s on the transformer performance. You may plot the voltages of the primary and secondary versus time to investigate the impact of each item.

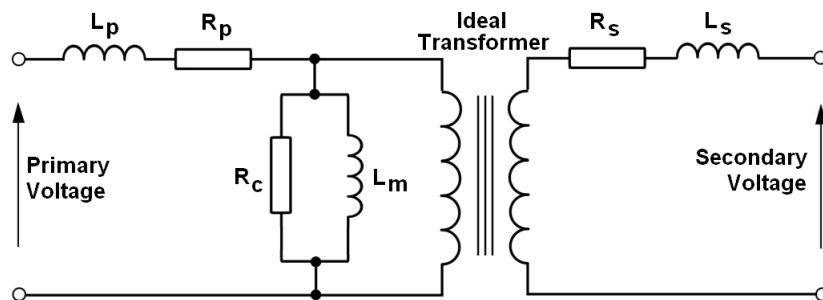


Figure 7: Real transformer equivalent circuits.

BONUS QUESTIONS

Question 7

Return your answers by filling the \LaTeX template of the assignment. If you want to add a circuit schematic, you can draw it directly using TikZ package, or draw it in a secondary application such as Microsoft Visio and then, import it as a figure.

EXTRA QUESTIONS

Question 8

Feel free to solve the following questions from the book *“Engineering Circuit Analysis”* by W. Hayt, J. Kemmerly, and S. Durbin.

1. Chapter 13, question 5.
2. Chapter 13, question 18.
3. Chapter 13, question 21.
4. Chapter 13, question 22.
5. Chapter 13, question 44.
6. Chapter 13, question 48.

Mohammad Hadi