
MATHEMATICAL QUESTIONS

Question 1

For the circuit of Fig. 1,

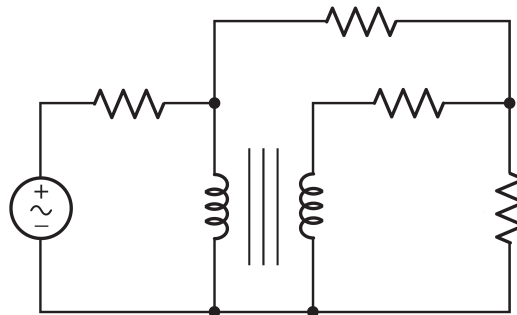


Figure 1: A sample circuit.

(a) Draw the circuit graph.

(b) Find a reduced node-to-branch incident matrix \mathbf{A} .

(c) Find a reduced mesh-to-branch incident matrix \mathbf{M} .

(d) Find a fundamental cut-set matrix \mathbf{Q} .

(e) Find a fundamental loop matrix \mathbf{B} .

(f) Can you introduce a tree for which the matrices \mathbf{A} and \mathbf{Q} are equal?

(g) Can you introduce a tree for which the matrices \mathbf{M} and \mathbf{B} are equal?

Question 2

Prove that the branch voltages of a tree of a given circuit graph provide a set of linearly independent voltages.

Question 3

The circuit of Fig. 2 includes LTI resistors and a voltage source. In an experimental measurement, we set $R_2 = 1 \Omega$, and find that $v_1 = 4 \text{ V}$, $i_1 = 1 \text{ A}$, and $v_2 = 1 \text{ V}$. In a second measurement, we set $R_2 = 2 \Omega$, and find that $v_1 = 2 \text{ V}$ and $i_1 = 1.2 \text{ A}$, but we forget to measure v_2 . Can you determine the value of v_2 in the second experiment? The inside of the sub-circuit N remains unchanged for the two experiments.

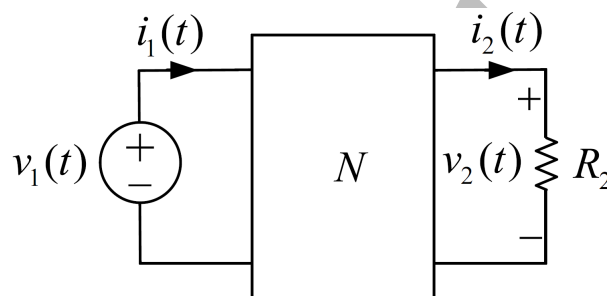


Figure 2: An LTI resistive network with a driving voltage source.

Question 4

Draw the dual circuit of the circuit shown in Fig. 3 and write at least two dual circuit equations for the two circuits.

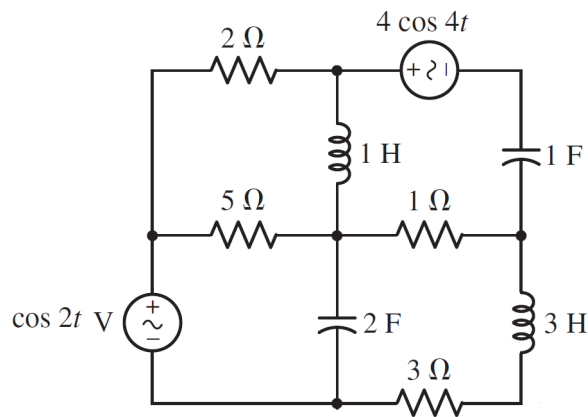


Figure 3: A circuit for which the dual network is required.

Question 5

Write the KCL and KVL equations corresponding to the fundamental cut sets and loops of the circuit graph shown in Fig. 4 having the highlighted tree.

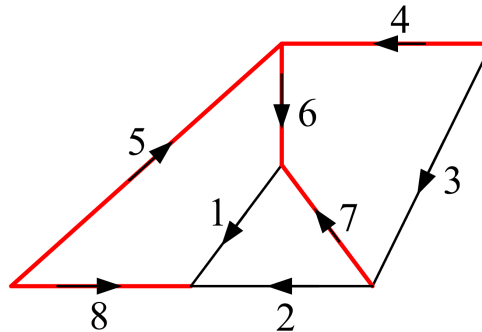


Figure 4: A circuit graph and one of its associated trees.

Question 6

Draw a directed graph whose node-to-branch incidence matrix A_a is given by

$$A_a = \begin{bmatrix} 1 & 1 & -1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & -1 & -1 & 1 & 0 & 0 & 0 & 0 & 0 \\ -1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & 1 & 1 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & -1 & 1 & 0 & 0 & 0 & -1 \\ 0 & -1 & 0 & -1 & 0 & 1 & 0 & -1 & 1 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & -1 & -1 & 1 \end{bmatrix}$$

SOFTWARE QUESTIONS

Question 7

Dijkstra's conventional algorithm is a systematic method to find the shortest path between two given nodes of a weighted graph. However, a more common variant of the algorithm fixes a single node as the reference node and finds shortest paths from the source to all other nodes in the graph, producing a shortest-path tree. Implement Dijkstra's algorithm as a MATLAB function and use it to find a tree of a given connected circuit graph.

Note: A circuit graph is a special weighted graph, where all the edges have a same weight.

Note: A graph can be represented by a matrix. In fact, for the graph $G(N = \{1, 2, \dots, n\}, E)$ with n node, the representing matrix of the graph is $A_{n \times n} = [a_{ij}]$, where a_{ij} is 1 if $(i, j) \in E$, and 0 otherwise.

BONUS QUESTIONS

Question 8

Return your answers by filling the \LaTeX template of the assignment. If you want to add a circuit schematic, you can draw it directly using TikZ package, or draw it in a secondary application such as Microsoft Visio and then, import it as a figure.

EXTRA QUESTIONS

Question 9

Feel free to solve the following questions from the book "*Basic Circuit Theory*" by C. Desoer and E. Kuh.

1. Chapter 9, question 1.
2. Chapter 9, question 3.
3. Chapter 9, question 4.
4. Chapter 9, question 9.

Mohammad Hadi