
MATHEMATICAL QUESTIONS

Question 1

Find the unidirectional Laplace transform of the following functions.

(a) $f(t) = 2|K|e^{-at} \cos(\beta t + \angle K)u(t)$.

(b) $f(t) = 2|K|te^{-at} \cos(\beta t + \angle K)u(t)$.

(c) $f(t) = g(t)u(t)$, $g(t) = at[u(t) - u(t - a)]$, $g(t - a) = g(t)$.

(d) $f(t) = e^{-at^2}$.

Question 2

Find the inverse unidirectional Laplace transform of the following functions.

(a) $F(s) = a \frac{-as-1+e^{as}}{s^2(e^{as}-1)}$.

(b) $F(s) = \frac{1}{s(s+1)^2(s^2+1)^2}$.

(c) $F(s) = \frac{s}{(s^2+2s+2)^3}$.

Question 3

Calculate the time-domain mesh currents for the circuit of Fig. 1.

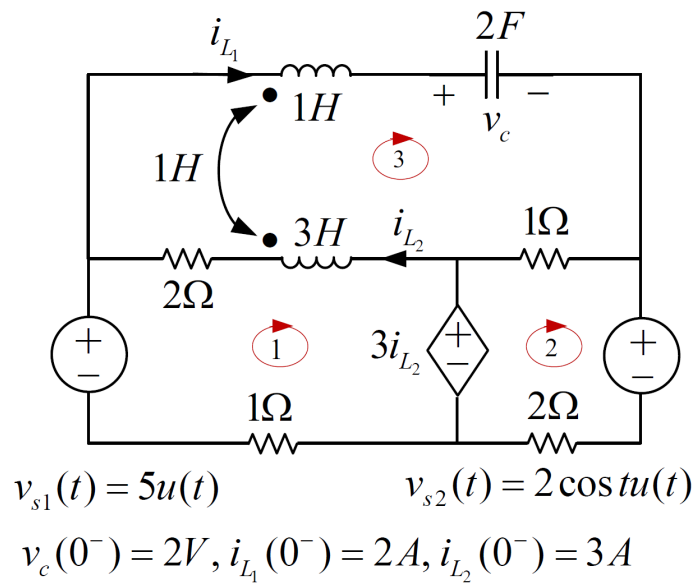


Figure 1: A coupled circuit for which the mesh currents are required.

Question 4

Obtain the time-domain node voltages for the circuit of Fig. 2.

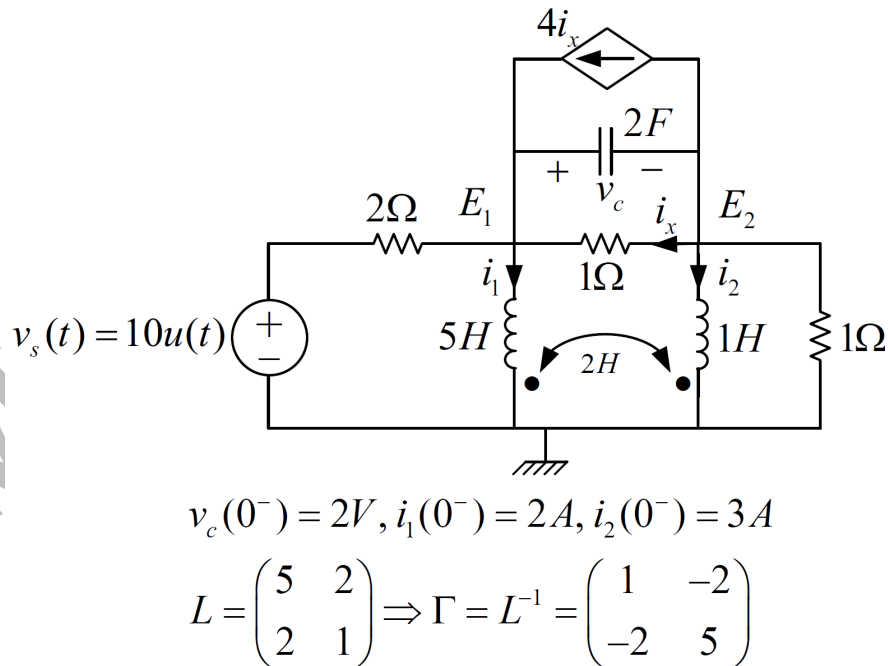


Figure 2: A coupled circuit for which the node voltages are required.

Question 5

Find an expression for $v(t)$ valid for all times in the circuit of Fig. 3.

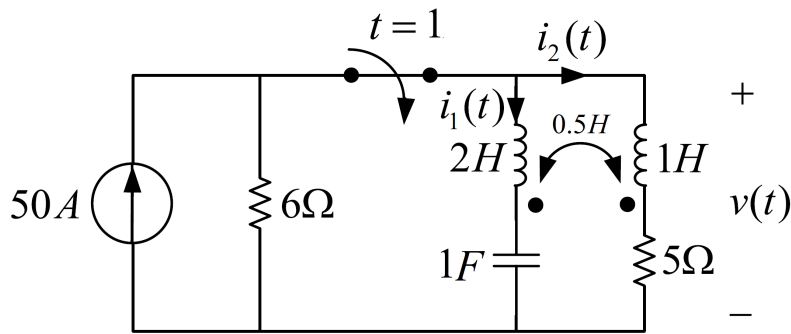


Figure 3: A circuit with a switch opened at $t = 1$.

SOFTWARE QUESTIONS

Question 6

Use AC analysis of PSpice to investigate the frequency response $H(j\omega) = \frac{V_o(j\omega)}{V_s(j\omega)}$ of the double-tuned circuit shown in Fig. 4. Analyze the impact of each parameter on the frequency response.

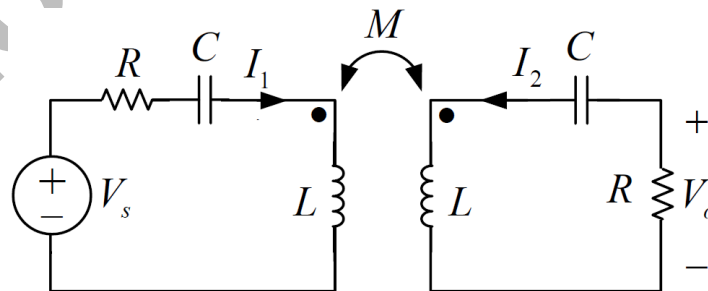


Figure 4: Double-tuned circuit.



BONUS QUESTIONS

Question 7

Return your answers by filling the \LaTeX template of the assignment. If you want to add a circuit schematic, you can draw it directly using TikZ package, or draw it in a secondary application such as Microsoft Visio and then, import it as a figure.

EXTRA QUESTIONS

Question 8

Feel free to solve the following questions from the book "*Engineering Circuit Analysis*" by W. Hayt, J. Kemmerly, and S. Durbin.

1. Chapter 15, question 14.
2. Chapter 15, question 19.
3. Chapter 15, question 22.
4. Chapter 15, question 24.
5. Chapter 15, question 27.