

MATHEMATICAL QUESTIONS

Question 1

Show that the circuits shown in Fig. 1 are degenerate, i.e., they may have no or several solutions.

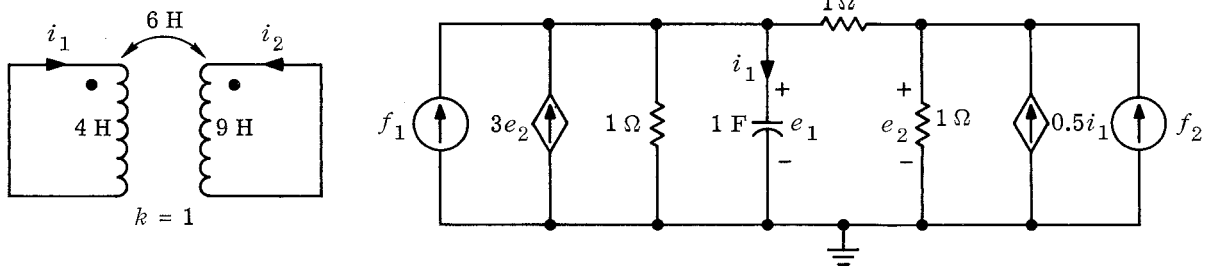


Figure 1: Degenerate LTI circuits.

Question 2

The results of two measurement scenarios for the reciprocal circuit of Fig. 2 are

$$\left\{ \begin{array}{l} v_1(t) = (-6e^{-t} + 14e^{-2t})u(t) \\ v_2(t) = 0 \\ v_3(t) = (-6e^{-t} + 12e^{-2t})u(t) \\ i_1(t) = \delta(t) \\ i_2(t) = -2e^{-2t}u(t) \\ i_3(t) = 0 \end{array} \right. , \quad \left\{ \begin{array}{l} \hat{v}_1(t) = ? \\ \hat{v}_2(t) = 24u(t) \\ \hat{v}_3(t) = (-12e^{-t} + 24e^{-2t})u(t) \\ \hat{i}_1(t) = 0 \\ \hat{i}_2(t) = 24e^{-2t}u(t) \\ \hat{i}_3(t) = 2\delta(t) \end{array} \right.$$

. Find $\hat{v}_1(t)$ in the second measurement scenario.

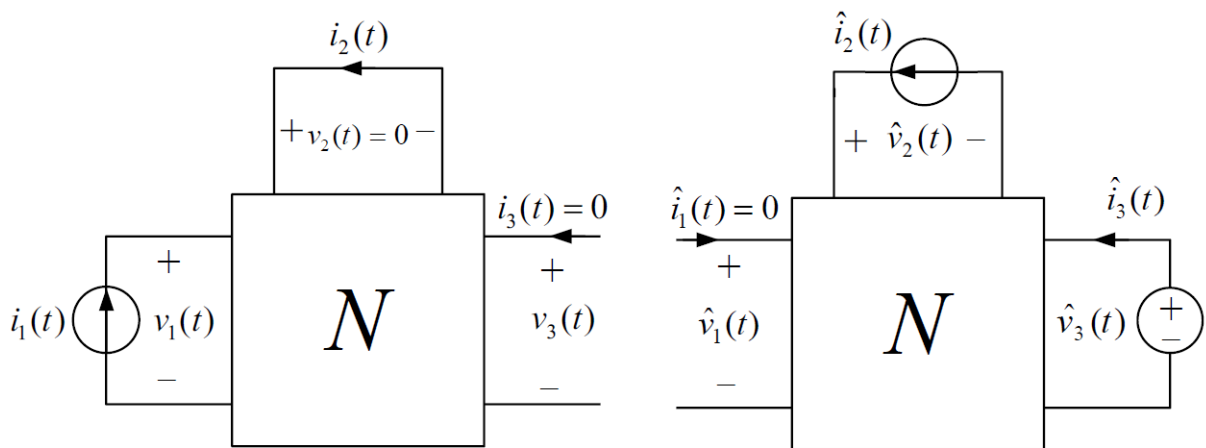


Figure 2: Two-measurement experiment for a reciprocal circuit.

Question 3

Verify that if the superposition theorem holds for the voltage response v at the nonlinear circuit of Fig. 3 or not.

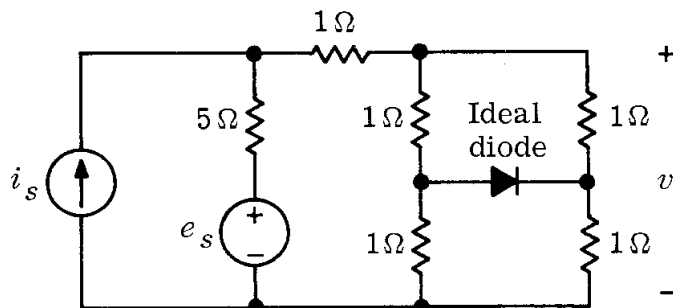


Figure 3: A balanced bridge nonlinear circuit.

Question 4

The small-signal model of the transistor amplifier of Fig. 4 is drawn.

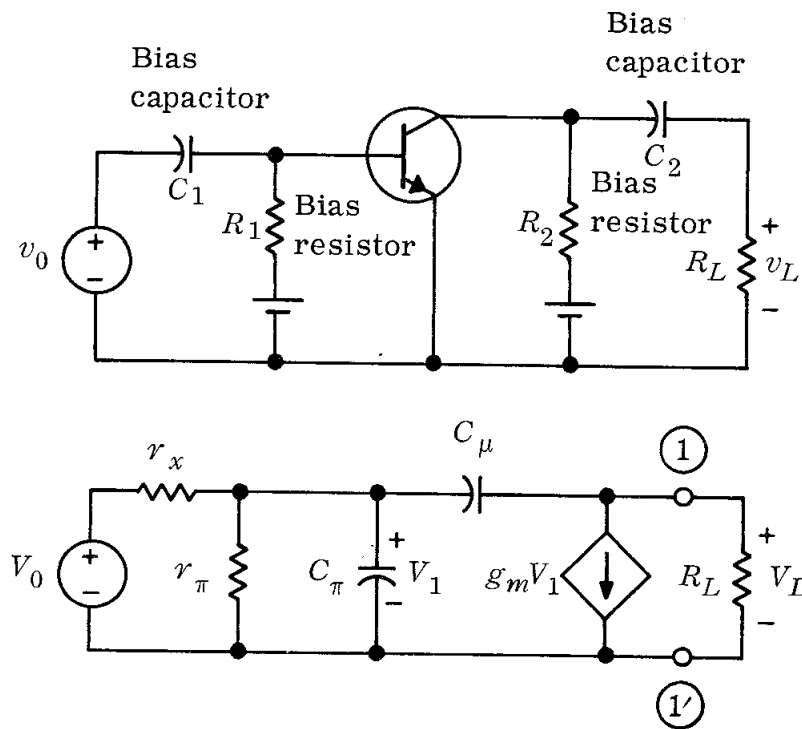


Figure 4: A simple transistor amplifier and its small-signal equivalent circuit.

(a) Find the Thevenin and Norton equivalent circuits seen from port 1 – 1' of the small-signal model.

(b) Find the voltage gain $H(s) = \frac{V_L(s)}{V_0(s)}$.

SOFTWARE QUESTIONS

Question 5

An audio file can be considered as the output voltage of a microphone versus time. Develop a MATLAB function that receives an audio file, passes it through the RC lowpass filter $H(j\omega) = \frac{1}{1+j\frac{\omega}{\omega_c}}$, $\omega_c = \frac{1}{RC}$, and generates a filtered audio file. Listen to the filtered output for different values of ω_c and examine the filtering impact on the quality of the filtered audio.

BONUS QUESTIONS

Question 6

Return your answers by filling the \LaTeX template of the assignment. If you want to add a circuit schematic, you can draw it directly using TikZ package, or draw it in a secondary application such as Microsoft Visio and then, import it as a figure.

EXTRA QUESTIONS

Question 7

Feel free to solve the following questions from the book "*Basic Circuit Theory*" by C. Desoer and E. Kuh.

1. Chapter 16, question 3.
2. Chapter 16, question 4.
3. Chapter 16, question 5.
4. Chapter 16, question 8.
5. Chapter 16, question 16.
6. Chapter 16, question 17.
7. Chapter 16, question 18.