

# Coupled Circuits

Mohammad Hadi

*mohammad.hadi@sharif.edu*

*@MohammadHadiDastgerdi*

Fall 2021

1 Coupled Inductors

2 Ideal Transformers

# Coupled Inductors

# Coupled Inductors

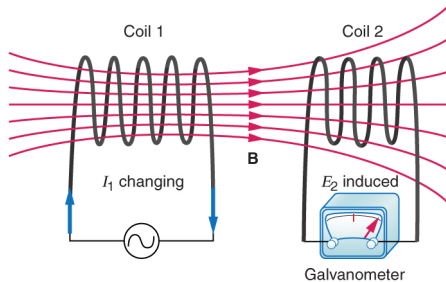


Figure: Coupled inductors as a method of wireless power transfer.

- Ampere's law:  $\phi \propto f(i)$
- Faraday's law  $v \propto \phi'$
- Ferromagnetic materials
- Mutual induction
- Self induction

# Coupled Inductors

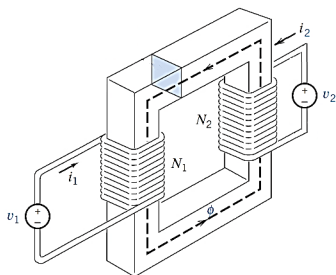


Figure: Coupled inductors.

- **NTV coupled inductors:** 
$$\begin{cases} f_1(\phi_1, \phi_2, i_1, i_2, t) = 0 \\ f_2(\phi_1, \phi_2, i_1, i_2, t) = 0 \end{cases}$$
- **LTI coupled inductors:** 
$$\begin{cases} \phi_1 = L_1 i_1 \pm M_{12} i_2 \\ \phi_2 = \pm M_{21} i_1 + L_2 i_2 \end{cases} \Rightarrow \begin{cases} v_1(t) = L_1 i_1'(t) \pm M_{12} i_2'(t) \\ v_2(t) = \pm M_{21} i_1'(t) + L_2 i_2'(t) \end{cases}$$

# Dot Convention

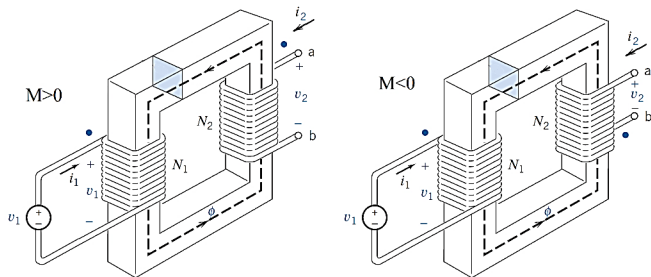


Figure: Additive and subtractive flux in coupled inductors.

- Additive flux:

$$\begin{cases} v_1(t) = L_1 i_1'(t) + M_{12} i_2'(t) \\ v_2(t) = +M_{21} i_1'(t) + L_2 i_2'(t) \end{cases}$$

- Subtractive flux:

$$\begin{cases} v_1(t) = L_1 i_1'(t) - M_{12} i_2'(t) \\ v_2(t) = -M_{21} i_1'(t) + L_2 i_2'(t) \end{cases}$$

# Dot Convention

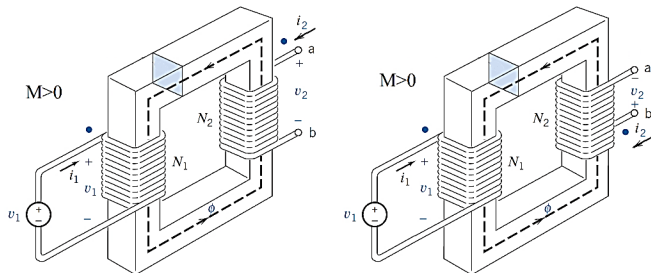


Figure: Dot convention, where the port are marked according to passive sign convention and the currents flow to the terminals that provide additive flux.

- Additive flux:

$$\begin{cases} v_1(t) = L_1 i_1'(t) + M_{12} i_2'(t) \\ v_2(t) = +M_{21} i_1'(t) + L_2 i_2'(t) \end{cases}$$

- Additive flux:

$$\begin{cases} v_1(t) = L_1 i_1'(t) + M_{12} i_2'(t) \\ v_2(t) = +M_{21} i_1'(t) + L_2 i_2'(t) \end{cases}$$

# Absorbed Energy

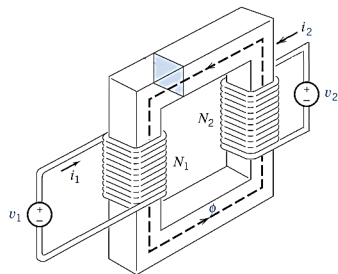


Figure:  $M_{12} = M_{21} = M$  in coupled inductors.

- $(i_1(t_0), i_2(t_0)) = (0, 0)$ :  $\mathcal{E} = 0 + 0$
- $(i_1(t_1), i_2(t_1)) = (I_1, 0)$ :  $\mathcal{E} = 0.5L_1I_1^2 + 0$
- $(i_1(t_2), i_2(t_2)) = (I_1, I_2)$ :  $\mathcal{E} = 0.5L_1I_1^2 + M_{12}I_2I_1 + 0.5L_2I_2^2$
- $(i_1(t_0), i_2(t_0)) = (0, 0)$ :  $\mathcal{E} = 0 + 0$
- $(i_1(t_1), i_2(t_1)) = (0, I_2)$ :  $\mathcal{E} = 0 + 0.5L_2I_2^2 + 0$
- $(i_1(t_2), i_2(t_2)) = (I_1, I_2)$ :  $\mathcal{E} = 0.5L_1I_1^2 + M_{21}I_2I_1 + 0.5L_2I_2^2$
- $M_{12} = M_{21} = M$



# Absorbed Energy

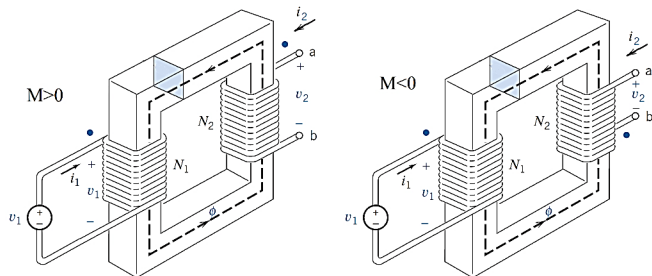


Figure: Absorbed energy in **passive** coupled inductors. The **initial energy** is zero.

- **Additive flux:**

$$\mathcal{E} = 0.5L_1i_1^2(t) + Mi_1(t)i_2(t) + 0.5L_2i_2^2(t) \geq 0$$

- **Subtractive flux:**

$$\mathcal{E} = 0.5L_1i_1^2(t) - Mi_1(t)i_2(t) + 0.5L_2i_2^2(t) \geq 0$$

- **Absorbed energy:**  $\mathcal{E} = 0.5(\sqrt{L_1}i_1(t) - \sqrt{L_2}i_2(t))^2 + i_1(t)i_2(t)[\sqrt{L_1L_2} \pm M] \geq 0$

- **Coupling coefficient:**  $|M| \leq \sqrt{L_1L_2} \Rightarrow k = \frac{|M|}{\sqrt{L_1L_2}} \leq 1$

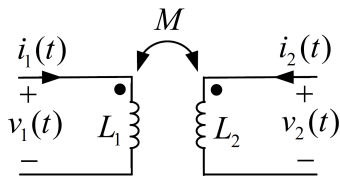



Figure: **Circuit model** of coupled inductors.

- **Time-domain model:** 
$$\begin{cases} v_1(t) = L_1 i_1'(t) + M i_2'(t) \\ v_2(t) = M i_1'(t) + L_2 i_2'(t) \end{cases}$$
- **Time-domain model:** 
$$\begin{cases} i_1(t) = i_1(0) + \Gamma_{11} \int_0^t v_1(t') dt' + \Gamma_{12} \int_0^t v_2(t') dt' \\ i_2(t) = i_2(0) + \Gamma_{21} \int_0^t v_1(t') dt' + \Gamma_{22} \int_0^t v_2(t') dt' \end{cases}$$
- **Phasor-domain model:** 
$$\begin{cases} V_1 = j\omega L_1 I_1 + j\omega M I_2 \\ V_2 = j\omega M I_1 + j\omega L_2 I_2 \end{cases}$$
- **Phasor-domain model:** 
$$\begin{cases} I_1 = \frac{\Gamma_{11}}{j\omega} V_1 + \frac{\Gamma_{12}}{j\omega} V_2 \\ I_2 = \frac{\Gamma_{21}}{j\omega} V_1 + \frac{\Gamma_{22}}{j\omega} V_2 \end{cases}$$
- **Reciprocal inductance matrix:** 
$$\Gamma = \begin{bmatrix} \Gamma_{11} & \Gamma_{12} \\ \Gamma_{21} & \Gamma_{22} \end{bmatrix} = L^{-1} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix}^{-1}$$
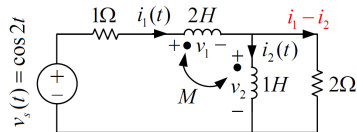
## Example (Mesh phasor analysis)

Mesh analysis for the circuit below with  $M = 0$  H yields  $i_1(t) = 0.19 \cos(2t - \underline{68.2^\circ})$  and  $i_2(t) = 0.13 \cos(2t - \underline{113.2^\circ})$ .

$$\begin{cases} -1\angle 0 + I_1 + 4jI_1 + 2jI_2 = 0 \\ -2jI_2 + 2(I_1 - I_2) = 0 \end{cases}$$
$$\begin{cases} I_1 = 0.19\angle -68.2^\circ \\ I_2 = 0.13\angle -113.2^\circ \end{cases}$$
$$\begin{cases} i_1(t) = 0.19 \cos(2t - \underline{68.2^\circ}) \\ i_2(t) = 0.13 \cos(2t - \underline{113.2^\circ}) \end{cases}$$




## Example (Mesh phasor analysis)

Mesh analysis for the circuit below with  $M = 1$  H yields  $i_1(t) = 0.13 \cos(2t - \underline{50.2^\circ})$  and  $i_2(t) = 0.13 \cos(2t - \underline{140.2^\circ})$ .

$$\begin{cases} -1\angle 0 + I_1 + 4jI_1 + 2jI_2 + 2jI_2 + 2jI_1 = 0 \\ -(2jI_2 + 2jI_1) + 2(I_1 - I_2) = 0 \end{cases}$$

$$\begin{cases} I_1 = 0.13\angle -50.2^\circ \\ I_2 = 0.13\angle -140.2^\circ \end{cases}$$
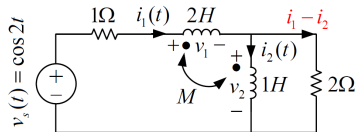
$$\begin{cases} i_1(t) = 0.13 \cos(2t - \underline{50.2^\circ}) \\ i_2(t) = 0.13 \cos(2t - \underline{140.2^\circ}) \end{cases}$$




## Example (Nodal phasor analysis)

Nodal analysis for the circuit below with  $M = 0$  H yields  $v_1(t) = 0.33 \cos(t + \underline{/30.53^\circ})$  and  $v_2(t) = 0.13 \cos(t + \underline{/57.09^\circ})$ .

$$\begin{cases} -1\angle 0 + \frac{V_1}{1} + \frac{V_1}{j3} + \frac{V_1 - V_2}{\frac{1}{j2}} = 0 \\ \frac{V_2}{2} + \frac{V_2}{j} + \frac{V_2 - V_1}{\frac{1}{j2}} = 0 \end{cases}$$

$$\begin{cases} V_1 = 0.33\angle 30.53^\circ \\ V_2 = 0.59\angle 57.09^\circ \end{cases}$$
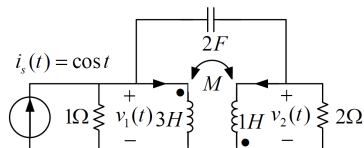
$$\begin{cases} v_1(t) = 0.33 \cos(t + \underline{/30.53^\circ}) \\ v_2(t) = 0.13 \cos(t + \underline{/57.09^\circ}) \end{cases}$$



## Example (Nodal phasor analysis)


Nodal analysis for the circuit below with  $M = 1$  H yields  $v_1(t) = 0.12 \cos(t + \underline{/33.23^\circ})$  and  $v_2(t) = 0.41 \cos(t + \underline{/78.23^\circ})$ .

$$L = \begin{bmatrix} 3 & -1 \\ -1 & 1 \end{bmatrix} \Rightarrow \Gamma = L^{-1} = \begin{bmatrix} 0.5 & 0.5 \\ 0.5 & 1.5 \end{bmatrix}$$

$$\begin{cases} -1 \underline{/0} + \frac{V_1}{1} + \frac{0.5V_1}{j} + \frac{0.5V_2}{j} + \frac{V_1 - V_2}{\frac{1}{j^2}} = 0 \\ \frac{V_2}{2} + \frac{0.5V_1}{j} + \frac{1.5V_2}{j} + \frac{V_2 - V_1}{\frac{1}{j^2}} = 0 \end{cases}$$

$$\begin{cases} V_1 = 0.12 \underline{/33.23^\circ} \\ V_2 = 0.41 \underline{/78.23^\circ} \end{cases}$$
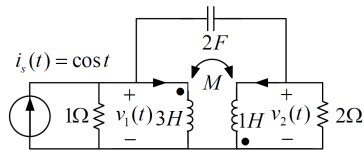
$$\begin{cases} v_1(t) = 0.12 \cos(t + \underline{/33.23^\circ}) \\ v_2(t) = 0.41 \cos(t + \underline{/78.23^\circ}) \end{cases}$$



# Multi-winding Inductors

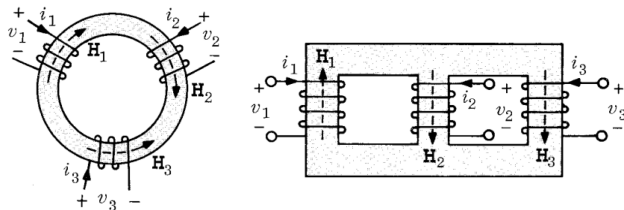


Figure: **Passive three-winding** coupled inductors.

- **Inductance matrix:**  $L = \begin{bmatrix} L_{11} & L_{12} & L_{13} \\ L_{21} & L_{22} & L_{23} \\ L_{31} & L_{32} & L_{33} \end{bmatrix}$
- **Passivity condition:** non-negative definite  $L$


# Series and Parallel Connection of Coupled Inductors

## Example (Series connection of coupled inductors)

The inductance of the series connection of two coupled inductors is  $L_{eq} = L_1 + L_2 + \pm 2|M|$ .

$$\begin{aligned}v(t) &= v_1(t) + v_2(t) \\ &= L_1 i'(t) + M i'(t) + M i'(t) + L_2 i'(t) \\ &= (L_1 + L_2 + 2M) i'(t)\end{aligned}$$
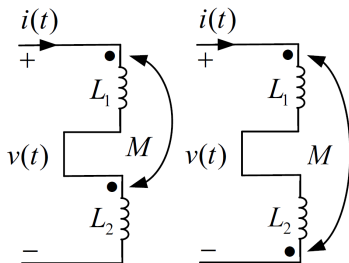
$$\begin{aligned}v(t) &= v_1(t) + v_2(t) \\ &= L_1 i'(t) - M i'(t) - M i'(t) + L_2 i'(t) \\ &= (L_1 + L_2 - 2M) i'(t)\end{aligned}$$





# Series and Parallel Connection of Coupled Inductors



## Example (Parallel connection of coupled inductors)

The reciprocal inductance of the parallel connection of two coupled inductors is

$$\Gamma_{eq} = \Gamma_{11} + \Gamma_{22} + \pm 2|\Gamma_{12}|.$$

$$\begin{aligned}i(t) &= i_1(t) + i_2(t) \\&= \Gamma_{11} \int_0^t v(t') dt' + \Gamma_{12} \int_0^t v(t') dt' \\&+ \Gamma_{12} \int_0^t v(t') dt' + \Gamma_{22} \int_0^t v(t') dt' \\&= (\Gamma_{11} + \Gamma_{22} + 2\Gamma_{12}) \int_0^t v(t') dt'\end{aligned}$$
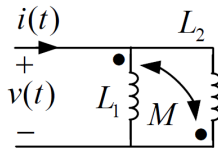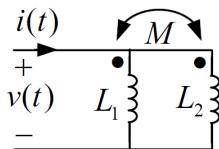
$$\begin{aligned}i(t) &= i_1(t) + i_2(t) \\&= \Gamma_{11} \int_0^t v(t') dt' - \Gamma_{12} \int_0^t v(t') dt' \\&- \Gamma_{12} \int_0^t v(t') dt' + \Gamma_{22} \int_0^t v(t') dt' \\&= (\Gamma_{11} + \Gamma_{22} - 2\Gamma_{12}) \int_0^t v(t') dt'\end{aligned}$$



# Equivalent Circuits for Coupled Inductors

## Example (T equivalent circuit for coupled inductors)

Two coupled inductors can be replaced with an inductive T network.

$$v_1(t) = L_1 i_1'(t) + M i_2'(t)$$

$$v_2(t) = M i_1'(t) + L_2 i_2'(t)$$



$$v_1(t) = L_a i_1'(t) + L_c i_1'(t) + i_2'(t)$$

$$v_2(t) = L_b i_2'(t) + L_c i_1'(t) + i_2'(t)$$

$$L_a = L_1 - M$$

$$L_b = L_2 - M$$

$$L_c = M$$

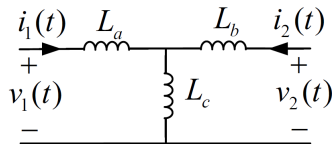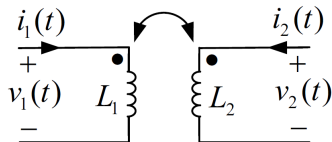

# Equivalent Circuits for Coupled Inductors

## Example ( $\Pi$ equivalent circuit for coupled inductors)

Two coupled inductors can be replaced with an inductive  $\Pi$  network.

$$i_1(t) = \Gamma_{11} \int_0^t v_1(t') dt' + \Gamma_{12} \int_0^t v_2(t') dt'$$

$$i_2(t) = \Gamma_{21} \int_0^t v_1(t') dt' + \Gamma_{22} \int_0^t v_2(t') dt'$$



$$i_1(t) = \Gamma_a \int_0^t v_1(t') dt' + \Gamma_c \int_0^t [v_1(t') - v_2(t')] dt'$$

$$i_2(t) = \Gamma_b \int_0^t v_2(t') dt' + \Gamma_c \int_0^t [v_2(t') - v_1(t')] dt'$$

$$\Gamma_a = \Gamma_{11} + \Gamma_{12}$$

$$\Gamma_b = \Gamma_{22} + \Gamma_{12}$$

$$\Gamma_c = -\Gamma_{12}$$

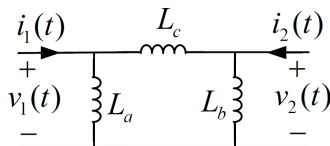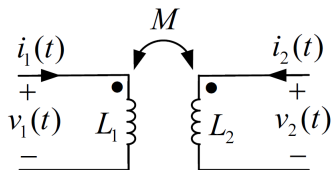

# Impedance Changing by Coupled Inductors


## Example (Impedance changing by coupled inductors)

The input impedance seen from a coupled inductor is  $Z_{in} = j\omega L_1 + M^2\omega^2/(j\omega L_2 + Z_L)$ .

$$\begin{cases} V_s = j\omega L_1 I_1 + j\omega M I_2 \\ V_2 = j\omega L_2 I_2 + j\omega M I_1 \\ V_2 = -Z_L I_2 \end{cases}$$

$$\Rightarrow V_1 = [j\omega L_1 + M^2\omega^2/(j\omega L_2 + Z_L)] I_1$$
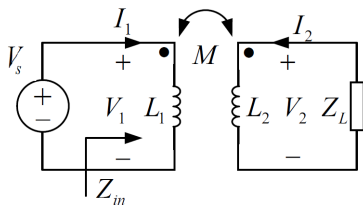
$$\Rightarrow Z_{in} = \frac{V_1}{I_1} = j\omega L_1 + \frac{M^2\omega^2}{j\omega L_2 + Z_L}$$



# Double-tuned Circuit

## Example (Double-tuned Circuit)

Double-tuned circuit can have a wider bandwidth than the single-tuned circuit.

$$I_+ = \frac{I_1 + I_2}{2}, \quad I_- = \frac{I_1 - I_2}{2}$$


$$\omega_+^2 = \frac{1}{LC(1+k)}, \quad Q_+ = \omega_+ \frac{L+M}{R}$$

$$\omega_-^2 = \frac{1}{LC(1-k)}, \quad Q_- = \omega_- \frac{L-M}{R}$$

$$H_+(j\omega) = \frac{I_+}{V_s} = \frac{0.5/R}{1 + jQ_+(\frac{\omega}{\omega_+} - \frac{\omega_+}{\omega})}$$

$$H_-(j\omega) = \frac{I_-}{V_s} = \frac{0.5/R}{1 + jQ_-(\frac{\omega}{\omega_-} - \frac{\omega_-}{\omega})}$$
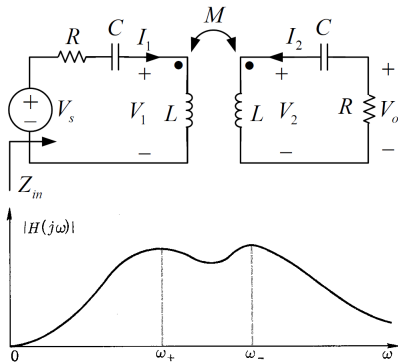
$$H(j\omega) = \frac{V_o}{V_s} = -R \frac{I_2}{V_s} = -R[H_+(j\omega) - H_-(j\omega)]$$



# Ideal Transformers

# Ideal Transformer

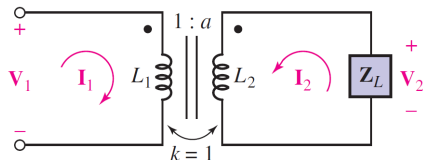


Figure: An **ideal transformer** is connected to a general load impedance.

- **Ideal transformer assumptions:**  $L_1, L_2 \rightarrow \infty$ ,  $L_2/L_1 = (n_2/n_1)^2 = a^2$ ,  $k = 1$
- **Circuit analysis:** 
$$\begin{cases} V_1 = j\omega L_1 I_1 + j\omega M I_2 \\ j\omega M I_1 + j\omega L_2 I_2 - Z_L I_2 = 0 \end{cases}$$
- **Current ratio:** 
$$\frac{I_2}{I_1} = \frac{j\omega M}{Z_L - j\omega L_2} \approx -\frac{M}{L_2} = -\sqrt{\frac{L_1}{L_2}} = -\frac{n_1}{n_2} = -\frac{1}{a}$$
- **Voltage ratio:** 
$$\frac{V_2}{V_1} = \frac{-I_2 Z_L}{I_1 Z_{in}} = \frac{1}{a} \frac{Z_L}{j\omega L_1 + \frac{\omega^2 M^2}{Z_L + j\omega L_2}} = \frac{1}{a} \frac{Z_L}{j\omega L_1 + \frac{\omega^2 a^2 L_1^2}{Z_L + j\omega a^2 L_1}} = \frac{1}{a} \frac{Z_L}{\frac{j\omega L_1 Z_L}{Z_L + j\omega a^2 L_1}} = a$$

# Multi-winding Ideal Transformer

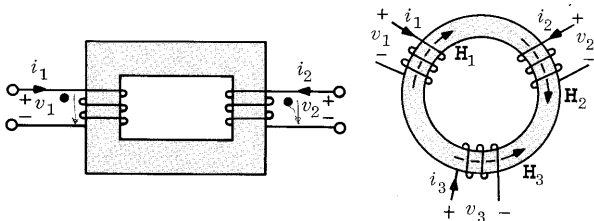


Figure: Two- and three-winding ideal transformers with the assumption of lossless operation without flux leakage.

- **Two-winding transformer:**

- **Voltage ratio:**  $\frac{v_2(t)}{v_1(t)} = \frac{\phi_2'(t)}{\phi_1'(t)} = \frac{n_2 \phi'(t)}{n_1 \phi'(t)} = \frac{n_2}{n_1}$

- **Current ratio:**  $v_1(t)i_1(t) + v_2(t)i_2(t) = 0 \Rightarrow \frac{i_2(t)}{i_1(t)} = -\frac{n_1}{n_2}$

- **Three-winding transformer:**

- **Voltage equation:**  $\frac{v_1(t)}{n_1} = \frac{v_2(t)}{n_2} = \frac{v_3(t)}{n_3}$

- **Current equation:**  $v_1(t)i_1(t) + v_2(t)i_2(t) + v_3(t)i_3(t) = 0$



# Circuit Model

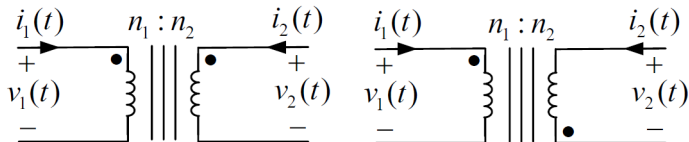


Figure: Circuit model of ideal transformers.

- Satisfied dot convention:

$$\begin{cases} \frac{v_2(t)}{v_1(t)} = \frac{n_2}{n_1} \\ \frac{i_2(t)}{i_1(t)} = -\frac{n_1}{n_2} \end{cases}$$

- Unsatisfied dot convention:

$$\begin{cases} \frac{v_2(t)}{v_1(t)} = -\frac{n_2}{n_1} \\ \frac{i_2(t)}{i_1(t)} = \frac{n_1}{n_2} \end{cases}$$

# Impedance Changing by Ideal Transformer

## Example (Impedance changing by ideal transformer)

The input impedance seen from an ideal transformer is  $Z_{in} = (n_1/n_2)^2 Z_L$ .


$$\begin{cases} \frac{V_1}{V_2} = \frac{n_1}{n_2} \\ \frac{I_1}{I_2} = -\frac{n_2}{n_1} \\ V_1 = V_s - Z_s I_1 \\ V_2 = -Z_L I_2 \end{cases}$$

$$Z_{in} = \frac{V_1}{I_1} = \frac{n_1 V_2 / n_2}{-n_2 I_2 / n_1} = \left(\frac{n_1}{n_2}\right)^2 \frac{-V_2}{I_2} = \left(\frac{n_1}{n_2}\right)^2 Z_L$$

$$Z_{eq} = \frac{V_2}{I_2} \Big|_{V_s=0} = \frac{n_2 V_1 / n_1}{-n_1 I_1 / n_2} = \left(\frac{n_2}{n_1}\right)^2 \frac{-V_1}{I_1} = \left(\frac{n_2}{n_1}\right)^2 Z_s$$

$$V_{oc} = V_2 \Big|_{I_2=0} = \frac{n_2}{n_1} V_1 = \frac{n_2}{n_1} V_s$$

$$I_{sc} = -I_2 \Big|_{V_2=0} = \frac{n_1}{n_2} \frac{V_s}{Z_s}$$

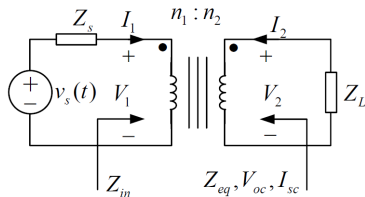

# Superposition in Ideal Transformers



## Example (Superposition in ideal transformers)

The average power consumed by the rightmost resistor is 0.0036 W.

$$\begin{cases} \frac{V_2}{-V_1} = 2 \\ \frac{I_2}{-I_1} = -\frac{1}{2} \\ V_1 + 1(h_1 + \frac{V_1 - V}{1}) = 1 \angle 0^\circ \\ 1(I_2) + V_2 - V = 0 \\ -V_1 + 1(\frac{1 - V_1}{1} - I_1) + 1(\frac{1 - V_1}{1} - I_1 - I_2) = 0 \end{cases}$$

$$\Rightarrow \begin{cases} 2V_1 + V_2 + 0I_1 + 0I_2 + 0V = 0 \\ 0V_1 + 0V_2 + I_1 - 2I_2 + 0V = 0 \\ 2V_1 + 0V_2 + I_1 + 0I_2 - V = 1 \\ 0V_1 + V_2 + 0I_1 + I_2 - V = 0 \\ -3V_1 + 0V_2 - 2I_1 - I_2 + 0V = -2 \end{cases}$$
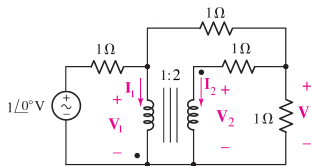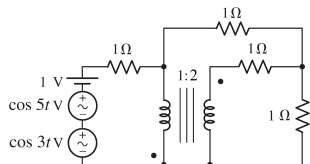
$$\Rightarrow \begin{cases} V_1 = 0.18 \\ V_2 = -0.35 \\ I_1 = 0.59 \\ I_2 = 0.29 \\ V = -0.06 \end{cases}$$



# Superposition in Ideal Transformers



## Example (Superposition in ideal transformers)

The average power consumed by the rightmost resistor is 0.0036 W.

$$\begin{aligned}v(t) &= v_1(t) + v_2(t) + v_3(t) \\ &= 0 - 0.06 \cos(3t) - 0.06 \cos(5t)\end{aligned}$$

$$p(t) = [-0.06 \cos(3t) - 0.06 \cos(5t)]^2$$
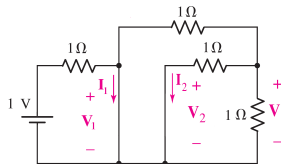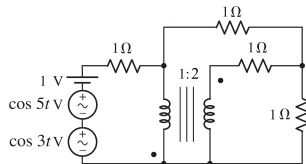
$$P = \frac{0.06^2}{2} + \frac{0.06^2}{2} = 0.0036$$



# The End