

Question 1

Consider the circuit shown in Fig. 1 that is made by interconnection of several two-ports and one-ports. Let the transmittance matrix of the two-port N_0 be $T_0 = \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix}$. Further, assume that the interconnection of the two-ports does not violate two-port current conditions.

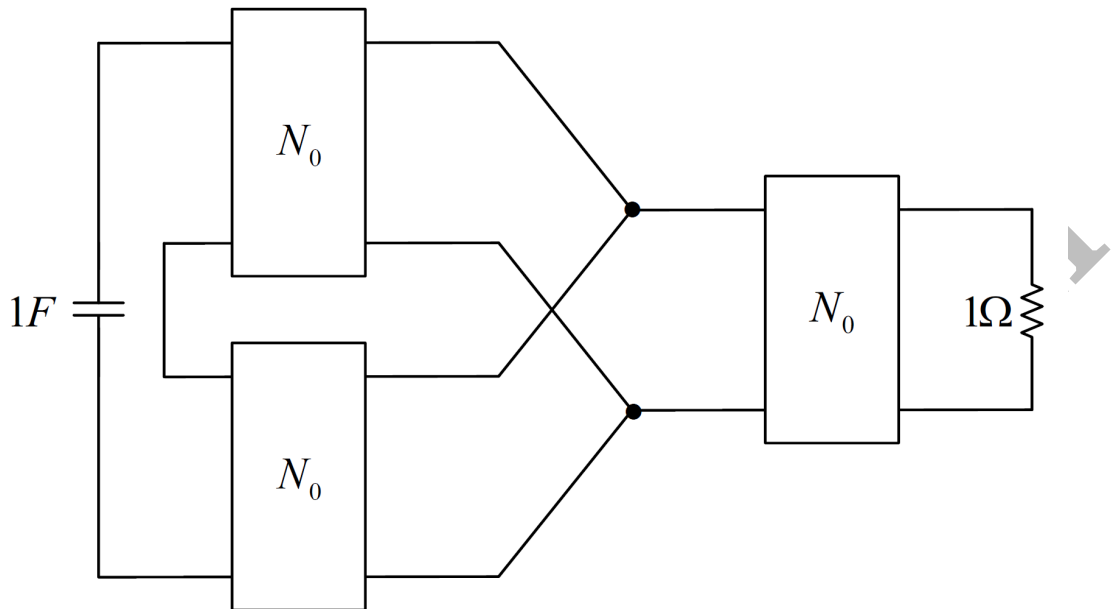


Figure 1: A circuit made from several internal two-ports.

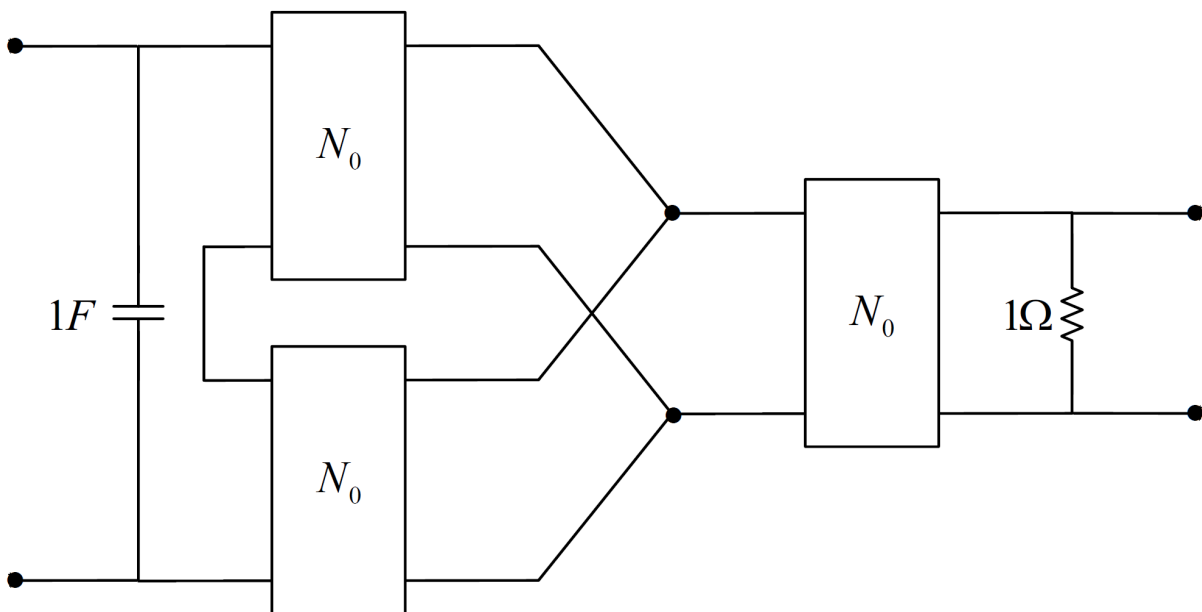


Figure 2: Two-port extension of the circuit shown in Fig. 1.

(a) Find as much as you can the natural frequencies of the circuit.

Clearly, the poles of the impedance matrix elements of the two-port shown in Fig. 2 give the natural frequencies of the circuit. So, we should find the impedance matrix of the two-port in Fig. 2.

$$\mathbf{T}_0 = \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix} \Rightarrow \mathbf{H}_0 = \begin{bmatrix} 1 & 0 \\ -1 & 1 \end{bmatrix}$$

Noting the series-parallel interconnection,

$$\mathbf{H}_1 = \mathbf{H}_0 + \mathbf{H}_0 = \begin{bmatrix} 2 & 0 \\ -2 & 2 \end{bmatrix} \Rightarrow \mathbf{T}_1 = \begin{bmatrix} 2 & 1 \\ 1 & 0.5 \end{bmatrix}$$

Now, we have a cascade interconnection.

$$\mathbf{T}_2 = \mathbf{T}_1 \mathbf{T}_0 = \begin{bmatrix} 3 & 3 \\ -1.5 & 1.5 \end{bmatrix} \Rightarrow \mathbf{Y}_2 = \begin{bmatrix} \frac{1}{2} & 0 \\ -\frac{1}{3} & 1 \end{bmatrix}$$

Finally, the desired two-port is created by adding the parallel admittances to the ports. So,

$$\mathbf{Y} = \begin{bmatrix} \frac{1}{2} + s & 0 \\ -\frac{1}{3} & 1 + 1 \end{bmatrix} \Rightarrow \mathbf{Z} = \mathbf{Y}^{-1} \begin{bmatrix} \frac{2}{2s+1} & 0 \\ \frac{1}{3(2s+1)} & \frac{s+0.5}{2s+1} \end{bmatrix}$$

So, the natural frequency is

$$2s + 1 = 0 \Rightarrow s = -0.5$$

(b) Now, consider the two-port shown in Fig. 2. The two-port is made from the circuit of Fig. 1 by adding the shown ports. How many descriptions does the two-port have? Determine which descriptions exist and which does not exist. Obtain two descriptions if the two-port has more than two descriptions.

We have already obtained the impedance and admittance descriptions in the previous part. Noting the table of "descriptions interrelation", since the element z_{12} of the impedance matrix is zero, the A'B'C'D' description does not exist. The determinant of the impedance matrix and three of its elements are nonzero. So, the two-port has 5 descriptions among which the impedance and admittance descriptions are calculated.