

Question 1

For the circuit shown in Fig. 1,

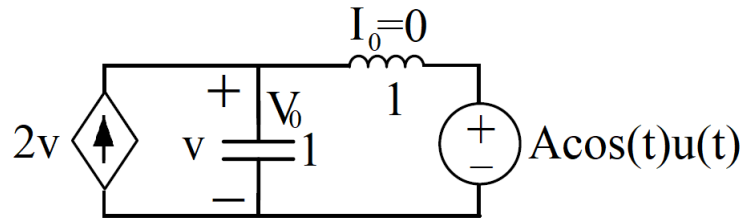


Figure 1: An LTI circuit.

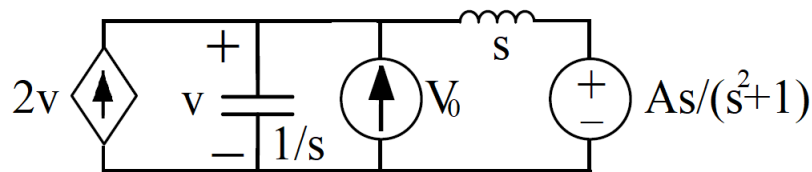


Figure 2: Laplace-domain model of the circuit shown in Fig. 1.

(a) Find the time-domain complete response of $v(t)$.

The circuit can be modeled in the Laplace domain as Fig. 2. Writing a KCL at the upper node of the capacitor,

$$\begin{aligned} \frac{V}{\frac{1}{s}} + \frac{V - A\frac{s}{s^2+1}}{s} - 2V - V_0 &= 0 \\ V(s + \frac{1}{s} - 2) &= V_0 + \frac{A}{s^2+1} \\ V &= \frac{s}{(s-1)^2} V_0 + \frac{As}{(s-1)^2(s^2+1)} \\ V &= V_0 \frac{s-1+1}{(s-1)^2} + A \left[\frac{\alpha}{s-1} + \frac{\beta}{(s-1)^2} + \frac{\gamma}{s-j} + \frac{\gamma^*}{s+j} \right] \\ V &= V_0 \frac{1}{s-1} + V_0 \frac{1}{(s-1)^2} + A \left[\frac{\alpha}{s-1} + \frac{\beta}{(s-1)^2} + \frac{\gamma}{s-j} + \frac{\gamma^*}{s+j} \right] \\ V &= V_0 \frac{1}{s-1} + V_0 \frac{1}{(s-1)^2} + A \left[\frac{0}{s-1} + \frac{\frac{1}{2}}{(s-1)^2} + \frac{\frac{j}{4}}{s-j} + \frac{-\frac{j}{4}}{s+j} \right] \\ V &= V_0 \frac{1}{s-1} + V_0 \frac{1}{(s-1)^2} + A \left[\frac{1}{2} \frac{1}{(s-1)^2} - \frac{1}{2} \frac{1}{s^2+1} \right] \end{aligned}$$

So,

$$v(t) = [V_0 e^t + V_0 t e^t + \frac{A}{2} t e^t - \frac{A}{2} \sin(t)] u(t)$$

(b) Find the sinusoidal steady state response of $v(t)$.

Since the time-domain response is not bounded as $t \rightarrow \infty$, the sinusoidal steady state does not exist.

Mohammad Hadi