

Question 1

For the circuit shown in Fig. 1, all the elements have unit values and the initial conditions are $i_2(0^-) = i_4(0^-) = v_1(0^-) = v_3(0^-) = 1$ and $i_5(0^-) = 0$.

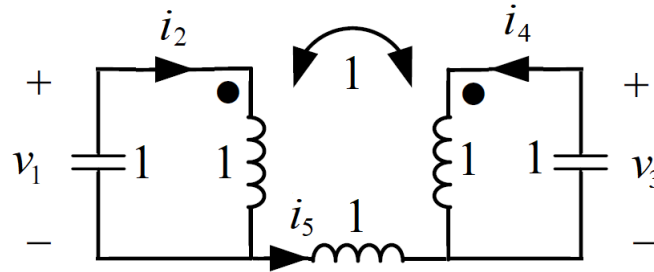


Figure 1: A coupled LTI circuit.

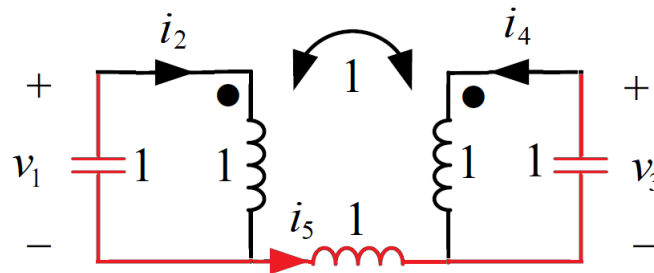


Figure 2: Network tree for the LTI circuit of Fig. 1.

(a) Find the state equations.

Considering the tree highlighted in red at Fig. 2,

$$\begin{cases} v_1'(t) + i_2(t) = 0 \\ v_3'(t) + i_4(t) = 0 \\ i_2'(t) + i_4'(t) - v_1(t) = 0 \\ i_4'(t) + i_2'(t) - v_3(t) = 0 \\ i_5(t) = 0 \end{cases}$$

Clearly,

$$v_1(t) = v_3(t) = i_2'(t) + i_4'(t)$$

and since $v_1(0^-) = v_3(0^-) = 1$,

$$i_2(t) = i_4(t) = -v_1'(t)$$

So, we have only two state equations as

$$\begin{cases} v_1'(t) = -i_2(t) \\ 2i_2'(t) = v_1(t) \end{cases} \Rightarrow \frac{d}{dt} \begin{bmatrix} v_1(t) \\ i_2(t) \end{bmatrix} = \begin{bmatrix} 0 & -1 \\ \frac{1}{2} & 0 \end{bmatrix} \begin{bmatrix} v_1(t) \\ i_2(t) \end{bmatrix}$$

(b) Solve the state equation.

$$\begin{aligned} \frac{d}{dt} \mathbf{X}(t) &= \mathbf{A} \mathbf{X}(t), \quad \mathbf{A} = \begin{bmatrix} 0 & -1 \\ \frac{1}{2} & 0 \end{bmatrix}, \quad \mathbf{X}(t) = \begin{bmatrix} v_1(t) \\ i_2(t) \end{bmatrix} \\ e^{\mathbf{A}t} &= \mathcal{L}^{-1} \{ (s\mathbf{I} - \mathbf{A})^{-1} \} = \mathcal{L}^{-1} \left\{ \begin{bmatrix} s & 1 \\ -\frac{1}{2} & s \end{bmatrix}^{-1} \right\} = \mathcal{L}^{-1} \left\{ \begin{bmatrix} \frac{s}{s^2 + \frac{1}{2}} & \frac{-1}{s^2 + \frac{1}{2}} \\ \frac{\frac{1}{2}}{s^2 + \frac{1}{2}} & \frac{s}{s^2 + \frac{1}{2}} \end{bmatrix} \right\} \\ \mathbf{X}(t) &= e^{\mathbf{A}t} \mathbf{X}_0 = \begin{bmatrix} \cos(\frac{1}{\sqrt{2}}t) & -\sqrt{2} \sin(\frac{1}{\sqrt{2}}t) \\ \frac{1}{\sqrt{2}} \sin(\frac{1}{\sqrt{2}}t) & \cos(\frac{1}{\sqrt{2}}t) \end{bmatrix} \begin{bmatrix} 1 \\ 1 \end{bmatrix} \\ \begin{cases} v_1(t) &= \cos(\frac{1}{\sqrt{2}}t) - \sqrt{2} \sin(\frac{1}{\sqrt{2}}t) \\ i_2(t) &= \frac{1}{\sqrt{2}} \sin(\frac{1}{\sqrt{2}}t) + \cos(\frac{1}{\sqrt{2}}t) \end{cases} \end{aligned}$$

(c) Find the natural frequencies of $i_5(t)$.

Clearly, $i_5(t) = 0$ and therefore, it has no natural frequency.

(d) Find the natural frequencies of the circuit.

To obtain the natural frequencies, we should analyze the circuit for an arbitrary set of initial conditions. Even for a general set of conditions,

$$\begin{cases} v_1'(t) + i_2(t) = 0 \\ v_3'(t) + i_4(t) = 0 \\ i_2'(t) + i_4'(t) - v_1(t) = 0 \\ i_4'(t) + i_2'(t) - v_3(t) = 0 \\ i_5(t) = 0 \end{cases} \Rightarrow \begin{cases} sV_1(s) - v_1(0^-) + I_2(s) = 0 \\ sV_3(s) - v_3(0^-) + I_4(s) = 0 \\ sI_2(s) - i_2(0^-) + sI_4(s) - i_4(0^-) - V_1(s) = 0 \\ sI_4(s) - i_4(0^-) + sI_2(s) - i_2(0^-) - V_3(s) = 0 \\ I_5(s) = 0 \end{cases}$$

So, $I_5(s) = 0$, $V_1(s) = V_3(s)$, and $I_4(s) = I_2(s) + v_3(0^-) - v_1(0^-)$. Note that $i_2(t)$ and $i_4(t)$ differ at least by $[v_3(0^-) - v_1(0^-)]\delta(t)$ and therefore, they still have the same natural frequencies. As a results, we have two independent state variables and two natural frequencies. The two natural frequencies can be found from the state equations in part (a) as

$$\Delta(s) = \det[s\mathbf{I} - \mathbf{A}] = \begin{vmatrix} s & 1 \\ -\frac{1}{2} & s \end{vmatrix} = s^2 + \frac{1}{2} = 0 \Rightarrow s = \pm j \frac{1}{\sqrt{2}}$$

Mohammad Hadi