

### Question 1

For the circuit shown in Fig. 1,

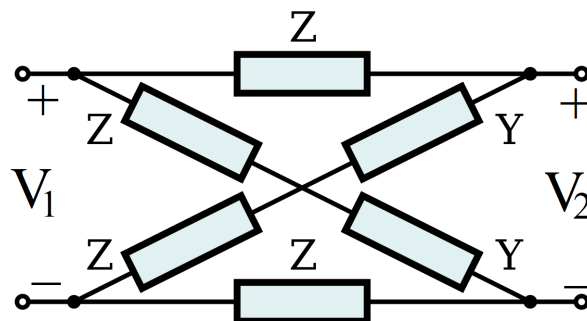


Figure 1: Lattice network.

(a) Find the transfer function  $H(s) = \frac{V_2(s)}{V_1(s)}$ , where  $Z(s)$  and  $Y(s)$  denote impedance and admittance of two single-port passive network.

$$V_2(s) = \frac{Y^{-1} + Z}{Y^{-1} + Z + Z} V_1(s) - \frac{Z}{Y^{-1} + Z + Z} V_1(s) = \frac{Y^{-1}}{Y^{-1} + 2Z} V_1(s) = \frac{1}{1 + 2ZY} V_1(s)$$

So,

$$H(s) = \frac{V_2(s)}{V_1(s)} = \frac{1}{1 + 2Z(s)Y(s)}$$

(b) Let  $Z = s + \frac{1}{s}$  and  $Y = s + \frac{1}{s}$  be a series and a parallel LC network, respectively. Find the simplified transfer function  $H(s) = \frac{V_2(s)}{V_1(s)}$  and the corresponding frequency response  $H(j\omega) = \frac{V_2(j\omega)}{V_1(j\omega)}$ .

$$H(s) = \frac{V_2(s)}{V_1(s)} = \frac{1}{1 + 2Z(s)Y(s)} = \frac{1}{1 + 2(s + \frac{1}{s})(s + \frac{1}{s})} = \frac{s^2}{2s^4 + 5s^2 + 2}$$

$$H(j\omega) = H(s)|_{s=j\omega} = \frac{-\omega^2}{2\omega^4 - 5\omega^2 + 2}$$

(c) Draw the zero-pole diagram of  $H(s)$  calculated in part (b).

The transfer function has two repeated zeros at  $z_{1,2} = 0$  and four simple imaginary conjugate poles at  $p_{1,2} = \pm j\sqrt{2}$  and  $p_{3,4} = \pm j\frac{1}{\sqrt{2}}$ . The zero-pole diagram is shown in Fig. 2.

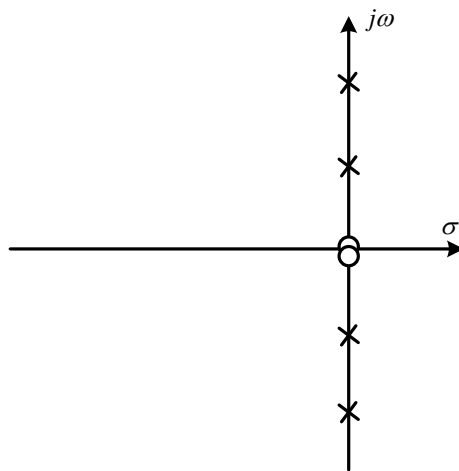


Figure 2: Zero-pole diagram.

(d) Draw the approximated amplitude and phase response of  $H(j\omega)$  calculated in part (b).

Magnitude and phase responses are shown in Fig. 3 and Fig. 4, respectively. The magnitude has two vertical asymptote lines at  $\omega = \frac{1}{\sqrt{2}}$  and  $\omega = \sqrt{2}$  due to the poles. The magnitude is zero at  $\omega = 0$  due to the zeros. The magnitude also approaches zero for  $\omega \rightarrow \infty$  since the number of poles is more than the number of zeros. The phase experiences sudden jumps at the pole frequencies  $\omega = \frac{1}{\sqrt{2}}$  and  $\omega = \sqrt{2}$ .

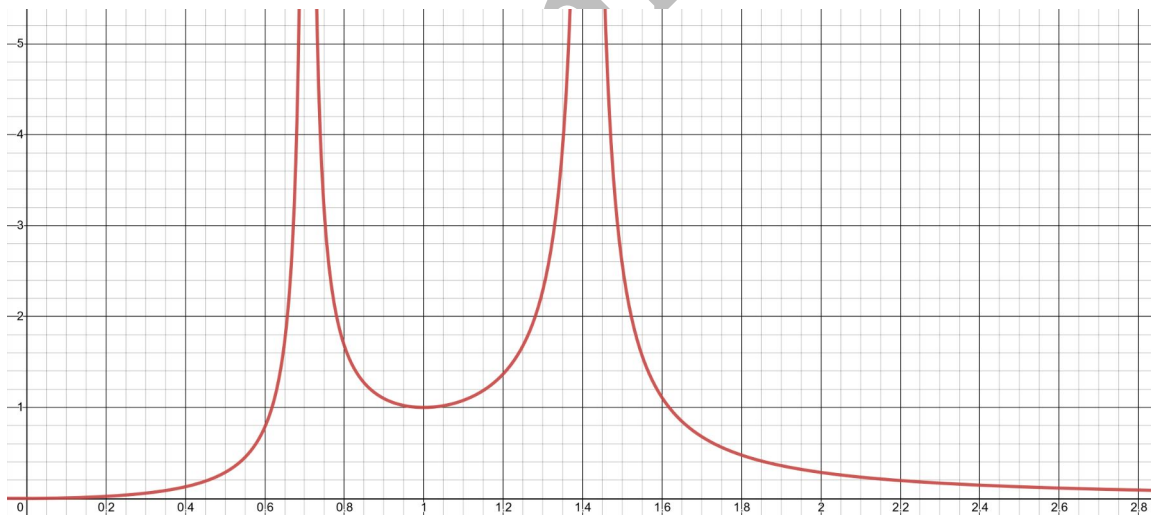


Figure 3: Magnitude response curve.

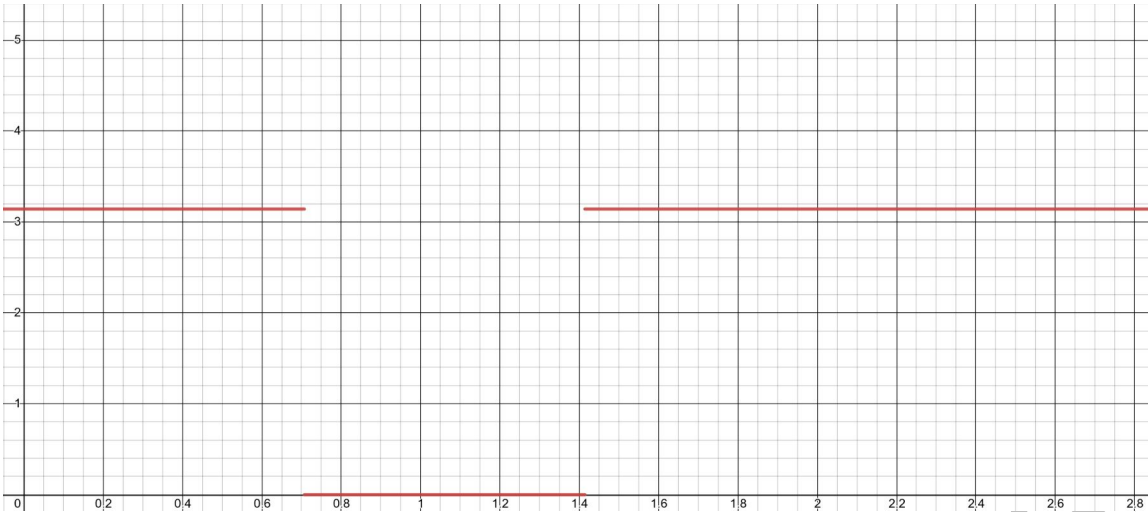


Figure 4: Phase response curve.

Mohammad Hadi