

## MATHEMATICAL QUESTIONS

### Question 1

Find the equivalent resistance of the ladder network in Fig. 1.

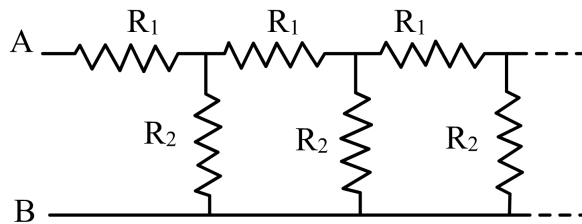


Figure 1: Ladder resistor network.

Let  $R$  be the equivalent resistor seen from the terminal point A and B. Since the ladder has infinite length, the same equivalent resistor  $R$  is seen from each vertical resistor  $R_2$ . Therefore,  $R = R_1 + R_2 || R = R_1 + R_2 R / (R_2 + R)$ . This is a second-order equation, whose acceptable solution is

$$R = \frac{R_1 + \sqrt{R_1^2 + 4R_1R_2}}{2}$$

### Question 2

How are  $\Delta$  and  $T$  resistor networks in Fig. 2 equivalent? (Hint: If two circuits are equivalent, the terminal voltages and currents must be equal.)


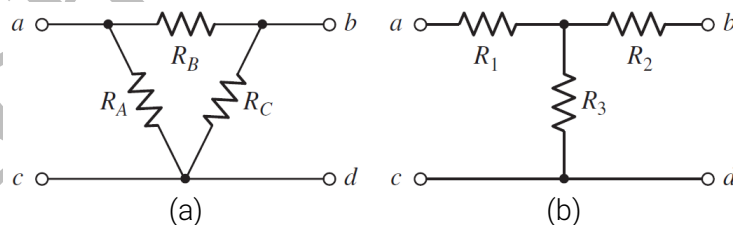


Figure 2: Two well-known equivalent resistor circuits. (a)  $\Delta$  network. (b)  $T$  network.

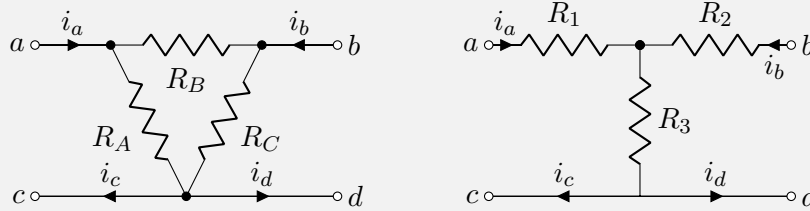

The networks should behave the same for any values of  $i_a, i_b, i_c, i_d$  and  $v_a, v_b, v_c, v_d$ . Especially, when  $i_b = 0$ , then  $v_c - v_a = i_a R_1 + i_a R_3 = i_a R_A || (R_B + R_C)$ , which results in  $R_1 + R_3 = R_A || (R_B + R_C)$ . Similarly, if  $i_a = 0$ ,  $R_2 + R_3 = R_C || (R_B + R_A)$ , and if  $i_c + i_d = 0$ ,  $R_1 + R_2 = R_B || (R_C + R_A)$ . These equations lead to

$$R_1 = \frac{R_A R_B}{R_A + R_B + R_C}$$

$$R_2 = \frac{R_B R_C}{R_A + R_B + R_C}$$

, and

$$R_3 = \frac{R_A R_C}{R_A + R_B + R_C}$$

. Further,

$$R_A = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

,

$$R_B = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

, and

$$R_C = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

### Question 3

Determine the Thevenin equivalent seen by  $-j10 \Omega$  impedance of Fig. 3 and use this to compute  $V_1$ .

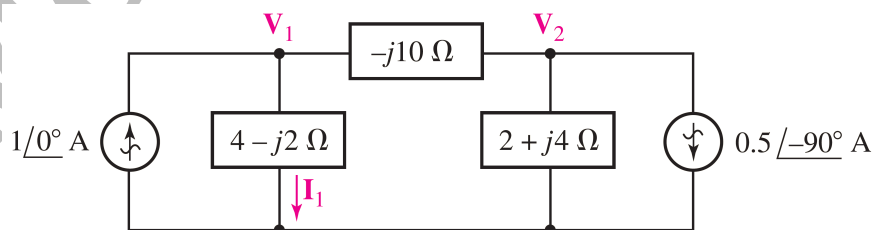


Figure 3: A circuit for which Thevenin equivalent seen by  $-j10 \Omega$  impedance is desired.

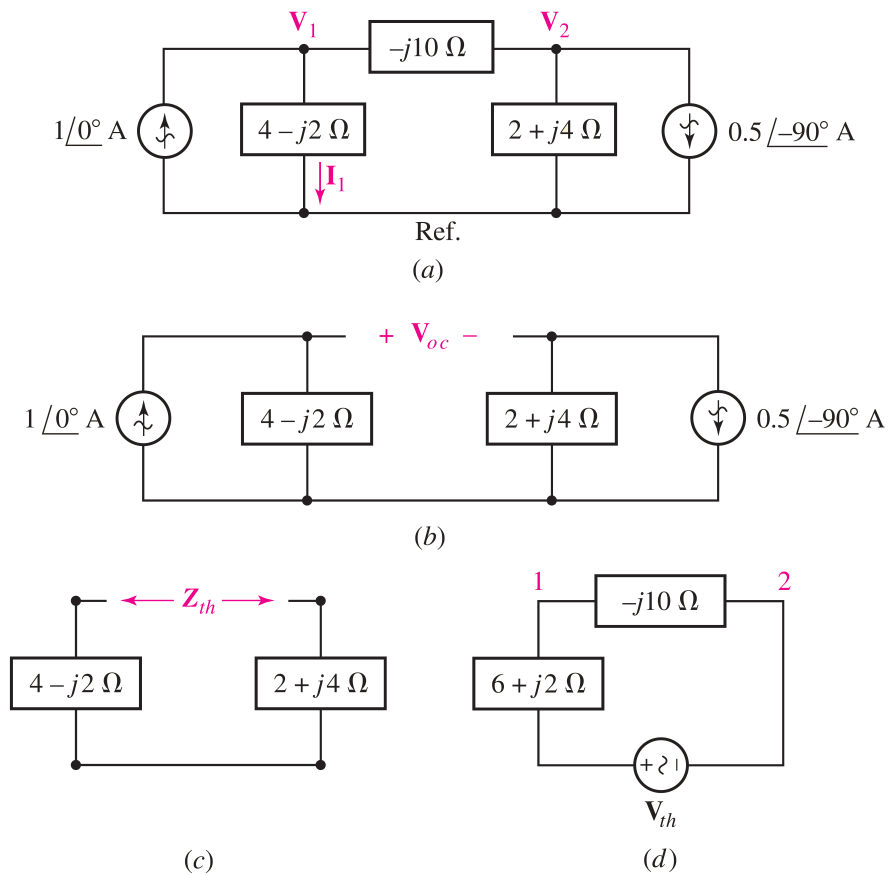


Figure 4: (a) The Thevenin equivalent seen by the  $-j10 \Omega$  impedance is desired. (b)  $V_{oc}$  is defined. (c)  $Z_{th}$  is defined. (d) The circuit is redrawn using the Thevenin equivalent.

The open-circuit voltage, defined in Fig. 4(b), is

$$V_{oc} = (1 \angle 0^\circ)(4 - j2) - (-0.5 \angle -90^\circ)(2 + j4) = 4 - j2 + 2 - j1 = 6 - j3 \text{ V}$$

. The impedance of the inactive circuit of Fig. 4(c) as viewed from the load terminals is simply the sum of the two remaining impedances. Hence,

$$Z_{th} = 6 + j2 \Omega$$

. When we reconnect the circuit as in Fig. 4(d), the current directed from node 1 toward node 2 through the  $-j10 \Omega$  load is

$$I_{12} = \frac{6 - j3}{6 + j2 - j10} = 0.6 + j0.3 \text{ A}$$

. We now know the current flowing through the  $-j10 \Omega$  impedance of Fig. 4(a). Note that we are unable to compute  $V_1$  using the circuit of Fig. 4(d) as the reference node no longer exists. Returning to the original circuit, then, and subtracting the  $0.6 + j0.3$  A current from the left source current, the downward current through the  $4 - j2 \Omega$  branch is found

$$I_1 = 1 - 0.6 - j0.3 = 0.4 - j0.3 \text{ A}$$

and, thus,

$$V_1 = (4 - j2)(0.4 - j03) = 1 - j2 \text{ V}$$

### Question 4

Household electrical voltages are typically quoted as 220 V in Iran. However, these values do not represent the peak ac voltage. Rather, they represent what is known as the root mean square of the voltage, defined as

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V_m^2 \cos^2(\omega t) dt}$$

where  $T = \frac{1}{f}$  is the period of the waveform,  $V_m$  is the peak voltage, and  $\omega = 2\pi f$  is the waveform angular frequency, where  $f = 50 \text{ Hz}$  in Iran.

(a) Perform the indicated integration, and show that for a sinusoidal voltage  $V_{rms} = \frac{V_m}{\sqrt{2}}$ .

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V_m^2 \cos^2(\omega t) dt} = \sqrt{\frac{1}{T} \int_0^T V_m^2 \frac{1 + \cos(2\omega t)}{2} dt} = \sqrt{\frac{1}{T} V_m^2 \frac{T+0}{2}} = \frac{V_m}{\sqrt{2}}$$

(b) Compute the peak voltages corresponding to the rms voltage 220 V.

$$V_m = 220\sqrt{2} = 311.13 \text{ V}$$

### Question 5

Consider the circuit shown in Fig. 5, where  $V_{ref}$  is provided by a regulated voltage source. Show that the circuit can act like a current source and find the constant current  $I_s$  flowing to the resistive load  $R_L$ .

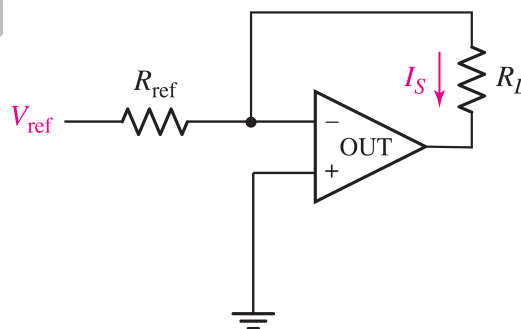


Figure 5: An Op Amp-based current source.

The voltage at the inputs of the Op Amp is 0. A KCL at the inverting leg of the Op Amp results in  $\frac{V_{ref}}{R_{ref}} = I_S$ . Clearly, the constant current  $I_S$  does not depend on  $R_L$  and flows through the load resistor  $R_L$ , regardless of its value.

### Question 6

Find the differential equation relating  $i_x(t)$  to  $v_s(t)$  for the circuit displayed in Fig. 6 and obtain the corresponding impulse and step responses.

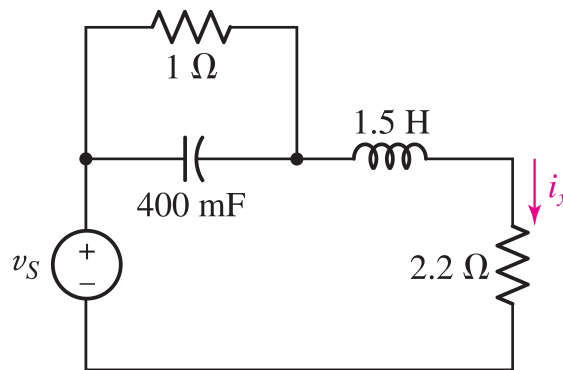


Figure 6: A circuit whose impulse and step responses are intended.

$$v_C(t) + 1.5i'_x(t) + 2.2i_x(t) = v_s(t), \quad i_x(t) = \frac{v_C(t)}{1} + 0.4v'_C(t) = v_C(t) + 0.4v'_C(t)$$

$$i_x(t) = (v_s(t) - 1.5i'_x(t) - 2.2i_x(t)) + 0.4(v_s(t) - 1.5i'_x(t) - 2.2i_x(t))'$$

$$i_x(t) = v_s(t) - 1.5i'_x(t) - 2.2i_x(t) + 0.4v'_s(t) - 0.6i''_x(t) - 0.88i'_x(t)$$

$$i''_x(t) + 3.97i'_x(t) + 5.33i_x(t) = 1.67v_s(t) + 0.67v'_s(t)$$

When the circuit is driven with  $v_s(t) = \delta(t)$ , the impulse response is the solution of

$$h''(t) + 3.97h'(t) + 5.33h(t) = 1.67\delta(t) + 0.67\delta'(t)$$

The characteristic equation of the corresponding homogeneous differential equation is  $s^2 + 3.97s + 5.33 = 0$  with the roots  $s_1 = -1.985 + j1.179$  and  $s_2 = -1.985 - j1.179$ . After  $t > 0$ , the differential equation is identical with its homogeneous form

$$h''(t) + 3.97h'(t) + 5.33h(t) = 0$$

because  $\delta(t) = \delta'(t) = 0$  for  $t > 0$ . Since, the characteristic equation has two complex conjugate roots, for  $t > 0$ , the solution is

$$h(t) = (B_1e^{-1.985t+j1.179t} + B_2e^{-1.985t-j1.179t})u(t)$$

or equivalently,

$$h(t) = e^{-1.985t}(A_1 \cos(1.179t) + A_2 \sin(1.179t))u(t)$$

. At  $t = 0$ , this solution should make both sides of the equation balanced. So,

$$h''(t) + 3.97h'(t) + 5.33h(t) = 1.67\delta(t) + 0.67\delta'(t)$$

. We have,

$$\begin{aligned} h'(t) &= \left[ -1.985e^{-1.985t}(A_1 \cos(1.179t) + A_2 \sin(1.179t)) \right. \\ &\quad \left. + e^{-1.985t}(-1.179A_1 \sin(1.179t) + 1.179A_2 \cos(1.179t)) \right] u(t) + A_1 \delta(t) \\ h''(t) &= \left[ 2.5504A_1 e^{-1.985t} \cos(1.179t) + 4.681A_1 e^{-1.985t} \sin(1.179t) \right. \\ &\quad \left. + 2.5504A_2 e^{-1.985t} \sin(1.179t) - 4.681A_2 e^{-1.985t} \cos(1.179t) \right] u(t) \\ &\quad + (-1.985A_1 + 1.179A_2)\delta(t) + A_1 \delta'(t) \end{aligned}$$

Substituting the derivatives in the differential equation,

$$(-1.985A_1 + 1.179A_2)\delta(t) + A_1 \delta'(t) + 3.97A_1 \delta(t) = 1.67\delta(t) + 0.67\delta'(t)$$

Therefore,

$$\Rightarrow \begin{cases} A_1 = 0.67 \\ 1.985A_1 + 1.179A_2 = 1.67 \end{cases} \Rightarrow \begin{cases} A_1 = 0.67 \\ A_2 = 0.29 \end{cases}$$

. Finally,

$$h(t) = e^{-1.985t}(0.67 \cos(1.179t) + 0.29 \sin(1.179t))u(t)$$

. Further,

$$s(t) = \int_{-\infty}^t h(\tau) d\tau = [0.0402e^{-1.985t} \sin(1.179t) - 0.3137e^{-1.985t} \cos(1.179t) + 0.3137]u(t)$$

## Question 7

Consider a series RL circuit driven with the voltage source  $v(t)$ , where the loop current  $i(t)$  should be calculated.

(a) Find the zero-input response if the initial current is  $i(0) = I_0$ .

$$Li'(t) + Ri(t) = 0, \quad i(0) = I_0$$

, which is a homogeneous first-order equation with the solution

$$i(t) = I_0 e^{-\frac{R}{L}t}$$

(b) Find the step response.

$$Li'(t) + Ri(t) = u(t), \quad i(0) = 0$$

, which is a non-homogeneous first-order equation with the solution

$$s(t) = i(t) = \frac{1}{R}(1 - e^{-\frac{R}{L}t})u(t)$$

(c) Find the impulse response.

$$h(t) = s'(t) = \frac{1}{R}(1 - e^{-\frac{R}{L}t})\delta(t) + \frac{1}{L}e^{-\frac{R}{L}t}u(t) = \frac{1}{L}e^{-\frac{R}{L}t}u(t)$$

(d) Find the zero-state response if  $v(t) = V_0e^{-t}u(t)$ .

At first, let evaluate  $e^{-\alpha t}u(t) * e^{-\beta t}u(t)$ . Assuming  $\alpha \neq \beta$ ,

$$\begin{aligned} e^{-\alpha t}u(t) * e^{-\beta t}u(t) &= \int_{-\infty}^{\infty} e^{-\alpha\tau}u(\tau)e^{-\beta(t-\tau)}u(t-\tau)d\tau = e^{-\beta t}u(t) \int_0^t e^{(\beta-\alpha)\tau}d\tau \\ &= u(t)e^{-\beta t} \frac{1}{\beta-\alpha} e^{(\beta-\alpha)\tau} \Big|_0^t = u(t) \frac{1}{\beta-\alpha} e^{-\beta t} (e^{(\beta-\alpha)t} - 1) = \frac{1}{\beta-\alpha} (e^{-\alpha t} - e^{-\beta t})u(t) \end{aligned}$$

. For  $\alpha = \beta$ ,

$$e^{-\alpha t}u(t) * e^{-\alpha t}u(t) = \int_{-\infty}^{\infty} e^{-\alpha\tau}u(\tau)e^{-\alpha(t-\tau)}u(t-\tau)d\tau = e^{-\alpha t}u(t) \int_0^t d\tau = te^{-\alpha t}u(t)$$

Now,

$$i(t) = V_0e^{-t}u(t) * \frac{1}{L}e^{-\frac{R}{L}t}u(t) = \frac{V_0}{L}e^{-t}u(t) * e^{-\frac{R}{L}t}u(t)$$

. If  $R \neq L$ ,

$$i(t) = \frac{V_0}{L} \frac{1}{\frac{R}{L} - 1} (e^{-t} - e^{-\frac{R}{L}t})u(t) = \frac{V_0}{R - L} (e^{-t} - e^{-\frac{R}{L}t})u(t)$$

. When  $R = L$ ,

$$i(t) = \frac{V_0}{L} te^{-t}u(t)$$

(e) Find the complete response if  $v(t) = V_0e^{-t}u(t)$  and  $i(0) = I_0$ .

If  $R \neq L$ ,

$$i(t) = I_0 e^{-\frac{R}{L}t} + \frac{V_0}{R-L} (e^{-t} - e^{-\frac{R}{L}t}) u(t)$$

. When  $R = L$ ,

$$i(t) = I_0 e^{-t} + \frac{V_0}{L} t e^{-t} u(t)$$

(f) Find the complete response if  $v(t) = V_0 \cos(\omega t + \theta) u(t)$  and  $i(0) = I_0$ . How does the complete response relate to the sinusoidal steady state response?

Mohammad Hadi



The zero-input, zero-state impulse, and zero-state step responses do not change by altering the input voltage. So, when the input is  $v(t) = V_0 \cos(\omega t + \theta)$ , the zero-state response equals

$$\begin{aligned} v(t) * h(t) &= V_0 \cos(\omega t + \theta) u(t) * \frac{1}{L} e^{-\frac{R}{L}t} u(t) = \frac{V_0}{L} \left[ \frac{e^{j(\omega t + \theta)} + e^{-j(\omega t + \theta)}}{2} \right] u(t) * e^{-\frac{R}{L}t} u(t) \\ &= \frac{V_0}{2L} \left[ e^{j\theta} e^{j\omega t} u(t) * e^{-\frac{R}{L}t} u(t) + e^{-j\theta} e^{-j\omega t} u(t) * e^{-\frac{R}{L}t} u(t) \right] \\ &= \frac{V_0}{2L} \left[ e^{j\theta} \frac{1}{\frac{R}{L} + j\omega} (e^{j\omega t} - e^{-\frac{R}{L}t}) u(t) + e^{-j\theta} \frac{1}{\frac{R}{L} - j\omega} (e^{-j\omega t} - e^{-\frac{R}{L}t}) u(t) \right] \\ &= \frac{V_0}{2L} u(t) \left[ \frac{1}{\frac{R}{L} + j\omega} e^{j(\omega t + \theta)} + \frac{1}{\frac{R}{L} - j\omega} e^{-j(\omega t + \theta)} \right] - \frac{V_0}{2L} u(t) e^{-\frac{R}{L}t} \left[ \frac{1}{\frac{R}{L} + j\omega} e^{j\theta} + \frac{1}{\frac{R}{L} - j\omega} e^{-j\theta} \right] \\ &= \frac{V_0}{2L} u(t) \times 2\text{Re} \left\{ \frac{1}{\frac{R}{L} + j\omega} e^{j(\omega t + \theta)} \right\} - \frac{V_0}{2L} u(t) e^{-\frac{R}{L}t} \times 2\text{Re} \left\{ \frac{1}{\frac{R}{L} + j\omega} e^{j\theta} \right\} \\ &= \frac{V_0}{L} u(t) \times \text{Re} \left\{ \frac{1}{\sqrt{\frac{R^2}{L^2} + \omega^2}} e^{j(\omega t + \theta - \tan^{-1}(\frac{\omega L}{R}))} \right\} - \frac{V_0}{L} u(t) e^{-\frac{R}{L}t} \times \text{Re} \left\{ \frac{1}{\sqrt{\frac{R^2}{L^2} + \omega^2}} e^{j(\theta - \tan^{-1}(\frac{\omega L}{R}))} \right\} \\ &= \frac{V_0}{L} u(t) \frac{1}{\sqrt{\frac{R^2}{L^2} + \omega^2}} \cos(\omega t + \theta - \tan^{-1}(\frac{\omega L}{R})) - \frac{V_0}{L} u(t) e^{-\frac{R}{L}t} \frac{1}{\sqrt{\frac{R^2}{L^2} + \omega^2}} \cos(\theta - \tan^{-1}(\frac{\omega L}{R})) \\ &= \frac{V_0}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \theta - \tan^{-1}(\frac{\omega L}{R})) u(t) - \frac{V_0}{\sqrt{R^2 + \omega^2 L^2}} e^{-\frac{R}{L}t} \cos(\theta - \tan^{-1}(\frac{\omega L}{R})) u(t) \end{aligned}$$

Finally, the complete solution equals

$$\begin{aligned} i(t) &= I_0 e^{-\frac{R}{L}t} + \\ &\frac{V_0}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \theta - \tan^{-1}(\frac{\omega L}{R})) u(t) - \frac{V_0}{\sqrt{R^2 + \omega^2 L^2}} e^{-\frac{R}{L}t} \cos(\theta - \tan^{-1}(\frac{\omega L}{R})) u(t) \end{aligned}$$

. When the transients die at  $t \rightarrow \infty$ , the complete response is equal to

$$i(t) = \frac{V_0}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \theta - \tan^{-1}(\frac{\omega L}{R})) u(t)$$

, which is exactly the steady state sinusoidal current. In a better presentation,

$$i(t) = \left| \frac{V_0 e^{j\theta}}{R + j\omega L} \right| \cos(\omega t + \angle \left[ \frac{V_0 e^{j\theta}}{R + j\omega L} \right]) u(t)$$

, where  $\frac{V_0 e^{j\theta}}{R + j\omega L}$  is the phasor of the current.

---

## SOFTWARE QUESTIONS

---



---

## BONUS QUESTIONS

---

### Question 8

Return your answers by filling the  $\LaTeX$  template of the assignment.

Mohammad Hadi