

MATHEMATICAL QUESTIONS

Question 1

For the circuit of Fig. 1,


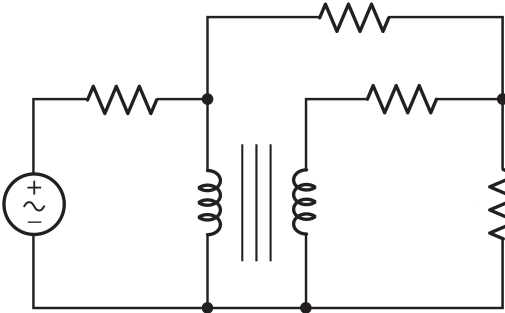


Figure 1: A sample circuit.

(a) Draw the circuit graph.

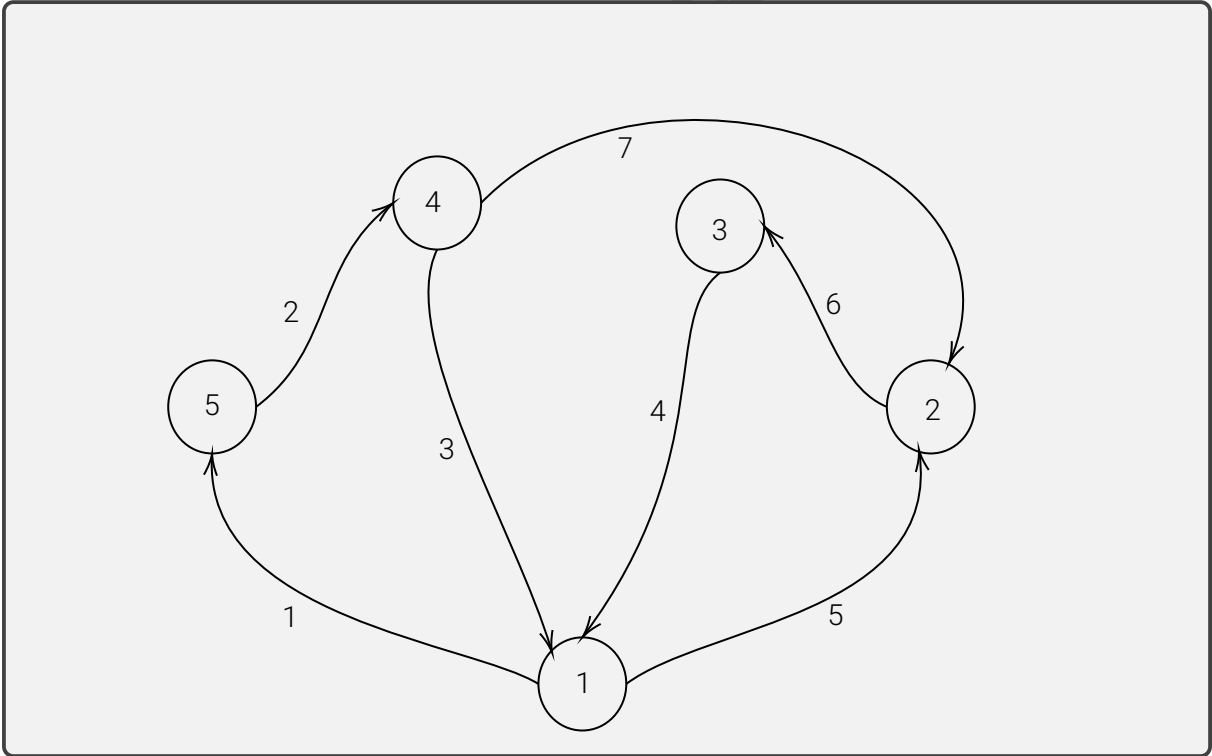

(b) Find a reduced node-to-branch incident matrix **A**.

Selecting node 5 as the reference node,


$$A = \begin{bmatrix} 1 & 0 & -1 & -1 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & -1 & 1 & -1 \\ 0 & 0 & 0 & 1 & 0 & -1 & 0 \\ 0 & -1 & 1 & 0 & 0 & 0 & 1 \end{bmatrix}$$

(c) Find a reduced mesh-to-branch incident matrix **M**.

$$M = \begin{bmatrix} 1 & 1 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & -1 & 1 & 0 & 1 & 1 \\ 0 & 0 & 0 & -1 & -1 & -1 & 0 \end{bmatrix}$$

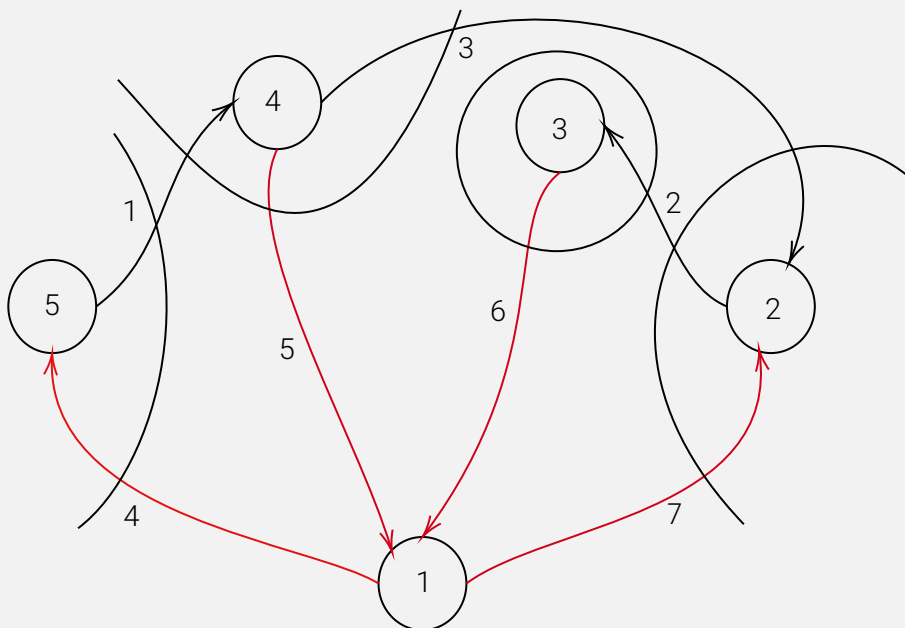(d) Find a fundamental cut-set matrix **Q**.


First we choose a tree that includes branches 1,3,4, and 5, and then, determine a cut-set for each tree branch.



The associative fundamental cut-set matrix **Q** is


$$Q = \begin{bmatrix} -1 & 0 & 0 & 1 & 0 & 0 & 0 \\ -1 & 0 & 1 & 0 & 1 & 0 & 0 \\ 0 & -1 & 0 & 0 & 0 & 1 & 0 \\ 0 & -1 & 1 & 0 & 0 & 0 & 1 \end{bmatrix}$$

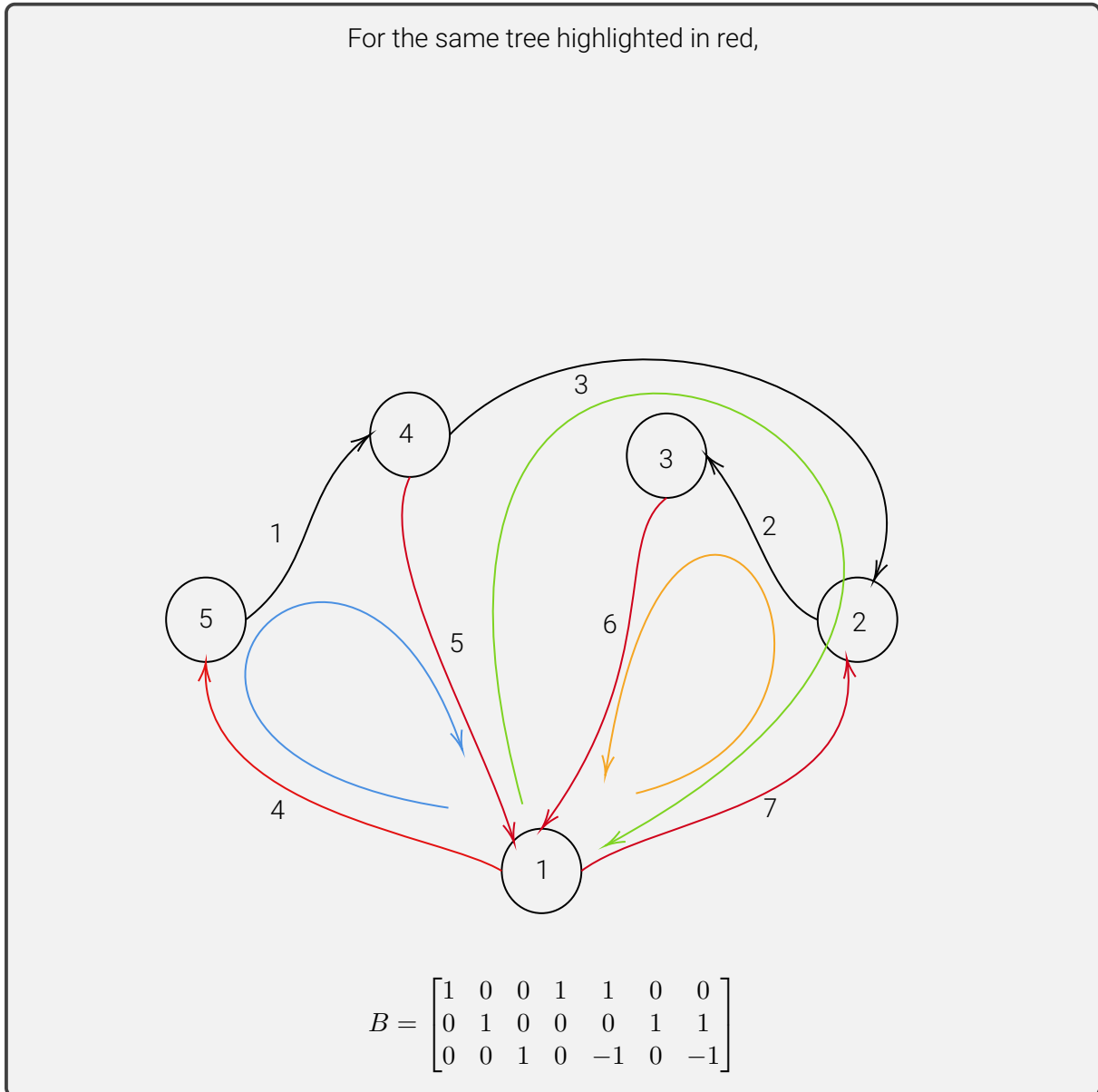(e) Find a fundamental loop matrix  $\mathbf{B}$ .



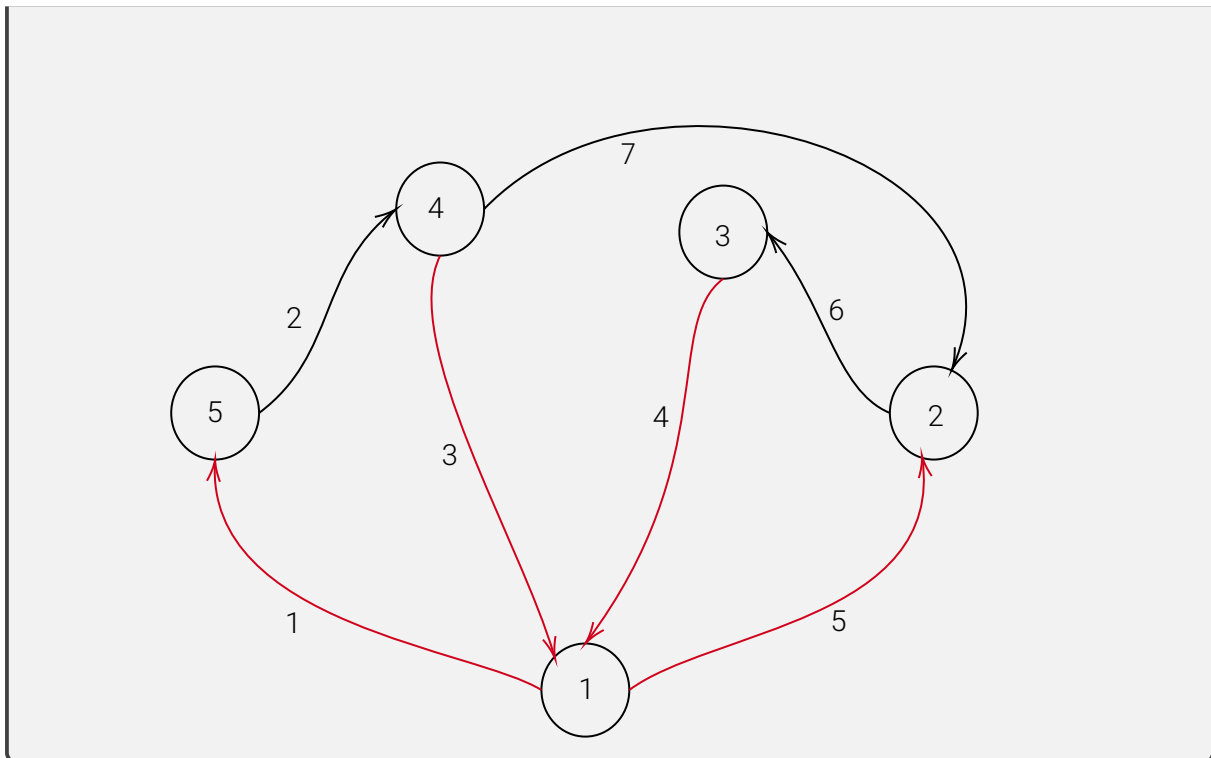
(f) Can you introduce a tree for which the matrices  $\mathbf{A}$  and  $\mathbf{Q}$  are equal?

In matrix  $\mathbf{A}$ , rows are related to nodes of the graph and columns are related to branches in an arbitrary order. In matrix  $\mathbf{Q}$ , rows are related to cut-sets and columns are related to branches. So if we want matrices  $\mathbf{A}$  and  $\mathbf{Q}$  equal, the set of branches that are connected to each node should be a cut-set. Therefore, every node except one of them should be connected to only one branch of tree, so we need a node in graph that is connected to all of the other nodes. Node 1 is the desired node and the desired tree is the set of branches  $\{1, 3, 4, 5\}$  shown below.



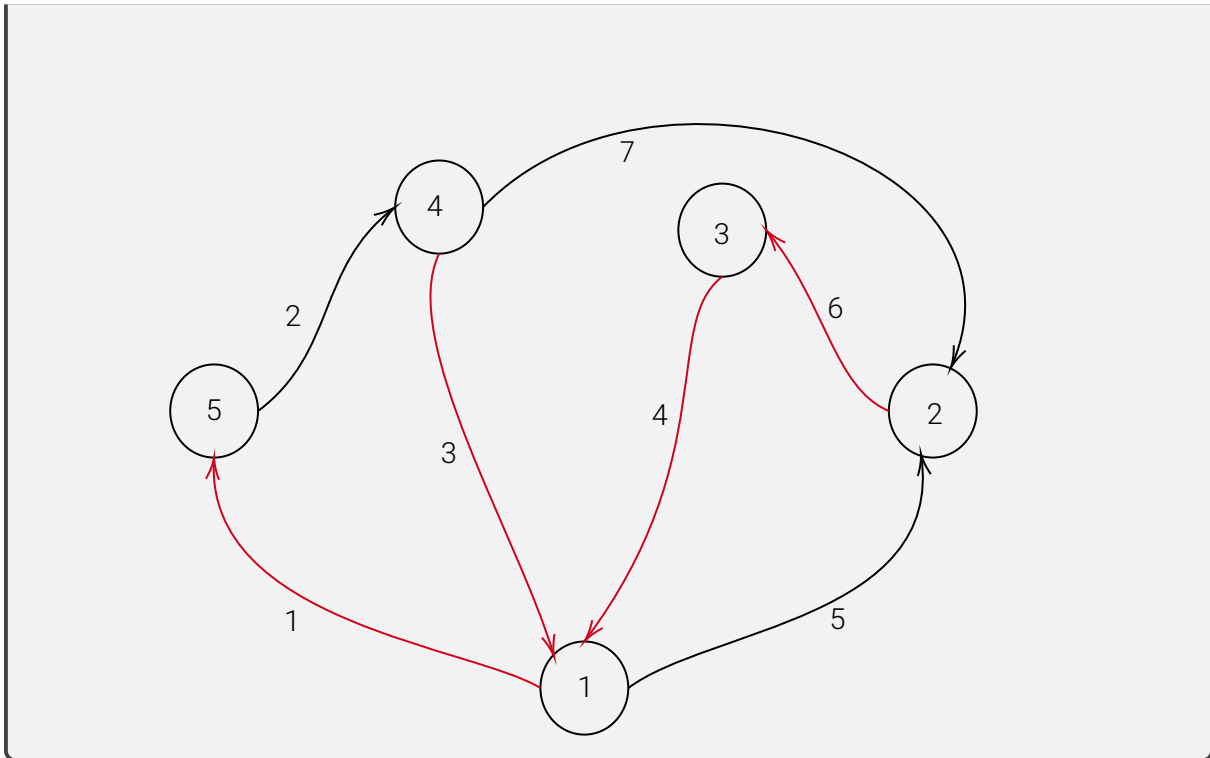(g) Can you introduce a tree for which the matrices  $\mathbf{M}$  and  $\mathbf{B}$  are equal?

In matrix  $M$ , rows are related to meshes of the graph and columns are related to branches in an arbitrary order. In matrix  $B$ , rows are related to loops and columns are related to branches. So, if we want matrices  $B$  and  $M$  equal, every mesh should be a loop. Therefore, every mesh should include only one link and other branches of it should belong to tree. So, the desired tree can be the set of branches  $\{1, 3, 4, 6\}$  in the graph below.



## Question 2

Prove that the branch voltages of a tree of a given circuit graph provide a set of linearly independent voltages.

Assume that some tree branch voltages are linearly dependent. Then, they should provide a KVL around a loop. This contradicts with the fact that there is no loop over tree.

## Question 3

The circuit of Fig. 2 includes LTI resistors and a voltage source. In an experimental measurement, we set  $R_2 = 1 \Omega$ , and find that  $v_1 = 4 \text{ V}$ ,  $i_1 = 1 \text{ A}$ , and  $v_2 = 1 \text{ V}$ . In a second measurement, we set  $R_2 = 2 \Omega$ , and find that  $v_1 = 2 \text{ V}$  and  $i_1 = 1.2 \text{ A}$ , but we forget to measure  $v_2$ . Can you determine the value of  $v_2$  in the second experiment? The inside of the sub-circuit  $N$  remains unchanged for the two experiments.

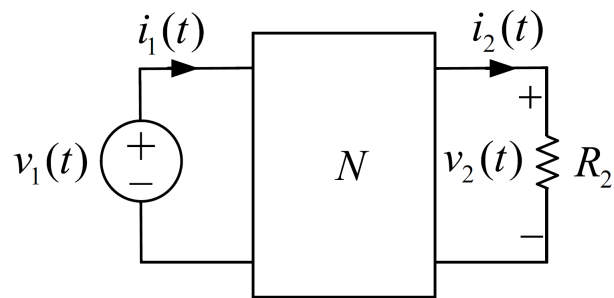


Figure 2: An LTI resistive network with a driving voltage source.

According to the Tellegan's theorem and resistive nature of the network,

$$\begin{aligned} \Rightarrow -v_1 \hat{i}_1 + \sum_k v_k \hat{i}_k + v_2 \hat{i}_2 &= -\hat{v}_1 i_1 + \sum_k \hat{v}_k i_k + \hat{v}_2 i_2 = 0 \\ \Rightarrow -v_1 \hat{i}_1 + \sum_k R_k \hat{i}_k \hat{i}_k + v_2 \hat{i}_2 &= -\hat{v}_1 i_1 + \sum_k R_k \hat{i}_k i_k + \hat{v}_2 i_2 = 0 \end{aligned}$$

So,

$$-v_1 \hat{i}_1 + v_2 \hat{i}_2 = -\hat{v}_1 i_1 + \hat{v}_2 i_2$$

First measurement yields

$$v_1 = 4 \text{ V} \quad i_1 = 1 \text{ A} \quad v_2 = 1 \text{ V} \quad i_2 = \frac{v_2}{R_2} = 1 \text{ A}$$

while for the second measurement,

$$\hat{v}_1 = 2 \text{ V} \quad \hat{i}_1 = 1.2 \text{ A} \quad \hat{R}_2 = 2 \Omega \quad i_2 = \frac{\hat{v}_2}{\hat{R}_2} = \frac{\hat{v}_2}{2}$$

Place the parameters:

$$-4 \times 1.2 + 1 \times \frac{\hat{v}_2}{2} = -2 \times 1 + 1 \times \hat{v}_2 \Rightarrow \hat{v}_2 = -5.6 \text{ V}$$

#### Question 4

Draw the dual circuit of the circuit shown in Fig. 3 and write at least two dual circuit equations for the two circuits.


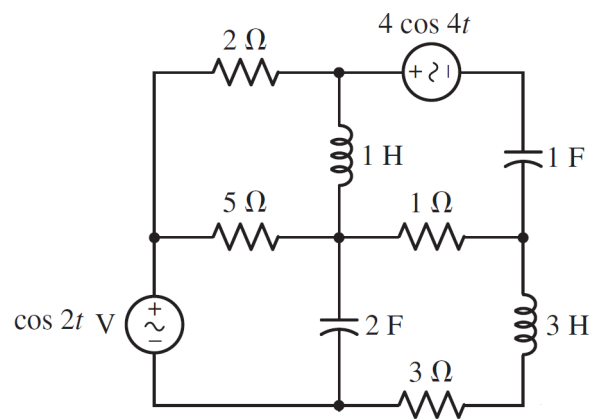


Figure 3: A circuit for which the dual network is required.

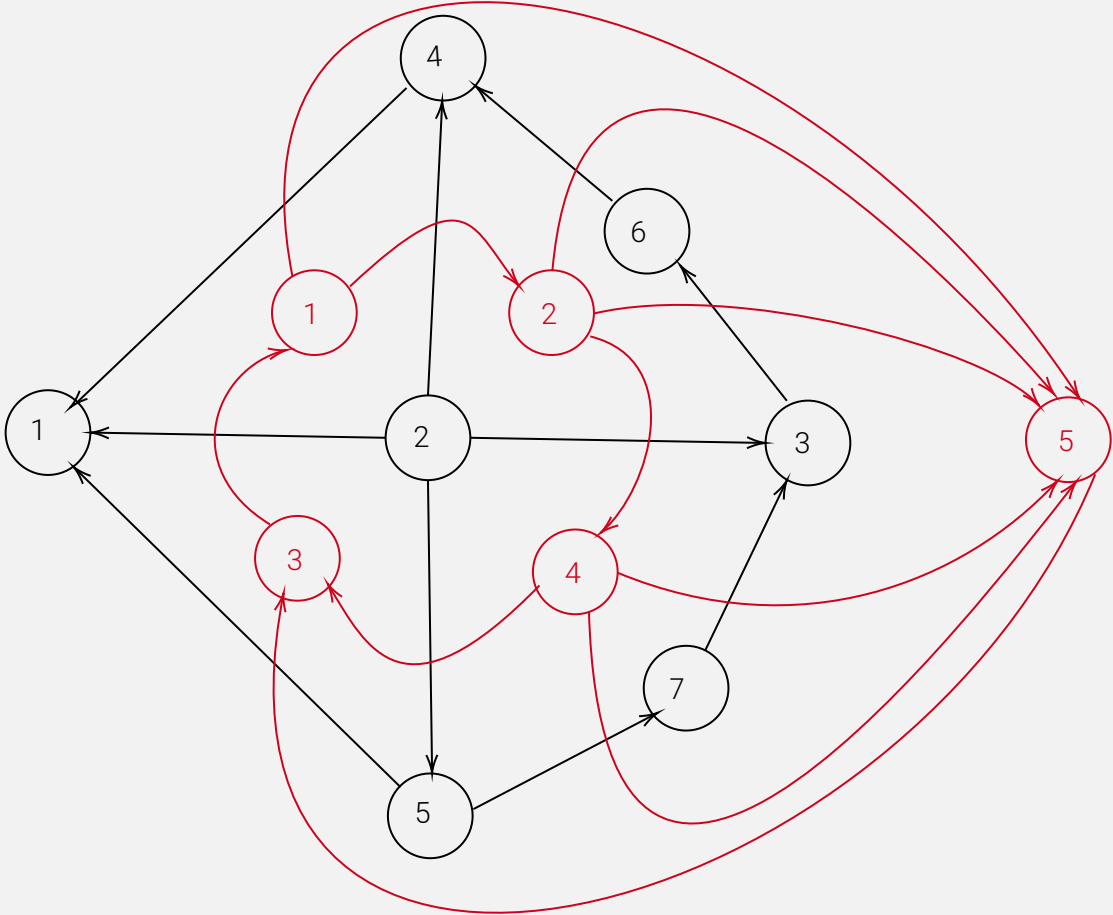
The circuit graph and its corresponding dual graph are as follows.



The dual circuit is drawn below.

MIC



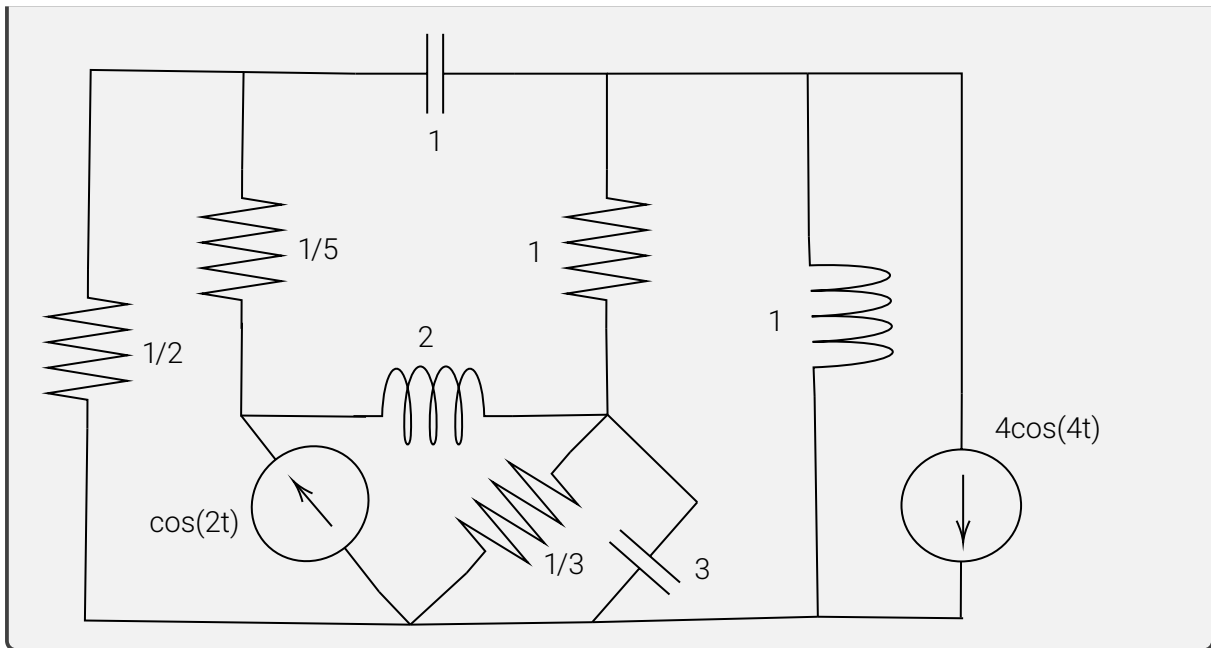

### Question 5

Write the KCL and KVL equations corresponding to the fundamental cut sets and loops of the circuit graph shown in Fig. 4 having the highlighted tree.

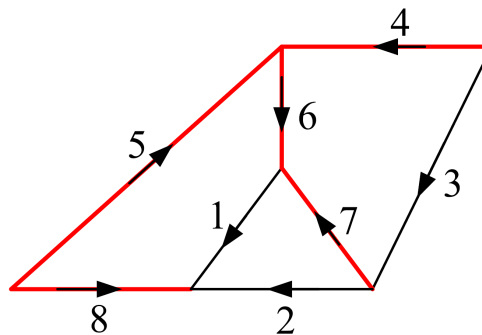


Figure 4: A circuit graph and one of its associated trees.

According to Fig. 5, we have  
 KCL:

$$Q = \begin{bmatrix} 0 & 0 & 1 & 1 & 0 & 0 & 0 & 0 \\ -1 & -1 & 0 & 0 & 1 & 0 & 0 & 0 \\ -1 & -1 & 1 & 0 & 0 & 1 & 0 & 0 \\ 0 & 1 & -1 & 0 & 0 & 0 & 1 & 0 \\ 1 & 1 & 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix}, \quad j = \begin{bmatrix} j_1 \\ j_2 \\ j_3 \\ j_4 \\ j_5 \\ j_6 \\ j_7 \\ j_8 \end{bmatrix}, \quad Qj = 0, \quad \begin{cases} j_3 + j_4 = 0 \\ -j_1 - j_2 + j_5 = 0 \\ -j_1 - j_2 + j_3 + j_6 = 0 \\ j_2 - j_3 + j_7 = 0 \\ j_1 + j_2 + j_8 = 0 \end{cases}$$

$$Q^T = \begin{bmatrix} 0 & -1 & -1 & 0 & 1 \\ 0 & -1 & -1 & 1 & 1 \\ 1 & 0 & 1 & -1 & 0 \\ 1 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 1 \end{bmatrix}, \quad \mathbf{e} = \begin{bmatrix} e_1 \\ e_2 \\ e_3 \\ e_4 \\ e_5 \end{bmatrix}, \quad \mathbf{v} = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \\ v_7 \\ v_8 \end{bmatrix}$$

$$\mathbf{v} = Q^T \mathbf{e}, \quad \begin{cases} v_1 = -e_2 - e_3 + e_5 \\ v_2 = -e_2 - e_3 + e_4 + e_5 \\ v_3 = e_1 + e_3 - e_4 \\ v_4 = e_1 \\ v_5 = e_2 \\ v_6 = e_3 \\ v_7 = e_4 \\ v_8 = e_5 \end{cases}$$

KVL:

$$\mathbf{B} = \begin{bmatrix} 1 & 0 & 0 & 0 & 1 & 1 & 0 & -1 \\ 0 & 1 & 0 & 0 & 1 & 1 & -1 & -1 \\ 0 & 0 & 1 & -1 & 0 & -1 & 1 & 0 \end{bmatrix}, \quad \mathbf{v} = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \\ v_7 \\ v_8 \end{bmatrix},$$

$$\mathbf{B}\mathbf{v} = \mathbf{0}, \quad \begin{cases} v_1 + v_5 + v_6 - v_8 = 0 \\ v_2 + v_5 + v_6 - v_7 - v_8 = 0 \\ v_3 - v_4 - v_6 + v_7 = 0 \end{cases}$$

$$\mathbf{B}^T = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ 0 & 0 & -1 \\ 1 & 1 & 0 \\ 1 & 1 & -1 \\ 0 & -1 & 1 \\ -1 & -1 & 0 \end{bmatrix}, \quad \mathbf{i} = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix}, \quad \mathbf{j} = \begin{bmatrix} j_1 \\ j_2 \\ j_3 \\ j_4 \\ j_5 \\ j_6 \\ j_7 \\ j_8 \end{bmatrix}, \quad \mathbf{j} = \mathbf{B}^T \mathbf{i}, \quad \begin{cases} j_1 = i_1 \\ j_2 = i_2 \\ j_3 = i_3 \\ j_4 = -i_3 \\ j_5 = i_1 + i_2 \\ j_6 = i_1 + i_2 - i_3 \\ j_7 = -i_2 + i_3 \\ j_8 = -i_1 - i_2 \end{cases}$$

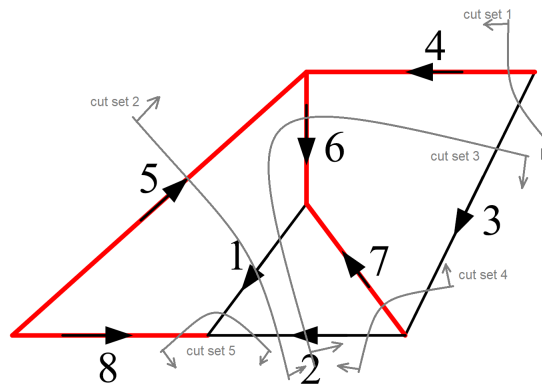


Figure 5: Cut-sets for the highlighted tree branches.


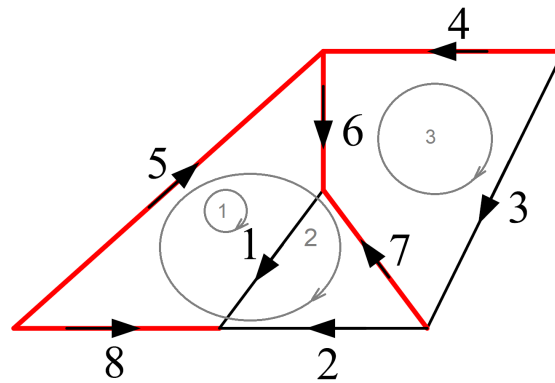


Figure 6: Loops for the highlighted link branches.
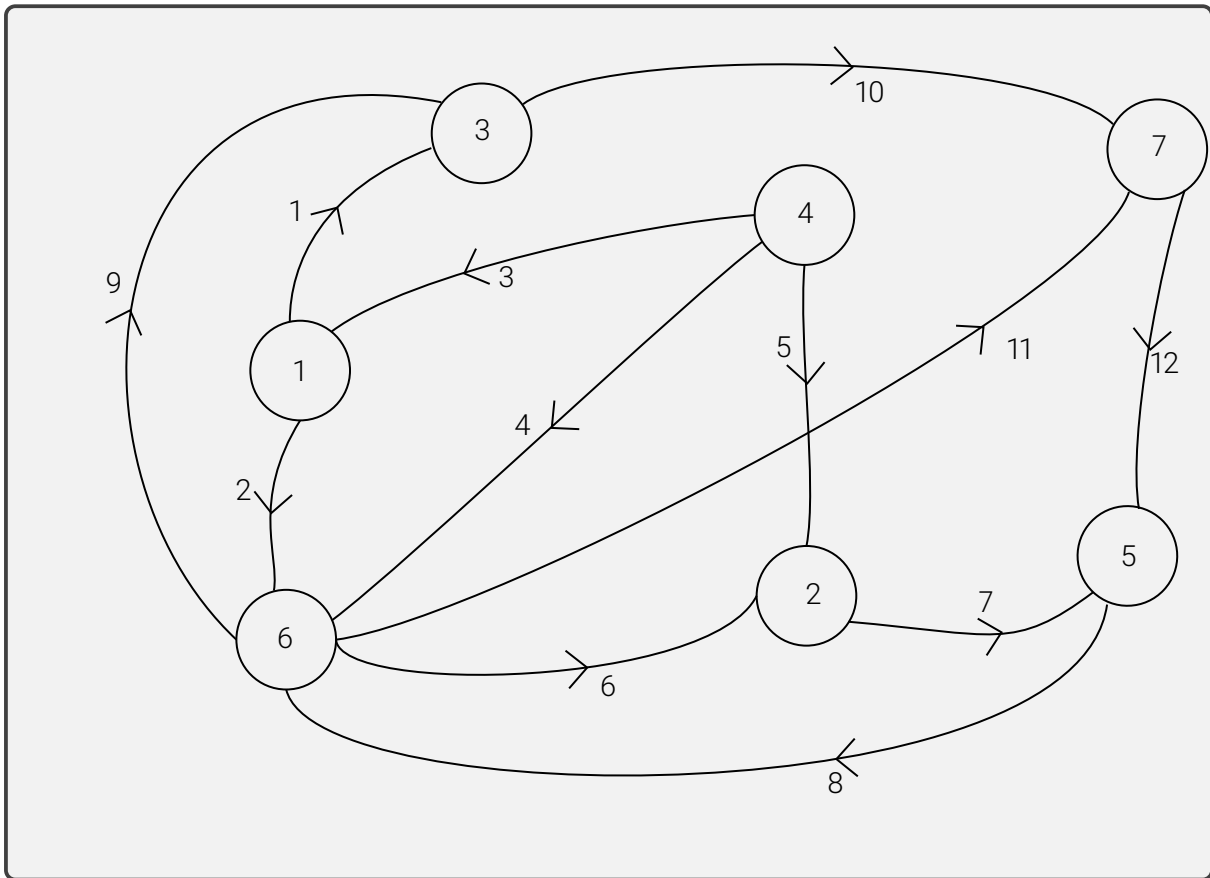
### Question 6

Draw a directed graph whose node-to-branch incidence matrix  $A_a$  is given by

$$A_a = \begin{bmatrix} 1 & 1 & -1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & -1 & -1 & 1 & 0 & 0 & 0 & 0 & 0 \\ -1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & 1 & 1 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & -1 & 1 & 0 & 0 & 0 & -1 \\ 0 & -1 & 0 & -1 & 0 & 1 & 0 & -1 & 1 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & -1 & -1 & 1 \end{bmatrix}$$



---

## SOFTWARE QUESTIONS

---

### Question 7

Dijkstra's conventional algorithm is a systematic method to find the shortest path between two given nodes of a weighted graph. However, a more common variant of the algorithm fixes a single node as the reference node and finds shortest paths from the source to all other nodes in the graph, producing a shortest-path tree. Implement Dijkstra's algorithm as a MATLAB function and use it to find a tree of a given connected circuit graph.

**Note:** A circuit graph is a special weighted graph, where all the edges have a same weight.

**Note:** A graph can be represented by a matrix. In fact, for the graph  $G(N = \{1, 2, \dots, n\}, E)$  with  $n$  node, the representing matrix of the graph is  $A_{n \times n} = [a_{ij}]$ , where  $a_{ij}$  is 1 if  $(i, j) \in E$ , and 0 otherwise.

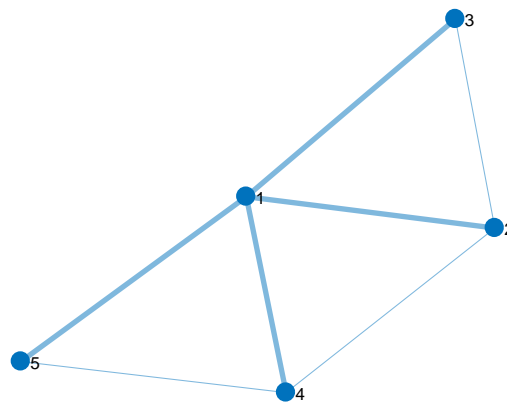


Figure 7: A graph and one of its trees.

Here is a MATLAB function that finds the spanning tree of a circuit graph.

```

1 %Minimum Spanning Tree Algorithm
2 function [route , tree]=mst(top) %top=topology matrix , start= initial node
3 [x y]= size(top);
4 if ne(x,y) % check if matrix is square
5     fprintf('enter square matrix');
6     return;end
7 for i=1 : size(top,1) %assigning large cost(inf) to not connected edges
8     for j=1 : size(top,1)
9         if top(i,j)==0; top(i,j)=inf;
10            end
11        end
12    end
13 route=zeros(x-1,3); %initialize route matrix (first node, second node, cost)
14 C=(1); %initial node
15 C_N=(1:x); % all nodes
16 C_N(:,1) = []; %removing selected node
17 for k = 2:x
18     counter=0;
19     min=inf; %can be set to infinity
20     for i=C
21         count=0;
22         for j=C_N
23             count=count+1;
24             if min>top(i,j)
25                 min=top(i,j);
26                 s=i;e=j;counter=count; %s=start node e=end node counter=node to remove
27             end
28         end
29     end
30     C(end+1)=e; % add node
31     C_N(:,counter) = []; % remove added none
32     route(k-1,:)= [s e min]; % [start_node end_node cost]
33 end
34
35 % make the tree matrix from its routes
36 tree=zeros(size(top));
37 for i=1:size(route,1)
38     tree(route(i,1) , route(i,2))=1;
39 end
40
41
42 end

```

You may use the following mfile to call the developed function and see its results.

```
1 clear all
2 clc
3
4 % sample circuit graph
5 top = [0 1 1 1 1;
6         1 0 1 1 0;
7         1 1 0 0 0;
8         1 1 0 0 1;
9         1 0 0 1 0];
10
11 % find the tree
12 [route , tree]=mst(top);
13
14 % show the tree
15 showTree(top , tree)
```

, where the function below is used to show the graph and its tree.

```
1 function showTree(ingraph , intree)
2
3 % convert the input graph to matlab graphs
4 sg = [];
5 dg = [];
6 wg = [];
7 for i=1:size(ingraph,1)
8     for j=i:size(ingraph,2)
9         if (ingraph(i,j)~=0)
10             sg = [sg i];
11             dg = [dg j];
12             wg = [wg 1];
13         end
14     end
15 end
16 G = graph(sg,dg,wg);
17
18 % convert the input tree to matlab graphs
19 st = [];
20 dt = [];
21 wt = [];
22 for i=1:size(intree,1)
23     for j=i:size(intree,2)
24         if (intree(i,j)~=0)
25             st = [st i];
26             dt = [dt j];
27             wt = [wt 1];
28         end
29     end
30 end
31 T = graph(st,dt,wt);
32
33 % plot graph
34 p = plot(G);
35 % highlight tree
36 highlight(p,T)
37
38 end
```

Sample output of the codes are shown in Fig. 7.

---

## BONUS QUESTIONS

---

## Question 8

Return your answers by filling the  $\text{\LaTeX}$  template of the assignment. If you want to add a circuit schematic, you can draw it directly using TikZ package, or draw it in a secondary application such as Microsoft Visio and then, import it as a figure.

---

## EXTRA QUESTIONS

---

## Question 9

Feel free to solve the following questions from the book "*Basic Circuit Theory*" by C. Desoer and E. Kuh.

1. Chapter 9, question 1.
2. Chapter 9, question 3.
3. Chapter 9, question 4.
4. Chapter 9, question 9.

Mohammad Hadi