

## MATHEMATICAL QUESTIONS

### Question 1

Find the unidirectional Laplace transform of the following functions.

(a)  $f(t) = 2|K|e^{-at} \cos(\beta t + \angle K)u(t)$ .

$$g(t) = \cos(\beta t + \angle K) = \cos(\beta t) \cos(\angle K) - \sin(\beta t) \sin(\angle K)$$

$$\Rightarrow G(s) = \mathcal{L}\{\cos(\beta t + \angle K)\} = \frac{s}{s^2 + \beta^2} \cos(\angle K) - \frac{\beta}{s^2 + \beta^2} \sin(\angle K)$$

$$f(t) = 2|K|e^{-at}g(t) \rightarrow F(s) = 2|K|G(s + a)$$

$$\Rightarrow F(s) = 2|K| \left( \frac{s+a}{(s+a)^2 + \beta^2} \cos(\angle K) - \frac{\beta}{(s+a)^2 + \beta^2} \sin(\angle K) \right)$$

$$= 2|K| \frac{(s+a)\cos(\angle K) - \beta \sin(\angle K)}{(s+a)^2 + \beta^2} = \frac{K}{s+a-j\beta} + \frac{K^*}{s+a+j\beta}$$

(b)  $f(t) = 2|K|te^{-at} \cos(\beta t + \angle K)u(t)$ .

$$g(t) = 2|K|e^{-at} \cos(\beta t + \angle K)u(t)$$

$$f(t) = tg(t) \rightarrow F(s) = -G'(s) = \frac{K}{(s+a-j\beta)^2} + \frac{K^*}{(s+a+j\beta)^2}$$

(c)  $f(t) = g(t)u(t)$ ,  $g(t) = at[u(t) - u(t - a)]$ ,  $g(t - a) = g(t)$ .

Since  $g(t)$  is periodic with period  $a$ ,

$$F(s) = \frac{\int_0^a ate^{-st} dt}{1 - e^{-sa}} = \frac{a(-ase^{-as} - e^{-as} + 1)}{s^2} \frac{1}{1 - e^{-sa}} = a \frac{-as - 1 + e^{as}}{s^2(e^{as} - 1)}$$

(d)  $f(t) = e^{-at^2}$ .

$$F(s) = \mathcal{L}\{e^{-at^2}\} = \int_0^\infty e^{-at^2-st} dt = \int_0^\infty e^{-(at^2+st)} dt = \int_0^\infty e^{-(at^2+st+\frac{s^2}{4a}-\frac{s^2}{4a})} dt$$

$$= e^{\frac{s^2}{4a}} \int_0^\infty e^{-(\sqrt{at+\frac{s}{2\sqrt{a}}})^2} dt = \frac{e^{\frac{s^2}{4a}}}{\sqrt{a}} \int_{\frac{s}{2\sqrt{a}}}^\infty e^{-\tau^2} d\tau = \frac{e^{\frac{s^2}{4a}}}{\sqrt{a}} \sqrt{\frac{\pi}{4a}} \frac{2}{\sqrt{\pi}} \int_{\frac{s}{2\sqrt{a}}}^\infty e^{-\tau^2} d\tau = e^{\frac{s^2}{4a}} \sqrt{\frac{\pi}{4a}} \operatorname{erfc}\left(\frac{s}{2\sqrt{a}}\right)$$

## Question 2

Find the inverse unidirectional Laplace transform of the following functions.

(a)  $F(s) = a \frac{-as-1+e^{as}}{s^2(e^{as}-1)}$ .

$$F(s) = a \frac{-as-1+e^{as}}{s^2(e^{as}-1)} \times \frac{e^{-as}}{e^{-as}} = \frac{X(s)}{1-e^{-as}}, \quad X(s) = a \frac{1-(as+1)e^{-as}}{s^2}$$

$$X(s) = \frac{a}{s^2} - \frac{a^2}{s} e^{-as} - \frac{a}{s^2} e^{-as} \Rightarrow x(t) = atu(t) - a^2u(t-a) - a(t-a)u(t-a) = at[u(t) - u(t-a)]$$

$$\Rightarrow f(t) = x(t), t \in [0, a], \quad f(t-a) = f(t)$$

(b)  $F(s) = \frac{1}{s(s+1)^2(s^2+1)^2}$ .

$$F(s) = \frac{1}{s(s+1)^2(s^2+1)^2} = \frac{a}{s} + \frac{b}{s+1} + \frac{c}{(s+1)^2} + \frac{d^*}{s+j} + \frac{d}{s-j} + \frac{e^*}{(s+j)^2} + \frac{e}{(s-j)^2}$$

$$a = sF(s)|_{s=0} = 1$$

$$b = ((s+1)^2 F(s))'|_{s=-1} = -\frac{5s^4 + 6s^2 + 1}{s^2(s^2+1)^4}|_{s=-1} = -\frac{3}{4}$$

$$c = (s+1)^2 F(s)|_{s=-1} = -\frac{1}{4}$$

$$d = ((s-j)^2 F(s))'|_{s=j} = -\frac{5s^4 + 8(j+1)s^3 + 12js^2 - 4(1-j)s - 1}{s^2(s+1)^4(s+j)^4}|_{s=j} = \frac{3j-1}{8}$$

$$e = (s-j)^2 F(s)|_{s=j} = \frac{1}{8}$$

$$\Rightarrow f(t) = [1 - \frac{3}{4}e^{-t} - \frac{1}{4}te^{-t} - \frac{1}{4}\cos(t) - \frac{3}{4}\sin(t) + \frac{1}{4}t\cos(t)]u(t)$$

(c)  $F(s) = \frac{s}{(s^2+2s+2)^3}$ .

$$F(s) = \frac{s}{(s^2+2s+2)^3} = \frac{a}{s+1-j} + \frac{b}{(s+1-j)^2} + \frac{c}{(s+1-j)^3}$$

$$+ \frac{a^*}{s+1+j} + \frac{b^*}{(s+1+j)^2} + \frac{c^*}{(s+1+j)^3}$$

$$a = \frac{1}{2}((s+1-j)^3 F(s))''|_{s=j-1} = \frac{1-2(s+1+j)^4 - 4(s+1+j)^3(1+j-2s)}{2(s+1+j)^8}|_{s=j-1} = \frac{3j}{16}$$

$$b = ((s+1-j)^3 F(s))'|_{s=j-1} = \frac{(s+1+j)^3 - 3(s+1+j)^2 s}{(s+1+j)^6}|_{s=j-1} = \frac{3-j}{16}$$

$$c = (s+1-j)^3 F(s)|_{s=j-1} = \frac{-1-j}{8}$$

$$\Rightarrow f(t) = \frac{1}{8}e^{-t}[(t^2+t-3)\sin(t) - (t-3)t\cos(t)]u(t)$$

### Question 3

Calculate the time-domain mesh currents for the circuit of Fig. 1.

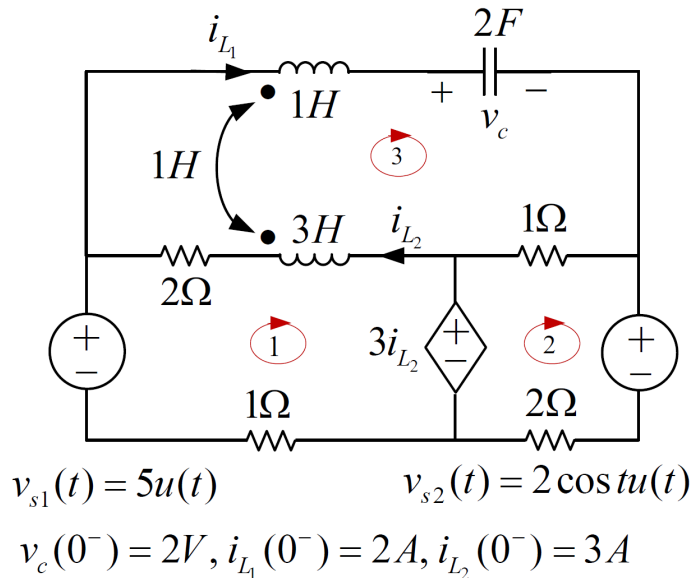


Figure 1: A coupled circuit for which the mesh currents are required.

We now that

$$V_c(s) = \frac{1}{cs} I_3 + \frac{v_c(0^-)}{s}$$

$$V_{L1}(s) = L_1 s I_{L1}(s) - M s I_{L2}(s) - L_1 i_{L1}(0^-) + M i_{L2}(0^-)$$

$$V_{L2}(s) = -L_2 s I_{L2}(s) + M s I_{L1}(s) + L_2 i_{L2}(0^-) - M i_{L1}(0^-)$$

So, we have

$$V_c(s) = \frac{1}{2s} I_3(s) + \frac{2}{s}$$

$$I_{L1} = I_3(s), \quad I_{L2} = I_3(s) - I_1(s)$$

$$V_{L1}(s) = s I_3(s) - s(I_3(s) - I_1(s)) - 2 + 3 = s I_1(s) + 1$$

$$V_{L2}(s) = -3s(I_3(s) - I_1(s)) + s I_3(s) + 3 \times 3 - 2 = 3s I_1(s) - 2s I_3(s) + 7$$

$$v_{s1}(s) = \mathcal{L}(5u(t)) = \frac{5}{s}$$

$$v_{s2}(s) = \mathcal{L}(2 \cos(t)u(t)) = \frac{2s}{s^2 + 1}$$

Now, we can write KVL equations for the meshes as

$$-\frac{5}{s} + 2(I_1(s) - I_3(s)) + (3s I_1(s) - 2s I_3(s) + 7) + 3(I_3(s) - I_1(s)) + I_1(s) = 0$$

$$(s I_1(s) + 1) \left( \frac{1}{2s} I_3(s) + \frac{2}{s} \right) + (I_3(s) - I_2(s)) - (3s I_1(s) - 2s I_3(s) + 7) + 2(I_3(s) - I_1(s)) = 0$$

$$\frac{2s}{s^2 + 1} + 2I_2(s) - 3(I_3(s) - I_1(s)) + (I_2(s) - I_3(s)) = 0$$

Simplify the equations,

$$(-3s)I_1(s) + (2s - 1)I_3(s) = -\frac{5}{s} + 7$$

$$(-s - 2)I_1(s) - I_2(s) + \left(\frac{1}{2s} + 2s + 3\right)I_3(s) = -\frac{2}{s} + 6$$

$$I_1(s) + 3I_2(s) - 4I_3(s) = -\frac{2s}{s^2 + 1}$$

Solving the equations,

$$I_1(s) = \frac{-33s^4 - 63s^3 + 33s^2 - 55s + 62}{s(33s^4 + 16s^3 + 43s^2 + 16s + 10)}$$

$$I_2(s) = \frac{77s^4 - 107s^3 + 137s^2 - 83s + 46}{s(33s^4 + 16s^3 + 43s^2 + 16s + 10)}$$

$$I_3(s) = \frac{66s^4 - 88s^3 + 116s^2 - 76s + 50}{s(33s^4 + 16s^3 + 43s^2 + 16s + 10)}$$

Finally, taking the inverse Laplace transform,


$$i_1(t) = -0.153 \sin(t) - 0.280 \cos(t) \\ - e^{-0.242t} [5.967 \sin(0.494t) + 6.920 \cos(0.494t)] + 6.200$$

$$i_2(t) = -0.418 \sin(t) - 0.899 \cos(t) \\ - e^{-0.242t} [8.675 \sin(0.494t) + 1.368 \cos(0.494t)] + 4.600$$

$$i_3(t) = -0.352 \sin(t) - 0.245 \cos(t) \\ - e^{-0.242t} [7.998 \sin(0.494t) + 2.755 \cos(0.494t)] + 5.000$$
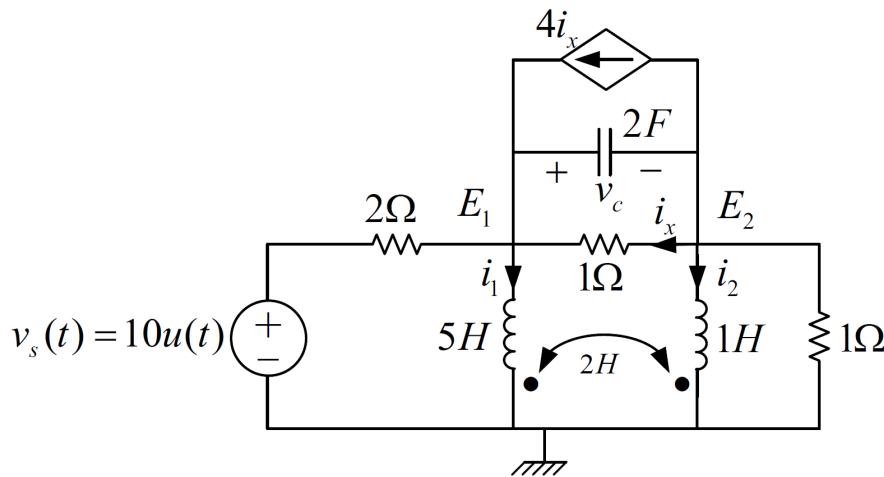
#### Question 4

Obtain the time-domain node voltages for the circuit of Fig. 2.



$$v_c(0^-) = 2V, i_1(0^-) = 2A, i_2(0^-) = 3A$$

$$L = \begin{pmatrix} 5 & 2 \\ 2 & 1 \end{pmatrix} \Rightarrow \Gamma = L^{-1} = \begin{pmatrix} 1 & -2 \\ -2 & 5 \end{pmatrix}$$

Figure 2: A coupled circuit for which the node voltages are required.

We know that

$$\begin{cases} -I_1(s) = -\frac{1}{s}E_1(s) - \frac{-2}{s}E_2(s) - \frac{2}{s} \\ -I_2(s) = -\frac{-2}{s}E_1(s) - \frac{5}{s}E_2(s) - \frac{3}{s} \\ I_C(s) = 2s(E_1(s) - E_2(s)) - 2 \times 2 \\ V_s(s) = \frac{10}{s} \\ I_x(s) = \frac{E_2 - E_1}{1} \end{cases}$$

Using KCL at the nodes,

$$\frac{E_1 - \frac{10}{s}}{2} + \frac{1}{s}E_1 + \frac{-2}{s}E_2 + \frac{2}{s} + \frac{E_1 - E_2}{1} - 4\frac{E_2 - E_1}{1} + 2s(E_1 - E_2) - 4 = 0$$

$$\frac{E_2}{1} + \frac{-2}{s}E_1 + \frac{5}{s}E_2 + \frac{3}{s} + \frac{E_2 - E_1}{1} + 4\frac{E_2 - E_1}{1} - 2s(E_1 - E_2) + 4 = 0$$

Simplifying the equations,

$$E_1\left(\frac{11}{2} + \frac{1}{s} + 2s\right) + E_2\left(-5 - \frac{2}{s} - 2s\right) = \frac{3}{s} + 4$$

$$E_1\left(-5 - \frac{2}{s} - 2s\right) + E_2\left(6 + \frac{5}{s} + 2s\right) = -\frac{3}{s} - 4$$

Solving the equations,

$$E_1 = -\frac{2(-4s-3)(s+3)}{6s^3+24s^2+27s+2} = -\frac{(-4s-3)(0.33s+1)}{s^3+4s^2+4.5s+0.33}$$

$$E_2 = \frac{(-4s-3)(s-2)}{6s^3+24s^2+27s+2} = \frac{(-0.67s-0.5)(s-2)}{s^3+4s^2+4.5s+0.33}$$

Finally, taking the inverse Laplace transform,

$$e_1(t) = -0.673e^{-0.0787t} - e^{-1.961t} [0.647 \cos(0.589t) - 1.752 \sin(0.589t)]$$

$$e_2(t) = 0.239e^{-0.0787t} - e^{-1.961t} [0.909 \cos(0.589t) - 2.981 \sin(0.589t)]$$

### Question 5

Find an expression for  $v(t)$  valid for all times in the circuit of Fig. 3.

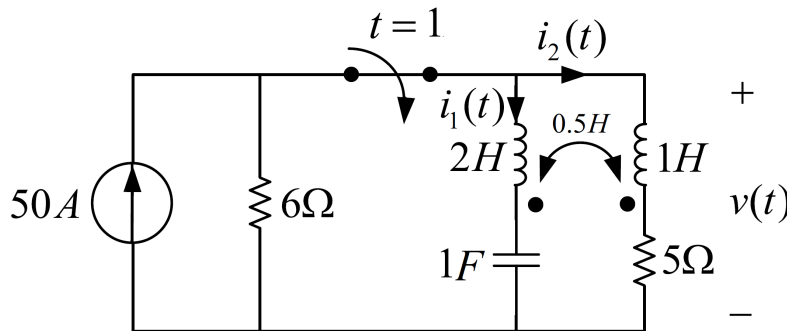


Figure 3: A circuit with a switch opened at  $t = 1$ .

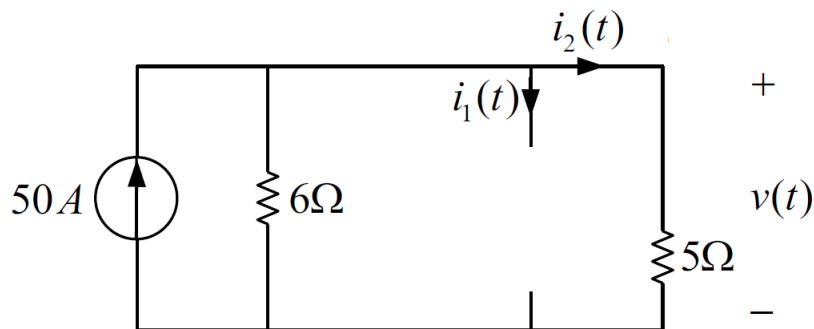


Figure 4: The circuit of Fig. 3 for  $t < 1$ .

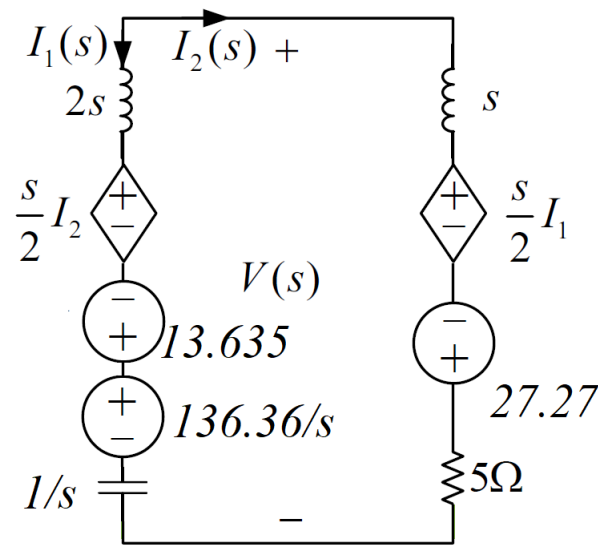


Figure 5: The circuit of Fig. 3 for  $t > 1$ .

We analyze the circuit by assuming that the switch opens at  $t = 0$ . Then, we shift the response to  $t = 1$ . Before  $t = 0$ , we have the circuit 4 and therefore,

$$\begin{aligned} i_1(0^-) &= 0 \\ i_2(0^-) &= 50 \frac{6}{6+5} = 27.27 \\ v(0^-) &= 5i_2(0^-) = 136.36 \\ v_c(0^-) &= (0^-) = 136.36 \end{aligned}$$

When the switch opens at  $t = 0$ , we get the circuit shown in Fig. 5. So,

$$\begin{cases} sI_2 + 0.5sI_1 - 27.27 + 5I_2 + \frac{I_2}{s} - \frac{136.36}{s} + 13.635 - 0.5sI_2 + 2sI_2 = 0 \\ I_1 = -I_2 \end{cases}$$

$$I_2(s) = \frac{s}{2s^2 + 5s + 1} \frac{13.635s + 136.36}{s} = \frac{13.635s + 136.36}{2s^2 + 5s + 1}$$

$$V(s) = sI_2 - 0.5sI_2 + 27.27 + 5I_2 = I_2 + 27.27 = \frac{(0.5s + 5)(13.635s + 136.36)}{2s^2 + 5s + 1} + 27.27$$

$$v(t) = 30.67875\delta(t) + 256.72502e^{-\frac{5t}{4}} \sinh(1.03077t) + 59.655625e^{-\frac{5t}{4}} \cosh(1.03077t)$$

Finally,

$$v(t) = \begin{cases} 136.36 & , t < 1 \\ 30.68\delta(t-1) + e^{-\frac{5(t-1)}{4}} [256.73 \sinh(1.03(t-1)) + 59.66 \cosh(1.03(t-1))] & , t \geq 1 \end{cases}$$

## SOFTWARE QUESTIONS

### Question 6

Use AC analysis of PSpice to investigate the frequency response  $H(j\omega) = \frac{V_o(j\omega)}{V_s(j\omega)}$  of the double-tuned circuit shown in Fig. 6. Analyze the impact of each parameter on the frequency response.

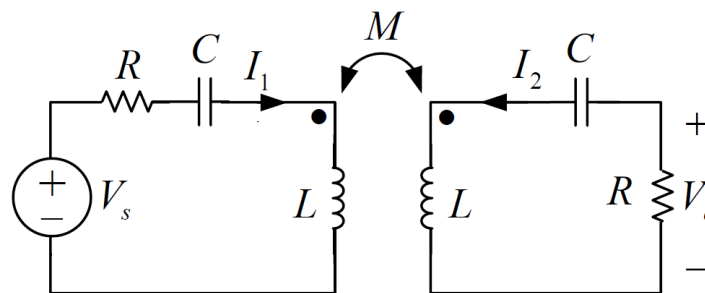


Figure 6: Double-tuned circuit.

The frequency responses of the circuit for a sinusoidal input with amplitude 10 are shown in Figs. 8-15. In each figure, a circuit parameter is changed and its impact on the magnitude or phase of the frequency response is shown.

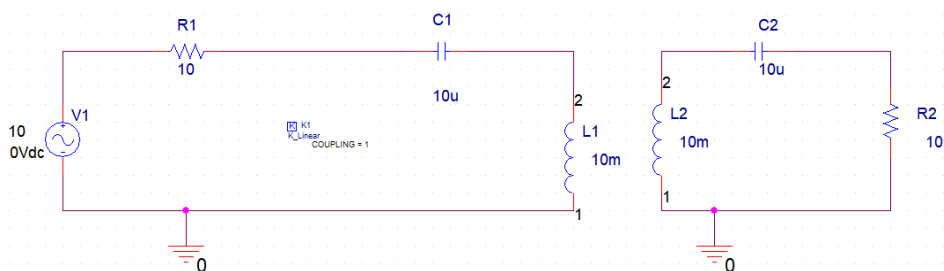


Figure 7: Schematic of the double-tuned circuit in PSpice.



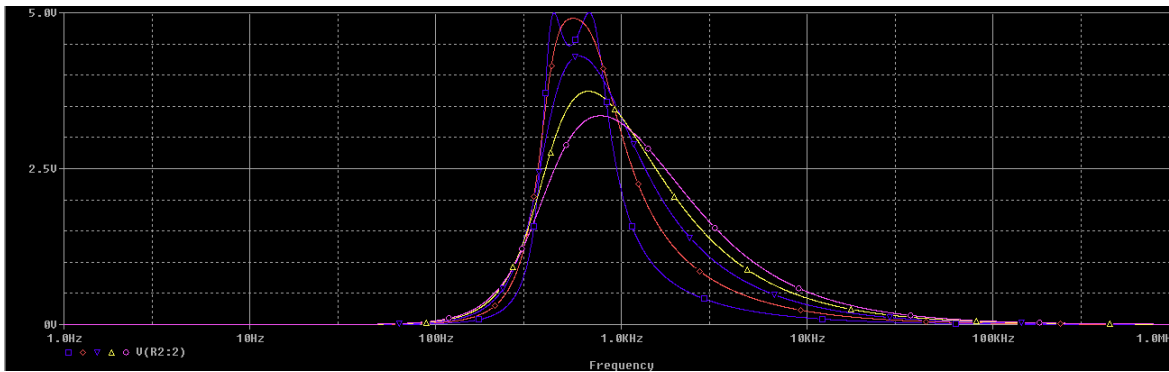


Figure 8: Frequency response magnitude for  $R = 10, 20, 30, 40, 50 \Omega$ . Increasing  $R$ , the bandwidth of the magnitude response increases.

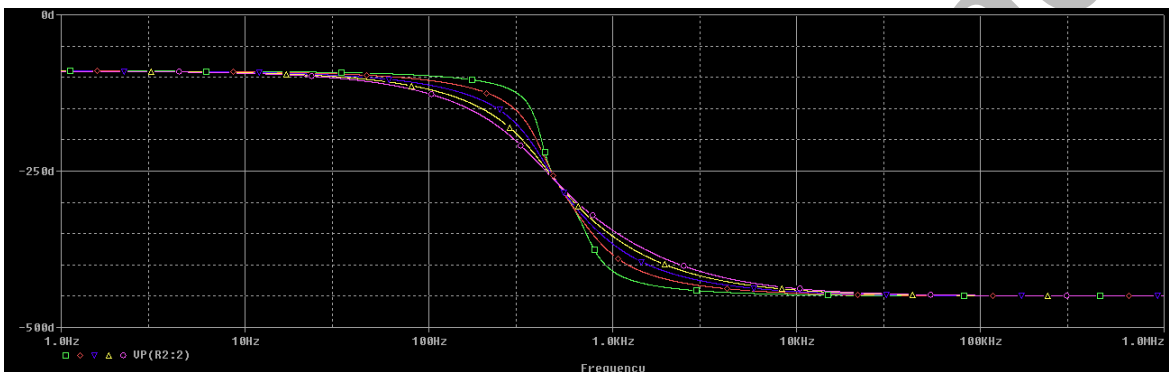


Figure 9: Frequency response phase for  $R = 10, 20, 30, 40, 50 \Omega$ . Increasing  $R$ , the smoothness of the phase response increases.

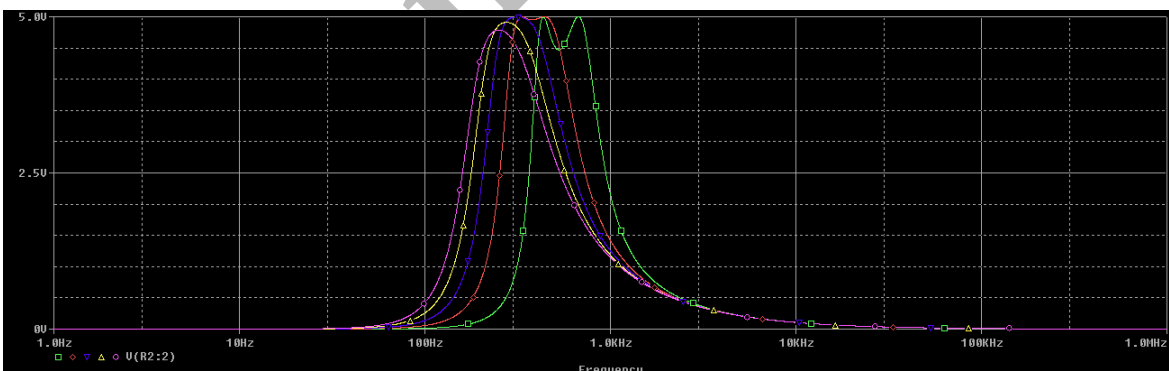


Figure 10: Frequency response magnitude for  $C = 10, 20, 30, 40, 50 \mu\text{F}$ . Increasing  $C$ , the central frequency of the magnitude response decreases.

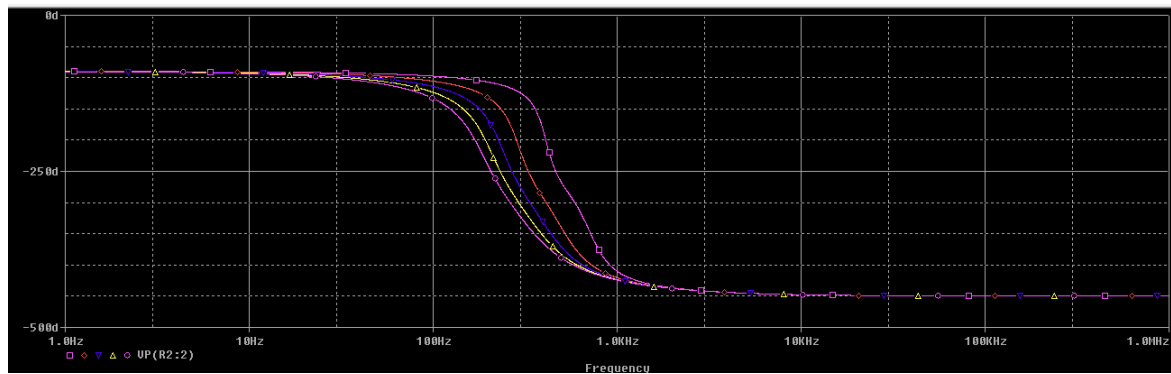


Figure 11: Frequency response phase for  $C = 10, 20, 30, 40, 50 \mu\text{F}$ . Increasing  $C$ , the turning frequency of the phase response decreases.

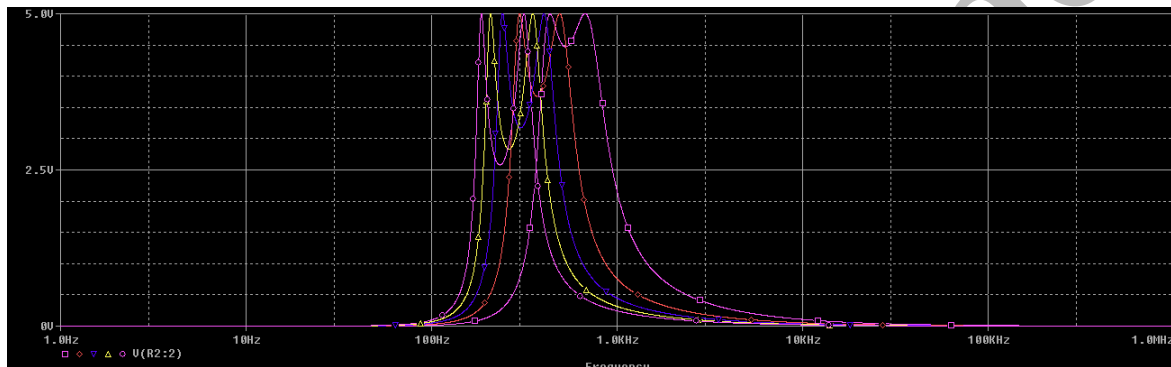


Figure 12: Frequency response magnitude for  $L = 10, 20, 30, 40, 50 \text{ mH}$ . Increasing  $L$ , the central frequency of the magnitude response decreases.

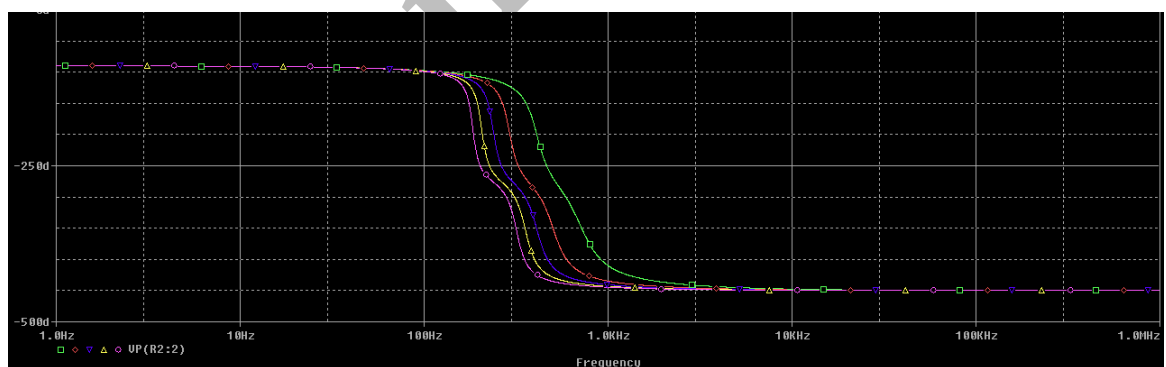


Figure 13: Frequency response phase for  $L = 10, 20, 30, 40, 50 \text{ mH}$ . Increasing  $L$ , the turning frequency of the phase response decreases.

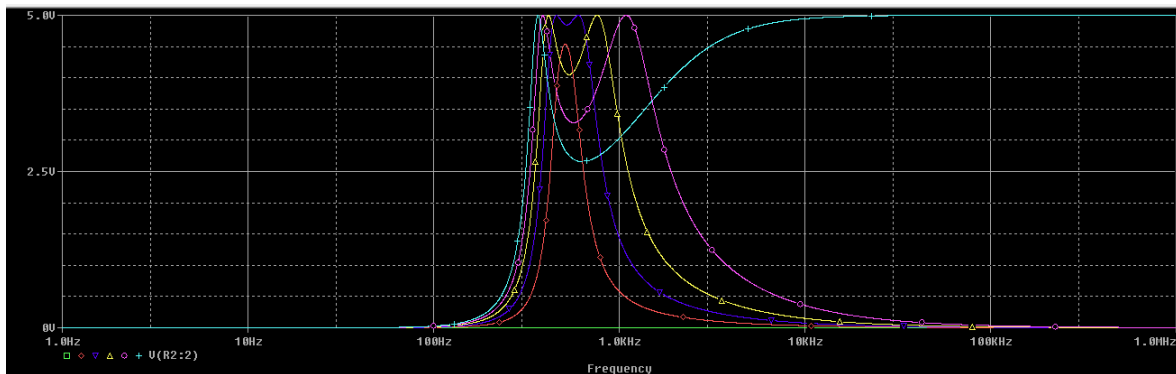


Figure 14: Frequency response magnitude for  $k = 0, 0.2, 0.4, 0.6, 0.8, 1$ . Increasing  $k$ , the bandwidth of the magnitude response increases.

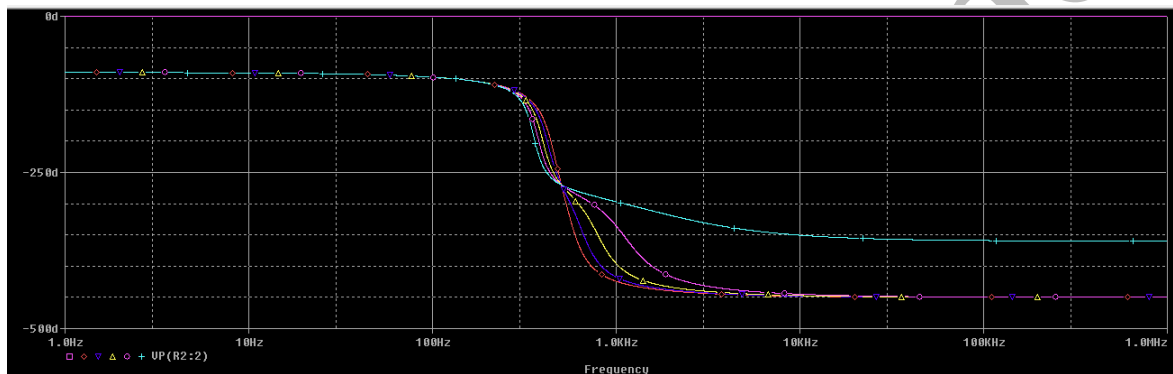


Figure 15: Frequency response phase for  $k = 0, 0.2, 0.4, 0.6, 0.8, 1$ . Increasing  $k$ , the turning point of the phase response almost remains unchanged.

---

## BONUS QUESTIONS

---

### Question 7

Return your answers by filling the  $\LaTeX$  template of the assignment. If you want to add a circuit schematic, you can draw it directly using TikZ package, or draw it in a secondary application such as Microsoft Visio and then, import it as a figure.

---

## EXTRA QUESTIONS

---

## Question 8

Feel free to solve the following questions from the book "*Engineering Circuit Analysis*" by W. Hayt, J. Kemmerly, and S. Durbin.

1. Chapter 15, question 14.
2. Chapter 15, question 19.
3. Chapter 15, question 22.
4. Chapter 15, question 24.
5. Chapter 15, question 27.

Mohammad Hadi