

MATHEMATICAL QUESTIONS

Question 1

For the circuit of Fig. 1,

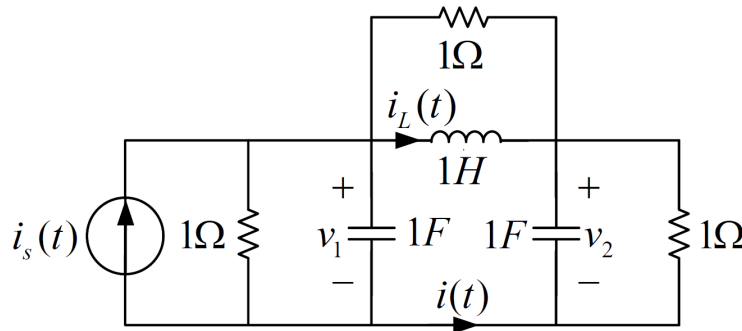


Figure 1: A circuit for which the natural frequencies are required.

(a) Find the natural frequencies of the node voltages.

Using nodal analysis for the unforced equivalent circuit,

$$\frac{V_1 - V_2}{1} + \frac{V_1 - V_2}{s} + \frac{V_1}{1} + \frac{V_1}{\frac{1}{s}} = v_1(0^-) - \frac{i_L(0^-)}{s}$$

$$\frac{V_2 - V_1}{1} + \frac{V_2 - V_1}{s} + \frac{V_2}{1} + \frac{V_2}{\frac{1}{s}} = v_2(0^-) + \frac{i_L(0^-)}{s}$$

So, we have

$$\left(1 + \frac{1}{s} + 1 + s\right)V_1 - \left(1 + \frac{1}{s}\right)V_2 = v_1(0^-) - \frac{i_L(0^-)}{s}$$

$$-\left(1 + \frac{1}{s}\right)V_1 + \left(1 + \frac{1}{s} + 1 + s\right)V_2 = v_2(0^-) + \frac{i_L(0^-)}{s}$$

Solving the equations,

$$V_1 = \frac{(s+1)v_1(0^-) + v_2(0^-) - i_L(0^-)}{(s+2)(s+1)} \Rightarrow s = -1, -2$$

$$V_2 = \frac{(s+1)v_2(0^-) + v_1(0^-) + i_L(0^-)}{(s+2)(s+1)} \Rightarrow s = -1, -2$$

(b) Find the natural frequencies of the circuit.

$$\mathbf{Y}_n(s) = \begin{bmatrix} 2 + \frac{1}{s} + s & -(1 + \frac{1}{s}) \\ -(1 + \frac{1}{s}) & 2 + \frac{1}{s} + s \end{bmatrix}$$

$$\Delta_n(s) = \det \mathbf{Y}_n(s) = \frac{s^3 + 4s^2 + 5s + 2}{s} = 0 \Rightarrow s = -2, -1, -1$$

Question 2

Calculate the natural frequencies of the circuits shown in Fig. 2.

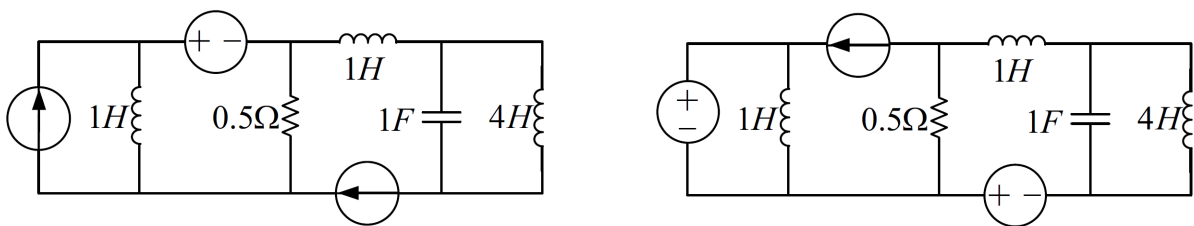


Figure 2: Two circuits with different types of independent sources.

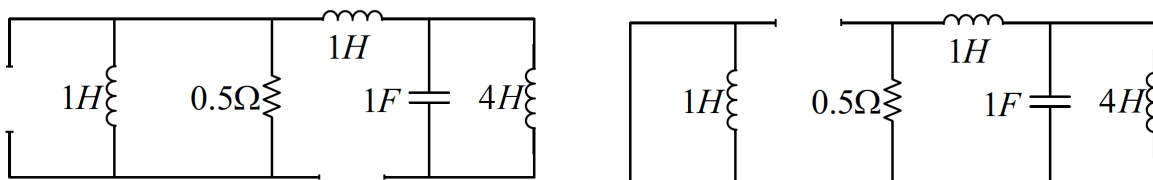


Figure 3: Circuits of Fig. 2 in the zero-input state.

The unforced circuits are shown in Fig. 3. For the right circuit, there is an inductive loop in the left part of the circuit that results in a zero natural frequency $s_1 = 0$. For the right part,

$$\mathbf{Y}_n(s) = \begin{bmatrix} 2 + \frac{1}{s} & \frac{-1}{s} \\ \frac{-1}{s} & \frac{1}{s} + s + \frac{1}{4s} \end{bmatrix}$$

So,

$$\Delta_n(s) = \det \mathbf{Y}_n(s) = \frac{8s^3 + 4s^2 + 10s + 1}{4s^2} = 0 \Rightarrow s_2 \approx -0.10339, s_3, s_4 \approx -0.1983 \pm j1.08151$$

Hence, all the natural frequencies are

$$s_1 = 0, s_2 \approx -0.10339, s_3, s_4 \approx -0.1983 \pm j1.08151$$

For the left circuit, The natural frequencies for the LC part is

$$s_1, s_2 = \pm \frac{j}{\sqrt{LC}} = \pm \frac{j}{2}$$

And for the RL part,

$$\tau = \frac{L}{R} = 2 \Rightarrow s_3 = \frac{-1}{\tau} = \frac{-1}{2}$$

Hence, all the natural frequencies are

$$s_1, s_2 = \pm \frac{j}{2}, s_3 = \frac{-1}{2}$$

Question 3

For the circuit of Fig. 4,

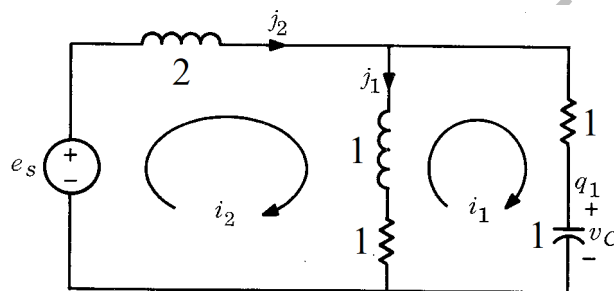


Figure 4: A circuit for which the minimal differential equation of j_2 is required.

(a) Find the minimal differential equation of j_2 .

Mesh analysis yields

$$\begin{cases} i_1 + D^{-1}i_1 + v_c(0^-) + i_1 - i_2 + D(i_1 - i_2) = 0 \\ 2Di_2 + D(i_2 - i_1) + i_2 - i_1 - e_s = 0 \end{cases}$$

So,

$$\begin{bmatrix} E_1 \\ E_2 \end{bmatrix} : \begin{bmatrix} D + 2 + D^{-1} & -D - 1 \\ -D - 1 & 3D + 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} -v_c(0^-) \\ e_s \end{bmatrix}$$

Replacing $i_1 = Dq_1$ with the q_1 in the equations,

$$\begin{bmatrix} E_1 \\ E_2 \end{bmatrix} : \begin{bmatrix} D^2 + 2D + 1 & -(D + 1) \\ -D(D + 1) & 3D + 1 \end{bmatrix} \begin{bmatrix} q_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} -v_c(0^-) \\ e_s \end{bmatrix}$$

Manipulating the matrix with the elementary row operations,

$$\begin{bmatrix} E_1 \\ E_2 + E_1 \end{bmatrix} : \begin{bmatrix} D^2 + 2D + 1 & -(D + 1) \\ D + 1 & 2D \end{bmatrix} \begin{bmatrix} q_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} -v_c(0^-) \\ e_s - v_c(0^-) \end{bmatrix}$$

$$\begin{bmatrix} E_1 - (D+1)(E_2 + E_1) \\ (E_2 + E_1) \end{bmatrix} : \begin{bmatrix} 0 & -(2D^2 + 3D + 1) \\ D + 1 & 2D \end{bmatrix} \begin{bmatrix} q_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} -(D+1)e_s \\ e_s - v_c(0^-) \end{bmatrix}$$

$$\begin{bmatrix} (E_2 + E_1) \\ E_1 - (D+1)(E_2 + E_1) \end{bmatrix} : \begin{bmatrix} D + 1 & 2D \\ 0 & -(2D^2 + 3D + 1) \end{bmatrix} \begin{bmatrix} q_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} e_s - v_c(0^-) \\ -(D+1)e_s \end{bmatrix}$$

Since $j_2 = i_2$, we have the corresponding minimal differential equation as

$$(2D^2 + 3D + 1)j_2 = (D + 1)e_s$$

(b) Find the natural frequencies of j_2 .

The characteristic equation of the minimal differential equation of j_2 gives the natural frequencies. So,

$$2s^2 + 3s + 1 = 0 \Rightarrow s_1 = -1, s_2 = -\frac{1}{2}$$

Question 4

Calculate the natural frequencies of the circuits shown in Fig. 5. How many zero natural frequencies does each circuit have?

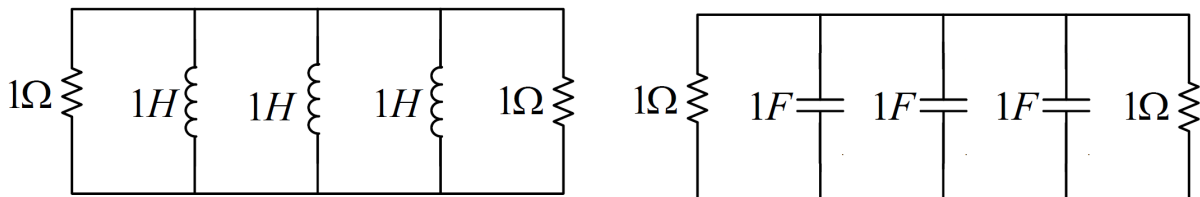


Figure 5: Two circuits with different types of energy storage elements.

For the right RC circuit, there are 3 capacitors and 2 independent capacitive loop, so the circuit has $3 - 2 = 1$ nonzero natural frequency. The nonzero natural frequency is

$$\Delta_n(s) = \det[\mathbf{Y}_n] = |s + s + s + 1 + 1| = 3s + 2 = 0 \Rightarrow s = -\frac{2}{3}$$

For the left RL circuit, there are 3 inductors and 2 independent inductive loops. So, there are 3 natural frequencies including 2 zero and 1 nonzero natural frequencies. The nonzero natural frequency is obtained as

$$\Delta_n(s) = \det[\mathbf{Y}_n] = \left| \frac{1}{s} + \frac{1}{s} + \frac{1}{s} + 1 + 1 \right| = \frac{3 + 2s}{s} = 0 \Rightarrow s = -\frac{3}{2}$$

Question 5

For the circuit shown in Fig. 6,

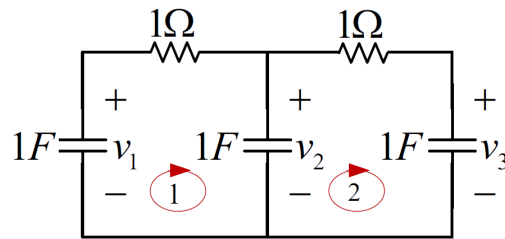


Figure 6: A circuit with three energy storage elements.

(a) Find the natural frequencies using the governing state equations.

We use capacitor voltages as the state variables.

$$\begin{cases} \frac{dv_1(t)}{dt} = v_2(t) - v_1(t) \\ \frac{dv_2(t)}{dt} = v_3(t) - v_2(t) + v_1(t) - v_2(t) = v_3(t) - 2v_2(t) + v_1(t) \\ \frac{dv_3(t)}{dt} = v_2(t) - v_3(t) \end{cases}$$

$$\mathbf{X}(t) = \begin{bmatrix} v_1(t) \\ v_2(t) \\ v_3(t) \end{bmatrix}, \mathbf{X}_0 = \mathbf{X}(0) = \begin{bmatrix} v_1(0^-) \\ v_2(0^-) \\ v_3(0^-) \end{bmatrix} \Rightarrow \frac{d\mathbf{X}(t)}{dt} = \begin{bmatrix} -1 & 1 & 0 \\ 1 & -2 & 1 \\ 0 & 1 & -1 \end{bmatrix} \mathbf{X}(t)$$

$$s\mathbf{I} - \mathbf{A} = \begin{bmatrix} s+1 & -1 & 0 \\ -1 & s+2 & -1 \\ 0 & -1 & s+1 \end{bmatrix}$$

$$\det[s\mathbf{I} - \mathbf{A}] = (s+1)[(s+2)(s+1)-1] - (s+1) = s^3 + 4s^2 + 3s = s(s+1)(s+3) \Rightarrow s = 0, -1, -3$$

(b) Introduce a set of initial conditions for which only one natural frequency exist in zero-input response of the state variables.

If the initial conditions is parallel to the eigen vectors of matrix \mathbf{A} , only one natural frequency appears in the state variables. The eigen vectors are

$$\mathbf{u}_1 = \begin{pmatrix} 1 \\ 1 \\ 1 \end{pmatrix}, \mathbf{u}_2 = \begin{pmatrix} -1 \\ 0 \\ 1 \end{pmatrix}, \mathbf{u}_3 = \begin{pmatrix} 1 \\ -2 \\ 1 \end{pmatrix}$$

and the zero-input response is

$$\mathbf{X}(t) = e^{\mathbf{A}t} \mathbf{X}_0 = K_1 \begin{pmatrix} 1 \\ 1 \\ 1 \end{pmatrix} + K_2 \begin{pmatrix} -1 \\ 0 \\ 1 \end{pmatrix} e^{-t} + K_3 \begin{pmatrix} 1 \\ -2 \\ 1 \end{pmatrix} e^{-3t}$$

If we set $\mathbf{X}(0) = K \begin{pmatrix} 1 \\ 1 \\ 1 \end{pmatrix}$, only natural frequency 0 appears in the response. To show this, we find the unknown K_1, K_2, K_3 as

$$\mathbf{X}_0 = K_1 \begin{pmatrix} 1 \\ 1 \\ 1 \end{pmatrix} + K_2 \begin{pmatrix} -1 \\ 0 \\ 1 \end{pmatrix} + K_3 \begin{pmatrix} 1 \\ -2 \\ 1 \end{pmatrix} = K \begin{pmatrix} 1 \\ 1 \\ 1 \end{pmatrix}$$

This yields

$$\begin{cases} K_1 - K_2 + K_3 = K \\ K_1 - 2K_3 = K \\ K_1 + K_2 + K_3 = K \end{cases} \Rightarrow K_1 = K, \quad K_2 = K_3 = 0$$

So,

$$\mathbf{X}(t) = K \begin{pmatrix} 1 \\ 1 \\ 1 \end{pmatrix}$$

Similarly, if $\mathbf{X}(0) = K \begin{pmatrix} -1 \\ 0 \\ 1 \end{pmatrix}$, the response only includes natural frequency -1 . Finally,

$\mathbf{X}(0) = K \begin{pmatrix} 1 \\ -2 \\ 1 \end{pmatrix}$ causes the response to have only natural frequency -3 .

SOFTWARE QUESTIONS

Question 6

Write a MATLAB function that finds the minimal differential equation and natural frequencies corresponding to the last variable in the matrix differential equation

$$A(D)\mathbf{X} = \mathbf{F}$$

Note 1: Here, we have a matrix differential equation, where the elements of $A(D)$ are polynomials of the differentiation operator $D^n, n \geq 0$. No element contains the integral operator D^{-1} .

Note 2: A polynomial can be expressed as a vector, i.e.,

$$\sum_{i=0}^n p_i D^i \equiv [p_n \quad p_{n-1} \quad \cdots \quad p_1 \quad p_0]$$

Here is a MATLAB function that computes the minimal differential equation and the corresponding natural frequencies.

```

1 function [natFreq, minDifEqu]=MDEC(A)
2
3 % the numbers in (-epsilon, epsilon) are assumed zero
4 epsilon = 1e-6;
5
6 for j = 1: size(A,2)-1
7     % manipulate column j
8     while (sum(abs(cell2mat(A(j+1:end,j)')))) > epsilon)
9         % find the minimum degree polynomial
10        minDegRow = Inf;
11        minDeg = Inf;
12        for i = j: size(A,1)
13            tmpDeg = length(cell2mat(A(i,j))) -1;
14            if (tmpDeg < minDeg)
15                minDegRow = i;
16                minDeg = tmpDeg;
17            end
18        end
19
20        % swap the polynomials
21        tmpRow = A(minDegRow,:);
22        A(minDegRow,:) = A(j,:);
23        A(j,:) = tmpRow;
24
25        % do elementary row operations
26        for i = j+1: size(A,1)
27            qTmp = deconv(cell2mat(A(i,j)), cell2mat(A(j,j)));
28            for k = j: size(A,2)
29                mulTmp = conv(qTmp, cell2mat(A(j,k)));
30                eltTmp = [zeros(1,max([length(mulTmp) length(cell2mat(A(i,k))])]-length(
31                    cell2mat(A(i,k)))) cell2mat(A(i,k))] - [zeros(1,max([length(mulTmp)
32                    length(cell2mat(A(i,k))])]-length(mulTmp)) mulTmp];
33                if (sum(abs(eltTmp)) < epsilon)
34                    eltTmp = 0;
35                else
36                    eltTmp = eltTmp( find(eltTmp~=0): end );
37                end
38                A(i,k) = {eltTmp};
39            end
40        end
41    end
42 end
43
44 % print minimal differential equation
45 minDifEqu = cell2mat(A(end,end));
46 % calculate natural frequencies
47 natFreq = roots(minDifEqu);
48
49 end

```

You may use the following mfile to call the developed function and see its results.

```

1 % example 1
2 A = cell(2);
3 A(1,1) = {[1 2 1]};
4 A(1,2) = {[ -1 -1]};
5 A(2,1) = {[ -1 -1 0]};
6 A(2,2) = {[3 1]};
7 [natFreq, minDifEqu] = MDEC(A)
8
9 % example 2
10 A = cell(3);
11 A(1,1,:) = {[1 3 1]};
12 A(1,2,:) = {[ -1]};

```

```
13 A(1,3,:) = {[ -3]};
14 A(2,1,:) = {[ -1]};
15 A(2,2,:) = {[1 3 1]};
16 A(2,3,:) = {[ -3]};
17 A(3,1,:) = {[ -3 0]};
18 A(3,2,:) = {[ -3 0]};
19 A(3,3,:) = {[1 6]};
20
21 [natFreq, minDifEqu] = MDEC(A)
```

BONUS QUESTIONS

Question 7

Return your answers by filling the \LaTeX template of the assignment. If you want to add a circuit schematic, you can draw it directly using TikZ package, or draw it in a secondary application such as Microsoft Visio and then, import it as a figure.

EXTRA QUESTIONS

Question 8

Feel free to solve the following questions from the book "*Basic Circuit Theory*" by C. Desoer and E. Kuh.

1. Chapter 14, question 1.
2. Chapter 14, question 2.
3. Chapter 14, question 4.
4. Chapter 14, question 5.
5. Chapter 14, question 6.