

# State Equations

Mohammad Hadi

*mohammad.hadi@sharif.edu*

*@MohammadHadiDastgerdi*


Fall 2021

# Overview

- 1 State Equations
- 2 State Equations for LTI circuits
- 3 State Equations for LTV circuits
- 4 State Equations for NTV circuits
- 5 Solving State Equations

# State Equations

# State Equations

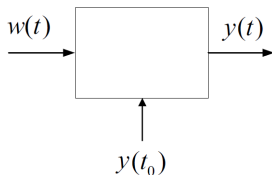

**Figure:** An LTI circuit with an input and initial conditions. State equations allow to solve a system of 1st-order linear differential equations instead of solving an  $n$ th order linear differential equation. State equations are very useful for analysis of time-varying circuits.

- $n$ th-order linear differential equation:

$$\sum_{k=0}^n a_k y^{(k)}(t) = \sum_{l=0}^m b_l w^{(l)}(t), \quad y(0^-), y'(0^-), \dots, y^{(n-1)}(0^-)$$

- System of 1st-order linear equations:

$$\begin{cases} x_1'(t) = a_{11}x_1(t) + \dots + a_{1n}x_n(t) + b_1w(t) \\ \vdots & \vdots & \vdots \\ x_n'(t) = a_{n1}x_1(t) + \dots + a_{nn}x_n(t) + b_nw(t) \end{cases}$$

- State equations:  $\frac{d}{dt}\mathbf{X}(t) = \mathbf{A}\mathbf{X}(t) + \mathbf{B}w(t), \quad \mathbf{X}(0) = \mathbf{X}_0$
- Output response:  $y(t) = \mathbf{C}^T\mathbf{X}(t) + dw(t)$

## Definition (Network state)

A set of data qualifies to be called the state of a network if it satisfies two conditions

- For any time  $t_0$ , the state at time  $t_0$  and the inputs from  $t_0$  on determine uniquely the state at any time  $t > t_0$ .
- For any time  $t$ , the state at time  $t$  and the inputs at time  $t$  (and sometimes some of their derivatives) determine uniquely every network variable at time  $t$ .

The components of the state are called state variables.

# State Equations for LTI Circuits

# State Variables

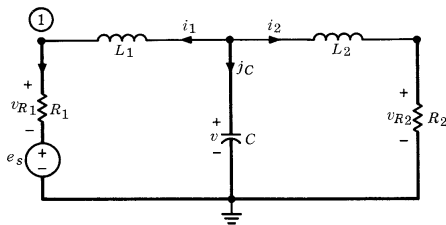


Figure: A **sample suitable tree** for writing **state equations**.

- **State variables:** Independent capacitor voltages and inductor currents.
- **Number of state variables:** Number of independent energy storage elements.
- **Number of state variables:** Circuit order.

# State Equations

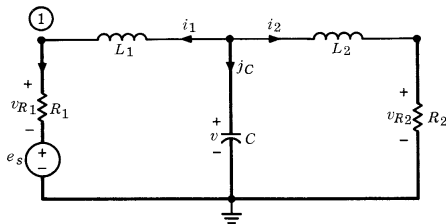


Figure: A **sample suitable tree** for writing **state equations**.


- **State variables:** Independent capacitor voltages and inductor currents.
- **Proper tree:** Capacitors in tree branches and inductors in link branches.
- **State equations:** KCL in fundamental cut sets and KVL in fundamental loops.
- **State equations:**  $\frac{d}{dt}\mathbf{X}(t) = \mathbf{A}\mathbf{X}(t) + \mathbf{B}\mathbf{W}(t)$ ,  $\mathbf{X}(0) = \mathbf{X}_0$
- **Output response:**  $y(t) = \mathbf{C}^T\mathbf{X}(t) + \mathbf{D}^T\mathbf{W}(t)$



# State Equations
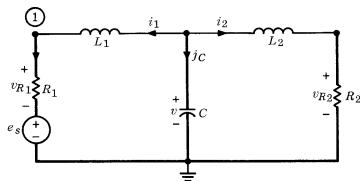
## Example (State equations for a circuit with three state variables)

The first voltage node of the circuit below can be given in terms of state variables.



$$Cv' = -i_1 - i_2$$

$$i_1 = v_{R_1}/R_1$$

$$i_2 = v_{R_2}/R_2$$

$$L_1 i_1' = v - v_{R_1} - e_s$$


$$L_2 i_2' = v - v_{R_2}$$

$$\begin{cases} Cv' = -i_1 - i_2 \\ L_1 i_1' = v - R_1 i_1 - e_s \\ L_2 i_2' = v - R_2 i_2 \end{cases} \Rightarrow \begin{bmatrix} v' \\ i_1' \\ i_2' \end{bmatrix} = \begin{bmatrix} 0 & -1/C & -1/C \\ 1/L_1 & -R_1/L_1 & 0 \\ 1/L_2 & 0 & -R_2/L_2 \end{bmatrix} \begin{bmatrix} v \\ i_1 \\ i_2 \end{bmatrix} + \begin{bmatrix} 0 \\ -1/L_1 \\ 0 \end{bmatrix} e_s$$

# State Equations
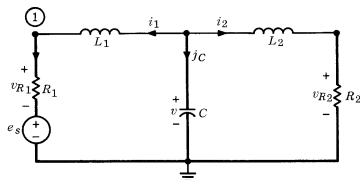
## Example (State equations for a circuit with three state variables (cont.))

The first voltage node of the circuit below can be given in terms of state variables.




$$\mathbf{X}(t) = \begin{bmatrix} v(t) \\ i_1(t) \\ i_2(t) \end{bmatrix}, \mathbf{X}_0 = \mathbf{X}(0) = \begin{bmatrix} v(0) \\ i_1(0) \\ i_2(0) \end{bmatrix} \Rightarrow \frac{d\mathbf{X}}{dt} = \begin{bmatrix} 0 & -1/C & -1/C \\ 1/L_1 & -R_1/L_1 & 0 \\ 1/L_2 & 0 & -R_2/L_2 \end{bmatrix} \mathbf{X} + \begin{bmatrix} 0 \\ -1/L_1 \\ 0 \end{bmatrix} e_s$$

$$e_1 = v_{R_1} + e_s = R_1 i_1 + e_s = \begin{bmatrix} 0 & R_1 & 0 \end{bmatrix} \mathbf{X} + \begin{bmatrix} 1 \end{bmatrix} e_s$$

# State Equations
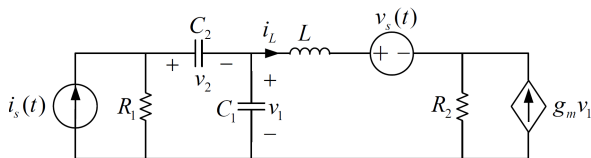
## Example (State equations for a circuit with two inputs)

The capacitor current  $i_2$  in the circuit below can be given in terms of state variables.



$$C_1 v_1' + v_{R_1}/R_1 + i_L - i_s = 0$$

$$v_{R_1} = v_1 + v_2$$

$$C_2 v_2' + v_{R_1}/R_1 - i_s = 0$$

$$v_{R_2} = R_2(i_L + g_m v_1)$$


$$L i_L' + v_s + v_{R_2} - v_1 = 0$$

$$\mathbf{X}(t) = \begin{bmatrix} v_1(t) \\ v_2(t) \\ i_L(t) \end{bmatrix}, \mathbf{X}_0 = \mathbf{X}(0) = \begin{bmatrix} v_1(0) \\ v_2(0) \\ i_L(0) \end{bmatrix} \Rightarrow \frac{d\mathbf{X}}{dt} = \begin{bmatrix} -\frac{1}{R_1 C_1} & -\frac{1}{R_1 C_1} & -\frac{1}{C_1} \\ -\frac{1}{R_1 C_2} & -\frac{1}{R_1 C_2} & 0 \\ \frac{1-g_m R_2}{L} & 0 & -\frac{R_2}{L} \end{bmatrix} \mathbf{X} + \begin{bmatrix} 0 \\ 0 \\ -\frac{1}{L} \end{bmatrix} \begin{bmatrix} v_s \\ i_s \end{bmatrix}$$

# State Equations
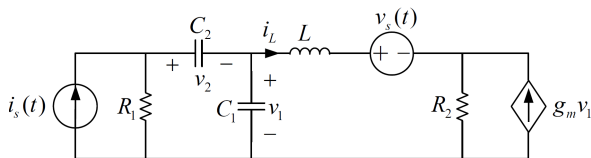
## Example (State equations for a circuit with two inputs (cont.))

The capacitor current  $i_2$  in the circuit below can be given in terms of state variables.



$$\mathbf{x}(t) = \begin{bmatrix} v_1(t) \\ v_2(t) \\ i_L(t) \end{bmatrix}, \mathbf{x}_0 = \mathbf{x}(0) = \begin{bmatrix} v_1(0) \\ v_2(0) \\ i_L(0) \end{bmatrix} \Rightarrow \frac{d\mathbf{x}}{dt} = \begin{bmatrix} -\frac{1}{R_1 C_1} & -\frac{1}{R_1 C_1} & -\frac{1}{C_1} \\ -\frac{1}{R_1 C_2} & -\frac{1}{R_1 C_2} & 0 \\ \frac{1-g_m R_2}{L} & 0 & -\frac{R_2}{L} \end{bmatrix} \mathbf{x} + \begin{bmatrix} 0 \\ 0 \\ -\frac{1}{L} \end{bmatrix} \begin{bmatrix} v_s \\ i_s \end{bmatrix}$$

$$\mathbf{w}(t) = \begin{bmatrix} v_s(t) \\ i_s(t) \end{bmatrix} \Rightarrow i_2 = C_2 v_2' = -\frac{v_1 + v_2}{R_1} + i_s = \begin{bmatrix} -\frac{1}{R_1} & -\frac{1}{R_1} & 0 \end{bmatrix} \mathbf{x} + \begin{bmatrix} 0 & 1 \end{bmatrix} \mathbf{w}$$




# State Equations for LTV circuits

# State Equations

- **State variables:** Independent capacitor voltages and inductor currents.
- **State variables:** Independent capacitor charges and inductor fluxes.
- **Number of state variables:** Number of independent energy storage elements.
- **Proper tree:** Capacitors in tree branches and inductors in link branches.
- **State equations:** KCL in fundamental cut sets and KVL in fundamental loops.
- **State equations:**  $\frac{d}{dt}\mathbf{X}(t) = \mathbf{A}(t)\mathbf{X}(t) + \mathbf{B}(t)\mathbf{W}(t), \quad \mathbf{X}(0) = \mathbf{X}_0$
- **Output response:**  $y(t) = \mathbf{C}^T(t)\mathbf{X}(t) + \mathbf{D}^T(t)\mathbf{W}(t)$
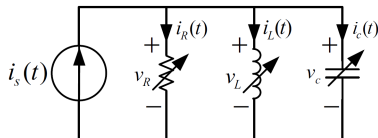
## Example (State equations for an LTV circuit)

Capacitor voltage and inductor current can be used as state variables in the LTV circuit below.



$$\begin{cases} \frac{dq(t)}{dt} + \frac{v_C(t)}{R(t)} + i_L(t) - i_s(t) = 0 \\ \frac{d\phi(t)}{dt} - v_c(t) = 0 \end{cases}, \quad \begin{cases} \frac{dq(t)}{dt} = C(t) \frac{dv_C(t)}{dt} + v_C(t) \frac{C'(t)}{C(t)} \\ \frac{d\phi(t)}{dt} = L(t) \frac{di_L(t)}{dt} + i_L(t) \frac{L'(t)}{L(t)} \end{cases}$$


$$\mathbf{X}(t) = \begin{bmatrix} v_C(t) \\ i_L(t) \end{bmatrix}, \quad \mathbf{X}_0 = \mathbf{X}(0) = \begin{bmatrix} v_C(0) \\ i_L(0) \end{bmatrix} \Rightarrow \frac{d\mathbf{X}(t)}{dt} = \begin{bmatrix} -\frac{1}{R(t)C(t)} - \frac{C'(t)}{C(t)} & 0 \\ 0 & -\frac{1}{L(t)} \end{bmatrix} \mathbf{X}(t) + \begin{bmatrix} -\frac{1}{C(t)} \\ 0 \end{bmatrix} i_s(t)$$



# State Equations
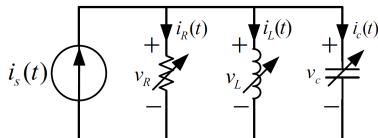
## Example (State equations for an LTV circuit)

Capacitor charge and inductor flux can be used as state variables in the LTV circuit below.



$$\begin{cases} \frac{dq(t)}{dt} + \frac{v_C(t)}{R(t)} + i_L(t) - i_s(t) = 0 \\ \frac{d\phi(t)}{dt} - v_C(t) = 0 \end{cases} \Rightarrow \begin{cases} \frac{dq(t)}{dt} + \frac{q(t)}{c(t)R(t)} + \frac{\phi(t)}{L(t)} - i_s(t) = 0 \\ \frac{d\phi(t)}{dt} - \frac{q(t)}{C(t)} = 0 \end{cases}$$

$$\mathbf{x}(t) = \begin{bmatrix} q(t) \\ \phi(t) \end{bmatrix}, \mathbf{x}_0 = \mathbf{x}(0) = \begin{bmatrix} q(0) \\ \phi(0) \end{bmatrix} \Rightarrow \frac{d\mathbf{x}(t)}{dt} = \begin{bmatrix} -\frac{1}{R(t)C(t)} & -\frac{1}{L(t)} \\ \frac{1}{C(t)} & 0 \end{bmatrix} \mathbf{x}(t) + \begin{bmatrix} 1 \\ 0 \end{bmatrix} i_s(t)$$

# State Equations for NTV circuits


# State Equations

- **State variables:** Independent capacitor charges and inductor fluxes.
- **Number of state variables:** Number of independent energy storage elements.
- **State equations:**  $\frac{d}{dt}\mathbf{X}(t) = f(\mathbf{X}(t), \mathbf{W}(t), t), \quad \mathbf{X}(0) = \mathbf{X}_0$
- **Output response:**  $y(t) = h(\mathbf{X}(t), \mathbf{W}(t), t)$

# State Equations
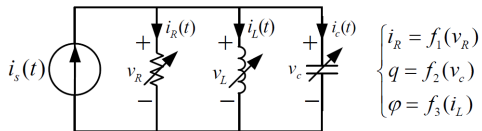
## Example (State equations for an NTI circuit)

Capacitor voltage and inductor current can be used as state variables in the NTI circuit below.




$$\begin{cases} \frac{dq(t)}{dt} + i_R(t) + i_L(t) - i_s(t) = 0 \\ \frac{d\phi(t)}{dt} - v_C(t) = 0 \end{cases}, \quad \begin{cases} \frac{dq(t)}{dt} = \frac{dq}{dv_C} \frac{dv_C}{dt} = f_2'(v_C) \frac{dv_C}{dt} \\ \frac{d\phi(t)}{dt} = \frac{d\phi}{di_L} \frac{di_L}{dt} = f_3'(i_L) \frac{di_L}{dt} \end{cases}$$

$$\mathbf{x}(t) = \begin{bmatrix} v_C(t) \\ i_L(t) \end{bmatrix}, \quad \mathbf{x}_0 = \mathbf{x}(0) = \begin{bmatrix} v_C(0) \\ i_L(0) \end{bmatrix} \Rightarrow \frac{d\mathbf{x}(t)}{dt} = \begin{bmatrix} -f_1(v_C(t)) - i_L(t) + i_s(t) \\ f_2'(v_C(t)) \\ v_C(t) \\ f_3'(i_L(t)) \end{bmatrix}$$

# State Equations
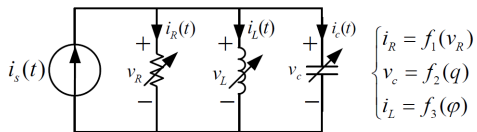
## Example (State equations for a an NTI circuit)

Capacitor charge and inductor flux can be used as state variables in the NTI circuit below.



$$\begin{cases} \frac{dq(t)}{dt} + i_R(t) + i_L(t) - i_s(t) = 0 \\ \frac{d\phi(t)}{dt} - v_c(t) = 0 \end{cases}, \quad \begin{cases} \frac{dq(t)}{dt} + f_1(f_2(q(t))) + f_3(\phi(t)) - i_s(t) = 0 \\ \frac{d\phi(t)}{dt} - f_2(q(t)) = 0 \end{cases}$$

$$\mathbf{x}(t) = \begin{bmatrix} q(t) \\ \phi(t) \end{bmatrix}, \quad \mathbf{x}_0 = \mathbf{x}(0) = \begin{bmatrix} q(0) \\ \phi(0) \end{bmatrix} \Rightarrow \frac{d\mathbf{x}(t)}{dt} = \begin{bmatrix} -f_1(f_2(q(t))) - f_3(\phi(t)) + i_s(t) \\ f_2(q(t)) \end{bmatrix}$$

# Solving State Equations

# Single State Equation

- **Single state equation:**  $x'(t) = ax(t) + bw(t), x(0)$
- **Zero-input response:**  $x_{zi}(t) = x(0)e^{at}, t \geq 0$
- **Zero-state response:**  $x_{zs}(t) = \int_0^t e^{a(t-t')}bw(t')dt', t \geq 0$
- **Complete response:**  $x_{cs}(t) = x_{zi}(t) + x_{zs}(t), t \geq 0$

# System of State Equations

- **Single state equation:**  $\frac{d}{dt}\mathbf{X}(t) = \mathbf{A}\mathbf{X}(t) + \mathbf{B}\mathbf{W}(t), \quad \mathbf{X}(0)$
- **Zero-input response:**  $\mathbf{X}_{zi}(t) = e^{\mathbf{A}t}\mathbf{X}(0), t \geq 0$
- **Zero-state response:**  $\mathbf{X}_{zs}(t) = \int_0^t e^{\mathbf{A}(t-t')}\mathbf{B}\mathbf{W}(t')dt', t \geq 0$
- **Complete response:**  $\mathbf{X}_{cs}(t) = \mathbf{X}_{zi}(t) + \mathbf{X}_{zs}(t), t \geq 0$
- **Matrix exponential:**  $e^{\mathbf{A}t} = \mathbf{I} + \mathbf{A}t + \frac{1}{2!}\mathbf{A}^2t^2 + \frac{1}{3!}\mathbf{A}^3t^3 + \dots$



# Exponential Matrix

- Eigen values and vectors:  $|\mathbf{A} - \lambda\mathbf{I}| = 0 \Rightarrow \lambda_1, \dots, \lambda_n, \mathbf{u}_1, \dots, \mathbf{u}_n$
- Diagonal decomposition:

$$\mathbf{U} = [\mathbf{u}_1 \quad \dots \quad \mathbf{u}_n], \quad \mathbf{\Lambda} = \begin{bmatrix} \lambda_1 & 0 & \dots & 0 \\ 0 & \lambda_2 & \dots & 0 \\ \vdots & \vdots & \ddots & \vdots \\ 0 & 0 & \dots & \lambda_n \end{bmatrix}$$

$$\Rightarrow \mathbf{A} = \mathbf{U}\mathbf{\Lambda}\mathbf{U}^{-1} \Rightarrow e^{\mathbf{A}t} = \mathbf{U}e^{\mathbf{\Lambda}t}\mathbf{U}^{-1}, \quad e^{\mathbf{\Lambda}t} = \begin{bmatrix} e^{\lambda_1 t} & 0 & \dots & 0 \\ 0 & e^{\lambda_2 t} & \dots & 0 \\ \vdots & \vdots & \ddots & \vdots \\ 0 & 0 & \dots & e^{\lambda_n t} \end{bmatrix}$$

# Exponential Matrix

- **Zero-input response:**  $\frac{d}{dt}\mathbf{X}_{zi}(t) = \mathbf{A}\mathbf{X}_{zi}(t), \mathbf{X}_{zi}(0) = \mathbf{X}_0 \Rightarrow \mathbf{X}_{zi}(t) = e^{\mathbf{A}t}\mathbf{X}_0$
- **Laplace-domain zero-input response:**  
 $s\mathbf{X}_{zi}(s) - \mathbf{X}_0 = \mathbf{A}\mathbf{X}_{zi}(s) \Rightarrow \mathbf{X}_{zi}(s) = (s\mathbf{I} - \mathbf{A})^{-1}\mathbf{X}_0$
- **Laplace-domain zero-input response:**  $\mathbf{X}_{zi}(s) = \mathcal{L}\{e^{\mathbf{A}t}\}\mathbf{X}_0$
- **Laplace transform of matrix exponential:**  $\mathcal{L}\{e^{\mathbf{A}t}\} = (s\mathbf{I} - \mathbf{A})^{-1}$
- **Matrix exponential:**  $e^{\mathbf{A}t} = \mathcal{L}^{-1}\{(s\mathbf{I} - \mathbf{A})^{-1}\}$

# State Equations

## Example (Solving state equation)

Matrix diagonal decomposition can be used to solve the matrix state equation below.

$$\frac{d}{dt}\mathbf{X}(t) = \mathbf{A}\mathbf{X}(t), \quad \mathbf{A} = \begin{bmatrix} -0.5 & 1 \\ 1 & -3 \end{bmatrix}$$

$$|\mathbf{A} - \lambda\mathbf{I}| = (-0.5 - \lambda)(-3 - \lambda) + 1 = 0 \Rightarrow \lambda = -1, -2.5$$

$$\mathbf{A}\mathbf{u} = \lambda\mathbf{u} \Rightarrow \mathbf{A}\mathbf{u} = -\mathbf{u} \Rightarrow \mathbf{u} = \begin{bmatrix} 2 \\ 1 \end{bmatrix}$$

$$\mathbf{A}\mathbf{u} = \lambda\mathbf{u} \Rightarrow \mathbf{A}\mathbf{u} = -2.5\mathbf{u} \Rightarrow \mathbf{u} = \begin{bmatrix} 1 \\ 2 \end{bmatrix}$$

$$\mathbf{A} = \mathbf{U}\mathbf{\Lambda}\mathbf{U}^{-1} = \begin{bmatrix} 2 & 1 \\ 1 & 2 \end{bmatrix} \begin{bmatrix} -1 & 0 \\ 0 & -2.5 \end{bmatrix} \begin{bmatrix} 2 & 1 \\ 1 & 2 \end{bmatrix}^{-1}$$

$$e^{\mathbf{A}t} = \mathbf{U}e^{\mathbf{\Lambda}t}\mathbf{U}^{-1} = \begin{bmatrix} 2 & 1 \\ 1 & 2 \end{bmatrix} \begin{bmatrix} e^{-t} & 0 \\ 0 & e^{-2.5t} \end{bmatrix} \begin{bmatrix} 2 & 1 \\ 1 & 2 \end{bmatrix}^{-1} = \frac{1}{3} \begin{bmatrix} 4e^{-t} - e^{-2.5t} & -2e^{-t} + 2e^{-2.5t} \\ 2e^{-t} - 2e^{-2.5t} & -e^{-t} + 4e^{-2.5t} \end{bmatrix}$$

$$\mathbf{X}(t) = e^{\mathbf{A}t}\mathbf{X}_0 = \frac{1}{3} \begin{bmatrix} 4e^{-t} - e^{-2.5t} & -2e^{-t} + 2e^{-2.5t} \\ 2e^{-t} - 2e^{-2.5t} & -e^{-t} + 4e^{-2.5t} \end{bmatrix} \mathbf{X}_0$$

## Example (Solving state equation)

Laplace transform can be used to solve the matrix state equation below.

$$\frac{d}{dt}\mathbf{X}(t) = \mathbf{A}\mathbf{X}(t), \quad \mathbf{A} = \begin{bmatrix} -0.5 & 1 \\ 1 & -3 \end{bmatrix}$$

$$e^{\mathbf{A}t} = \mathcal{L}^{-1}\{(s\mathbf{I} - \mathbf{A})^{-1}\} = \mathcal{L}^{-1}\left\{ \begin{bmatrix} s + 0.5 & 1 \\ -1 & s + 3 \end{bmatrix}^{-1} \right\} = \mathcal{L}^{-1}\left\{ \begin{bmatrix} \frac{s+3}{(s+1)(s+2.5)} & \frac{-1}{(s+1)(s+2.5)} \\ \frac{1}{(s+1)(s+2.5)} & \frac{s+0.5}{(s+1)(s+2.5)} \end{bmatrix} \right\}$$

$$\mathbf{X}(t) = e^{\mathbf{A}t}\mathbf{X}_0 = \frac{1}{3} \begin{bmatrix} 4e^{-t} - e^{-2.5t} & -2e^{-t} + 2e^{-2.5t} \\ 2e^{-t} - 2e^{-2.5t} & -e^{-t} + 4e^{-2.5t} \end{bmatrix} \mathbf{X}_0$$


# Response Equation

- **State equations:**  $\frac{d}{dt}\mathbf{X}(t) = \mathbf{A}\mathbf{X}(t) + \mathbf{B}w(t), \quad \mathbf{X}(0) = \mathbf{X}_0$
- **Laplace-domain state equations:**  
 $s\mathbf{X}(s) - \mathbf{X}_0 = \mathbf{A}\mathbf{X}(s) + \mathbf{B}W(s) \Rightarrow \mathbf{X}(s) = (s\mathbf{I} - \mathbf{A})^{-1}\mathbf{B}W(s) + (s\mathbf{I} - \mathbf{A})^{-1}\mathbf{X}_0$
- **Single-input Output response:**  $y(t) = \mathbf{C}^T\mathbf{X}(t) + dw(t)$
- **Laplace transform of Output response:**  
 $Y(s) = \mathbf{C}^T\mathbf{X}(s) + dW(s) = \mathbf{C}^T[(s\mathbf{I} - \mathbf{A})^{-1}\mathbf{B}W(s) + (s\mathbf{I} - \mathbf{A})^{-1}\mathbf{X}_0] + dW(s)$
- **Transfer function:**  $H(s) = \left. \frac{Y(s)}{W(s)} \right|_{\mathbf{X}_0=0} = \mathbf{C}^T(s\mathbf{I} - \mathbf{A})^{-1}\mathbf{B} + d$

# Single-input Response Equation
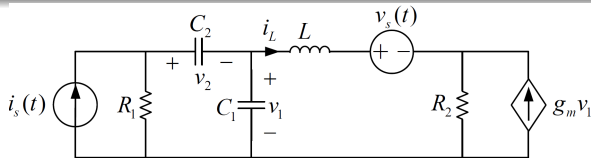
## Example (Transfer function)

Transfer function can be found by the matrices involved in state equations



$$\mathbf{X}(t) = \begin{bmatrix} v_1(t) \\ v_2(t) \\ i_L(t) \end{bmatrix} \Rightarrow \frac{d\mathbf{X}}{dt} = \begin{bmatrix} -\frac{1}{R_1 C_1} & -\frac{1}{R_1 C_1} & -\frac{1}{C_1} \\ -\frac{1}{R_1 C_2} & -\frac{1}{R_1 C_2} & 0 \\ \frac{1-gmR_2}{L} & 0 & -\frac{R_2}{L} \end{bmatrix} \mathbf{X} + \begin{bmatrix} 0 \\ 0 \\ -\frac{1}{L} \end{bmatrix} v_s + \begin{bmatrix} \frac{1}{C_1} \\ \frac{1}{C_2} \\ 0 \end{bmatrix} i_s$$

$$\mathbf{W}(t) = \begin{bmatrix} v_s(t) \\ i_s(t) \end{bmatrix} \Rightarrow i_2 = C_2 v_2' = \begin{bmatrix} -\frac{1}{R_1} & -\frac{1}{R_1} & 0 \end{bmatrix} \mathbf{X} + 0 \times v_s(t) + 1 \times i_s(t)$$

$$H_1(s) = \frac{i_2(s)}{V_s(s)} \Big|_{i_s(s)=0} = \begin{bmatrix} -\frac{1}{R_1} & -\frac{1}{R_1} & 0 \end{bmatrix} \begin{bmatrix} s + \frac{1}{R_1 C_1} & \frac{1}{R_1 C_1} & \frac{1}{C_1} \\ \frac{1}{R_1 C_2} & s + \frac{1}{R_1 C_2} & 0 \\ -\frac{1-gmR_2}{L} & 0 & s + \frac{R_2}{L} \end{bmatrix}^{-1} \begin{bmatrix} 0 \\ 0 \\ -\frac{1}{L} \end{bmatrix} + 0$$

$$H_2(s) = \frac{i_2(s)}{i_s(s)} \Big|_{V_s(s)=0} = \begin{bmatrix} -\frac{1}{R_1} & -\frac{1}{R_1} & 0 \end{bmatrix} \begin{bmatrix} s + \frac{1}{R_1 C_1} & \frac{1}{R_1 C_1} & \frac{1}{C_1} \\ \frac{1}{R_1 C_2} & s + \frac{1}{R_1 C_2} & 0 \\ -\frac{1-gmR_2}{L} & 0 & s + \frac{R_2}{L} \end{bmatrix}^{-1} \begin{bmatrix} \frac{1}{C_1} \\ \frac{1}{C_2} \\ 0 \end{bmatrix} + 1$$

# Approximated Solution

- General state equations:  $\frac{d}{dt}\mathbf{X}(t) = f(\mathbf{X}(t)), \quad \mathbf{X}(0) = \mathbf{X}_0$
- Approximated solution for general state equations:

$$\mathbf{X}(\Delta t) \approx \mathbf{X}(0) + \left. \frac{d}{dt}\mathbf{X}(t) \right|_{t=0} \Delta t = \mathbf{X}(0) + f(\mathbf{X}(0))\Delta t$$

$$\mathbf{X}(2\Delta t) \approx \mathbf{X}(\Delta t) + f(\mathbf{X}(\Delta t))\Delta t$$

⋮

$$\mathbf{X}((k+1)\Delta t) \approx \mathbf{X}(k\Delta t) + f(\mathbf{X}(k\Delta t))\Delta t$$

- Approximated solution for LTI state equations:

$$\mathbf{X}((k+1)\Delta t) \approx \mathbf{X}(k\Delta t) + f(\mathbf{X}(k\Delta t))\Delta t = \mathbf{X}(k\Delta t) + \mathbf{A}\mathbf{X}(k\Delta t)\Delta t$$

$$\mathbf{X}((k+1)\Delta t) \approx (\mathbf{I} + \mathbf{A}\Delta t)\mathbf{X}(k\Delta t)$$

# State Trajectory

## Example (State trajectory)

State trajectory can be plotted using approximated numerical methods.

$$\frac{d}{dt}\mathbf{X}(t) = \mathbf{A}\mathbf{X}(t), \quad \mathbf{A} = \begin{bmatrix} -1 & 0 \\ -1 & -3 \end{bmatrix}, \quad \mathbf{X}_0 = \begin{bmatrix} 1 \\ 0 \end{bmatrix}$$

$$e^{\mathbf{A}t} = \mathcal{L}^{-1}\{(s\mathbf{I} - \mathbf{A})^{-1}\} = \mathcal{L}^{-1}\left\{ \begin{bmatrix} s+1 & 0 \\ -1 & s+3 \end{bmatrix}^{-1} \right\} = \mathcal{L}^{-1}\left\{ \begin{bmatrix} \frac{1}{s+1} & 0 \\ \frac{-1}{(s+1)(s+3)} & \frac{1}{s+3} \end{bmatrix} \right\}$$

$$\mathbf{X}(t) = \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix} = e^{\mathbf{A}t}\mathbf{X}_0 = \begin{bmatrix} e^{-t} & 0 \\ -0.5e^{-t} + 0.5e^{-3t} & e^{-3t} \end{bmatrix} \begin{bmatrix} 1 \\ 0 \end{bmatrix} = \begin{bmatrix} e^{-t} \\ -0.5e^{-t} + 0.5e^{-3t} \end{bmatrix} \Rightarrow x_2 = \frac{-x_1 + x_1^3}{2}$$

$$\Delta t = 0.1 \Rightarrow \mathbf{I} + \mathbf{A}\Delta t = \begin{bmatrix} 0.9 & 0 \\ -0.1 & 0.7 \end{bmatrix} \Rightarrow \mathbf{X}(0) = \begin{bmatrix} 1 \\ 0 \end{bmatrix}, \mathbf{X}(0.1) = \begin{bmatrix} 0.9 & 0 \\ -0.1 & 0.7 \end{bmatrix} \begin{bmatrix} 1 \\ 0 \end{bmatrix} = \begin{bmatrix} 0.9 \\ -0.1 \end{bmatrix}$$


$$\mathbf{X}(0.2) = \begin{bmatrix} 0.81 \\ -0.16 \end{bmatrix}, \mathbf{X}(0.3) = \begin{bmatrix} 0.729 \\ -0.193 \end{bmatrix}, \dots, \mathbf{X}(0.2) = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$



# State Trajectory
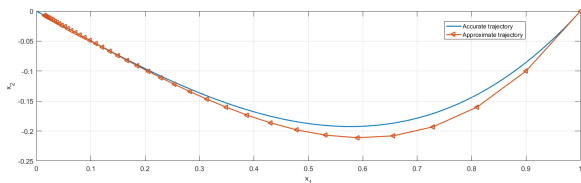
## Example (State trajectory)

State trajectory can be plotted using approximated numerical methods.



## Example (State trajectory)

Natural frequencies involved in the response can be removed if the initial condition equal eigen vectors.

$$\frac{d}{dt}\mathbf{X}(t) = \mathbf{A}\mathbf{X}(t), \quad \mathbf{A} = \begin{bmatrix} -1 & 0 \\ -1 & -3 \end{bmatrix}, \quad \mathbf{X}_0 = \begin{bmatrix} a \\ b \end{bmatrix}$$

$$\mathbf{X}(t) = \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix} = \begin{bmatrix} e^{-t} & 0 \\ -0.5e^{-t} + 0.5e^{-3t} & e^{-3t} \end{bmatrix} \begin{bmatrix} a \\ b \end{bmatrix} = \begin{bmatrix} ae^{-t} \\ -0.5ae^{-t} + (0.5a + b)e^{-3t} \end{bmatrix}$$

$$\Rightarrow x_2 = -0.5x_1 + 0.5x_1^3 + \frac{b}{a}x_1^3$$

$$\mathbf{A} = \begin{bmatrix} -1 & 0 \\ -1 & -3 \end{bmatrix} \Rightarrow \lambda_{1,2} = -1, -2, \quad \mathbf{u}_1 = \begin{bmatrix} 0 \\ 1 \end{bmatrix}, \mathbf{u}_2 = \begin{bmatrix} 1 \\ 1 \end{bmatrix}$$

$$\mathbf{X}_0 = \begin{bmatrix} a \\ b \end{bmatrix} = \begin{bmatrix} 0 \\ 1 \end{bmatrix} \Rightarrow \mathbf{X}(t) = \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix} = \begin{bmatrix} 0 \\ e^{-3t} \end{bmatrix} \Rightarrow x_1 = 0, x_2 \in [0, 1]$$

# The End