

Three-phase Circuits

Mohammad Hadi

mohammad.hadi@sharif.edu

@MohammadHadiDastgerdi

Fall 2021

Overview

- 1 Electricity Delivery System
- 2 Three-phase Voltage Source
- 3 Three-phase Balanced Circuits
- 4 Three-phase Inter-connection
- 5 Power Measurement
- 6 Phase Sequence Determination

Electricity Delivery System

Electricity Delivery System

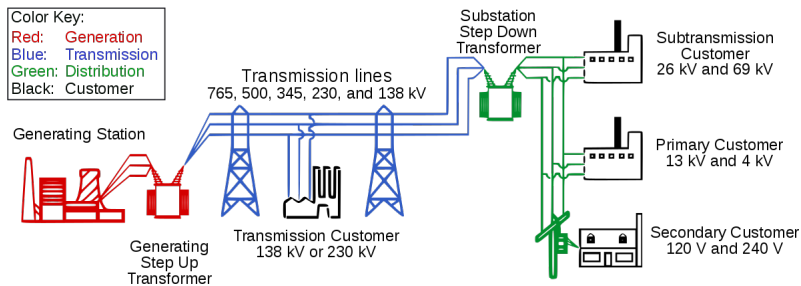


Figure: Electricity delivery system.

- **Generation**, **transmission**, and **distribution** subsystems
- **Three-phase** and **high-voltage** transmission

High-voltage Transmission

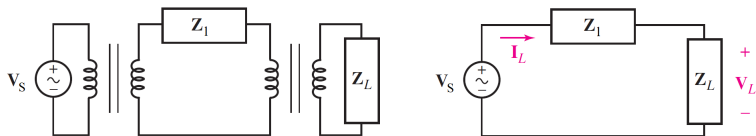


Figure: Simplified power transmission model with $Z_L = R_L + jX_L$ and $Z_1 = R_1 + jX_1$.

- **Load power:** $P_L = |V_L||I_L| \cos(\angle V_L - \angle I_L)$
- **Transmission loss:** $P_I = R_1 |I_L|^2 = \frac{R_1 P_L^2}{V_L^2 \cos^2(\angle V_L - \angle I_L)}$
- **High transmission voltage** to reduce transmission loss
- **Unit power factor** to reduce transmission loss

Three-phase Transmission

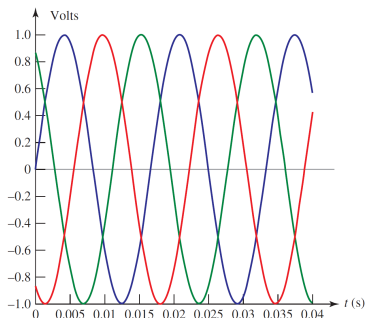


Figure: An example set of three voltages, each of which is 120° out of phase with the other two.

- Three-phase synchronous **generators**
- Three-phase **loads** and motors
- **Three-wire** transmission line
- **Constant** instantaneous power delivery
- Efficient **rectification** for DC generation

Three-phase Voltage Source

Three-phase Voltage Source

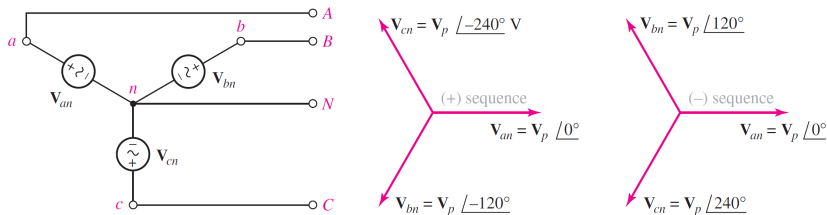


Figure: Positive (abc) and negative (acb) phase sequence in three-phase voltage source.

- Positive sequence:

$$\begin{cases} v_{an}(t) = V \cos(\omega t) & \equiv V_{an} = V \angle 0^\circ \\ v_{bn}(t) = V \cos(\omega t - 120^\circ) & \equiv V_{bn} = V \angle -120^\circ \\ v_{cn}(t) = V \cos(\omega t + 120^\circ) & \equiv V_{cn} = V \angle 120^\circ \end{cases}$$

- Negative sequence:

$$\begin{cases} v_{an}(t) = V \cos(\omega t) & \equiv V_{an} = V \angle 0^\circ \\ v_{bn}(t) = V \cos(\omega t + 120^\circ) & \equiv V_{bn} = V \angle 120^\circ \\ v_{cn}(t) = V \cos(\omega t - 120^\circ) & \equiv V_{cn} = V \angle -120^\circ \end{cases}$$

$$v_{an}(t) + v_{bn}(t) + v_{cn}(t) = 0 \Rightarrow V_{an} + V_{bn} + V_{cn} = 0$$

Three-phase Balanced Circuits

Three-phase Balanced Circuits

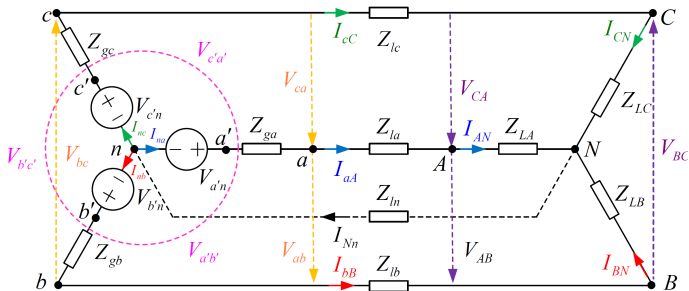


Figure: A three-phase system, connected Y-Y and including a neutral.

- KCL:
$$\frac{V_{Nn}}{Z_{ln}} + \frac{V_{Nn} - V_{a'n}}{Z_{ga} + Z_{la} + Z_{LA}} + \frac{V_{Nn} - V_{b'n}}{Z_{gb} + Z_{lb} + Z_{LB}} + \frac{V_{Nn} - V_{c'n}}{Z_{gc} + Z_{lc} + Z_{LC}} = 0$$

- Balanced condition:
$$\begin{cases} V_{a'n} + V_{b'n} + V_{c'n} = 0 \\ Z_{ga} = Z_{gb} = Z_{gc} = Z_g \\ Z_{la} = Z_{lb} = Z_{lc} = Z_l \\ Z_{LA} = Z_{LB} = Z_{LC} = Z_L \end{cases} \Rightarrow V_{Nn} = 0 \Rightarrow I_{Nn} = 0$$

Three-phase Balanced Circuits

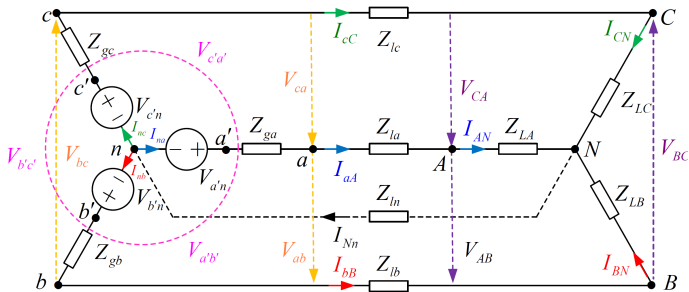


Figure: A three-phase system, connected Y-Y and including a neutral.

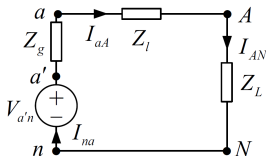


Figure: Single-phase equivalent circuit for a balanced positive-sequence Y-Y three-phase system.

Three-phase Inter-connection

Three-phase Inter-connection

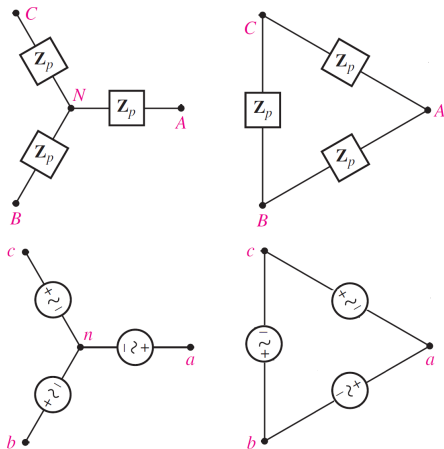


Figure: Typical three-phase connections for source and load.

Phase/Line Quantities

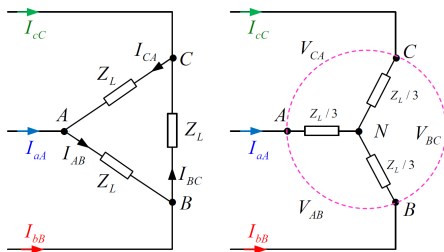


Figure: Phase and line quantities for load in Δ and Y connections.

- Δ load:

- Line voltages: (V_{AB}, V_{BC}, V_{CA})
- Line currents: (I_{aA}, I_{bB}, I_{cC})
- Phase voltages: (V_{AB}, V_{BC}, V_{CA})
- Phase currents: (I_{AB}, I_{BC}, I_{CA})

- Y load:

- Line voltages: (V_{AB}, V_{BC}, V_{CA})
- Line currents: (I_{aA}, I_{bB}, I_{cC})
- Phase voltages: (V_{AN}, V_{BN}, V_{CN})
- Phase currents: (I_{aA}, I_{bB}, I_{cC})

Phase/Line Quantities

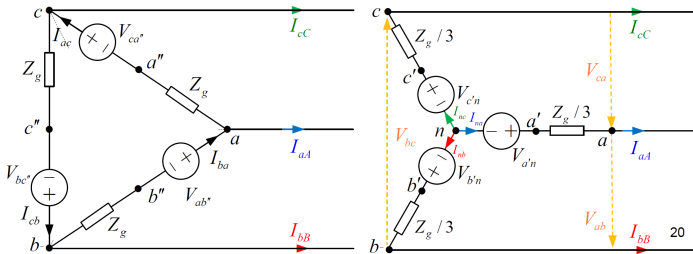


Figure: Phase and line quantities for source in Δ and Y connections.

- Δ source:

- Line voltages: (V_{ab}, V_{bc}, V_{ca})
- Line currents: (I_{aA}, I_{bB}, I_{cC})
- Phase voltages: (V_{ab}, V_{bc}, V_{ca})
- Phase currents: (I_{ba}, I_{cb}, I_{ac})

- Y source:

- Line voltages: (V_{ab}, V_{bc}, V_{ca})
- Line currents: (I_{aA}, I_{bB}, I_{cC})
- Phase voltages: (V_{an}, V_{bn}, V_{cn})
- Phase currents: (I_{aA}, I_{bB}, I_{cC})

Δ -Y Conversion

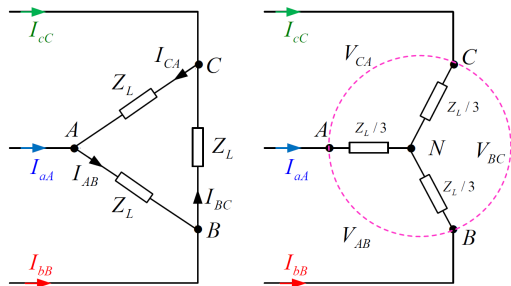


Figure: Δ -Y conversion for **balanced load**.

Δ -Y Conversion

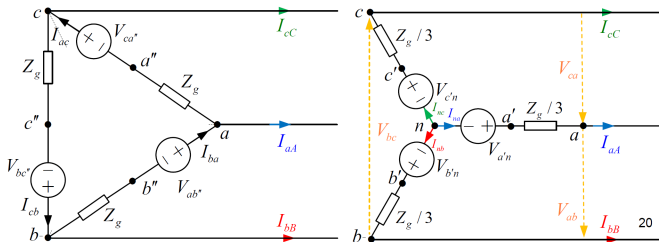


Figure: Δ -Y conversion for **balanced source**, where $(V_{a'n}, V_{b'n}, V_{c'n}) = (\frac{1}{\sqrt{3}}\underline{-30^\circ})(V_{ab''}, V_{bc''}, V_{ca''})$ for **positive** sequence and $(V_{a'n}, V_{b'n}, V_{c'n}) = (\frac{1}{\sqrt{3}}\underline{30^\circ})(V_{ab''}, V_{bc''}, V_{ca''})$ for **negative** sequence.

$$\begin{cases} V_{c'n} - V_{a'n} = V_{ca''} \\ V_{a'n} - V_{b'n} = V_{ab''} \\ V_{b'n} - V_{c'n} = V_{bc''} \\ V_{a'n} + V_{b'n} + V_{c'n} = 0 \end{cases} \Rightarrow \begin{cases} V_{a'n} = \frac{1}{3}V_{ab''} - \frac{1}{3}V_{ca''} \\ V_{b'n} = \frac{1}{3}V_{bc''} - \frac{1}{3}V_{ab''} \\ V_{c'n} = \frac{1}{3}V_{ca''} - \frac{1}{3}V_{bc''} \\ V_{ab''} + V_{bc''} + V_{ca''} = 0 \end{cases}$$

Y-Y Balanced Connection

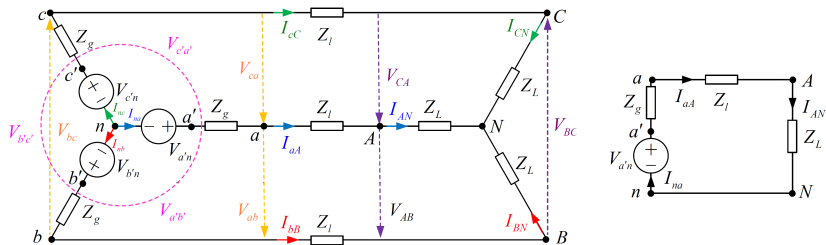


Figure: Single-phase equivalent circuit for a balanced positive-sequence Y-Y three-phase system.

- At source:

- $|V_{ab}| = \sqrt{3}|V_{a'n}|$
- $|I_{aA}|$
- $|S_S| = \sqrt{3}|V_{ab}||I_{aA}|$

- At load:

- $|V_{AB}| = \sqrt{3}|V_{AN}|$
- $|I_{aA}|$
- $|S_L| = \sqrt{3}|V_{AB}||I_{aA}|$

Y-Y Balanced Connection

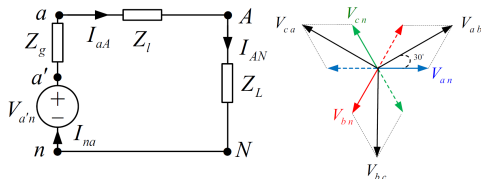


Figure: Single-phase equivalent circuit for a balanced positive-sequence Y-Y three-phase system.

• Source:

- KVL: $I_{aA} = \frac{V_{a'n}}{Z_g + Z_l + Z_L}$
- KVL: $V_{an} = V_{a'n} - I_{na}Z_g$
- KVL: $V_{ab} = V_{an} - V_{bn} = V_{an} - V_{an} \angle -120^\circ = V_{an} \sqrt{3} \angle 30^\circ$
- **Line currents:** $(I_{aA}, I_{bB}, I_{cC}) = I_{aA} (1, 1 \angle -120^\circ, 1 \angle +120^\circ)$
- **Line voltage:** $(V_{ab}, V_{bc}, V_{ca}) = V_{ab} (1, 1 \angle -120^\circ, 1 \angle +120^\circ)$
- **Phase currents:** (I_{aA}, I_{bB}, I_{cC})
- **Phase voltage:** $(V_{an}, V_{bn}, V_{cn}) = \frac{1}{\sqrt{3}} \angle -30^\circ (V_{ab}, V_{bc}, V_{ca})$

Y-Y Balanced Connection

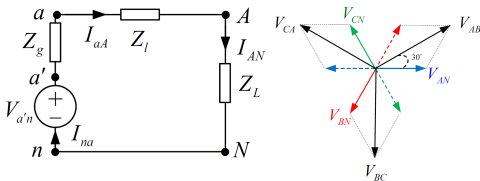


Figure: Single-phase equivalent circuit for a balanced positive-sequence Y-Y three-phase system.

● Load:

- KVL: $I_{aA} = \frac{V_{a'n}}{Z_g + Z_l + Z_L}$
- KVL: $V_{AN} = I_{AN} Z_L$
- KVL: $V_{AB} = V_{AN} - V_{BN} = V_{AN} - V_{AN} \angle -120^\circ = V_{AN} \sqrt{3} \angle 30^\circ$
- **Line currents:** $(I_{aA}, I_{bB}, I_{cC}) = I_{aA} (1, 1 \angle -120^\circ, 1 \angle +120^\circ)$
- **Line voltage:** $(V_{AB}, V_{BC}, V_{CA}) = V_{AB} (1, 1 \angle -120^\circ, 1 \angle +120^\circ)$
- **Phase currents:** (I_{aA}, I_{bB}, I_{cC})
- **Phase voltage:** $(V_{AN}, V_{BN}, V_{CN}) = \frac{1}{\sqrt{3}} \angle -30^\circ (V_{AB}, V_{BC}, V_{CA})$

Y-Y Connection

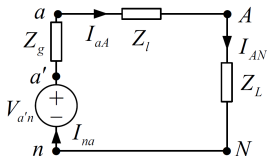


Figure: Single-phase equivalent circuit for a balanced positive-sequence Y-Y three-phase system.

- Delivered instantaneous power:

$$\begin{aligned} p_S(t) &= v_{an}(t)i_{na}(t) + v_{bn}(t)i_{nb}(t) + v_{cn}(t)i_{nc}(t) \\ &= |V_{an}||I_{aA}|\left[\cos(\angle V_{an} - \angle I_{aA}) + \cos(2\omega t + \angle V_{an} + \angle I_{aA})\right] \\ &\quad + |V_{bn}||I_{bB}|\left[\cos(\angle V_{bn} - \angle I_{bB}) + \cos(2\omega t + \angle V_{bn} + \angle I_{bB})\right] \\ &\quad + |V_{cn}||I_{cC}|\left[\cos(\angle V_{cn} - \angle I_{cC}) + \cos(2\omega t + \angle V_{cn} + \angle I_{cC})\right] \\ &= |V_{an}||I_{aA}|\left[\cos(2\omega t + \angle V_{an} + \angle I_{aA}) + \cos(2\omega t + \angle V_{an} + \angle I_{aA} - 240^\circ)\right. \\ &\quad \left. + \cos(2\omega t + \angle V_{an} + \angle I_{aA} + 240^\circ)\right] + 3|V_{an}||I_{aA}|\cos(\angle V_{an} - \angle I_{aA}) \\ &= 3|V_{an}||I_{aA}|\cos(\angle V_{an} - \angle I_{aA}) \\ &= \sqrt{3}|V_{ab}||I_{aA}|\cos(\angle V_{an} - \angle I_{aA}) \end{aligned}$$

Y-Y Connection

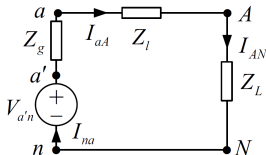


Figure: Single-phase equivalent circuit for a balanced positive-sequence Y-Y three-phase system.

- Delivered apparent power:

$$\begin{aligned} S_S &= V_{an}I_{na}^* + V_{bn}I_{nb}^* + V_{cn}I_{nc}^* \\ &= |V_{an}||I_{aA}|(\angle V_{an} - \angle I_{aA}) + |V_{bn}||I_{bB}|(\angle V_{bn} - \angle I_{bB}) + |V_{cn}||I_{cC}|(\angle V_{cn} - \angle I_{cC}) \\ &= 3|V_{an}||I_{aA}|(\angle V_{an} - \angle I_{aA}) = \sqrt{3}|V_{ab}||I_{aA}|(\angle V_{an} - \angle I_{aA}) \end{aligned}$$

- Delivered real power:

$$P_S = 3|V_{an}||I_{aA}| \cos(\angle V_{an} - \angle I_{aA}) = \sqrt{3}|V_{ab}||I_{aA}| \cos(\angle V_{an} - \angle I_{aA})$$

- Delivered reactive power:

$$Q_S = 3|V_{an}||I_{aA}| \sin(\angle V_{an} - \angle I_{aA}) = \sqrt{3}|V_{ab}||I_{aA}| \sin(\angle V_{an} - \angle I_{aA})$$

Y-Y Connection

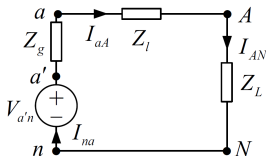


Figure: Single-phase equivalent circuit for a balanced positive-sequence Y-Y three-phase system.

- Absorbed instantaneous power:

$$\begin{aligned} p_L(t) &= v_{AN}(t)i_{AN}(t) + v_{BN}(t)i_{BN}(t) + v_{CN}(t)i_{CN}(t) \\ &= |V_{AN}||I_{aA}|\cos(\angle V_{AN} - \angle I_{aA}) + \cos(2\omega t + \angle V_{AN} + \angle I_{aA}) \\ &\quad + |V_{BN}||I_{bB}|\cos(\angle V_{BN} - \angle I_{bB}) + \cos(2\omega t + \angle V_{BN} + \angle I_{bB}) \\ &\quad + |V_{CN}||I_{cC}|\cos(\angle V_{CN} - \angle I_{cC}) + \cos(2\omega t + \angle V_{CN} + \angle I_{cC}) \\ &= |V_{AN}||I_{aA}|\cos(2\omega t + \angle V_{AN} + \angle I_{aA}) + \cos(2\omega t + \angle V_{AN} + \angle I_{aA} - 240^\circ) \\ &\quad + \cos(2\omega t + \angle V_{AN} + \angle I_{aA} + 240^\circ) + 3|V_{AN}||I_{aA}|\cos(\angle V_{AN} - \angle I_{aA}) \\ &= 3|V_{AN}||I_{aA}|\cos(\angle V_{AN} - \angle I_{aA}) \\ &= \sqrt{3}|V_{AB}||I_{aA}|\cos(\angle V_{AN} - \angle I_{aA}) \\ &= \sqrt{3}|V_{AB}||I_{aA}|\cos(\angle Z_L) \end{aligned}$$

Y-Y Connection

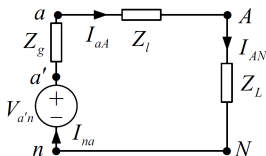


Figure: Single-phase equivalent circuit for a balanced positive-sequence Y-Y three-phase system.

- Absorbed apparent power:

$$\begin{aligned} S_L &= V_{AN} I_{AN}^* + V_{BN} I_{BN}^* + V_{CN} I_{CN}^* \\ &= |V_{AN}| |I_{aA}| (\angle V_{AN} - \angle I_{aA}) + |V_{BN}| |I_{bB}| (\angle V_{BN} - \angle I_{bB}) + |V_{CN}| |I_{cC}| (\angle V_{CN} - \angle I_{cC}) \\ &= 3 |V_{AN}| |I_{aA}| (\angle V_{AN} - \angle I_{aA}) = \sqrt{3} |V_{AB}| |I_{aA}| (\angle V_{AN} - \angle I_{aA}) = \sqrt{3} |V_{AB}| |I_{aA}| (\angle Z_L) \end{aligned}$$

- Absorbed real power:

$$P_L = 3 |V_{AN}| |I_{aA}| \cos(\angle V_{AN} - \angle I_{aA}) = \sqrt{3} |V_{AB}| |I_{aA}| \cos(\angle V_{AN} - \angle I_{aA}) = \sqrt{3} |V_{AB}| |I_{aA}| \cos(\angle Z_L)$$

- Absorbed reactive power:

$$Q_L = 3 |V_{AN}| |I_{aA}| \sin(\angle V_{AN} - \angle I_{aA}) = \sqrt{3} |V_{AB}| |I_{aA}| \sin(\angle V_{AN} - \angle I_{aA}) = \sqrt{3} |V_{AB}| |I_{aA}| \sin(\angle Z_L)$$

Y-Δ Balanced Connection

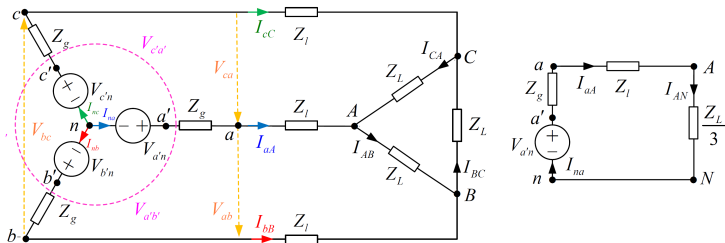


Figure: Single-phase equivalent circuit for a balanced positive-sequence Y-Δ three-phase system.

- At source:

- $|V_{ab}| = \sqrt{3}|V_{an}|$
- $|I_{aA}|$
- $|S_S| = \sqrt{3}|V_{ab}||I_{aA}|$

- At load:

- $|V_{AB}|$
- $|I_{aA}| = \sqrt{3}|I_{AB}|$
- $|S_L| = \sqrt{3}|V_{AB}||I_{aA}|$

Y-Δ Connection

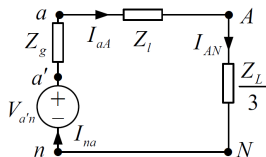


Figure: Single-phase equivalent circuit for a balanced positive-sequence Y-Δ three-phase system.

- Absorbed instantaneous power:

$$p_L(t) = 3|V_{AB}||I_{AB}|\cos(\angle V_{AB} - \angle I_{AB}) = \sqrt{3}|V_{AB}||I_{aA}|\cos(\angle V_{AB} - \angle I_{AB}) = \sqrt{3}|V_{AB}||I_{aA}|\cos(\angle Z_L)$$

- Absorbed apparent power:

$$S_L = 3|V_{AB}||I_{AB}|(\angle V_{AB} - \angle I_{AB}) = \sqrt{3}|V_{AB}||I_{aA}|(\angle V_{AB} - \angle I_{AB}) = \sqrt{3}|V_{AB}||I_{aA}|(\angle Z_L)$$

- Absorbed real power:

$$P_L = 3|V_{AB}||I_{AB}|\cos(\angle V_{AB} - \angle I_{AB}) = \sqrt{3}|V_{AB}||I_{aA}|\cos(\angle V_{AB} - \angle I_{AB}) = \sqrt{3}|V_{AB}||I_{aA}|\cos(\angle Z_L)$$

- Absorbed reactive power:

$$Q_L = 3|V_{AB}||I_{AB}|\sin(\angle V_{AB} - \angle I_{AB}) = \sqrt{3}|V_{AB}||I_{aA}|\sin(\angle V_{AB} - \angle I_{AB}) = \sqrt{3}|V_{AB}||I_{aA}|\sin(\angle Z_L)$$

Δ -Y Balanced Connection

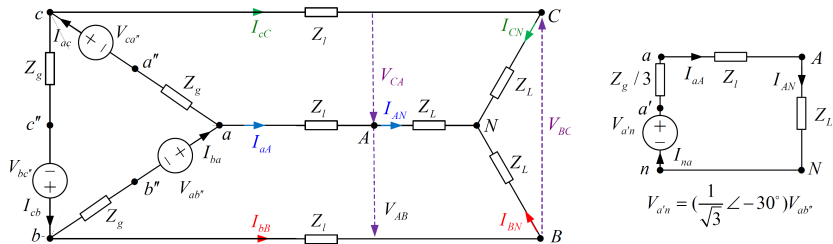


Figure: Single-phase equivalent circuit for a balanced positive-sequence Δ -Y three-phase system.

- At source:

- $|V_{ab}|$
- $|I_{aA}| = \sqrt{3}|I_{ba}|$
- $|S_S| = \sqrt{3}|V_{ab}||I_{aA}|$

- At load:

- $|V_{AB}| = \sqrt{3}|V_{AN}|$
- $|I_{aA}|$
- $|S_L| = \sqrt{3}|V_{AB}||I_{aA}|$

Δ - Δ Balanced Connection

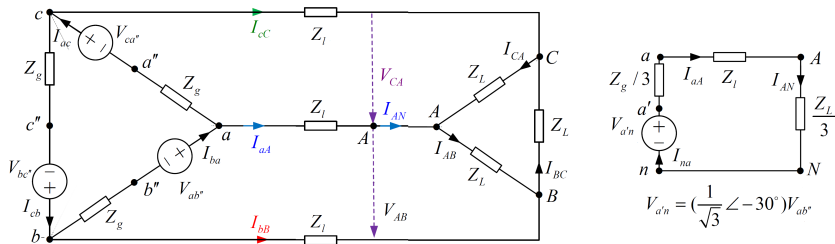


Figure: Single-phase equivalent circuit for a balanced positive-sequence Δ - Δ three-phase system.

- At source:

- $|V_{ab}|$
- $|I_{aA}| = \sqrt{3}|I_{ba}|$
- $|S_S| = \sqrt{3}|V_{ab}||I_{aA}|$

- At load:

- $|V_{AB}|$
- $|I_{aA}| = \sqrt{3}|I_{AB}|$
- $|S_L| = \sqrt{3}|V_{AB}||I_{aA}|$

Balanced Three-phase Interconnection

Example (Delta-Wye connection for induction motors)


Induction motors provide much torque for Δ connection.

• Y connection:

$$\begin{aligned}P_Y &= \sqrt{3} |V_{AB}| |I_{aA}| \cos(\angle Z_L) \\&= \sqrt{3} |V_{AB}| \frac{|V_{AN}|}{|Z_L|} \cos(\angle Z_L) \\&= \frac{|V_{AB}|^2}{|Z_L|} \cos(\angle Z_L)\end{aligned}$$

• Δ connection:

$$\begin{aligned}P_\Delta &= \sqrt{3} |V_{AB}| |I_{aA}| \cos(\angle Z_L) \\&= \sqrt{3} |V_{AB}| \sqrt{3} |I_{AB}| \cos(\angle Z_L) \\&= 3 |V_{AB}| \frac{|V_{AB}|}{|Z_L|} \cos(\angle Z_L) = 3P_Y\end{aligned}$$

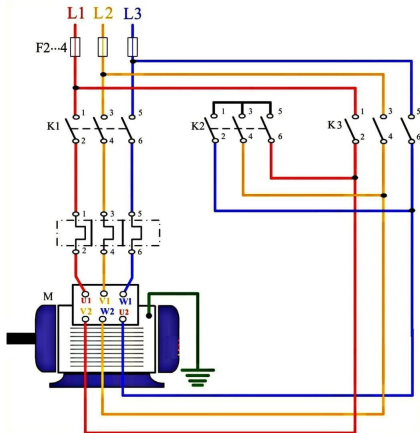

Balanced Three-phase Interconnection

Example (Reactive power compensation)

The pure leading capacitive load Z_1 can compensate for the reactive power absorbed by the lagging inductive load Z_2 with $\text{PF}_2 = 0.75$ and $|S_2| = 30 \text{ kVA}$, where the line voltage is $381 \text{ V}_{\text{rms}}$.

- **Inductive load:**

$$S_2 = 30 / \angle +\cos^{-1}(0.75) = 30 / \angle 41.41^\circ = 22.5 + j19.84 \text{ kVA}$$

- **Capacitive load:**


$$S_1 = 3V_{A_1B_1} I_{A_1B_1}^* = 3(jB_c)^* |V_{A_1B_1}|^2 = -j3B_c \times 381^2 \text{ VA}$$

- **Overall load:**

$$S = S_1 + S_2 = 22.5 + j19.84 - j435.5B_c$$

$$\Im S = 0 \Rightarrow B_c = 0.0456 \text{ } \Omega^{-1}$$
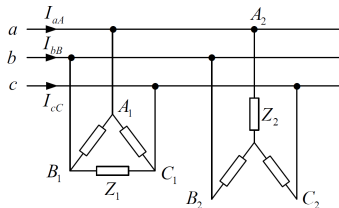
$$f = 50 \text{ Hz} \Rightarrow B_c = \omega C = 2\pi f C = 0.0286 \Rightarrow C = 145 \text{ } \mu\text{F}$$



Balanced Three-phase Interconnection

Example (Reactive power compensation)

The pure leading capacitive load Z_1 can compensate for the reactive power absorbed by the lagging inductive load Z_2 with $\text{PF}_2 = 0.75$ and $|S_2| = 30 \text{ kVA}$, where the line voltage is $381 \text{ V}_{\text{rms}}$.

- **Inductive load:**

$$S_2 = 3V_{A_2N}I_{aA_2}^*, V_{A_2N} = \frac{381}{\sqrt{3}} \angle 0^\circ$$


$$\Rightarrow I_{aA_2} = 45.5 \angle -41.41^\circ$$

- **Capacitive load:**

$$I_{aA_1} = (jB_c) |V_{A_1B_1}| \angle 30^\circ (\sqrt{3} \angle -30^\circ) = 30.1 \angle 90^\circ$$

- **Overall load:**

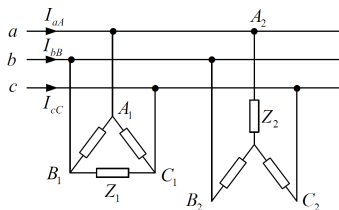
$$I_{aA} = I_{aA_1} + I_{aA_2} = 34.1 - j0.0 = 34.1 \angle 0^\circ$$



Imbalanced Three-phase Interconnection

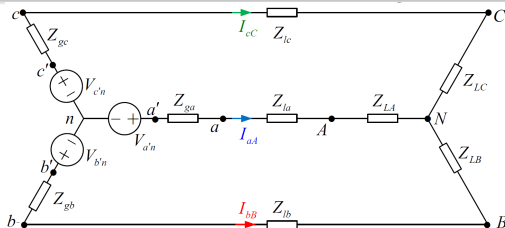Example (Imbalanced three-phase circuit analysis)

Nodal or mesh analysis can be used to analyze the imbalanced three-phase circuit below.



$$(V_{a'n}, V_{b'n}, V_{c'n}) = 1000(1, 1\angle -120^\circ, 1\angle 120^\circ) \text{ V}_{\text{rms}}$$

$$Z_{ga} = Z_{gb} = Z_{gc} = 2 + j8, Z_{la} = Z_{lb} = Z_{lc} = 1 + j2, Z_{LA} = 19 + j18, Z_{LB} = 49 - j2, Z_{LC} = 29 + j50 \Omega$$

$$\begin{cases} (z_{gc} + Z_{lc} + Z_{LC})I_{cC} + (Z_{LA} + Z_{la} + Z_{ga})(I_{cC} + I_{bB}) = V_{c'n} - V_{a'n} \\ (z_{gb} + Z_{lb} + Z_{LB})I_{bB} + (Z_{LA} + Z_{la} + Z_{ga})(I_{cC} + I_{bB}) = V_{b'n} - V_{a'n} \end{cases}$$

$$\Rightarrow \begin{cases} I_{aA} = 13.15 - j19.15 \\ I_{bB} = -19.95 - j10.38 \\ I_{cC} = 6.8 + j19.53 \end{cases} \Rightarrow S = Z_{LA}|I_{aA}|^2 + Z_{LB}|I_{bB}|^2 + Z_{LC}|I_{cC}|^2 = 42057 + 24994 \text{ VA, Lag}$$

Power Measurement

Ideal Power Meter

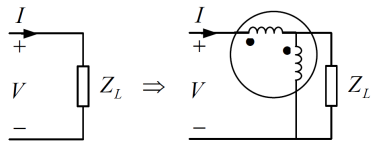


Figure: Ideal **single-phase wattmeter** with having no **voltage drop** and no **drawn current** in series and parallel measuring branch, respectively.

$$W = \Re\{VI^*\} = |V||I|\text{PF} = P_L$$

Three-phase Power Measurement

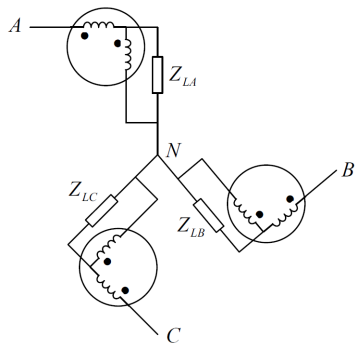


Figure: Three-phase power measurement using three wattmeters.

$$W_1 + W_2 + W_3 = \Re\{V_{AN}I_{AN}^*\} + \Re\{V_{BN}I_{BN}^*\} + \Re\{V_{CN}I_{CN}^*\} = P_L$$

Three-phase Power Measurement

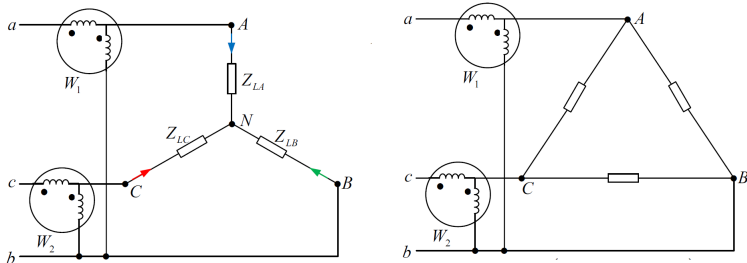


Figure: Three-phase power measurement using two wattmeters.

$$\begin{aligned}
 W_1 + W_2 &= \Re\{V_{AB}I_{aA}^* + V_{CB}I_{cC}^*\} \\
 &= \Re\{(V_{AN} + V_{NB})I_{aA}^* + (V_{CN} + V_{NB})I_{cC}^*\} \\
 &= \Re\{V_{AN}I_{aA}^* + V_{NB}(I_{aA} + I_{cC})^* + V_{CN}I_{cC}^*\} \\
 &= \Re\{V_{AN}I_{aA}^* + V_{BN}I_{bB}^* + V_{CN}I_{cC}^*\} = P_L
 \end{aligned}$$

$$\begin{aligned}
 W_1 + W_2 &= \Re\{V_{AB}I_{aA}^* + V_{CB}I_{cC}^*\} \\
 &= \Re\{V_{AB}(I_{AB} - I_{CA})^* + V_{CB}(I_{CA} - I_{BC})^*\} \\
 &= \Re\{V_{AB}I_{AB}^* + (V_{CB} - V_{AB})I_{CA}^* + V_{BC}I_{BC}^*\} \\
 &= \Re\{V_{AB}I_{AB}^* + V_{CA}I_{CA}^* + V_{BC}I_{BC}^*\} = P_L
 \end{aligned}$$

Three-phase Power Measurement

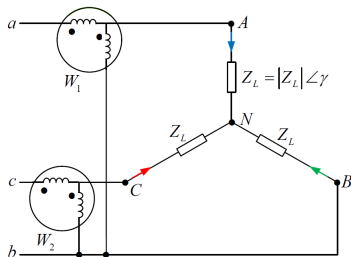


Figure: Three-phase balanced power measurement using two wattmeters for positive phase sequence.

$$\begin{aligned}
 W_1 + W_2 &= \Re\{V_{AB}I_{aA}^* + V_{CB}I_{cC}^*\} \\
 &= \Re\{(\sqrt{3}\angle 30^\circ)V_{aA}I_{AN}^* + (\sqrt{3}\angle -30^\circ)V_{cN}I_{cC}^*\} \\
 &= \Re\{[(\sqrt{3}\angle 30^\circ) + (\sqrt{3}\angle -30^\circ)]V_{AN}I_{aA}^*\} \\
 &= \Re\{2\sqrt{3}\cos(30^\circ)V_{AN}I_{aA}^*\} \\
 &= 3\Re\{V_{AN}I_{aA}^*\} = P_L
 \end{aligned}$$

$$\begin{aligned}
 W_2 - W_1 &= \Re\{V_{CB}I_{cC}^* - V_{AB}I_{aA}^*\} \\
 &= \Re\{(\sqrt{3}\angle -30^\circ)V_{cN}I_{cC}^* - (\sqrt{3}\angle 30^\circ)V_{aA}I_{aA}^*\} \\
 &= \Re\{[(\sqrt{3}\angle -30^\circ) - (\sqrt{3}\angle 30^\circ)]V_{AN}I_{aA}^*\} \\
 &= \Re\{-j2\sqrt{3}\sin(30^\circ)V_{AN}I_{aA}^*\} \\
 &= \frac{1}{\sqrt{3}}3\Im\{V_{AN}I_{aA}^*\} = \frac{Q}{\sqrt{3}}
 \end{aligned}$$


$$PF = \cos\left(\tan^{-1}\left(\frac{\sqrt{3}(W_2 - W_1)}{W_1 + W_2}\right)\right)$$

Phase Sequence Determination

Phase Sequence Determination

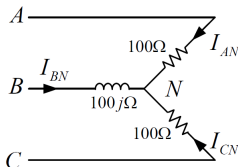Example (Phase sequence determination by imbalance load)

An imbalanced load of $100(1, \underline{90}^\circ, 1)$ can be used to determine the phase sequence in the circuit below, where the absolute phase voltage is $220 \text{ V}_{\text{rms}}$.



Positive phase sequence:

$$\begin{cases} 100I_{AN} + j100(I_{AN} + I_{CN}) = V_{AB} = 381\angle 0^\circ \\ -100I_{CN} - j100(I_{AN} + I_{CN}) = V_{BC} = 381\angle -120^\circ \end{cases}$$

$$\Rightarrow \begin{cases} I_{AN} = 1.9\angle -48.45^\circ \\ I_{CN} = 0.51\angle 71.55^\circ \end{cases} \Rightarrow |V_{AN}| > |V_{CN}|$$

Negative phase sequence:


$$\begin{cases} 100I_{AN} + j100(I_{AN} + I_{CN}) = V_{AB} = 381\angle 0^\circ \\ -100I_{CN} - j100(I_{AN} + I_{CN}) = V_{BC} = 381\angle 120^\circ \end{cases}$$

$$\Rightarrow \begin{cases} I_{AN} = 0.51\angle 11.55^\circ \\ I_{CN} = 1.9\angle -108.45^\circ \end{cases} \Rightarrow |V_{AN}| < |V_{CN}|$$

Phase Sequence Determination

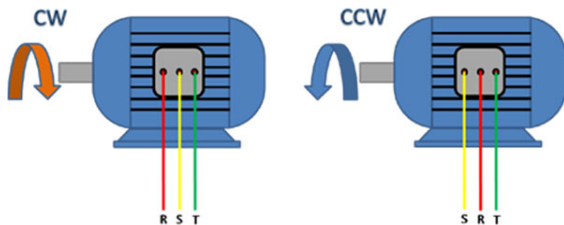Example (Phase sequence determination by induction motors)

The direction of rotation in three-phase induction motors is an indicator of the phase sequence.



The End