

Two-ports

Mohammad Hadi

mohammad.hadi@sharif.edu

@MohammadHadiDastgerdi

Fall 2021

Overview

- 1 One-ports
- 2 Two-ports
- 3 Description of Two-ports
- 4 Extension of Two-ports
- 5 Interconnection of Two-ports
- 6 Two-ports Models
- 7 Natural Frequencies
- 8 Calculation Techniques
- 9 Multi-ports

One-ports

One-ports

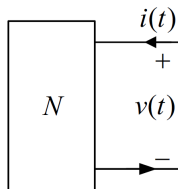


Figure: **NTV one-port** with the characteristic equation $f(v(t), i(t), t) = 0$.

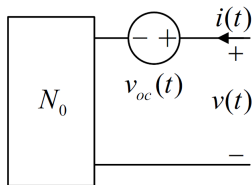


Figure: **LTV one-port** with the characteristic equation $v(t) = v_{oc}(t) + v_1(t) = v_{oc}(t) + \int_0^t h(t, \tau) i(\tau) d\tau$, where $v_{oc}(t)$ is the open circuit voltage and $v_1(t) = \int_0^t h(t, \tau) i(\tau) d\tau$ describes the **in-rest network**.

One-ports

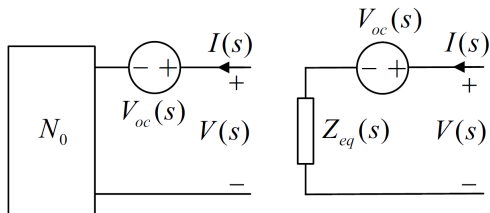


Figure: LTI one-port with the characteristic equation $V(s) = V_{oc}(s) + Z_{eq}(s)I(s)$ or $I(s) = -I_{sc}(s) + Y_{eq}(s)V(s)$, where $V_{oc}(s)$ is the open circuit voltage, $I_{sc}(s)$ is the short circuit current, $Z_{eq}(s)$ is the equivalent impedance, and $Y_{eq}(s)$ is the equivalent admittance. Clearly, $Y_{eq}(s) = Z_{eq}^{-1}(s)$ and $V_{oc}(s) = Z_{eq}(s)I_{sc}(s)$.

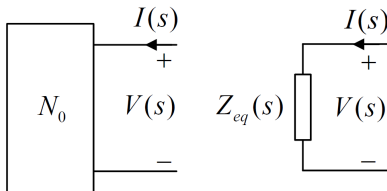


Figure: In-rest LTI one-port with the characteristic equation $V(s) = Z_{eq}(s)I(s)$ or $I(s) = Y_{eq}(s)V(s)$, where $Z_{eq}(s)$ is the equivalent impedance, and $Y_{eq}(s)$ is the equivalent admittance. Clearly, $Y_{eq}(s) = Z_{eq}^{-1}(s)$.

Two-ports

Two-ports

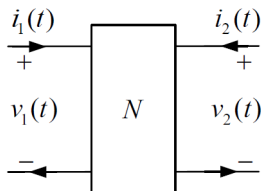


Figure: **NTV two-port** with the characteristic equation
$$\begin{cases} f_1(v_1(t), i_1(t), v_2(t), i_2(t), t) = 0 \\ f_2(v_1(t), i_1(t), v_2(t), i_2(t), t) = 0 \end{cases}$$

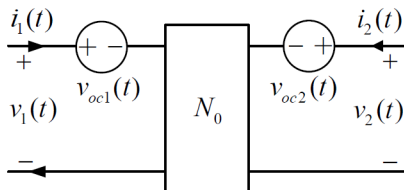


Figure: **LTV two-port** can be characterized with its **open circuit voltages** and **in-rest network** in time domain.

Two-ports

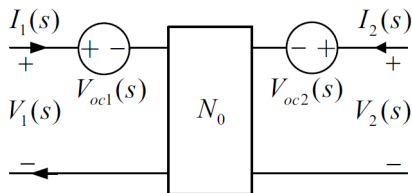


Figure: LTI two-port can be characterized with its open circuit voltages and in-rest network in time or Laplace domain.

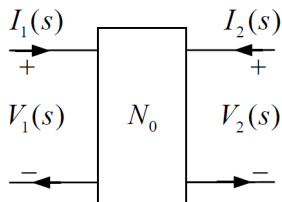


Figure: In-rest LTI two-port can be characterized with its in-rest network in time or Laplace domain.

Four-terminal

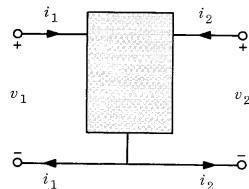
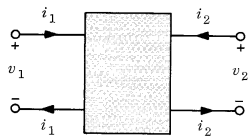
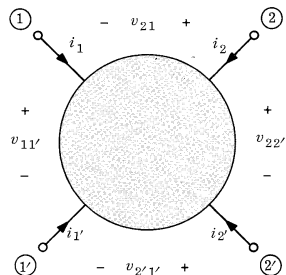


Figure: A **Four-terminal** element can be characterized by **three independent voltages** and **three independent currents**. A **two-port** is a **special four-terminal** with extra constraints on its currents. Every **three-terminal** element can be treated as a **two-port**.

Description of Two-ports

Description of Two-ports

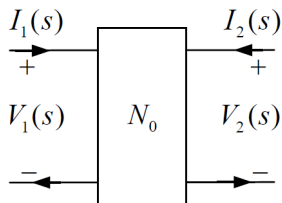


Figure: A **Two-port** may be described in one of the six common ways.

- **Impedance (Z -parameters) description:** $\begin{bmatrix} V_1(s) \\ V_2(s) \end{bmatrix} = f_1\left(\begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix}\right)$
- **Admittance (Y -parameters) description:** $\begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = f_2\left(\begin{bmatrix} V_1(s) \\ V_2(s) \end{bmatrix}\right)$
- **Hybrid (H -parameters) description:** $\begin{bmatrix} V_1(s) \\ I_2(s) \end{bmatrix} = f_3\left(\begin{bmatrix} I_1(s) \\ V_2(s) \end{bmatrix}\right)$
- **Hybrid (G -parameters) description:** $\begin{bmatrix} I_1(s) \\ V_2(s) \end{bmatrix} = f_4\left(\begin{bmatrix} V_1(s) \\ I_2(s) \end{bmatrix}\right)$
- **Transmittance ($ABCD$ -parameters) description:** $\begin{bmatrix} V_1(s) \\ I_1(s) \end{bmatrix} = f_5\left(\begin{bmatrix} V_2(s) \\ -I_2(s) \end{bmatrix}\right)$
- **Transmittance ($A'B'C'D'$ -parameters) description:** $\begin{bmatrix} V_2(s) \\ -I_2(s) \end{bmatrix} = f_6\left(\begin{bmatrix} V_1(s) \\ I_1(s) \end{bmatrix}\right)$

Impedance Description

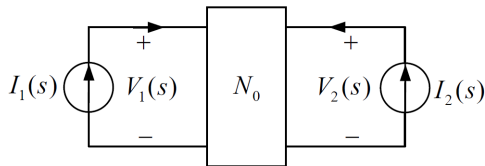



Figure: Impedance description for two-port.

- Impedance description:
$$\begin{cases} V_1(s) = z_{11}(s)I_1(s) + z_{12}(s)I_2(s) \\ V_2(s) = z_{21}(s)I_1(s) + z_{22}(s)I_2(s) \end{cases}$$
- Impedance matrix:
$$\mathbf{Z}(s) = \begin{bmatrix} z_{11}(s) & z_{12}(s) \\ z_{21}(s) & z_{22}(s) \end{bmatrix}, \quad \begin{bmatrix} V_1(s) \\ V_2(s) \end{bmatrix} = \mathbf{Z}(s) \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix}$$
- First port input impedance:
$$z_{11}(s) = \left. \frac{V_1(s)}{I_1(s)} \right|_{I_2(s)=0}$$
- Second port input impedance:
$$z_{22}(s) = \left. \frac{V_2(s)}{I_2(s)} \right|_{I_1(s)=0}$$
- Transfer impedance from second to first port:
$$z_{12}(s) = \left. \frac{V_1(s)}{I_2(s)} \right|_{I_1(s)=0}$$
- Transfer impedance from first to second port:
$$z_{21}(s) = \left. \frac{V_2(s)}{I_1(s)} \right|_{I_2(s)=0}$$

Impedance Description

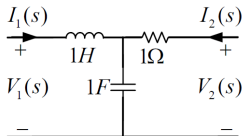Example (Impedance description)

The two-port below can be described by its impedance matrix.



$$\begin{cases} z_{11}(s) = \frac{V_1(s)}{I_1(s)} \Big|_{I_2(s)=0} = s + \frac{1}{s} \\ z_{22}(s) = \frac{V_2(s)}{I_2(s)} \Big|_{I_1(s)=0} = 1 + \frac{1}{s} \\ z_{12}(s) = \frac{V_1(s)}{I_2(s)} \Big|_{I_1(s)=0} = \frac{1}{s} \\ z_{21}(s) = \frac{V_2(s)}{I_1(s)} \Big|_{I_2(s)=0} = \frac{1}{s} \end{cases} \Rightarrow \mathbf{Z} = \begin{bmatrix} s^2+1 & 1 \\ \frac{1}{s} & \frac{s^2+1}{s} \end{bmatrix}$$

Admittance Description

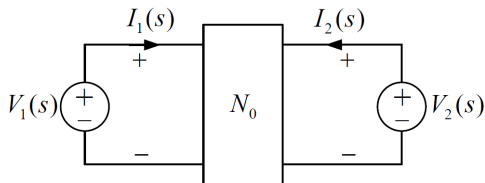



Figure: Admittance description for two-port.

- Admittance description:
$$\begin{cases} I_1(s) = y_{11}(s)V_1(s) + y_{12}(s)V_2(s) \\ I_2(s) = y_{21}(s)V_1(s) + y_{22}(s)V_2(s) \end{cases}$$
- Admittance matrix: $\mathbf{Y}(s) = \begin{bmatrix} y_{11}(s) & y_{12}(s) \\ y_{21}(s) & y_{22}(s) \end{bmatrix} = \mathbf{Z}^{-1}(s), \quad \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \mathbf{Y}(s) \begin{bmatrix} V_1(s) \\ V_2(s) \end{bmatrix}$
- First port input admittance: $y_{11}(s) = \frac{I_1(s)}{V_1(s)} \Big|_{V_2(s)=0} \neq \frac{1}{z_{11}(s)}$
- Second port input admittance: $y_{22}(s) = \frac{I_2(s)}{V_2(s)} \Big|_{V_1(s)=0} \neq \frac{1}{z_{22}(s)}$
- Transfer admittance from second to first port: $y_{12}(s) = \frac{I_1(s)}{V_2(s)} \Big|_{V_1(s)=0}$
- Transfer admittance from first to second port: $y_{21}(s) = \frac{I_2(s)}{V_1(s)} \Big|_{V_2(s)=0}$

Admittance Description

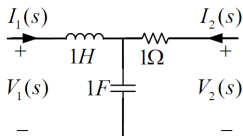Example (Admittance description)

The two-port below can be described by its admittance matrix.



$$\left\{ \begin{array}{l} y_{11}(s) = \frac{i_1(s)}{V_1(s)} \Big|_{V_2(s)=0} = \left[\frac{1}{s} \parallel 1 + s \right]^{-1} = \frac{s+1}{s^2+s+1} \\ y_{22}(s) = \frac{i_2(s)}{V_2(s)} \Big|_{V_1(s)=0} = \left[\frac{1}{s} \parallel s + 1 \right]^{-1} = \frac{s^2+1}{s^2+s+1} \\ y_{12}(s) = \frac{i_1(s)}{V_2(s)} \Big|_{V_1(s)=0} = -\frac{s \parallel \frac{1}{s}}{s \parallel \frac{1}{s} + 1} \frac{1}{s} = \frac{-1}{s^2+s+1} \\ y_{21}(s) = \frac{i_2(s)}{V_1(s)} \Big|_{V_2(s)=0} = -\frac{1 \parallel \frac{1}{s}}{1 \parallel \frac{1}{s} + s} \frac{1}{1} = \frac{-1}{s^2+s+1} \end{array} \right. \Rightarrow \mathbf{Y} = \begin{bmatrix} \frac{s+1}{s^2+s+1} & \frac{-1}{s^2+s+1} \\ \frac{-1}{s^2+s+1} & \frac{s^2+1}{s^2+s+1} \end{bmatrix} = \mathbf{Z}^{-1}$$

Hybrid H Description

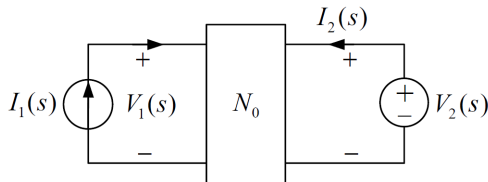



Figure: Hybrid H description for two-port.

- Hybrid H description:
$$\begin{cases} V_1(s) = h_{11}(s)I_1(s) + h_{12}(s)V_2(s) \\ I_2(s) = h_{21}(s)I_1(s) + h_{22}(s)V_2(s) \end{cases}$$
- Hybrid H matrix:
$$\mathbf{H}(s) = \begin{bmatrix} h_{11}(s) & h_{12}(s) \\ h_{21}(s) & h_{22}(s) \end{bmatrix}, \quad \begin{bmatrix} V_1(s) \\ I_2(s) \end{bmatrix} = \mathbf{H}(s) \begin{bmatrix} I_1(s) \\ V_2(s) \end{bmatrix}$$
- First port input impedance:
$$h_{11}(s) = \left. \frac{V_1(s)}{I_1(s)} \right|_{V_2(s)=0} = \frac{1}{y_{11}(s)}$$
- Second port input admittance:
$$h_{22}(s) = \left. \frac{I_2(s)}{V_2(s)} \right|_{I_1(s)=0} = \frac{1}{z_{22}(s)}$$
- Voltage gain from second to first port:
$$h_{12}(s) = \left. \frac{V_1(s)}{V_2(s)} \right|_{I_1(s)=0}$$
- Current gain from first to second port:
$$h_{21}(s) = \left. \frac{I_2(s)}{I_1(s)} \right|_{V_2(s)=0}$$

Hybrid H Description

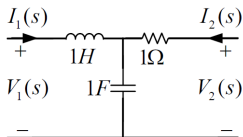Example (Hybrid H description)

The two-port below can be described by its hybrid H matrix.



$$\left\{ \begin{array}{l} h_{11}(s) = \frac{V_1(s)}{I_1(s)} \Big|_{V_2(s)=0} = s + \frac{1}{s} \parallel 1 = \frac{s^2+s+1}{s+1} \\ h_{22}(s) = \frac{I_2(s)}{V_2(s)} \Big|_{I_1(s)=0} = \left[1 + \frac{1}{s} \right]^{-1} = \frac{s}{s+1} \\ h_{12}(s) = \frac{V_1(s)}{V_2(s)} \Big|_{I_1(s)=0} = \frac{\frac{1}{s}}{\frac{1}{s+1}} = \frac{1}{s+1} \\ h_{21}(s) = \frac{I_2(s)}{I_1(s)} \Big|_{V_2(s)=0} = -\frac{\frac{1}{s}}{\frac{1}{s+1}} = \frac{-1}{s+1} \end{array} \right. \Rightarrow \mathbf{H} = \begin{bmatrix} \frac{s^2+s+1}{s+1} & \frac{1}{s+1} \\ \frac{-1}{s+1} & \frac{s}{s+1} \end{bmatrix}$$

Hybrid G Description

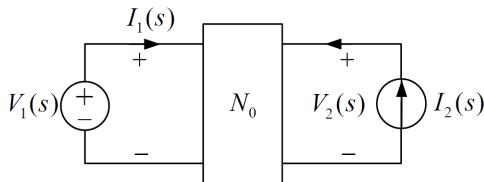



Figure: Hybrid G description for two-port.

- Hybrid G description:
$$\begin{cases} I_1(s) = g_{11}(s)V_1(s) + g_{12}(s)I_2(s) \\ V_2(s) = g_{21}(s)V_1(s) + g_{22}(s)I_2(s) \end{cases}$$
- Hybrid G matrix:
$$\mathbf{G}(s) = \begin{bmatrix} g_{11}(s) & g_{12}(s) \\ g_{21}(s) & g_{22}(s) \end{bmatrix} = \mathbf{H}^{-1}(s), \quad \begin{bmatrix} I_1(s) \\ V_2(s) \end{bmatrix} = \mathbf{G}(s) \begin{bmatrix} V_1(s) \\ I_2(s) \end{bmatrix}$$
- First port input admittance:
$$g_{11}(s) = \left. \frac{I_1(s)}{V_1(s)} \right|_{I_2(s)=0} = \frac{1}{z_{11}(s)}$$
- Second port input impedance:
$$g_{22}(s) = \left. \frac{V_2(s)}{I_2(s)} \right|_{V_1(s)=0} = \frac{1}{y_{22}(s)}$$
- Current gain from second to first port:
$$g_{12}(s) = \left. \frac{I_1(s)}{I_2(s)} \right|_{V_1(s)=0}$$
- Voltage gain from first to second port:
$$g_{21}(s) = \left. \frac{V_2(s)}{V_1(s)} \right|_{I_2(s)=0}$$

Hybrid G Description

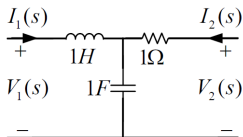Example (Hybrid G description)

The two-port below can be described by its hybrid G matrix.



$$\left\{ \begin{array}{l} g_{11}(s) = \frac{I_1(s)}{V_1(s)} \Big|_{I_2(s)=0} = [s + \frac{1}{s}]^{-1} = \frac{s}{s^2+1} \\ g_{22}(s) = \frac{V_2(s)}{I_2(s)} \Big|_{V_1(s)=0} = s \parallel \frac{1}{s} + 1 = \frac{s^2+s+1}{s^2+1} \\ g_{12}(s) = \frac{I_1(s)}{I_2(s)} \Big|_{V_1(s)=0} = -\frac{1}{\frac{1}{s}+s} = -\frac{1}{s^2+1} \\ g_{21}(s) = \frac{V_2(s)}{V_1(s)} \Big|_{I_2(s)=0} = \frac{1}{\frac{1}{s}+s} = \frac{1}{s^2+1} \end{array} \right. \Rightarrow \mathbf{G} = \begin{bmatrix} \frac{s}{s^2+1} & -\frac{1}{s^2+1} \\ \frac{1}{s^2+1} & \frac{s^2+s+1}{s^2+1} \end{bmatrix} = \mathbf{H}^{-1}$$

Transmittance ABCD Description

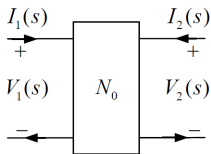



Figure: Transmittance ABCD description for two-port.

- Transmittance ABCD description:
$$\begin{cases} V_1(s) = A(s)V_2(s) + B(s)(-I_2(s)) \\ I_1(s) = C(s)V_2(s) + D(s)(-I_2(s)) \end{cases}$$
- Transmittance ABCD matrix:
$$\mathbf{T}(s) = \begin{bmatrix} A(s) & B(s) \\ C(s) & D(s) \end{bmatrix}, \quad \begin{bmatrix} V_1(s) \\ I_1(s) \end{bmatrix} = \mathbf{T}(s) \begin{bmatrix} V_2(s) \\ -I_2(s) \end{bmatrix}$$
- A parameter: $A(s) = \left. \frac{V_1(s)}{V_2(s)} \right|_{I_2(s)=0}$
- B parameter: $B(s) = \left. \frac{V_1(s)}{-I_2(s)} \right|_{V_2(s)=0}$
- C parameter: $C(s) = \left. \frac{I_1(s)}{V_2(s)} \right|_{I_2(s)=0}$
- D parameter: $D(s) = \left. \frac{I_1(s)}{-I_2(s)} \right|_{V_2(s)=0}$

Transmittance ABCD Description

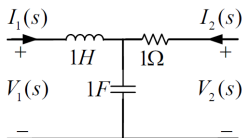Example (Transmittance ABCD description)

The two-port below can be described by its transmittance ABCD matrix.



$$\left\{ \begin{array}{l} A(s) = \frac{V_1(s)}{V_2(s)} \Big|_{I_2(s)=0} = \left[\frac{\frac{1}{s}}{\frac{1}{s}+s} \right]^{-1} = s^2 + 1 \\ B(s) = \frac{V_1(s)}{-I_2(s)} \Big|_{V_2(s)=0} = \left[\frac{\frac{1}{s} \parallel 1}{\frac{1}{s} \parallel 1 + s} \right]^{-1} = s^2 + s + 1 \\ C(s) = \frac{I_1(s)}{V_2(s)} \Big|_{I_2(s)=0} = \left[\frac{1}{s} \right]^{-1} = s \\ D(s) = \frac{I_1(s)}{-I_2(s)} \Big|_{V_2(s)=0} = \left[\frac{\frac{1}{s}}{\frac{1}{s}+1} \right]^{-1} = s + 1 \end{array} \right. \Rightarrow \mathbf{T} = \begin{bmatrix} s^2 + 1 & s^2 + s + 1 \\ s & s + 1 \end{bmatrix}$$

Transmittance $A'B'C'D'$ Description

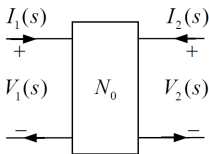



Figure: Transmittance $A'B'C'D'$ description for two-port.

- Transmittance $A'B'C'D'$ description:
$$\begin{cases} V_2(s) = A'(s)V_1(s) + B'(s)I_1(s) \\ -I_2(s) = C'(s)V_1(s) + D'(s)I_1(s) \end{cases}$$
- Transmittance $A'B'C'D'$ matrix:
$$\mathbf{T}'(s) = \begin{bmatrix} A'(s) & B'(s) \\ C'(s) & D'(s) \end{bmatrix} = \mathbf{T}^{-1}(s), \quad \begin{bmatrix} V_2(s) \\ -I_2(s) \end{bmatrix} = \mathbf{T}'(s) \begin{bmatrix} V_1(s) \\ I_1(s) \end{bmatrix}$$
- A' parameter: $A'(s) = \left. \frac{V_2(s)}{V_1(s)} \right|_{I_1(s)=0}$
- B' parameter: $B'(s) = \left. \frac{V_2(s)}{I_1(s)} \right|_{V_1(s)=0}$
- C' parameter: $C'(s) = \left. \frac{-I_2(s)}{V_1(s)} \right|_{I_1(s)=0}$
- D' parameter: $D'(s) = \left. \frac{-I_2(s)}{I_1(s)} \right|_{V_1(s)=0}$

Transmittance A'B'C'D' Description

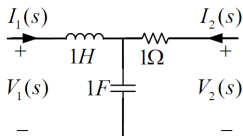Example (Transmittance A'B'C'D' description)

The two-port below can be described by its transmittance A'B'C'D' matrix.



$$\left\{ \begin{array}{l} A'(s) = \frac{V_2(s)}{V_1(s)} \Big|_{I_2(s)=0} = \left[\frac{1}{\frac{1}{s}+1} \right]^{-1} = s+1 \\ B'(s) = \frac{V_2(s)}{I_1(s)} \Big|_{V_1(s)=0} = -\left[\frac{\frac{1}{s} \parallel s}{\frac{1}{s} \parallel s+1} \right]^{-1} = -s^2 - s - 1 \\ C'(s) = \frac{-I_2(s)}{V_1(s)} \Big|_{I_1(s)=0} = -\left[\frac{1}{s} \right]^{-1} = s \\ D'(s) = \frac{-I_2(s)}{I_1(s)} \Big|_{V_1(s)=0} = \left[\frac{1}{\frac{1}{s}+s} \right]^{-1} = s+1 \end{array} \right. \Rightarrow \mathbf{T}' = \begin{bmatrix} s+1 & -s^2 - s - 1 \\ -s & s^2 + 1 \end{bmatrix} = \mathbf{T}^{-1}$$

Reciprocal Two-ports

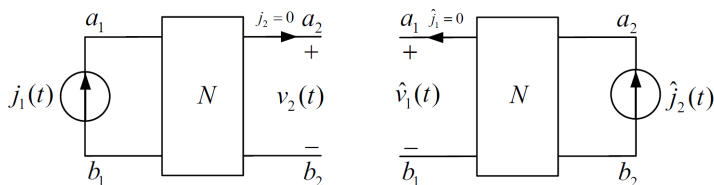


Figure: Reciprocal two-port.

- Impedance (Z -parameters) description: $z_{12}(s) = z_{21}(s)$
- Admittance (Y -parameters) description: $y_{12}(s) = y_{21}(s)$
- Hybrid (H -parameters) description: $h_{12}(s) = -h_{21}(s)$
- Hybrid (G -parameters) description: $g_{12}(s) = -g_{21}(s)$
- Transmittance ($ABCD$ -parameters) description: $\det[\mathbf{T}] = 1$
- Transmittance ($A'B'C'D'$ -parameters) description: $\det[\mathbf{T}'] = 1$

Symmetric Two-ports

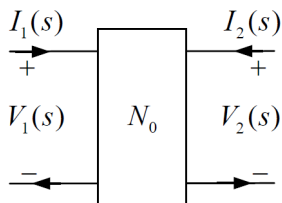


Figure: Symmetric two-port.

- Impedance (Z -parameters) description: $z_{12}(s) = z_{21}(s)$, $z_{11}(s) = z_{22}(s)$
- Admittance (Y -parameters) description: $y_{12}(s) = y_{21}(s)$, $y_{11}(s) = y_{22}(s)$
- Hybrid (H -parameters) description: $h_{12}(s) = -h_{21}(s)$, $\det[\mathbf{H}] = 1$
- Hybrid (G -parameters) description: $g_{12}(s) = -g_{21}(s)$, $\det[\mathbf{G}] = 1$
- Transmittance ($ABCD$ -parameters) description: $\det[\mathbf{T}] = 1$, $A = D$
- Transmittance ($A'B'C'D'$ -parameters) description: $\det[\mathbf{T}'] = 1$, $A' = D'$

Interrelation of Descriptions

	Z	Y	H	G	T	T'
Z	$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix}$	$\begin{bmatrix} \frac{y_{22}}{\Delta_Y} & -\frac{y_{12}}{\Delta_Y} \\ -\frac{y_{21}}{\Delta_Y} & \frac{y_{11}}{\Delta_Y} \end{bmatrix}$	$\begin{bmatrix} \frac{\Delta_H}{h_{22}} & \frac{h_{12}}{h_{22}} \\ -\frac{h_{21}}{h_{22}} & \frac{1}{h_{22}} \end{bmatrix}$	$\begin{bmatrix} \frac{1}{g_{11}} & -\frac{g_{12}}{g_{11}} \\ \frac{g_{21}}{g_{11}} & \frac{g_{22}}{g_{11}} \end{bmatrix}$	$\begin{bmatrix} \frac{A}{C} & \frac{\Delta_T}{C} \\ \frac{1}{C} & \frac{D}{C} \end{bmatrix}$	$\begin{bmatrix} \frac{D'}{C'} & \frac{1}{C'} \\ -\frac{\Delta_{T'}}{C'} & \frac{A'}{C'} \end{bmatrix}$
Y	$\begin{bmatrix} \frac{z_{22}}{\Delta_Z} & -\frac{z_{12}}{\Delta_Z} \\ -\frac{z_{21}}{\Delta_Z} & \frac{z_{11}}{\Delta_Z} \end{bmatrix}$	$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$	$\begin{bmatrix} \frac{1}{h_{11}} & -\frac{h_{12}}{h_{11}} \\ \frac{h_{21}}{h_{11}} & \frac{\Delta_H}{h_{11}} \end{bmatrix}$	$\begin{bmatrix} \frac{\Delta_G}{g_{22}} & \frac{g_{12}}{g_{22}} \\ -\frac{g_{21}}{g_{22}} & \frac{1}{g_{22}} \end{bmatrix}$	$\begin{bmatrix} \frac{D}{B} & -\frac{\Delta_T}{B} \\ -\frac{1}{B} & \frac{A}{B} \end{bmatrix}$	$\begin{bmatrix} \frac{A'}{B'} & -\frac{1}{B'} \\ -\frac{\Delta_{T'}}{B'} & \frac{D'}{B'} \end{bmatrix}$
H	$\begin{bmatrix} \frac{\Delta_Z}{z_{22}} & \frac{z_{12}}{z_{22}} \\ -\frac{z_{21}}{z_{22}} & \frac{1}{z_{22}} \end{bmatrix}$	$\begin{bmatrix} \frac{1}{y_{11}} & -\frac{y_{12}}{\Delta_Y} \\ \frac{y_{21}}{y_{11}} & \frac{\Delta_Y}{y_{11}} \end{bmatrix}$	$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix}$	$\begin{bmatrix} \frac{g_{22}}{\Delta_G} & -\frac{g_{12}}{\Delta_G} \\ -\frac{g_{21}}{\Delta_G} & \frac{g_{11}}{\Delta_G} \end{bmatrix}$	$\begin{bmatrix} \frac{B}{D} & \frac{\Delta_T}{D} \\ -\frac{1}{D} & \frac{C}{D} \end{bmatrix}$	$\begin{bmatrix} \frac{B'}{A'} & \frac{1}{A'} \\ -\frac{\Delta_{T'}}{A'} & \frac{C'}{A'} \end{bmatrix}$
G	$\begin{bmatrix} \frac{1}{z_{11}} & -\frac{z_{12}}{z_{11}} \\ \frac{z_{21}}{z_{11}} & \frac{\Delta_Z}{z_{11}} \end{bmatrix}$	$\begin{bmatrix} \frac{\Delta_Y}{y_{22}} & \frac{y_{12}}{y_{22}} \\ -\frac{y_{21}}{y_{22}} & \frac{1}{y_{22}} \end{bmatrix}$	$\begin{bmatrix} \frac{h_{22}}{\Delta_H} & -\frac{h_{12}}{\Delta_H} \\ -\frac{h_{21}}{\Delta_H} & \frac{h_{11}}{\Delta_H} \end{bmatrix}$	$\begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix}$	$\begin{bmatrix} \frac{C}{A} & -\frac{\Delta_T}{A} \\ \frac{1}{A} & \frac{B}{A} \end{bmatrix}$	$\begin{bmatrix} \frac{C'}{D'} & -\frac{1}{D'} \\ \frac{\Delta_{T'}}{D'} & \frac{B'}{D'} \end{bmatrix}$
T	$\begin{bmatrix} z_{11} & \Delta_Z \\ z_{21} & z_{22} \\ \frac{1}{z_{21}} & \frac{1}{z_{21}} \end{bmatrix}$	$\begin{bmatrix} -\frac{y_{22}}{y_{21}} & -\frac{1}{y_{21}} \\ \frac{y_{21}}{-\Delta_Y} & \frac{y_{11}}{y_{21}} \end{bmatrix}$	$\begin{bmatrix} -\frac{\Delta_H}{h_{21}} & -\frac{h_{11}}{h_{21}} \\ \frac{h_{21}}{-h_{22}} & -\frac{1}{h_{21}} \end{bmatrix}$	$\begin{bmatrix} \frac{1}{g_{21}} & \frac{g_{22}}{g_{21}} \\ \frac{g_{21}}{g_{21}} & \frac{\Delta_G}{g_{21}} \end{bmatrix}$	$\begin{bmatrix} A & B \\ C & D \end{bmatrix}$	$\begin{bmatrix} \frac{D'}{\Delta_{T'}} & \frac{B'}{\Delta_{T'}} \\ \frac{C'}{\Delta_{T'}} & \frac{A'}{\Delta_{T'}} \end{bmatrix}$
T'	$\begin{bmatrix} z_{22} & \Delta_Z \\ z_{12} & z_{12} \\ \frac{1}{z_{12}} & \frac{1}{z_{12}} \end{bmatrix}$	$\begin{bmatrix} -\frac{y_{11}}{y_{12}} & -\frac{1}{y_{12}} \\ \frac{y_{12}}{-\Delta_Y} & \frac{y_{22}}{y_{12}} \end{bmatrix}$	$\begin{bmatrix} \frac{1}{h_{12}} & \frac{h_{11}}{h_{12}} \\ \frac{h_{22}}{h_{12}} & \frac{\Delta_H}{h_{12}} \end{bmatrix}$	$\begin{bmatrix} -\frac{\Delta_G}{g_{12}} & -\frac{g_{22}}{g_{12}} \\ \frac{g_{12}}{g_{12}} & -\frac{1}{g_{12}} \end{bmatrix}$	$\begin{bmatrix} \frac{D}{\Delta_T} & \frac{B}{\Delta_T} \\ \frac{C}{\Delta_T} & \frac{A}{\Delta_T} \end{bmatrix}$	$\begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix}$

Table: Interrelation of different descriptions of two-ports. Four elements and one determinant of each description are used in interrelations. If an element or determinant of a description is zero, a corresponding description does not exist.

Description of Two-ports

Example (Description of a two-port)


The two-port below can be described using different methods.

$$\begin{cases} V_1 = 5sI_1 + 4I_2 + \frac{10}{s}(I_1 + I_2) \\ V_2 = 10I_2 + 4I_2 + \frac{10}{s}(I_1 + I_2) \end{cases}$$

$$\begin{cases} V_1 = \frac{5s^2+10}{s}I_1 + \frac{4s+10}{s}I_2 \\ V_2 = \frac{10}{s}I_1 + \frac{14s+10}{s}I_2 \end{cases} \Rightarrow \mathbf{Z} = \mathbf{Y}^{-1} = \begin{bmatrix} \frac{5s^2+10}{s} & \frac{4s+10}{s} \\ \frac{10}{s} & \frac{14s+10}{s} \end{bmatrix}$$

$$\begin{cases} V_1 = \frac{5s^2+10}{s}I_1 + \frac{4s+10}{s}I_2 \\ I_2 = \frac{-10}{14s+10}I_1 + \frac{s}{14s+10}V_2 \end{cases} \Rightarrow \mathbf{H} = \mathbf{G}^{-1} = \begin{bmatrix} \frac{70s^2+50s+100}{14s+10} & \frac{4s+10}{14s+10} \\ \frac{-10}{14s+10} & \frac{s}{14s+10} \end{bmatrix}$$
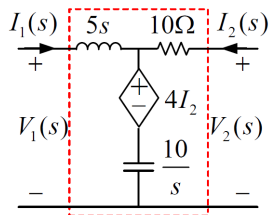
$$\begin{cases} V_1 = \frac{5s^2+10}{s}I_1 + \frac{4s+10}{s}I_2 \\ I_1 = \frac{s}{10}V_2 - \frac{14s+10}{10}I_2 \end{cases} \Rightarrow \mathbf{T} = \mathbf{T}'^{-1} = \begin{bmatrix} \frac{5s^2+10}{10} & \frac{70s^2+50s+100}{10} \\ \frac{s}{10} & \frac{14s+10}{10} \end{bmatrix}$$



Description of Two-ports

Example (Description of a two-port)


The two-port below has three different descriptions.

$$\begin{cases} I_1 + I_2 + I_1 = 0 \Rightarrow I_2 = -2I_1 \\ V_2 = \frac{1}{s}(I_2 - I_1) = \frac{-3}{s}I_1 \end{cases}$$

$$\mathbf{T}' = \begin{bmatrix} 0 & \frac{-3}{s} \\ 0 & 2 \end{bmatrix}$$

$$\mathbf{Y} = \begin{bmatrix} 0 & \frac{-s}{3} \\ 0 & \frac{2s}{3} \end{bmatrix}$$
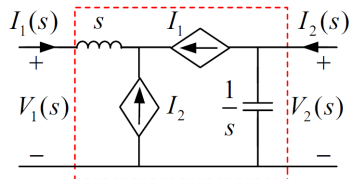
$$\mathbf{G} = \begin{bmatrix} 0 & \frac{-1}{2} \\ 0 & \frac{3}{2s} \end{bmatrix}$$



Description of Two-ports

Example (Dependent sources as two-ports)





Dependent sources can be modeled by two-ports.

$$\begin{cases} I_1 = 0 \\ I_2 = g_m V_1 \end{cases} \Rightarrow \begin{cases} \mathbf{Y} = \begin{bmatrix} 0 & 0 \\ g_m & 0 \\ 0 & \frac{-1}{g_m} \\ 0 & 0 \end{bmatrix} \\ \mathbf{T} = \begin{bmatrix} 0 & 0 \\ 0 & \frac{-1}{g_m} \\ 0 & 0 \end{bmatrix} \end{cases}$$

$$\begin{cases} V_1 = 0 \\ I_2 = \alpha I_1 \end{cases} \Rightarrow \begin{cases} \mathbf{H} = \begin{bmatrix} 0 & 0 \\ \alpha & 0 \\ 0 & 0 \\ 0 & \frac{-1}{\alpha} \end{bmatrix} \\ \mathbf{T} = \begin{bmatrix} 0 & 0 \\ 0 & 0 \\ 0 & \frac{-1}{\alpha} \end{bmatrix} \end{cases}$$

$$\begin{cases} I_1 = 0 \\ V_2 = \mu V_1 \end{cases} \Rightarrow \begin{cases} \mathbf{G} = \begin{bmatrix} 0 & 0 \\ \mu & 0 \\ \frac{1}{\mu} & 0 \\ 0 & 0 \end{bmatrix} \\ \mathbf{T} = \begin{bmatrix} 0 & 0 \\ \frac{1}{\mu} & 0 \\ 0 & 0 \end{bmatrix} \end{cases}$$
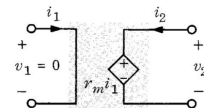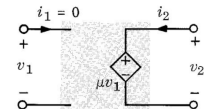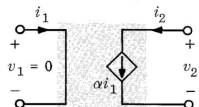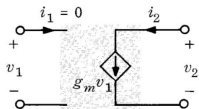
$$\begin{cases} V_1 = 0 \\ V_2 = r_m I_1 \end{cases} \Rightarrow \begin{cases} \mathbf{Z} = \begin{bmatrix} 0 & 0 \\ r_m & 0 \\ 0 & 0 \\ \frac{-1}{r_m} & 0 \end{bmatrix} \\ \mathbf{T} = \begin{bmatrix} 0 & 0 \\ 0 & 0 \\ \frac{-1}{r_m} & 0 \end{bmatrix} \end{cases}$$



Description of Two-ports

Example (Two-ports with single description)





A two-port may only have one description.

$$\mathbf{Z} = \begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix}$$

$$\mathbf{Y} = \begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix}$$

$$\mathbf{H} = \begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix}$$
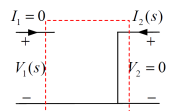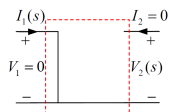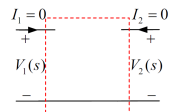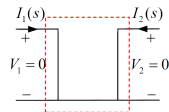
$$\mathbf{G} = \begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix}$$



Description of Two-ports

Example (Some simple two-ports)





Some simple two-ports are shown below.

$$\mathbf{Y} = \begin{bmatrix} Y_s & -Y_s \\ -Y_s & Y_s \end{bmatrix}$$

$$\mathbf{Z} = \begin{bmatrix} Z_p & Z_p \\ Z_p & Z_p \end{bmatrix}$$

$$\mathbf{Z} = \begin{bmatrix} Z_1 & 0 \\ 0 & Z_2 \end{bmatrix}$$
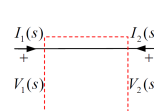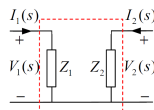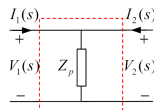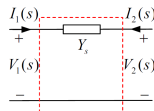
$$\mathbf{T} = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$$




Description of Two-ports

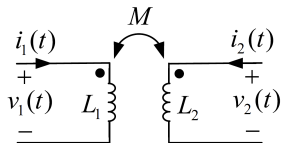
Example (Well-known two-ports)

Some well-known two-ports are shown below.


$$\mathbf{Z} = \begin{bmatrix} L_1 s & Ms \\ Ms & L_2 s \end{bmatrix}$$


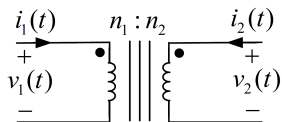
$$\mathbf{T} = \begin{bmatrix} \frac{n_1}{n_2} & 0 \\ 0 & \frac{n_2}{n_1} \end{bmatrix}$$


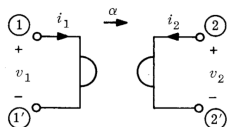
$$\mathbf{Z} = \begin{bmatrix} 0 & \alpha \\ -\alpha & 0 \end{bmatrix}$$



Extension of Two-ports

Extension of Two-ports

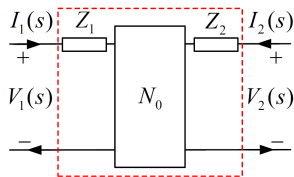


Figure: Adding **series impedances** in the first and second ports of a two-port results in an **extended two-port**

with the **impedance matrix** $\mathbf{Z} = \begin{bmatrix} z_{11}(s) + Z_1(s) & z_{12}(s) \\ z_{21}(s) & z_{22}(s) + Z_2(s) \end{bmatrix}$.

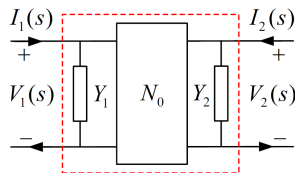


Figure: Adding **parallel admittances** in the first and second ports of a two-port results in an **extended two-port**

with the **admittance matrix** $\mathbf{Y} = \begin{bmatrix} y_{11}(s) + Y_1(s) & y_{12}(s) \\ y_{21}(s) & y_{22}(s) + Y_2(s) \end{bmatrix}$.

Extension of Two-ports

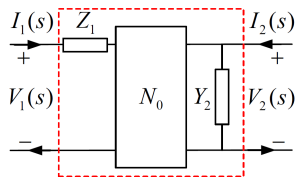


Figure: Adding **series impedance** in the first port and **parallel admittance** in the second port of a two-port results in an **extended two-port** with the **hybrid H matrix** $\mathbf{H} = \begin{bmatrix} h_{11}(s) + Z_1(s) & h_{12}(s) \\ h_{21}(s) & h_{22}(s) + Y_2(s) \end{bmatrix}$.

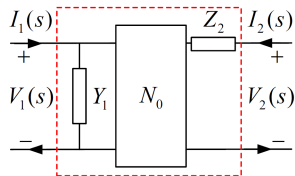


Figure: Adding **parallel admittance** in the first port and **series impedance** in the second port of a two-port results in an **extended two-port** with the **hybrid G matrix** $\mathbf{G} = \begin{bmatrix} g_{11}(s) + Y_1(s) & g_{12}(s) \\ g_{21}(s) & g_{22}(s) + Z_2(s) \end{bmatrix}$.

Extension of Two-ports

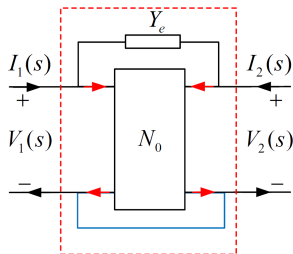


Figure: Connecting the first and second ports of a two-port using an added admittance and a short circuit

leads to an extended two-port with the admittance matrix $\mathbf{Y} = \begin{bmatrix} y_{11}(s) + Y_e(s) & y_{12}(s) - Y_e(s) \\ y_{21}(s) - Y_e(s) & y_{22}(s) + Y_e(s) \end{bmatrix}$.

$$I_1 = Y_e(V_1 - V_2) + y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_e(V_2 - V_1) + y_{21} V_1 + Y_{22} V_2$$



Extension of Two-ports

Example (Π and T two-ports)

Π and T networks can be considered as two-ports.

$$\mathbf{z}_0 = \begin{bmatrix} Z_p & Z_p \\ Z_p & Z_p \end{bmatrix} \Rightarrow \mathbf{z} = \begin{bmatrix} Z_p + Z_1 & Z_p \\ Z_p & Z_p + Z_2 \end{bmatrix}$$

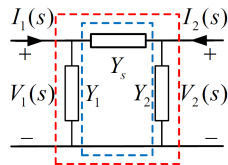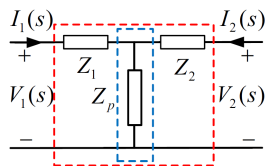
$$\mathbf{y}_0 = \begin{bmatrix} Y_s & -Y_s \\ -Y_s & Y_s \end{bmatrix} \Rightarrow \mathbf{y} = \begin{bmatrix} Y_s + Y_1 & -Y_s \\ -Y_s & Y_s + Y_2 \end{bmatrix}$$



Extension of Two-ports

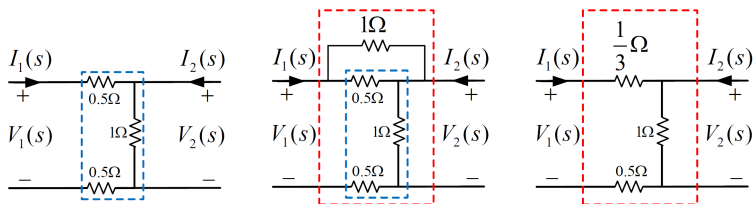Example (Two-port current condition)

Two-port current condition should be held while extending the two-port.




$$\mathbf{Z}_0 = \begin{bmatrix} 1 + 0.5 + 0.5 & 1 \\ 1 & 1 \end{bmatrix} \Rightarrow \mathbf{Y}_0 = \mathbf{Z}_0^{-1} = \begin{bmatrix} 1 & -1 \\ -1 & 2 \end{bmatrix}$$

$$\mathbf{Z} = \begin{bmatrix} 1 + 0.5 + \frac{1}{3} & 1 \\ 1 & 1 \end{bmatrix} \Rightarrow \mathbf{Y} = \mathbf{Z}^{-1} \begin{bmatrix} \frac{6}{5} & -\frac{6}{5} \\ -\frac{6}{5} & \frac{11}{5} \end{bmatrix} \neq \begin{bmatrix} 1 + 1 & -1 - 1 \\ -1 - 1 & 2 + 1 \end{bmatrix}$$

Extension of Two-ports

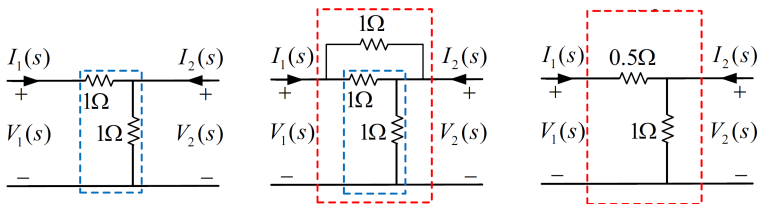Example (Two-port current condition)

Two-port current condition should be held while extending the two-port.



$$\mathbf{Z}_0 = \begin{bmatrix} 1+1 & 1 \\ 1 & 1 \end{bmatrix} \Rightarrow \mathbf{Y}_0 = \mathbf{Z}_0^{-1} = \begin{bmatrix} 1 & -1 \\ -1 & 2 \end{bmatrix}$$

$$\mathbf{Z} = \begin{bmatrix} 1+0.5 & 1 \\ 1 & 1 \end{bmatrix} \Rightarrow \mathbf{Y} = \mathbf{Z}^{-1} \begin{bmatrix} 2 & -2 \\ -2 & 3 \end{bmatrix} = \begin{bmatrix} 1+1 & -1-1 \\ -1-1 & 2+1 \end{bmatrix}$$

Extension of Two-ports

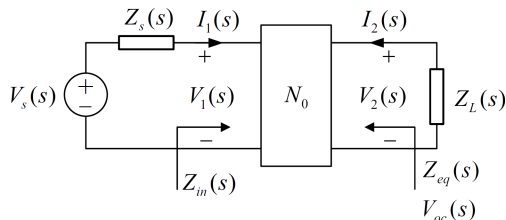


Figure: A terminated two-port with the open circuit voltage $V_{oc}(s) = V_2(s)|_{I_2=0} = \frac{z_{21}(s)}{z_{11}(s)+Z_s(s)} V_s(s)$.


	Z	Y	H	G	T	T'
Z_{in}	$z_{11} - \frac{z_{12}z_{21}}{z_{22}+Z_L}$	$[y_{11} - \frac{y_{12}y_{21}}{y_{22}+y_L}]^{-1}$	$h_{11} - \frac{h_{12}h_{21}}{h_{22}+Y_L}$	$[g_{11} - \frac{g_{12}g_{21}}{g_{22}+Z_L}]^{-1}$	$\frac{AZ_L+B}{CZ_L+D}$	$\frac{B'+D'Z_L}{A'+C'Z_L}$
Z_{eq}	$z_{22} - \frac{z_{12}z_{21}}{z_{11}+Z_s}$	$[y_{22} - \frac{y_{12}y_{21}}{y_{11}+y_s}]^{-1}$	$[h_{22} - \frac{h_{12}h_{21}}{h_{11}+Z_s}]^{-1}$	$g_{22} - \frac{g_{12}g_{21}}{g_{11}+Y_s}$	$\frac{B+DZ_s}{A+CZ_s}$	$\frac{A'Z_s+B'}{C'Z_s+D'}$

Table: Input impedance and equivalent impedance for a terminated two-port.

Extension of Two-ports

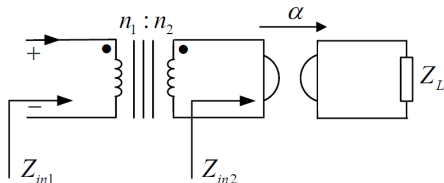Example (Terminated two-port)

The input impedance for a terminated two-port can be found using two-port descriptions.



$$\mathbf{Z}_2 = \begin{bmatrix} 0 & \alpha \\ -\alpha & 0 \end{bmatrix} \Rightarrow \mathbf{T}_2 = \begin{bmatrix} 0 & -\alpha \\ -\frac{1}{\alpha} & 0 \end{bmatrix} \Rightarrow Z_{in2}(s) = \frac{AZ_L + B}{CZ_L + D} = \frac{-\alpha}{-\frac{1}{\alpha}Z_L} = \frac{\alpha^2}{Z_L(s)} \Rightarrow Z_{in1}(s) = \left(\frac{n_1}{n_2}\right)^2 Z_{in2}(s)$$

$$\mathbf{T}_1 = \begin{bmatrix} \frac{n_1}{n_2} & 0 \\ 0 & \frac{n_1}{n_2} \end{bmatrix} \Rightarrow \mathbf{T} = \mathbf{T}_1 \mathbf{T}_2 = \begin{bmatrix} 0 & -\alpha \frac{n_1}{n_2} \\ -\frac{1}{\alpha} \frac{n_1}{n_2} & 0 \end{bmatrix} \Rightarrow Z_{in1}(s) = \frac{AZ_L + B}{CZ_L + D} = \frac{-\alpha \frac{n_1}{n_2}}{-\frac{1}{\alpha} \frac{n_1}{n_2} Z_L} = \left(\frac{n_1}{n_2}\right)^2 \frac{\alpha^2}{Z_L(s)}$$

Interconnection of Two-ports

Interconnection of Two-ports

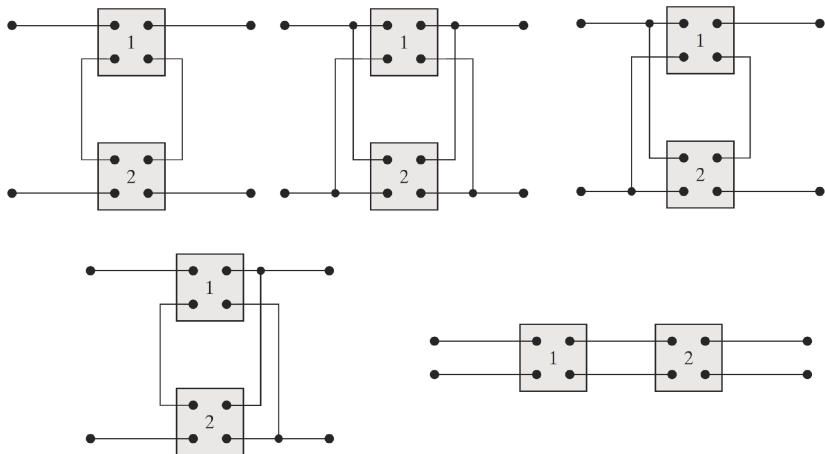


Figure: Various interconnections of two-ports including series-series, parallel-parallel, series-parallel, parallel-series, and cascade connections. Brune test provides a sufficient condition for possibility of each connection. For reciprocal two-ports, the Brune test specifies a sufficient and necessary condition.

Series-Series Connection

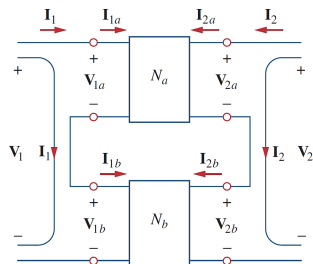


Figure: The overall impedance matrix in series-series connection is $\mathbf{Z} = \mathbf{Z}_a + \mathbf{Z}_b$.

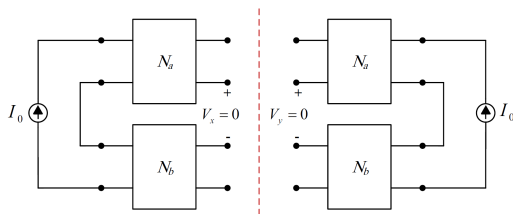


Figure: The Brune test configuration for checking the validity of the current condition for the overall series-series connected two-port.

Parallel-Parallel Connection

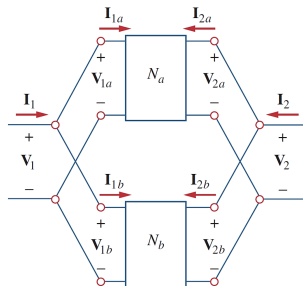


Figure: The overall admittance matrix in parallel-parallel connection is $\mathbf{Y} = \mathbf{Y}_a + \mathbf{Y}_b$.

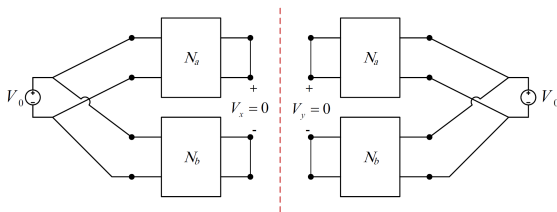


Figure: The Brune test configuration for checking the validity of the current condition for the overall parallel-parallel connected two-port.

Series-Parallel Connection

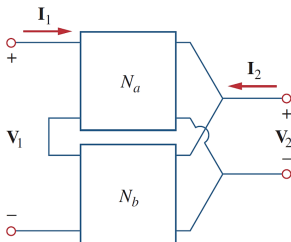


Figure: The overall hybrid H matrix in series-parallel connection is $H = H_a + H_b$.

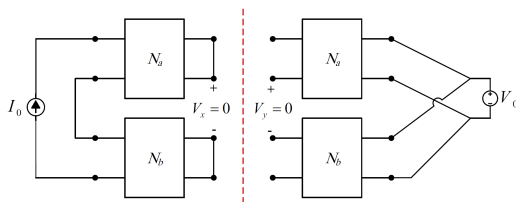


Figure: The Brune test configuration for checking the validity of the current condition for the overall series-parallel connected two-port.

Parallel-Series Connection

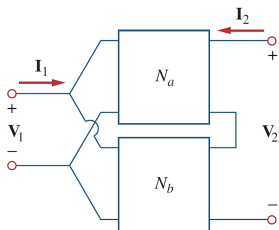


Figure: The overall hybrid G matrix in parallel-series connection is $\mathbf{G} = \mathbf{G}_a + \mathbf{G}_b$.

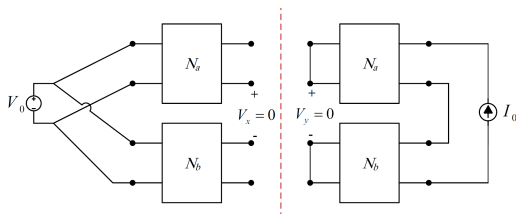


Figure: The Brune test configuration for checking the validity of the current condition for the overall parallel-series connected two-port.

Cascade Connection

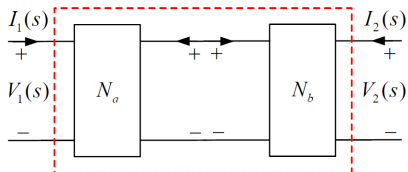


Figure: The overall transmittance ABCD matrix in cascade connection is $T = T_a T_b$.


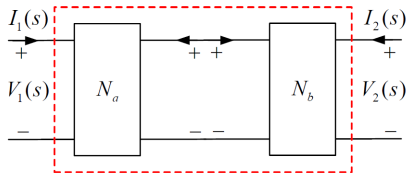
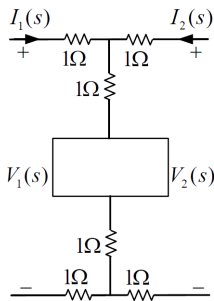
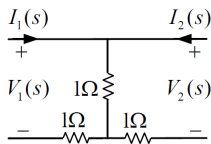


Figure: The overall transmittance A'B'C'D' matrix in cascade connection is $T' = T'_b T'_a$.

Interconnection of Two-ports

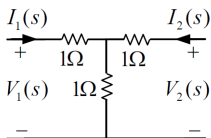Example (Series-series connection)

Interconnection rules can be used to find a suitable description for a complex two-port.






$$\mathbf{Z}_a = \begin{bmatrix} 2 & 1 \\ 1 & 2 \end{bmatrix}, \quad \mathbf{Z}_b = \begin{bmatrix} 2 & 1 \\ 1 & 2 \end{bmatrix} \Rightarrow \mathbf{Z} = \mathbf{Z}_a + \mathbf{Z}_b = \begin{bmatrix} 4 & 2 \\ 2 & 4 \end{bmatrix}$$

Interconnection of Two-ports

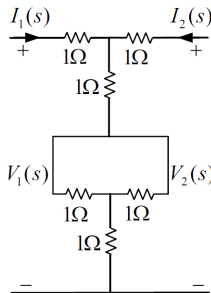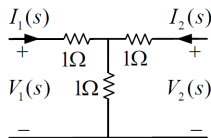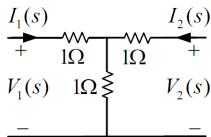Example (Current condition violation)

Current condition may be violated while interconnecting two-ports.



$$\mathbf{z}_a = \begin{bmatrix} 2 & 1 \\ 1 & 2 \end{bmatrix}, \quad \mathbf{z}_b = \begin{bmatrix} 2 & 1 \\ 1 & 2 \end{bmatrix}, \quad \mathbf{z} = \begin{bmatrix} 3.5 & 2.5 \\ 2.5 & 3.5 \end{bmatrix} \neq \mathbf{z}_a + \mathbf{z}_b = \begin{bmatrix} 4 & 2 \\ 2 & 4 \end{bmatrix}$$

Two-ports Models

Two-ports Models

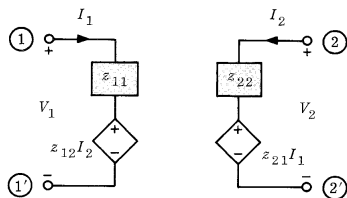


Figure: An **equivalent circuit** of a two-port in terms of the open circuit **impedance parameters**.

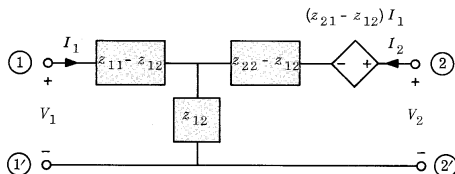


Figure: **T equivalent circuit** of a two-port in terms of the open circuit **impedance parameters**. Note that the terminals **1'** and **2'** have the **same voltage**. If the two-port is **reciprocal**, the **dependent current source** vanishes.

Two-ports Models

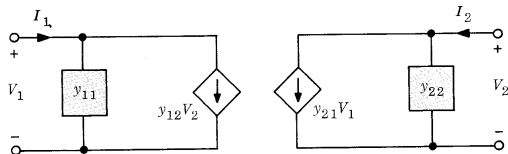


Figure: An equivalent circuit of a two-port in terms of the short circuit admittance parameters.

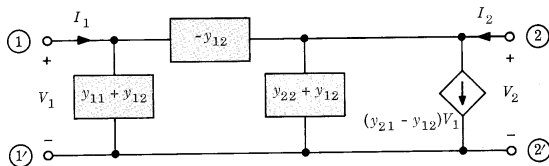


Figure: \square equivalent circuit of a two-port in terms of the short circuit admittance parameters. Note that the terminals 1' and 2' have the same voltage. If the two-port is reciprocal, the dependent current source vanishes.

Two-ports Models


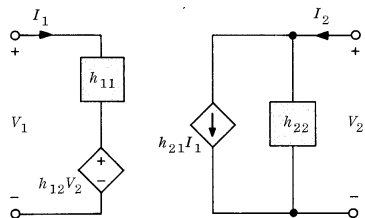


Figure: An equivalent circuit of a two-port in terms of the H parameters.

Two-ports Models

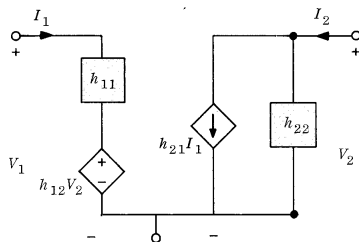Example (BJT transistor)

A BJT transistor can be modeled using its small-signal hybrid H parameters.



$$\begin{cases} h_{ie} = r_{\pi} = h_{11} \approx 1.0\text{--}10 \text{ k}\Omega \\ h_{re} = h_{12} \approx 0.5\text{--}8.0 \times 10^{-4} \\ h_{fe} = \beta = h_{21} \approx 100\text{--}400 \\ h_{oe} = h_{22} \approx .0\text{--}40 \mu\text{S} \end{cases}$$

Natural Frequencies

Natural Frequencies

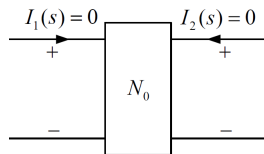


Figure: The poles of the impedance matrix elements are the natural frequencies of the circuit obtained by making the first and second ports open circuit.

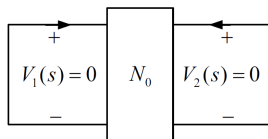


Figure: The poles of the admittance matrix elements are the natural frequencies of the circuit obtained by making the first and second ports short circuit.

Natural Frequencies

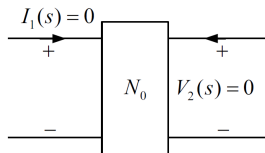


Figure: The poles of the hybrid H matrix elements are the natural frequencies of the circuit obtained by making the first port open circuit and the second port short circuit.


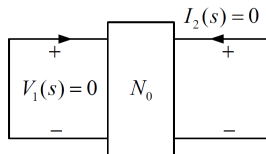


Figure: The poles of the hybrid G matrix elements are the natural frequencies of the circuit obtained by making the first port short circuit and the second port open circuit.

Natural Frequencies

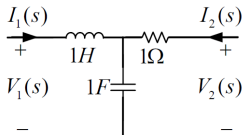Example (Natural frequencies)

Natural frequencies can be found using different two-port descriptions.



$$\mathbf{Z} = \begin{bmatrix} \frac{s^2+1}{s} & \frac{1}{s} \\ \frac{1}{s} & \frac{s+1}{s} \end{bmatrix}, \quad \mathbf{Y} = \begin{bmatrix} \frac{s+1}{s^2+s+1} & \frac{-1}{s^2+s+1} \\ \frac{-1}{s^2+s+1} & \frac{s^2+1}{s^2+s+1} \end{bmatrix}, \quad \mathbf{H} = \begin{bmatrix} \frac{s^2+s+1}{s+1} & \frac{1}{s+1} \\ \frac{-1}{s+1} & \frac{s}{s+1} \end{bmatrix}, \quad \mathbf{G} = \begin{bmatrix} \frac{s}{s^2+1} & -\frac{1}{s^2+1} \\ \frac{1}{s^2+1} & \frac{s^2+s+1}{s^2+1} \end{bmatrix}$$

$$s_1 = 0,$$

$$s_{1,2} = -\frac{1}{2} \pm j\frac{\sqrt{3}}{2},$$

$$s_1 = -1,$$

$$s_{1,2} = \pm j$$

Calculation Techniques


Calculation Techniques

- Element definitions
- Circuit analysis
- Two-port extension
- Two-port interconnection
- Description interrelation

Calculation Techniques

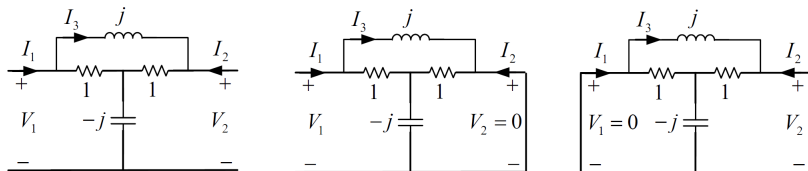Example (Element definition technique)


Two-port description may be found using its element definitions.



$$\begin{cases} y_{11}(j\omega) = \frac{I_1(j\omega)}{V_1(j\omega)} \Big|_{V_2(j\omega)=0} = \frac{3+6j}{5} \\ y_{22}(j\omega) = \frac{I_2(j\omega)}{V_2(j\omega)} \Big|_{V_1(j\omega)=0} = \frac{3+6j}{5} \\ y_{12}(j\omega) = \frac{I_1(j\omega)}{V_2(j\omega)} \Big|_{V_1(j\omega)=0} = \frac{-2-4j}{5} \\ y_{21}(j\omega) = \frac{I_2(j\omega)}{V_1(j\omega)} \Big|_{V_2(j\omega)=0} = \frac{-2-4j}{5} \end{cases} \Rightarrow \mathbf{Y} = \begin{bmatrix} \frac{3+6j}{5} & \frac{-2-4j}{5} \\ \frac{-2-4j}{5} & \frac{3+6j}{5} \end{bmatrix}$$

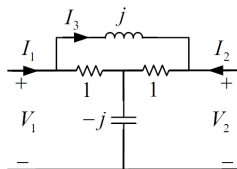Example (Circuit analysis technique)


Two-port description may be found using circuit analysis.



$$\begin{bmatrix} 1-j & j & -1 \\ j & 1-j & -1 \\ -1 & -1 & j+2 \end{bmatrix} \begin{bmatrix} I_1 \\ -I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ -V_2 \\ 0 \end{bmatrix} \Rightarrow \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{3+6j}{-5} & \frac{-2-4j}{5} \\ \frac{-2-4j}{5} & \frac{3+6j}{5} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \Rightarrow \mathbf{Y} = \begin{bmatrix} \frac{3+6j}{5} & \frac{-2-4j}{5} \\ \frac{-2-4j}{5} & \frac{3+6j}{5} \end{bmatrix}$$

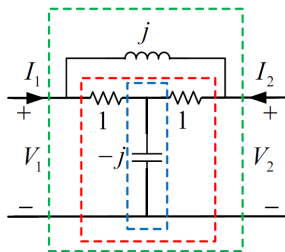Example (Two-port extension)

Two-port description may be found by extending a simple two-port.




$$\mathbf{Z}_1 = \begin{bmatrix} -j & -j \\ -j & -j \end{bmatrix} \Rightarrow \mathbf{Z}_2 = \begin{bmatrix} 1-j & -j \\ -j & 1-j \end{bmatrix} \Rightarrow \mathbf{Y}_2 = \begin{bmatrix} \frac{3+j}{5} & \frac{-2+j}{5} \\ \frac{-2+j}{5} & \frac{3+j}{5} \end{bmatrix}$$

$$\mathbf{Y} = \begin{bmatrix} \frac{3+j}{5} + j & \frac{-2+j}{5} - j \\ \frac{-2+j}{5} - j & \frac{3+j}{5} + j \end{bmatrix} = \begin{bmatrix} \frac{3+6j}{5} & \frac{-2-4j}{5} \\ \frac{-2-4j}{5} & \frac{3+6j}{5} \end{bmatrix}$$

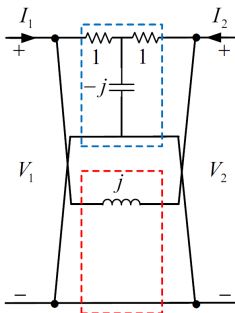Example (Two-port interconnection)

Two-port description may be found by interconnecting several simple two-ports.






$$\mathbf{Z}_1 = \begin{bmatrix} -j & -j \\ -j & -j \end{bmatrix} \Rightarrow \mathbf{Z}_a = \begin{bmatrix} 1-j & -j \\ -j & 1-j \end{bmatrix} \Rightarrow \mathbf{Y}_a = \begin{bmatrix} \frac{3+j}{5} & \frac{-2+j}{5} \\ \frac{-2+j}{5} & \frac{3+j}{5} \end{bmatrix}, \quad \mathbf{Y}_b = \begin{bmatrix} j & -j \\ -j & j \end{bmatrix}$$

$$\mathbf{Y} = \mathbf{Y}_a + \mathbf{Y}_b = \begin{bmatrix} \frac{3+6j}{5} & \frac{-2-4j}{5} \\ \frac{-2-4j}{5} & \frac{3+6j}{5} \end{bmatrix}$$

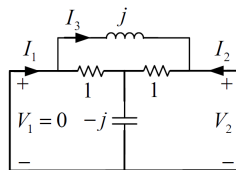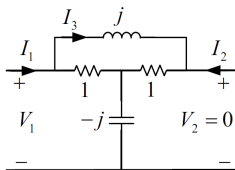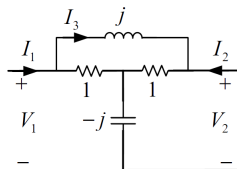Example (Description interrelation)

Two-port description may be found using description interrelations from another available description.



$$\mathbf{Y} = \begin{bmatrix} \frac{3+6j}{5} & \frac{-2-4j}{5} \\ \frac{-2-4j}{5} & \frac{3+6j}{5} \end{bmatrix} \Rightarrow \mathbf{Z} = \mathbf{Y}^{-1} = \begin{bmatrix} \frac{3-6j}{5} & \frac{-2-4j}{5} \\ \frac{-2-4j}{5} & \frac{3-6j}{5} \end{bmatrix}$$

Multi-ports

Multi-ports

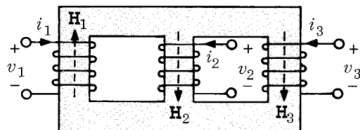


Figure: **Three-winding coupled inductors** create a three-port with
$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} L_{1s} & M_{12s} & M_{13s} \\ M_{21s} & L_{2s} & M_{23s} \\ M_{31s} & M_{32s} & L_{3s} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}.$$

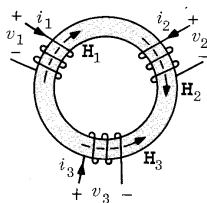


Figure: **Three-winding ideal transformers** create a three-port with
$$\begin{bmatrix} V_1 \\ V_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 & 0 & \frac{n_1}{n_3} \\ 0 & 0 & \frac{n_2}{n_3} \\ -\frac{n_1}{n_3} & -\frac{n_2}{n_3} & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ V_3 \end{bmatrix}.$$

The End