

## MATHEMATICAL QUESTIONS

### Question 1

Find an expression for  $v_c(t)$  in Fig. 1 valid for all time  $t$ .

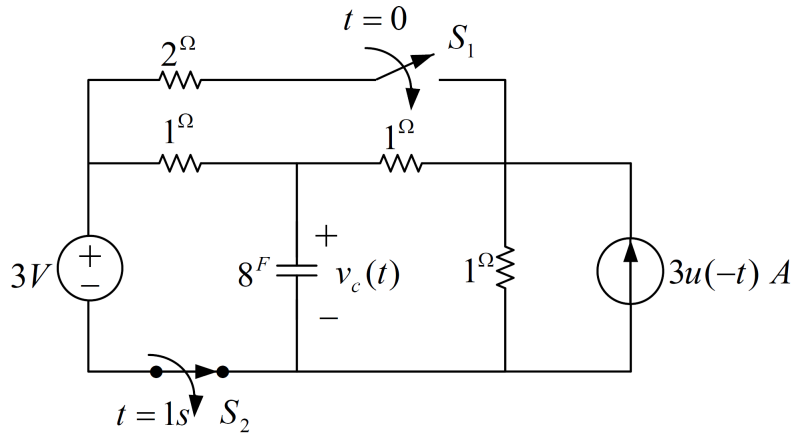


Figure 1: An RC circuit with two switches.

### Question 2

Find an expression for  $v(t)$  in Fig. 2 valid for all time  $t$ .

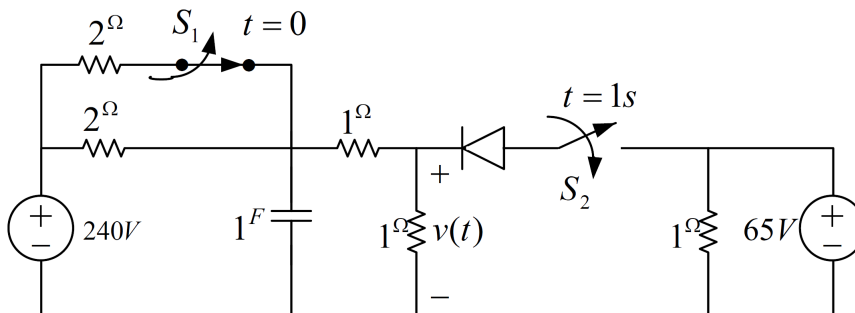


Figure 2: A nonlinear RC circuit with diode.

### Question 3

Determine both  $i_1$  and  $i_L$  in the circuit shown in Fig. 3 for  $t > 0$ .

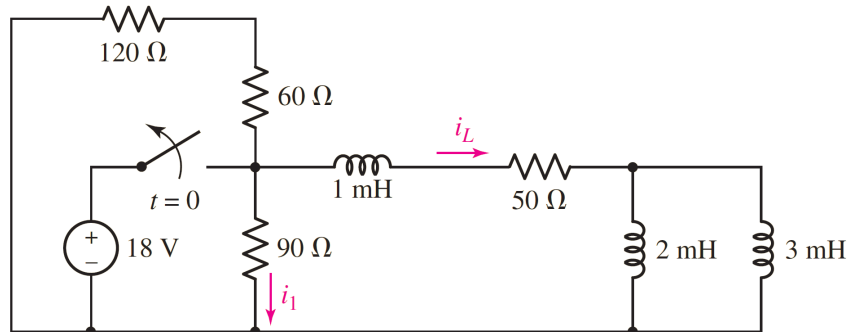


Figure 3: A circuit with multiple resistors and inductors.

### Question 4

Consider the circuit shown in Fig. 4.

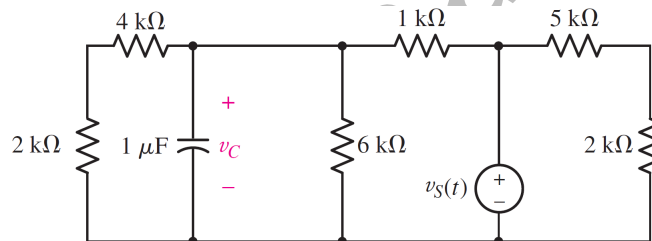


Figure 4: A first-order LIT RC circuit.

(a) Find the step response of  $v_c(t)$ .

(b) Find the impulse response of  $v_c(t)$ .

(c) Find the zero-state response of  $v_c(t)$  if  $v_s(t) = 5u(t) + 2\delta'(t)$ .

(d) Find the zero-state response of  $v_c(t)$  if  $v_s(t) = 2e^{-2t}u(t)$ .

(e) Find the zero-state response of  $v_c(t)$  if  $v_s(t) = 2\cos(t)u(t)$ .

---

## SOFTWARE QUESTIONS

---

### Question 5

Consider the circuit shown in Fig. 5, where the diodes are 1N4148 and  $v_s(t)$  is a periodic square signal with low level 0, high level 15 V, duty cycle 0.5, and period  $T$ . Simulate the circuit in PSpice and plot the capacitor voltage versus time when  $\tau_1 = R_1C \ll T$  and  $\tau_2 = R_2C \ll T$  and when  $\tau_1 = R_1C \gg T$  and  $\tau_2 = R_2C \gg T$ . Discuss and compare the results.

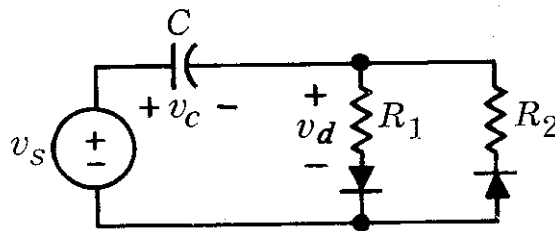


Figure 5: A first-order NTI RC circuit.

---

## BONUS QUESTIONS

---

### Question 6

Find an expression for the NTI resistor voltage in Fig. 6 valid for  $t > 0$ . Assume that  $v_c(0^+) = V_0 = 3$ .

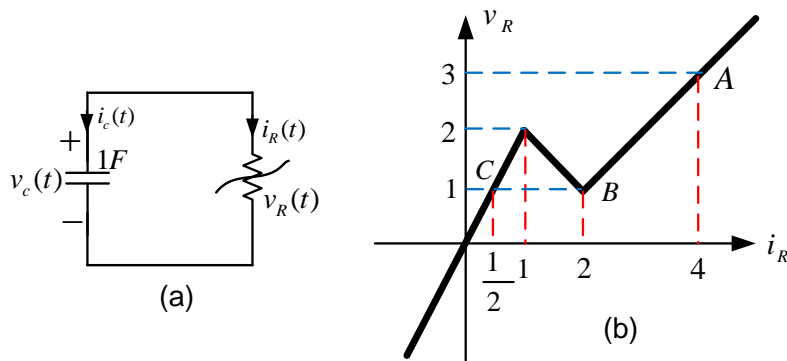


Figure 6: (a) A nonlinear RC circuit with an NTI resistor (b) Characteristic curve of the NTI resistor.

### Question 7

Return your answers by filling the  $\LaTeX$  template of the assignment.

---

EXTRA QUESTIONS

---

### Question 8

Feel free to solve the following questions from the book "Engineering Circuit Analysis" by W. Hayt, J. Kemmerly, and S. Durbin.

1. Chapter 8, question 29.
2. Chapter 8, question 31.
3. Chapter 8, question 37.
4. Chapter 8, question 38.
5. Chapter 8, question 39.
6. Chapter 8, question 48.
7. Chapter 8, question 50.
8. Chapter 8, question 51.
9. Chapter 8, question 52.
10. Chapter 8, question 58.

11. Chapter 8, question 60.
12. Chapter 8, question 61.
13. Chapter 8, question 64.

Mohammad Hadi