

MATHEMATICAL QUESTIONS

Question 1

Find the step and impulse responses of the current $i(t)$ in Fig. 1.

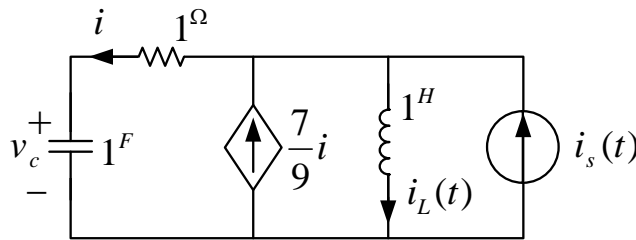


Figure 1: An LTI RLC circuit with dependent source.

Question 2

Find an expression for the zero-input response of $v_1(t)$ in Fig. 2 valid for $t > 0$ if $v_1(0^+) = V_1$ and $v_2(0^+) = V_2$.

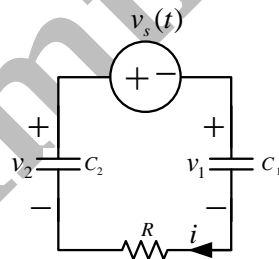


Figure 2: A circuit with two capacitors.

Question 3

Calculate $i_L(t), t > 0$ in Fig. 3, where

$$R(t) = \begin{cases} 2, & t < 0 \\ 1, & 0 < t < 2 \\ 3, & t > 2 \end{cases}$$

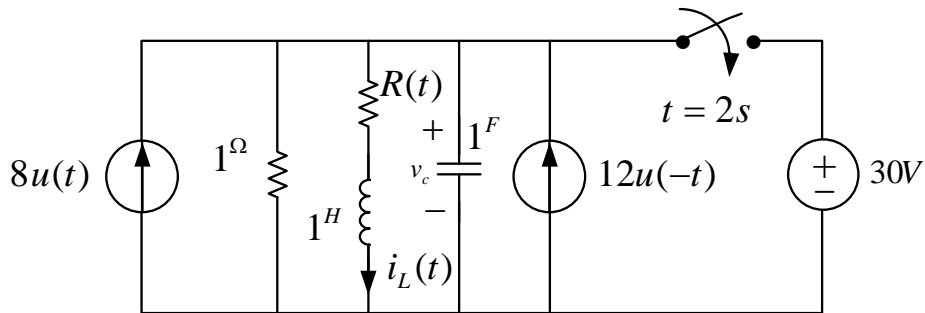


Figure 3: A second-order time-variant circuit.

Question 4

Let $v_c(0^-) = 2 \text{ V}$ and $i_L(0^-) = 1 \text{ A}$ and find $v_c(t), t > 0$ in Fig. 4.

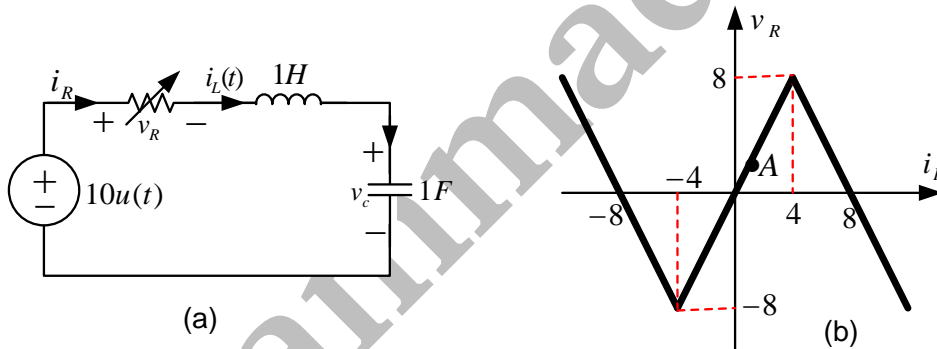


Figure 4: A nonlinear second-order circuit.

SOFTWARE QUESTIONS

Question 5

Consider the parallel RLC circuit shown in Fig. 5. Use PSpice transient simulation to plot the step responses of $v_c(t), i_L(t), i_R(t),$ and $i_c(t)$ for $L = 1, C = 1,$ and $R = 0.25, 0.5, 1, 1000.$

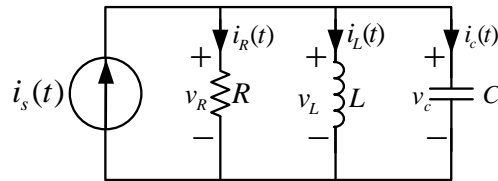


Figure 5: A parallel RLC circuit.

BONUS QUESTIONS

Question 6

Return your answers by filling the \LaTeX template of the assignment.

EXTRA QUESTIONS

Question 7

Feel free to solve the following questions from the book "*Engineering Circuit Analysis*" by W. Hayt, J. Kemmerly, and S. Durbin.

1. Chapter 9, question 13.
2. Chapter 9, question 14.
3. Chapter 9, question 20.
4. Chapter 9, question 26.
5. Chapter 9, question 35.
6. Chapter 9, question 37.
7. Chapter 9, question 39.
8. Chapter 9, question 48.
9. Chapter 9, question 50.

10. Chapter 9, question 51.
11. Chapter 9, question 53.
12. Chapter 9, question 61.
13. Chapter 9, question 65.

Mohammad Hadi