

# Basic Circuit Elements

Mohammad Hadi

*mohammad.hadi@sharif.edu*

*@MohammadHadiDastgerdi*

Spring 2022

# Overview

- 1 Signals
- 2 Resistor
- 3 Capacitor
- 4 Inductor
- 5 Memristor
- 6 Power and Energy
- 7 Elements Interconnections

# Signals

# Elementary Signals

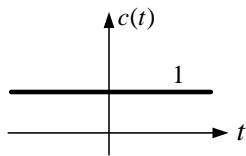


Figure: Constant signal  
 $c(t) = 1, \forall t$ .

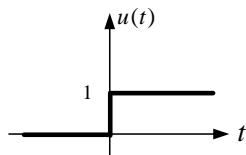


Figure: Step signal  
$$u(t) = \begin{cases} 1, & t \geq 0 \\ 0, & t < 0 \end{cases}$$

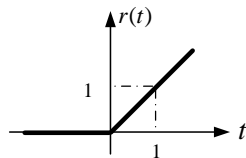


Figure: Step signal

$$r(t) = \begin{cases} t, & t \geq 0 \\ 0, & t < 0 \end{cases} = tu(t) = \int_{-\infty}^t u(\lambda) d\lambda.$$

# Elementary Signals


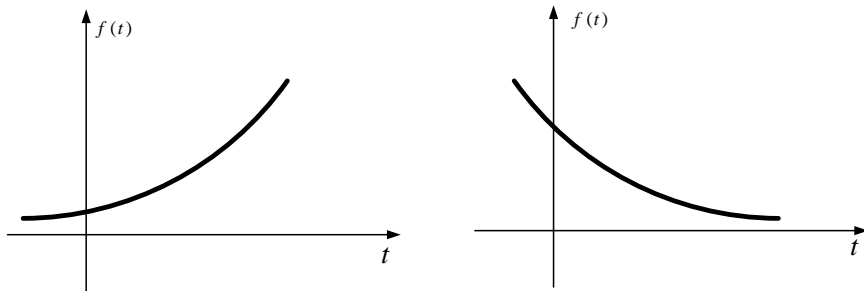


Figure: Exponential signal  $f(t) = Ae^{at}$ .


## Example (Rectangular signal)

$$\Pi(t) = u(t + 0.5) - u(t - 0.5).$$

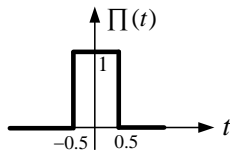
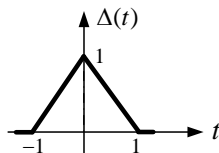
## Example (Triangle signal)

$$\Lambda(t) = r(t+1) - 2r(t) + r(t-1).$$



$$\Lambda(t) = (t+1)[u(t+1) - u(t)] + (1-t)[u(t) - u(t-1)] = r(t+1) - 2r(t) + r(t-1)$$

# Singular Signals

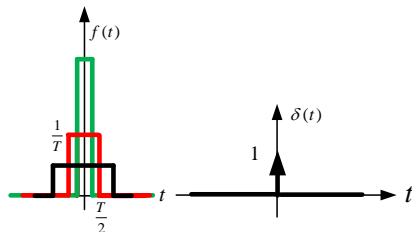


Figure: Impulse signal  $\delta(t)$ .

- Definition:**  $\delta(t) = \lim_{T \rightarrow 0} \frac{1}{T} \Pi\left(\frac{t}{T}\right) = \lim_{T \rightarrow 0} \frac{u(t+0.5T) - u(t-0.5T)}{T} = \begin{cases} \infty, & t = 0 \\ 0, & t \neq 0 \end{cases}$
- Surface:**  $\int_{-\infty}^{+\infty} \delta(t) dt = \int_{0^-}^{0^+} \delta(t) dt = 1$
- Sampling:**  $\int_{-\infty}^{+\infty} f(t) \delta(t) dt = \int_{t_1}^{t_2} f(t) \delta(t) dt = f(0), 0 \in (t_1, t_2), \quad f(t) \delta(t) = f(0) \delta(t)$
- Scaling:**  $\delta(at) = \frac{1}{|a|} \delta(t)$
- Integral:**  $u(t) = \int_{-\infty}^t \delta(\lambda) d\lambda$
- Derivative:**  $\delta'(t) = \frac{d\delta(t)}{dt}$



# Singular Signals

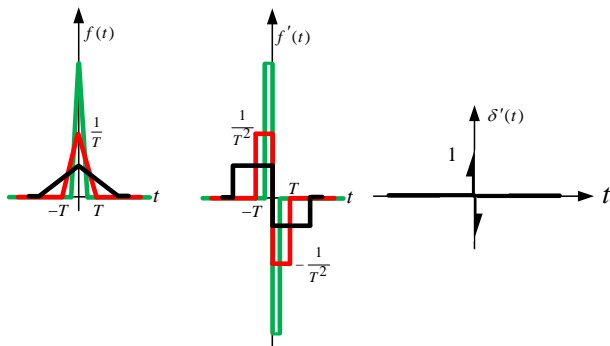



Figure: Doublet signal  $\delta'(t)$ .

- 1 **Definition:**  $\delta(t) = \lim_{T \rightarrow 0} \frac{1}{T} \Lambda\left(\frac{t}{T}\right) = \begin{cases} \infty, & t = 0 \\ 0, & t \neq 0 \end{cases}, \quad \delta'(t) = \frac{d\delta(t)}{dt}$
- 2 **Surface:**  $\int_{-\infty}^{+\infty} \delta'(t) dt = \int_{0^-}^{0^+} \delta'(t) dt = 0$
- 3 **Sampling:**  $\int_{t_1}^{t_2} f(t) \delta'(t) dt = -f'(0), 0 \in (t_1, t_2), \quad f(t) \delta'(t) = -f'(0) \delta(t) + f(0) \delta'(t)$
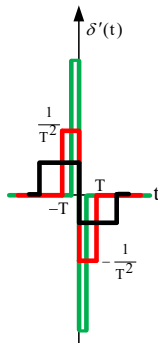
## Example (Sampling property of $\delta'(t)$ )


The sampling property of  $\delta'(t)$  can be roughly verified as the limit of  $\frac{1}{T}\Lambda(\frac{t}{T})$ .

$$\begin{aligned} 0 \in (t_1, t_2) \\ \int_{t_1}^{t_2} f(t)\delta'(t)dt &= \lim_{T \rightarrow 0} [f(-0.5T)\frac{1}{T^2}T - f(0.5T)\frac{1}{T^2}T] \\ &= \lim_{T \rightarrow 0} \frac{f(-0.5T) - f(+0.5T)}{T} \\ &= - \lim_{T \rightarrow 0} \frac{f(0.5T) - f(-0.5T)}{0.5T - (-0.5T)} = -f'(0) \end{aligned}$$


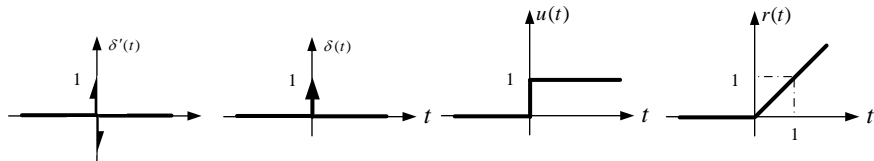
## Example (Relations of singular functions)

Singular functions relate to each other using derivative and integral operations.




$$\dots, \quad \delta'(t) = \frac{d\delta(t)}{dt}, \quad \delta(t) = \frac{du(t)}{dt}, \quad u(t) = \frac{dr(t)}{dt}, \quad \dots$$

$$\dots, \quad \delta(t) = \int_{-\infty}^t \delta'(\lambda) d\lambda, \quad u(t) = \int_{-\infty}^t \delta(\lambda) d\lambda, \quad r(t) = \int_{-\infty}^t u(\lambda) d\lambda, \quad \dots$$

# Singular Signals
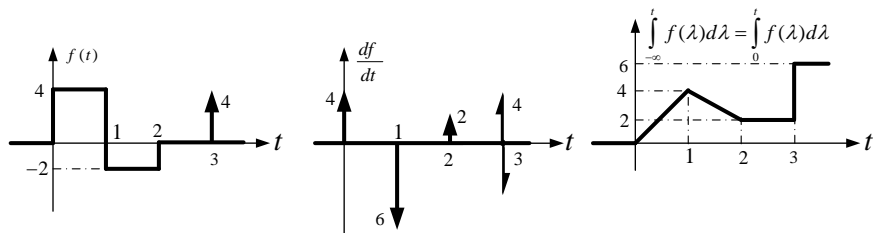
## Example (Derivative and integral of discontinuous function)

Singular functions can be used in derivative and integral calculations.



$$f(t) = 4u(t) - 6u(t-1) + 2u(t-2) + 4\delta(t-3)$$

$$\frac{df(t)}{dt} = 4\delta(t) - 6\delta(t-1) + 2\delta(t-2) + 4\delta'(t-3)$$

$$\int_{-\infty}^t f(\lambda) d\lambda = 4tu(t) - 6(t-1)u(t-1) + 2(t-2)u(t-2) + 4u(t-3)$$

# Periodic Signals

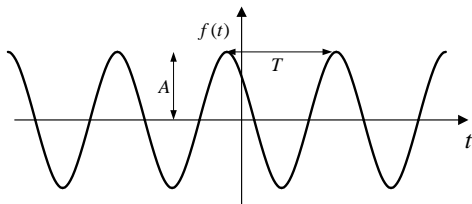


Figure: Sinusoidal periodic signals with period  $T$ .

1 Expression:  $f(t) = A \cos(\omega t + \theta) \equiv A \sin(\omega t + \theta)$

2 Period:  $T = \frac{2\pi}{\omega} = \frac{1}{f}$

3 Frequency:  $f = \frac{\omega}{2\pi} = \frac{1}{T}$

4 Phase:  $\theta$

5 Amplitude:  $A$

6 Peak to peak amplitude:  $2A$

7 Average:  $f_{av} = \frac{1}{T} \int_T f(t) dt = \frac{1}{T} \int_T A \cos(\omega t + \theta) dt = 0$

8 RMS:  $f_{rms} = \sqrt{\frac{1}{T} \int_T |f(t)|^2 dt} = \sqrt{\frac{1}{T} \int_T A^2 \cos^2(\omega t + \theta) dt} = \frac{A}{\sqrt{2}}$

# Periodic Signals


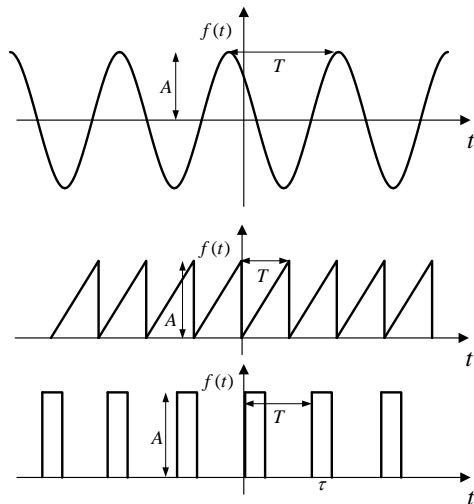


Figure: Sinusoidal, sawtooth, and pulse train periodic signals with period  $T$ .
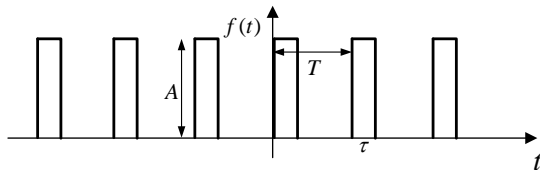
## Example (Pulse train)

A pulse train can be characterized in terms of its average, rms, and duty cycle.



$$f(t) = A \Pi\left(\frac{t - 0.5\tau}{\tau}\right), 0 \leq t < T, f(t \pm T) = f(t)$$


$$D = \frac{\tau}{T}$$

$$f_{av} = \frac{1}{T} \int_T f(t) dt = A \frac{\tau}{T} = AD$$

$$f_{rms} = \sqrt{\frac{1}{T} \int_T |f(t)|^2 dt} = A \sqrt{\frac{\tau}{T}} = A\sqrt{D}$$
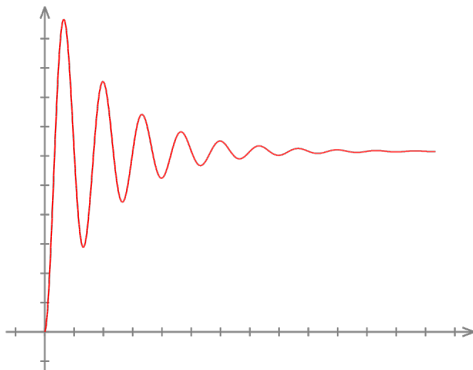
## Example (Underdamped signal)

An underdamped signal can be expressed as the multiplication of sinusoidal and exponential signals.



$$f(t) = A + Be^{-\alpha t} \cos(\omega t + \phi)$$



## Example (Complex exponential signal)

A complex signal can be described using its polar or Cartesian presentations.

$$f(t) = Ae^{-\alpha t} e^{j(\omega t + \phi)} = \Re\{f(t)\} + j\Im\{f(t)\} = |f(t)|e^{j\angle f(t)}$$

$$\Re\{f(t)\} = Ae^{-\alpha t} \cos(\omega t + \phi)$$

$$\Im\{f(t)\} = Ae^{-\alpha t} \sin(\omega t + \phi)$$

$$|f(t)| = |A|e^{-\alpha t}$$

$$\angle f(t) = \omega t + \phi + \pi u(-A)$$

# Resistor

## Statement (Linear Function)

The function  $f(x)$  is (map-) linear if it is homogeneous, i.e.,  $f(\alpha x) = \alpha f(x)$ , and additive, i.e.,  $f(x_1 + x_2) = f(x_1) + f(x_2)$ .

## Statement (Continuous Function)

The function  $f(x)$  is continuous if  $\lim_{x \rightarrow x_0} f(x) = f(x_0), \forall x_0$ .

## Statement (Bounded Function)

The function  $f(x)$  is bounded if  $|f(x_0)| < M, \forall x_0$ .

- 1  $f(x) = ax$  is a linear function.
- 2  $f(x) = ax + b, b \neq 0$  is not a linear function.
- 3  $f(x(t)) = \frac{dx(t)}{dt}$  is a linear function.
- 4  $f(x) = u(x)$  is not continuous but is bounded.
- 5  $f(x) = \delta(x)$  is not continuous and is not bounded.

# Resistor

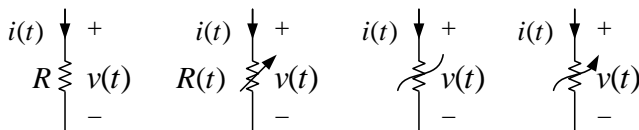


Figure: LTI, LTV, NTV, NTV resistors. The units of voltage, current, resistance, and conductance are  $V$ ,  $A$ ,  $\Omega$ ,  $\mathcal{U}$ .

- 1 **Linear time-invariant resistor:**  $v(t) = Ri(t) \equiv i(t) = Gv(t)$
- 2 **Linear time-variant resistor:**  $v(t) = R(t)i(t) \equiv i(t) = G(t)v(t)$
- 3 **Nonlinear time-invariant resistor:**  $f(v(t), i(t)) = 0$
- 4 **Nonlinear time-variant resistor:**  $f(v(t), i(t), t) = 0$
- 5 **Voltage-controlled resistor:**  $i(t) = f(v(t), t)$
- 6 **Current-controlled resistor:**  $v(t) = f(i(t), t)$
- 7 **Bilateral resistor:**  $f(v(t), i(t)) = f(-v(t), -i(t))$

# Resistor


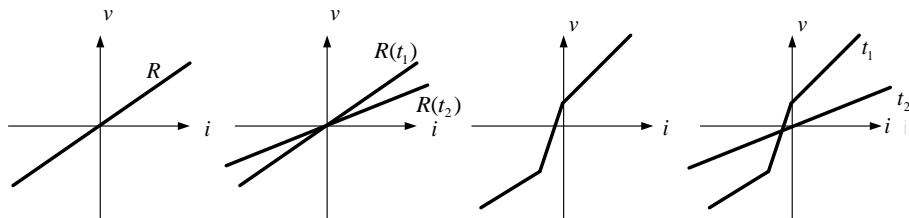


Figure: LTI, LTV, NTV resistors. The units of voltage, current, resistance, and conductance are V, A,  $\Omega$ ,  $\mathcal{U}$ .

- 1 **Linear time-invariant resistor:**  $v(t) = Ri(t) \equiv i(t) = Gv(t)$
- 2 **Linear time-variant resistor:**  $v(t) = R(t)i(t) \equiv i(t) = G(t)v(t)$
- 3 **Nonlinear time-invariant resistor:**  $f(v(t), i(t)) = 0$
- 4 **Nonlinear time-variant resistor:**  $f(v(t), i(t), t) = 0$
- 5 **Voltage-controlled resistor:**  $i(t) = f(v(t), t)$
- 6 **Current-controlled resistor:**  $v(t) = f(i(t), t)$
- 7 **Bilateral resistor:**  $f(v(t), i(t)) = f(-v(t), -i(t))$

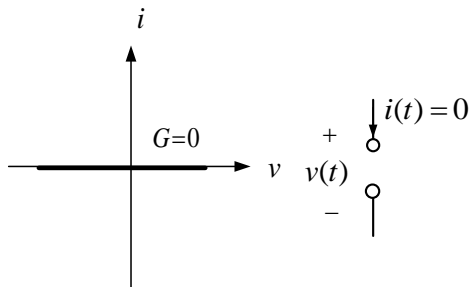
## Example (Open circuit)

Open circuit is a voltage-controlled bilateral LTI resistor with  $G = 0$ .



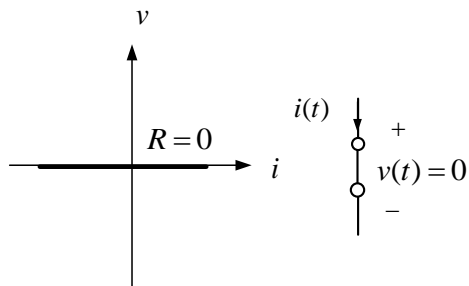
## Example (Short circuit)

Short circuit is a current-controlled bilateral LTI resistor with  $R = 0$ .


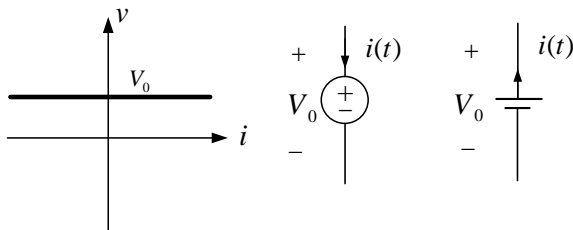
## Example (DC voltage source)


DC voltage source is a current-controlled NTI resistor.





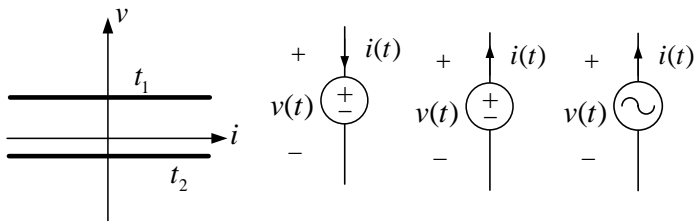
## Example (AC voltage source)

AC voltage source is a current-controlled NTV resistor.



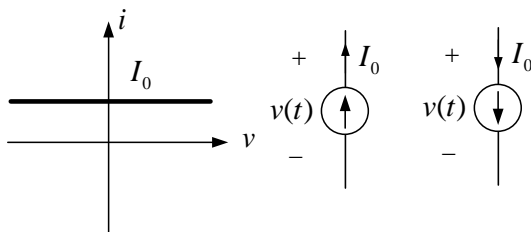
## Example (DC current source)

DC current source is a voltage-controlled NTI resistor.



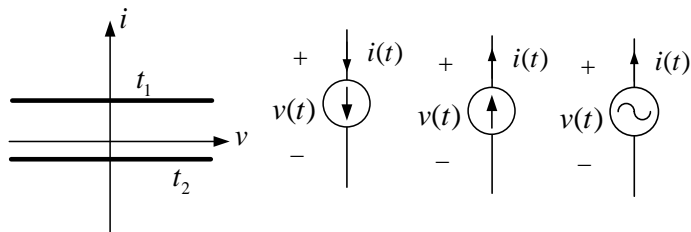
## Example (AC current source)

AC current source is a voltage-controlled NTV resistor.




## Example (Ideal diode)

An ideal diode is an NTI resistor.

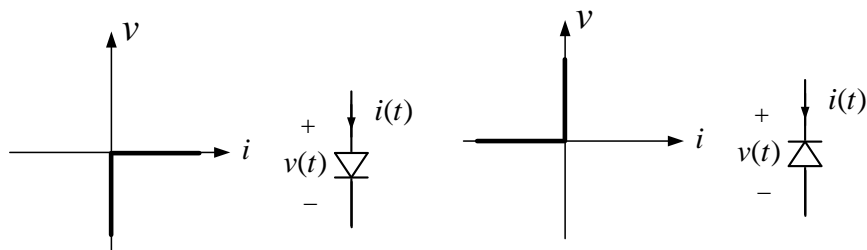



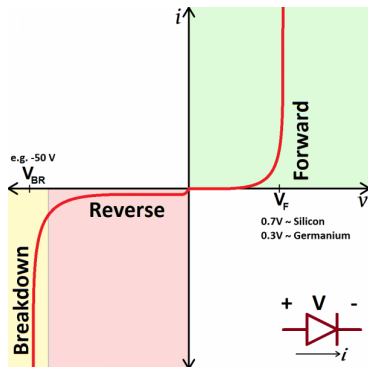
## Example (Ideal diode)

A real diode with the characteristic curve  $i = I_s(e^{\frac{qv}{kT}} - 1) = I_s(e^{\frac{v}{V_T}} - 1)$  is an NTI resistor, where the thermal voltage equals  $V_T = kT/q \approx 26$  mV in room temperature.


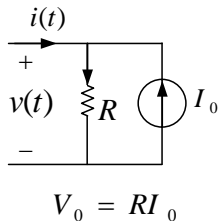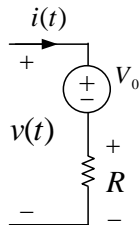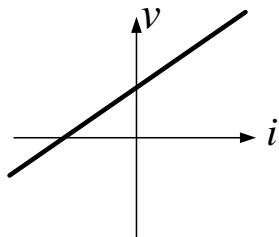
## Example (Battery)

A battery can be modeled as a series connection of a resistor and a voltage source.



$$v(t) = V_0 + V_R(t) = V_0 + Ri(t)$$

$$i(t) = -I_0 + i_R(t) = -\frac{V_0}{R} + \frac{v(t)}{R}$$

## Example (Time-variant resistor)



A time-variant resistor can create new frequencies from an input single-frequency tone signal.

$$i_s(t) = I \sin(2\pi f_1 t)$$

$$R = 1 \Rightarrow v(t) = I \sin(2\pi f_1 t)$$


$$R(t) = 1 + 2 \cos(2\pi f_2 t) \Rightarrow$$
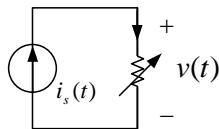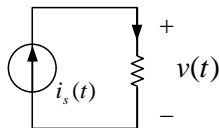
$$v(t) = I \sin(2\pi f_1 t) + I \sin(2\pi(f_1 + f_2)t) + I \sin(2\pi(f_1 - f_2)t)$$


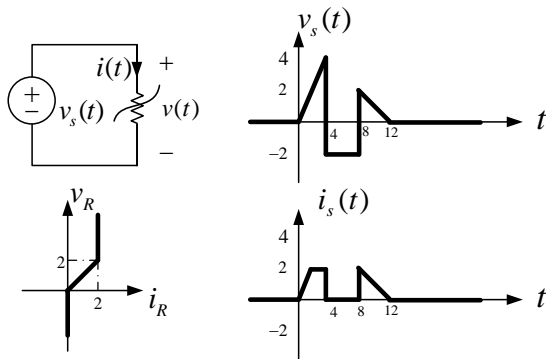
## Example (Nonlinear resistor)




The characteristic curve of a nonlinear resistor can be used to draw its voltage or current.





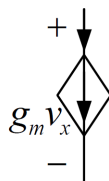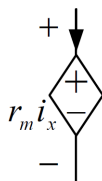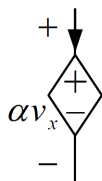
## Example (Dependent sources)

Linear dependent sources can be usually considered as NTV resistors.


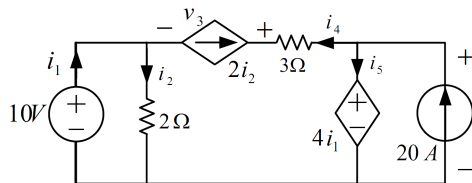
## Example (Circuit with dependent sources)

Tellegen's theorem can be verified for the circuit below.



$$i_6 = 20, i_2 = \frac{10}{2} = 5, i_3 = 2i_2 = 10, i_4 = -i_3 = -10, i_1 = i_2 - i_4 = 15, i_5 = 20 - i_4 = 30$$

$$v_1 = 10, v_2 = 10, v_4 = 3i_4 = -30, v_5 = 4i_1 = 60, v_6 = v_5 = 60, v_3 = -v_4 + v_5 - v_2 = 80$$

$$p_1 = -10i_1 = -150, p_2 = v_2i_2 = 50, p_3 = -v_3i_3 = -800$$

$$p_4 = v_4i_4 = 300, p_5 = v_5i_5 = 1800, p_6 = -v_6i_6 = -1200$$

$$p_1 + p_2 + p_3 + p_4 + p_5 + p_6 = 0$$

## Example (Small-signal analysis)


Circuits with nonlinear resistors can be investigated using small-signal analysis.

$$i = f(v)$$

$$i(t) = f(V_0 + v_s(t)), |v_s(t)| \ll |V_0|$$

$$i(t) \approx f(V_0) + \left. \frac{df}{dv} \right|_{v=V_0} v_s(t)$$

$$i(t) \approx I_0 + g v_s(t)$$

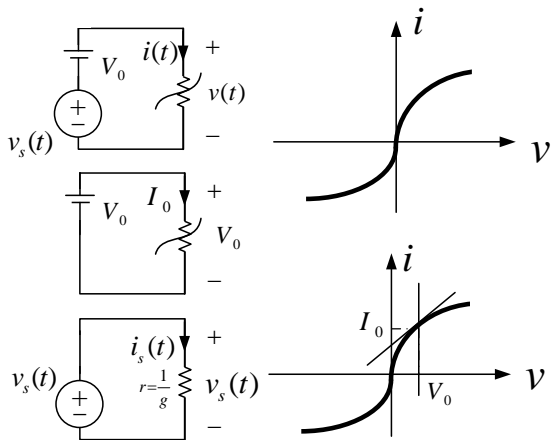

# Capacitor

# Capacitor

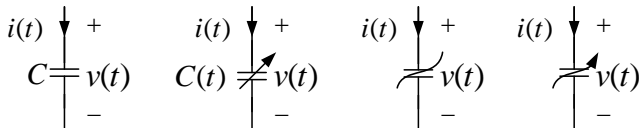


Figure: LTI, LTV, NTI, NTV capacitors. The units of charge, voltage, capacitance, and elastance are  $C$ ,  $V$ ,  $F$ ,  $F^{-1}$ .

- 1 **Linear time-invariant capacitor:**  $q(t) = Cv(t) \equiv v(t) = Sq(t)$
- 2 **Linear time-variant capacitor:**  $q(t) = C(t)v(t) \equiv v(t) = S(t)q(t)$
- 3 **Nonlinear time-invariant capacitor:**  $f(q(t), v(t)) = 0$
- 4 **Nonlinear time-variant capacitor:**  $f(q(t), v(t), t) = 0$
- 5 **Voltage-controlled capacitor:**  $q(t) = f(v(t), t)$
- 6 **Charge-controlled capacitor:**  $v(t) = f(q(t), t)$
- 7 **Bilateral capacitor:**  $f(q(t), v(t)) = f(-q(t), -v(t))$

# Capacitor

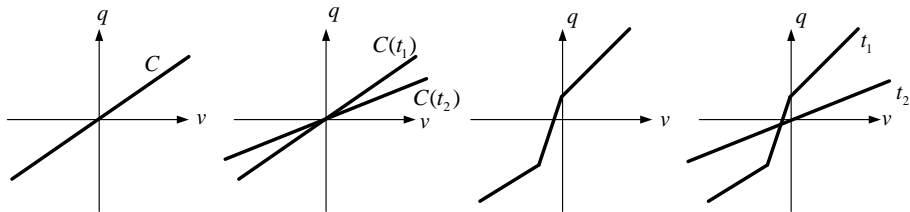


Figure: LTI, LTV, NTV **capacitors**. The units of charge, voltage, capacitance, and elastance are  $C$ ,  $V$ ,  $F$ ,  $F^{-1}$ .

- 1 **Linear time-invariant capacitor:**  $q(t) = Cv(t) \equiv v(t) = Sq(t)$
- 2 **Linear time-variant capacitor:**  $q(t) = C(t)v(t) \equiv v(t) = S(t)q(t)$
- 3 **Nonlinear time-invariant capacitor:**  $f(q(t), v(t)) = 0$
- 4 **Nonlinear time-variant capacitor:**  $f(q(t), v(t), t) = 0$
- 5 **Voltage-controlled capacitor:**  $q(t) = f(v(t), t)$
- 6 **Charge-controlled capacitor:**  $v(t) = f(q(t), t)$
- 7 **Bilateral capacitor:**  $f(q(t), v(t)) = f(-q(t), -v(t))$

# Capacitor

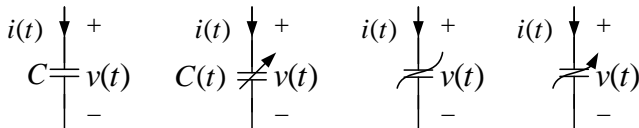


Figure: LTI, LTV, NTI, NTV capacitors. The units of charge, voltage, capacitance, and elastance are  $C$ ,  $V$ ,  $F$ ,  $F^{-1}$ .

## 1 Linear time-invariant capacitor:

- **Current** equation:  $i(t) = \frac{dq(t)}{dt} = C \frac{dv(t)}{dt}$ ,  $v(t_0)$
- **Voltage** equation:  $v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i(\lambda) d\lambda$
- Full description by **capacitance  $C$**  and **initial voltage  $v(t_0)$**
- **Memory** element
- **Linearity of current** in terms of voltage
- **Continuity of voltage** for bounded current




## 2 Linear time-variant capacitor: $i(t) = C(t) \frac{dv(t)}{dt} + v(t) \frac{dC(t)}{dt}$ , $v(t_0), C(t_0)$

## 3 Voltage-controlled capacitor: $i(t) = \frac{\partial f}{\partial v} \frac{dv(t)}{dt} + \frac{\partial f}{\partial t}$

# Capacitor
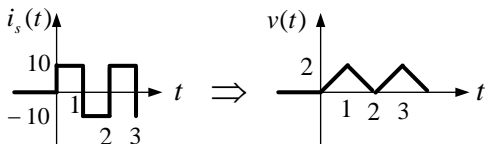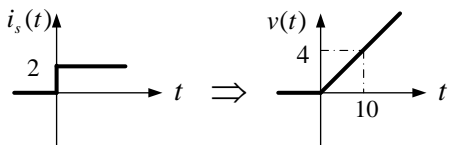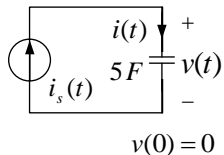
## Example (LTI capacitor)

A capacitor integrates its flowing current.









# Capacitor
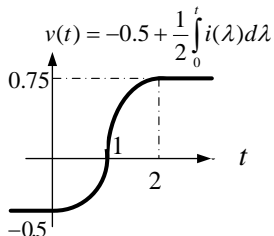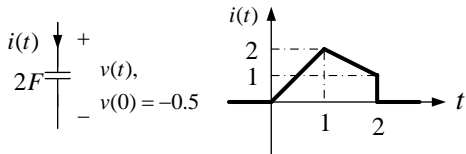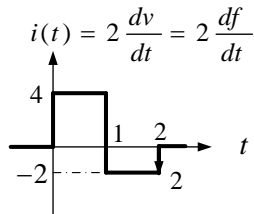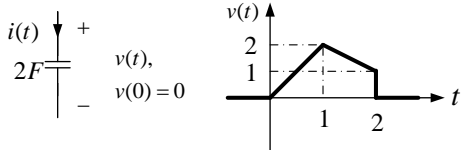
## Example (LTI capacitor)


The capacitor voltage remains continuous for the bounded flowing current.



# Capacitor

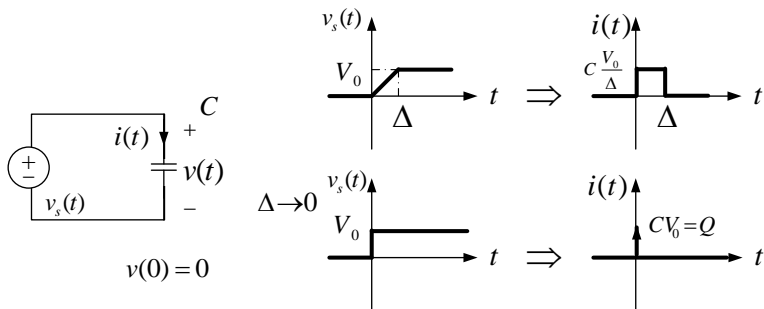
## Example (LTI capacitor)

The capacitor voltage experiences discontinuity for the unbounded flowing current.


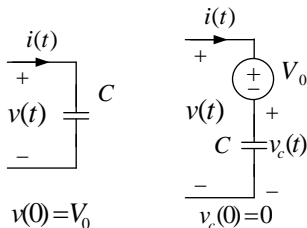
## Example (Initial condition modeling)


The initial voltage can be modeled using an independent voltage source.



$$v(t) = v(0) + \frac{1}{C} \int_0^t i(\lambda) d\lambda = V_0 + \frac{1}{C} \int_0^t i(\lambda) d\lambda$$
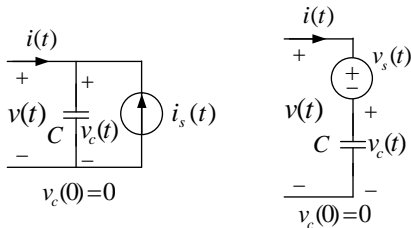
## Example (Thevenin-Norton Equivalency)

The two circuits below are equivalent if  $i_s(t) = C \frac{dv_s(t)}{dt} \equiv v_s(t) = \frac{1}{C} \int_0^t i_s(\lambda) d\lambda$  and  $v_C(0) = 0$



$$v(t) = v_s(t) + \frac{1}{C} \int_0^t i_s(\lambda) d\lambda$$

$$i(t) = -i_s(t) + C \frac{dv(t)}{dt}$$

# Inductor

# Inductor

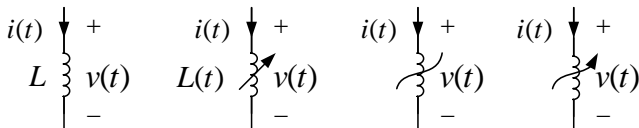


Figure: LTI, LTV, NTI, NTV **inductors**. The units of flux, current, inductance, and reciprocal inductance are  $Wb$ ,  $A$ ,  $H$ ,  $H^{-1}$ .

- 1 **Linear time-invariant inductor:**  $\phi(t) = Li(t) \equiv i(t) = \Gamma\phi(t)$
- 2 **Linear time-variant inductor:**  $\phi(t) = L(t)i(t) \equiv i(t) = \Gamma(t)\phi(t)$
- 3 **Nonlinear time-invariant inductor:**  $f(\phi(t), i(t)) = 0$
- 4 **Nonlinear time-variant inductor:**  $f(\phi(t), i(t), t) = 0$
- 5 **Current-controlled inductor:**  $\phi(t) = f(i(t), t)$
- 6 **Flux-controlled inductor:**  $i(t) = f(\phi(t), t)$
- 7 **Bilateral inductor:**  $f(\phi(t), i(t)) = f(-\phi(t), -i(t))$

# Inductor

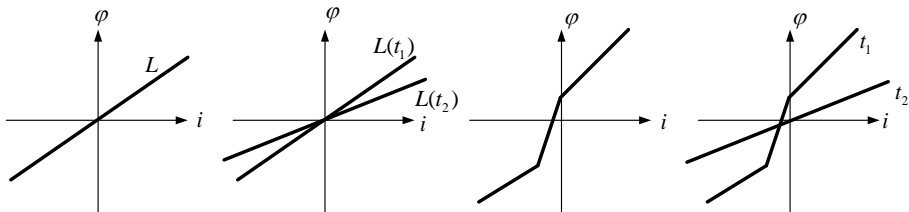


Figure: LTI, LTV, NTI, NTV inductors. The units of flux, current, inductance, and reciprocal inductance are  $\text{Wb}$ ,  $\text{A}$ ,  $\text{H}$ ,  $\text{H}^{-1}$ .

- 1 **Linear time-invariant inductor:**  $\phi(t) = Li(t) \equiv i(t) = \Gamma\phi(t)$
- 2 **Linear time-variant inductor:**  $\phi(t) = L(t)i(t) \equiv i(t) = \Gamma(t)\phi(t)$
- 3 **Nonlinear time-invariant inductor:**  $f(\phi(t), i(t)) = 0$
- 4 **Nonlinear time-variant inductor:**  $f(\phi(t), i(t), t) = 0$
- 5 **Current-controlled inductor:**  $\phi(t) = f(i(t), t)$
- 6 **Flux-controlled inductor:**  $i(t) = f(\phi(t), t)$
- 7 **Bilateral inductor:**  $f(\phi(t), i(t)) = f(-\phi(t), -i(t))$

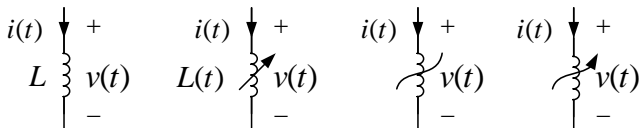


Figure: LTI, LTV, NTI, NTV inductors. The units of flux, current, inductance, and reciprocal inductance are  $Wb$ ,  $A$ ,  $H$ ,  $H^{-1}$ .

## 1 Linear time-invariant inductor:

- **Voltage** equation:  $v(t) = \frac{d\phi(t)}{dt} = L \frac{di(t)}{dt}$ ,  $i(t_0)$
- **Current** equation:  $i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v(\lambda) d\lambda$
- Full description by **inductance**  $L$  and **initial current**  $i(t_0)$
- **Memory** element
- **Linearity of voltage** in terms of current
- **Continuity of current** for bounded voltage


## 2 Linear time-variant inductor: $v(t) = L(t) \frac{di(t)}{dt} + i(t) \frac{dL(t)}{dt}$ , $i(t_0), L(t_0)$

## 3 Current-controlled inductor: $i(t) = \frac{\partial f}{\partial i} \frac{di(t)}{dt} + \frac{\partial f}{\partial t}$



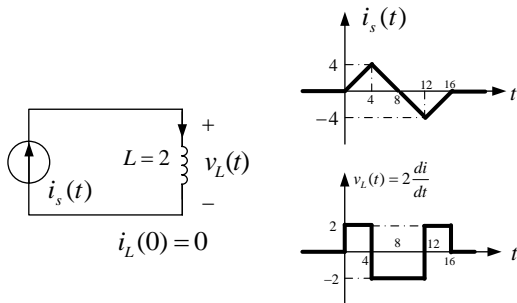
## Example (LTI inductor)

An inductor differentiates its flowing current.



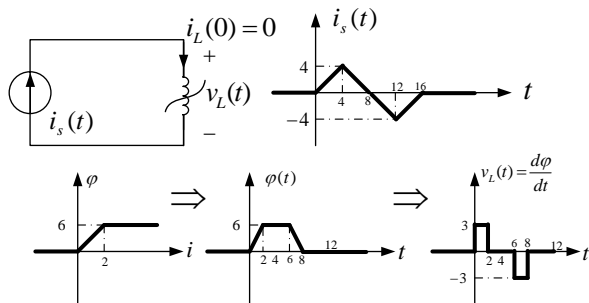
## Example (NTI inductor)

An NTI inductor can be described by its characteristic curve.


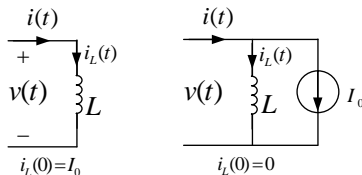
## Example (Initial condition modeling)


The initial current can be modeled using an independent current source.



$$i(t) = i(0) + \frac{1}{L} \int_0^t v(\lambda) d\lambda = I_0 + \frac{1}{L} \int_0^t v(\lambda) d\lambda$$
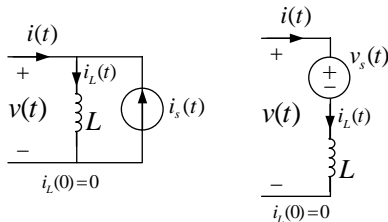
## Example (Thevenin-Norton Equivalency)

The two circuits below are equivalent if  $v_s(t) = L \frac{di_s(t)}{dt} \equiv i_s(t) = \frac{1}{L} \int_0^t v_s(\lambda) d\lambda$  and  $i_L(0) = 0$





$$i(t) = -i_s(t) + \frac{1}{L} \int_0^t v(\lambda) d\lambda$$

$$v(t) = v_s(t) + L \frac{di(t)}{dt}$$

# Inductor

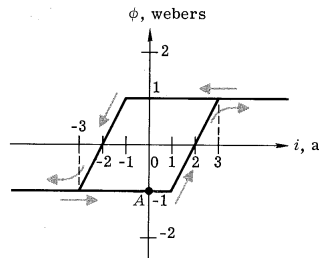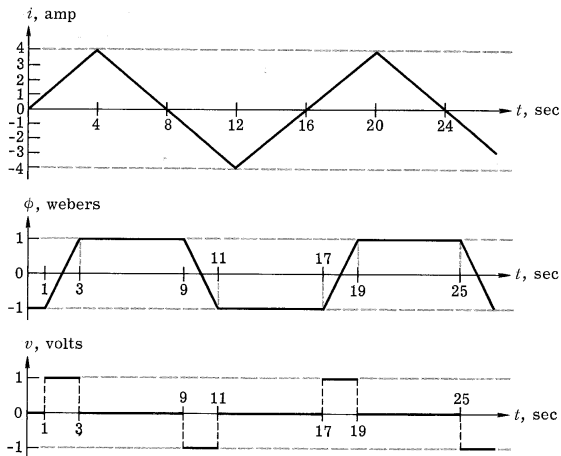
## Example (Hysteresis)

An inductor with hysteresis characteristic is an NTI inductor.


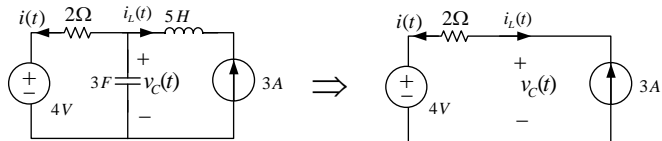
## Example (DC steady state)

If a DC driven inductor (capacitor) reaches its steady state situation, it acts like a short (open) circuit.



# Memristor

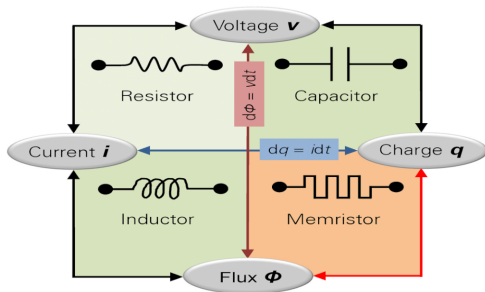


Figure: Basic one-port circuit elements.

- **Nonlinear time-variant memristor:**  $f(q(t), \phi(t), t) = 0$



# Power and Energy

# Power and Energy

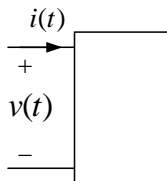


Figure: A general **one-port** element with **passive sign convention**.

- 1 **Absorbed power:**  $p(t) = v(t)i(t) = \frac{d\epsilon(t)}{dt}$
- 2 **Absorbed energy:**  $w(t_0, t) = \epsilon(t) - \epsilon(t_0) = \int_{t_0}^t p(\lambda)d\lambda$
- 3 **Absolute energy:**  $\epsilon(t) = \epsilon(t_0) + w(t_0, t)$

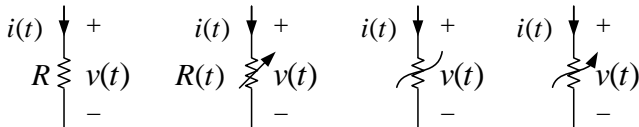


Figure: LTI, LTV, NTI, NTV resistors. Resistors dissipate power.

- ① **LTI resistor absorbed energy:**  $w(t_0, t) = \int_{t_0}^t v(\lambda)i(\lambda)d\lambda = R \int_{t_0}^t i^2(\lambda)d\lambda$
- ② **LTI resistor passivity condition:**  $w(t_0, t) = R \int_{t_0}^t i^2(\lambda)d\lambda \geq 0 \Rightarrow R \geq 0$
- ③ **LTV resistor passivity condition:**  $R(t) \geq 0, \forall t$
- ④ **NTV resistor passivity condition:**  
 $w(t_0, t) = \int_{t_0}^t p(\lambda)d\lambda \geq 0 \Rightarrow p(t) = v(t)i(t) \geq 0, \forall t$

# Capacitor

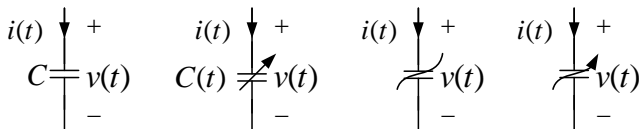


Figure: LTI, LTV, NTI, NTV capacitors. Capacitors store electrical energy.

- 1 **LTI capacitor absorbed energy:**  $w(t_0, t) = \int_{t_0}^t v(\lambda)i(\lambda)d\lambda = \int_{t_0}^t v(\lambda)C \frac{dv(\lambda)}{d\lambda} d\lambda = C \int_{v(t_0)}^{v(t)} u du = \frac{C}{2}(v^2(t) - v^2(t_0))$
- 2 **LTI capacitor absolute energy:**  $\epsilon_E(t) = \frac{C}{2}v^2(t) = \frac{1}{2C}q^2(t)$
- 3 **LTI capacitor passivity condition:**  $\epsilon_E(t) = \frac{C}{2}v^2(t) \geq 0 \Rightarrow C \geq 0$
- 4 **LTV capacitor passivity condition:**  $C(t), C'(t) \geq 0, \forall t$
- 5 **NTI capacitor passivity condition:**  $q(t)v(t) \geq 0, \forall t$

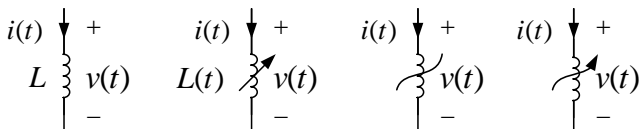


Figure: LTI, LTV, NTI, NTV inductors. Inductors store magnetic energy.

① LTI inductor absorbed energy:

$$w(t_0, t) = \int_{t_0}^t v(\lambda) i(\lambda) d\lambda = \int_{t_0}^t L \frac{di(\lambda)}{d\lambda} i(\lambda) d\lambda = L \int_{i(t_0)}^{i(t)} u du = \frac{L}{2} (i^2(t) - i^2(t_0))$$

② LTI inductor absolute energy:  $\epsilon_M(t) = \frac{L}{2} i^2(t) = \frac{1}{2L} \phi^2(t)$

③ LTI inductor passivity condition:  $\epsilon_M(t) = \frac{L}{2} i^2(t) \geq 0 \Rightarrow L \geq 0$

④ LTV inductor passivity condition:  $L(t), L'(t) \geq 0, \forall t$

⑤ NTI inductor passivity condition:  $\phi(t) i(t) \geq 0, \forall t$

## Example (Activity)

A DC voltage source with the voltage  $V_0$  is active since  $p(t) = v(t)i(t) = V_0(-V_0) = -V_0^2 < 0$ .

## Example (Passivity)

The NTV resistor with the characteristic curve  $i(t) = 2(v(t))^3$  is passive since  $p(t) = v(t)i(t) = 2(v(t))^4 \geq 0$ .




## Example (Activity)

The LTV resistor with the resistance  $R(t) = -(2t+1)$  is active since  $R(0) = -1 < 0$ .

# Power and Energy
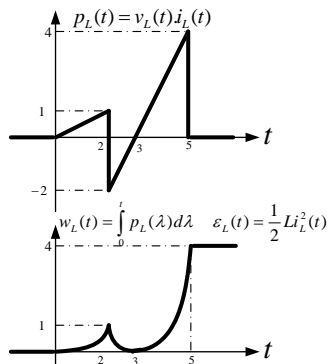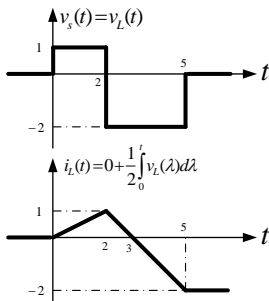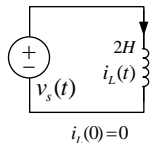
## Example (Power and Energy)


The energy and power curves for the shown inductor are plotted as below.



# Power and Energy
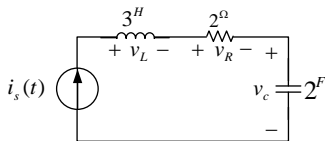
## Example (Power and Energy)

For the circuit below,  $i(t) = 3t$ ,  $t > 0$ ,  $v_C(0) = 3$ , and  $i_L(0) = 0$ .  $w_R(0, 1) = 6$ ,  $p_L(2) = 54$ , and  $\epsilon_C(4) = 225$ .



$$w_R(0, 1) = 2 \int_0^1 (3\lambda)^2 d\lambda = 6$$

$$i_L(2) = 6, v_L(2) = 3i_L'(2) = 9 \Rightarrow p_L(2) = v_L(2)i_L(2) = 54$$

$$v_C(4) = 3 + \frac{1}{2} \int_0^4 3\lambda d\lambda = 15 \Rightarrow \epsilon_C(4) = \frac{1}{2}(2)v_C^2(4) = 225$$



# Elements Interconnections

# Equivalent One-ports

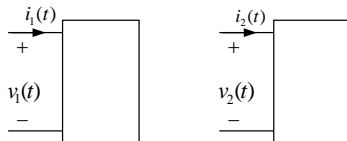


Figure: A same equation governs ports of two equivalent one-ports.

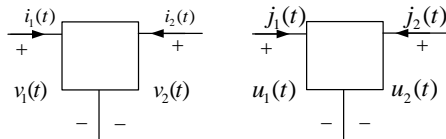


Figure: Same equations govern ports of two equivalent two-ports.

# Resistors

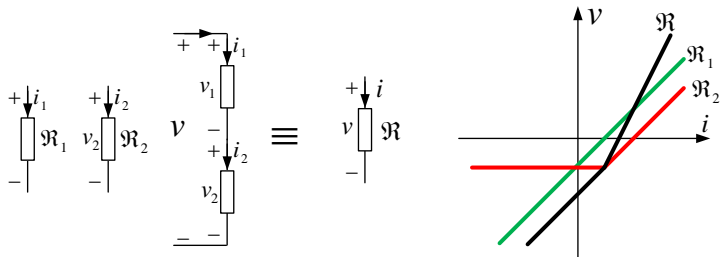


Figure: Two **series resistors** with  $i = i_1 = i_2$  and  $v = v_1 + v_2$ . Series connection of two current-controlled resistors has the characteristic curve  $v = v_1 + v_2 = f_1(i_1) + f_2(i_2) = f(i)$ .

# Resistors


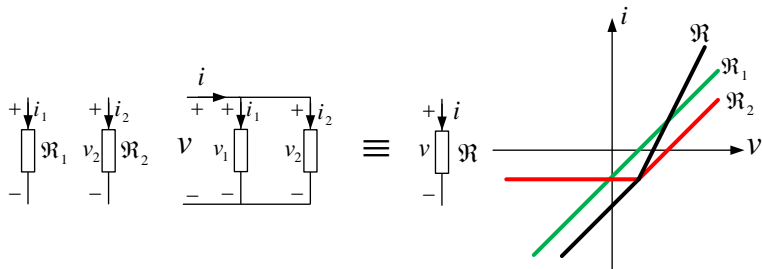


Figure: Two parallel resistors with  $v = v_1 = v_2$  and  $i = i_1 + i_2$ . Parallel connection of two voltage-controlled resistors has the characteristic curve  $i = i_1 + i_2 = f_1(v_1) + f_2(v_2) = f(v)$ .
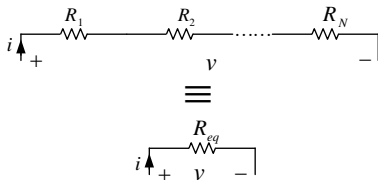
## Example (Series connection of LTI resistors)


If the LTI resistors  $R_1, R_2, \dots, R_N$  are connected in series, they can be replaced with the equivalent LTI resistor  $R_{eq} = \sum_{k=1}^N R_k$ .



$$v = \sum_{k=1}^N v_k = \sum_{k=1}^N R_k i_k = i \sum_{k=1}^N R_k = R_{eq} i$$
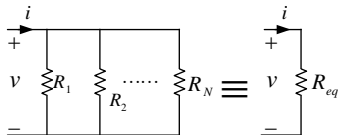
## Example (Parallel connection of LTI resistors)


If the LTI resistors  $G_1, G_2, \dots, G_N$  are connected in parallel, they can be replaced with the equivalent LTI resistor  $G_{eq} = \sum_{k=1}^N G_k$ .



$$i = \sum_{k=1}^N i_k = \sum_{k=1}^N G_k v_k = v \sum_{k=1}^N G_k = G_{eq} i$$
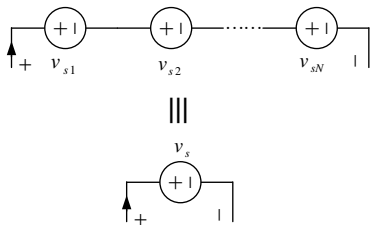
## Example (Series connection of voltage sources)


If the voltage sources  $v_{s1}$ ,  $v_{s2}$ , ...,  $v_{sN}$  are connected in series, they can be replaced with the equivalent voltage source  $v_s = \sum_{k=1}^N v_{sk}$ .



$$v_s = \sum_{k=1}^N v_{sk}$$
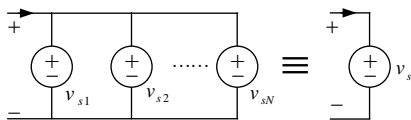
## Example (Parallel connection of voltage sources)

The parallel connection of the voltage sources  $v_{s1}$ ,  $v_{s2}$ , ...,  $v_{sN}$  is possible if  $v_{s1} = v_{s2} = \dots = v_{sN}$ .




$$v_s = v_{s1} = v_{s2} = \dots = v_{sN}$$


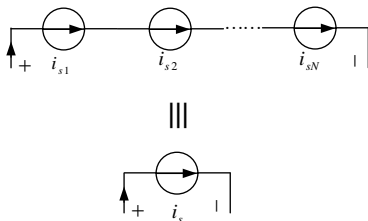
## Example (Series connection of current sources)


The series connection of the current sources  $i_{s1}$ ,  $i_{s2}$ , ...,  $i_{sN}$  is possible if  $i_{s1} = i_{s2} = \dots = i_{sN}$ .



$$i_s = i_{s1} = i_{s2} = \dots = i_{sN}$$
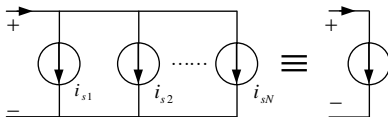
## Example (Parallel connection of current sources)


If the current sources  $i_{s1}$ ,  $i_{s2}$ , ...,  $i_{sN}$  are connected in parallel, they can be replaced with the equivalent current source  $i_s = \sum_{k=1}^N i_{sk}$ .



$$i_s = \sum_{k=1}^N i_{sk}$$



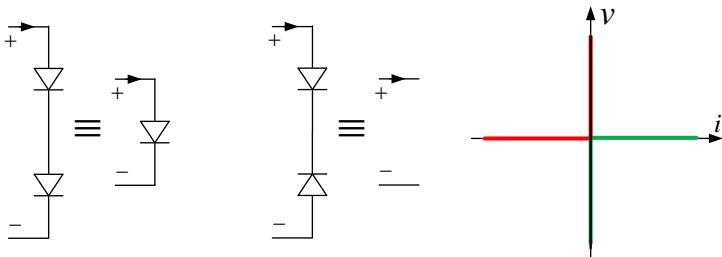
## Example (Series connection of diodes)

Series connection of two ideal diodes results in an equivalent ideal diode or open circuit.


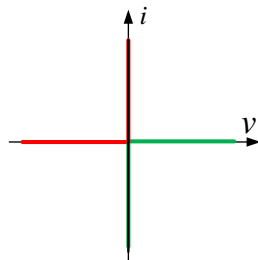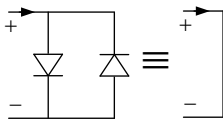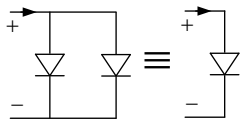
## Example (Parallel connection of diodes)


Parallel connection of two ideal diodes results in an equivalent ideal diode or short circuit.



# Resistors

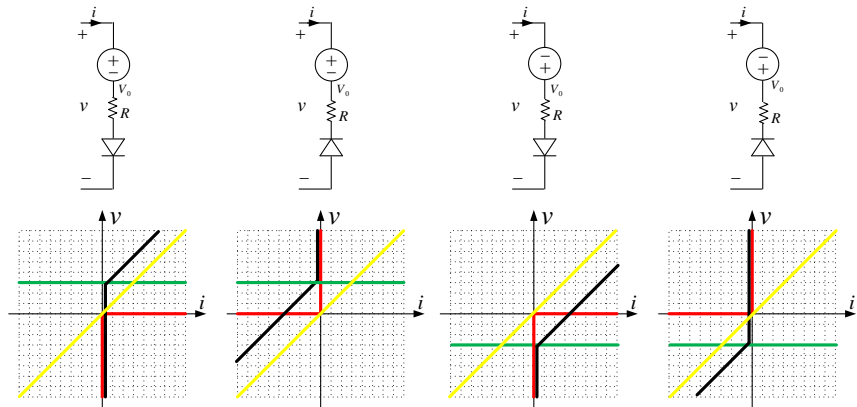
## Example (Series connection of several elements)

The direction of elements is important in elements interconnection.




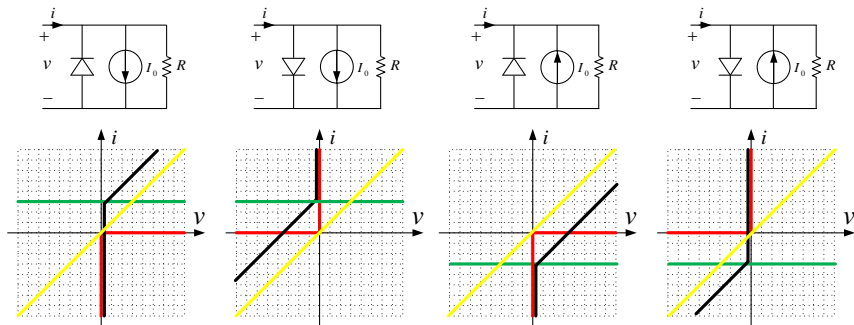
## Example (Parallel connection of several elements)

The direction of elements is important in elements interconnection.



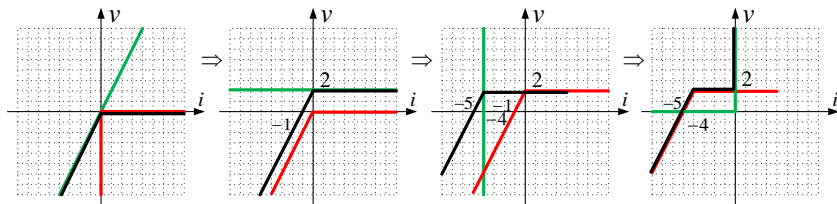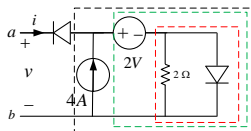
## Example (Interconnection of several elements)

Interconnection of various elements leads to interesting characteristic curves.


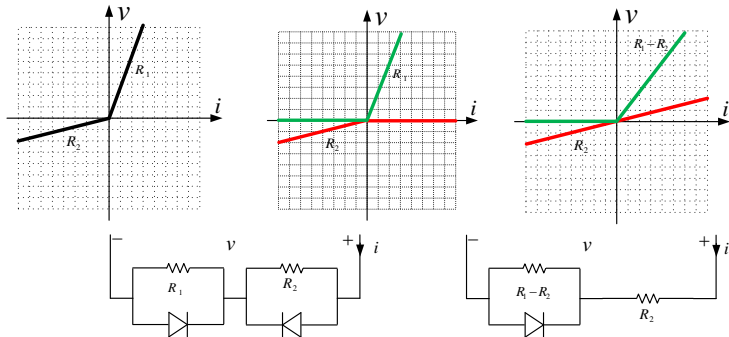
## Example (Circuit Synthesis)






A desired circuit can be synthesized in different ways.





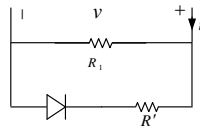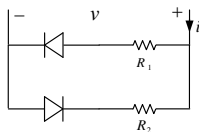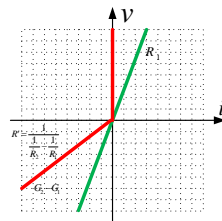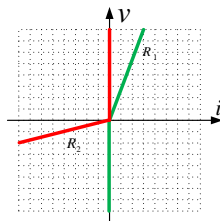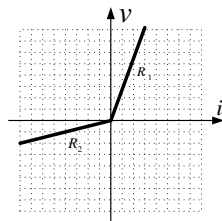
## Example (Circuit Synthesis)

A desired circuit can be synthesized in different ways.



## Example (Rectifier)

Diodes can be used for rectification.

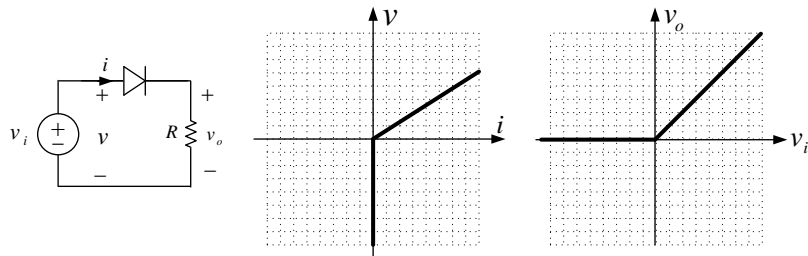

$$v_o = v_i u(v_i)$$

# Resistors

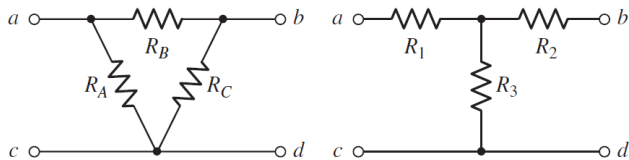


Figure: Resistive  $\Delta$  (triangle,  $\Pi$ ) and  $Y$  (star,  $T$ ) networks. If the two networks are **equivalent**, then the port voltages and currents must be equal.

$$R_A = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2}$$

$$R_B = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_3}$$

$$R_C = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1}$$

$$R_1 = \frac{R_A R_B}{R_A + R_B + R_C}$$

$$R_2 = \frac{R_B R_C}{R_A + R_B + R_C}$$

$$R_3 = \frac{R_C R_A}{R_A + R_B + R_C}$$

# Capacitors

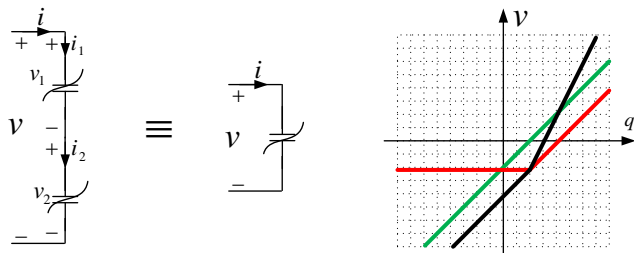


Figure: Two **series NTC capacitors** with  $i = i_1 = i_2$  and  $v = v_1 + v_2$ . Series connection of two charge-controlled capacitors has the characteristic curve  $v = v_1 + v_2 = f_1(q_1) + f_2(q_2) = f(q)$  provided that  $q_1(0) = q_2(0)$ .

$$i = i_1 = i_2 \Rightarrow \frac{dq}{dt} = \frac{dq_1}{dt} = \frac{dq_2}{dt} \Rightarrow q(t) - q(0) = q_1(t) - q_1(0) = q_2(t) - q_2(0)$$

$$q(0) = q_1(0) = q_2(0) \Rightarrow q(t) = q_1(t) = q_2(t)$$

# Capacitors


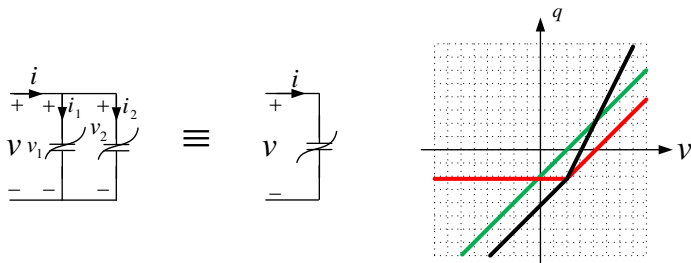


Figure: Two parallel NTC capacitors with  $v = v_1 = v_2$  and  $i = i_1 + i_2$ . Parallel connection of two voltage-controlled capacitors has the characteristic curve  $q = q_1 + q_2 = f_1(v_1) + f_2(v_2) = f(v)$ .

$$i = i_1 + i_2 \Rightarrow \frac{dq}{dt} = \frac{dq_1}{dt} + \frac{dq_2}{dt} \Rightarrow q(t) - q(0) = q_1(t) - q_1(0) + q_2(t) - q_2(0)$$
$$q(0) = q_1(0) + q_2(0) \Rightarrow q(t) = q_1(t) + q_2(t)$$
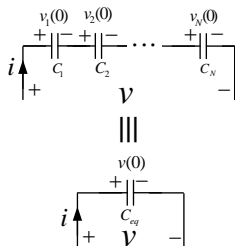
## Example (Series connection of LTI capacitors)


If the LTI capacitors  $S_1, S_2, \dots, S_N$  with the initial voltages  $v_1(0), v_2(0), \dots, v_N(0)$  are connected in series, they can be replaced with the equivalent LTI capacitor  $S_{eq} = \sum_{k=1}^N S_k$  with the initial voltage  $v(0) = \sum_{k=1}^N v_k(0)$ .



$$v = \sum_{k=1}^N v_k = \sum_{k=1}^N [v_k(0) + S_k \int_0^t i_k(\lambda) d\lambda] = \sum_{k=1}^N v_k(0) + \left( \sum_{k=1}^N S_k \right) \int_0^t i(\lambda) d\lambda$$
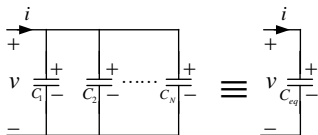
## Example (Parallel connection of LTI capacitors)


If the LTI capacitors  $C_1, C_2, \dots, C_N$  with the initial voltages  $v_1(0^-), v_2(0^-), \dots, v_N(0^-)$  are connected in parallel, they can be replaced with the equivalent LTI capacitor  $C_{eq} = \sum_{k=1}^N C_k$  with a suitable initial voltage  $v(0^+) = v_1(0^+) = \dots = v_N(0^+)$ .



$$i = \sum_{k=1}^N i_k = \sum_{k=1}^N C_k \frac{dv_k}{dt} = \left( \sum_{k=1}^N C_k \right) \frac{dv}{dt}$$
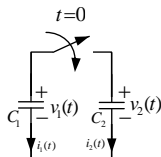
## Example (Initial voltage of two parallel LTI capacitors)

If the LTI capacitors  $C_1$  and  $C_2$  with the initial voltages  $v_1(0^-)$  and  $v_2(0^-)$  are connected in parallel, they can be replaced with the equivalent LTI capacitor  $C_{eq} = C_1 + C_2$  with having the initial voltage  $v(0^+) = \frac{C_1 v_1(0^-) + C_2 v_2(0^-)}{C_1 + C_2}$ .




$$q(0^-) = q(0^+) \Rightarrow C_1 v_1(0^-) + C_2 v_2(0^-) = C_1 v_1(0^+) + C_2 v_2(0^+) = (C_1 + C_2)v(0^+)$$


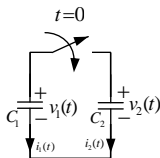
## Example (Initial voltage of two parallel LTI capacitors)


If the LTI capacitors  $C_1$  and  $C_2$  with the initial voltages  $v_1(0^-)$  and  $v_2(0^-)$  are connected in parallel, they can be replaced with the equivalent LTI capacitor  $C_{eq} = C_1 + C_2$  with having the initial voltage  $v(0^+) = \frac{C_1 v_1(0^-) + C_2 v_2(0^-)}{C_1 + C_2}$ .



$$i_1(t) + i_2(t) = C_1 \frac{dv_1}{dt} + C_2 \frac{dv_2}{dt} = 0 \Rightarrow \int_{0^-}^{0^+} [C_1 \frac{dv_1}{dt} + C_2 \frac{dv_2}{dt}] dt = 0 \Rightarrow C_1 \int_{v_1(0^-)}^{v_1(0^+)} dv_1 + C_2 \int_{v_2(0^-)}^{v_2(0^+)} dv_2 = 0$$

$$C_1[v_1(0^+) - v_1(0^-)] + C_2[v_2(0^+) - v_2(0^-)] = 0 \Rightarrow C_1 v_1(0^-) + C_2 v_2(0^-) = (C_1 + C_2)v(0^+)$$


# Inductors

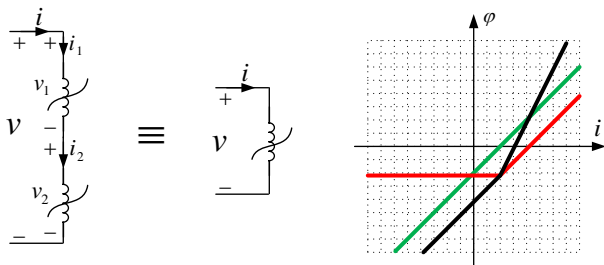

**Figure:** Two **series NLI inductors** with  $i = i_1 = i_2$  and  $v = v_1 + v_2$ . Series connection of two current-controlled inductors has the characteristic curve  $\phi = \phi_1 + \phi_2 = f_1(i_1) + f_2(i_2) = f(i)$ .

$$v = v_1 + v_2 \Rightarrow \frac{d\phi}{dt} = \frac{d\phi_1}{dt} + \frac{d\phi_2}{dt} \Rightarrow \phi(t) - \phi(0) = \phi_1(t) - \phi_1(0) + \phi_2(t) - \phi_2(0)$$
$$\phi(0) = \phi_1(0) + \phi_2(0) \Rightarrow \phi(t) = \phi_1(t) + \phi_2(t)$$

# Inductors

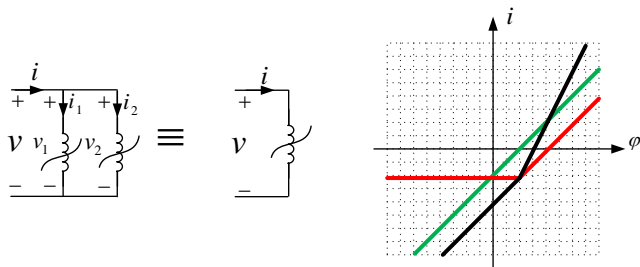


**Figure:** Two **parallel NTI inductors** with  $v = v_1 = v_2$  and  $i = i_1 + i_2$ . Parallel connection of two flux-controlled inductors has the characteristic curve  $i = i_1 + i_2 = f_1(\phi_1) + f_2(\phi_2) = f(\phi)$  provided that  $\phi_1(0) = \phi_2(0)$ .
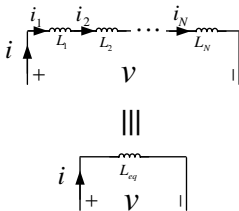
$$v = v_1 = v_2 \Rightarrow \frac{d\phi}{dt} = \frac{d\phi_1}{dt} = \frac{d\phi_2}{dt} \Rightarrow \phi(t) - \phi(0) = \phi_1(t) - \phi_1(0) = \phi_2(t) - \phi_2(0)$$
$$\phi(0) = \phi_1(0) = \phi_2(0) \Rightarrow \phi(t) = \phi_1(t) = \phi_2(t)$$

## Example (Series connection of LTI inductors)


If the LTI inductors  $L_1, L_2, \dots, L_N$  with the initial currents  $i_1(0^-), i_2(0^-), \dots, i_N(0^-)$  are connected in series, they can be replaced with the equivalent LTI inductor  $L_{eq} = \sum_{k=1}^N L_k$  with a suitable initial current  $i(0^+) = i_1(0^+) = \dots = i_N(0^+)$ .



$$v = \sum_{k=1}^N v_k = \sum_{k=1}^N L_k \frac{di_k}{dt} = \left( \sum_{k=1}^N L_k \right) \frac{di}{dt}$$
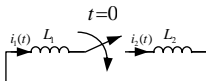
## Example (Initial current of two series LTI inductors)


If the LTI inductors  $L_1$  and  $L_2$  with the initial currents  $i_1(0^-)$  and  $i_2(0^-)$  are connected in series, they can be replaced with the equivalent LTI inductor  $L_{eq} = L_1 + L_2$  with having the initial current  $i(0^+) = \frac{L_1 i_1(0^-) + L_2 i_2(0^-)}{L_1 + L_2}$ .



$$\phi(0^-) = \phi(0^+) \Rightarrow L_1 i_1(0^-) + L_2 i_2(0^-) = L_1 i_1(0^+) + L_2 i_2(0^+) = (L_1 + L_2) i(0^+)$$
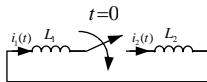
## Example (Initial current of two series LTI inductors)

If the LTI inductors  $L_1$  and  $L_2$  with the initial currents  $i_1(0^-)$  and  $i_2(0^-)$  are connected in series, they can be replaced with the equivalent LTI inductor  $L_{eq} = L_1 + L_2$  with having the initial current  $i(0^+) = \frac{L_1 i_1(0^-) + L_2 i_2(0^-)}{L_1 + L_2}$ .




$$v_1(t) + v_2(t) = L_1 \frac{di_1}{dt} + L_2 \frac{di_2}{dt} = 0 \Rightarrow \int_{0^-}^{0^+} [L_1 \frac{di_1}{dt} + L_2 \frac{di_2}{dt}] dt = 0 \Rightarrow L_1 \int_{i_1(0^-)}^{i_1(0^+)} di_1 + L_2 \int_{i_2(0^-)}^{i_2(0^+)} di_2 = 0$$

$$L_1 [i_1(0^+) - i_1(0^-)] + L_2 [i_2(0^+) - i_2(0^-)] = 0 \Rightarrow L_1 i_1(0^-) + L_2 i_2(0^-) = (L_1 + L_2) i(0^+)$$
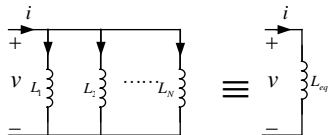
## Example (Parallel connection of LTI inductors)

If the LTI inductors  $\Gamma_1, \Gamma_2, \dots, \Gamma_N$  with the initial currents  $i_1(0), i_2(0), \dots, i_N(0)$  are connected in parallel, they can be replaced with the equivalent LTI inductor  $\Gamma_{eq} = \sum_{k=1}^N \Gamma_k$  with the initial current  $i(0) = \sum_{k=1}^N i_k(0)$ .



$$i = \sum_{k=1}^N i_k = \sum_{k=1}^N \left[ i_k(0) + \Gamma_k \int_0^t v_k(\lambda) d\lambda \right] = \sum_{k=1}^N i_k(0) + \left( \sum_{k=1}^N \Gamma_k \right) \int_0^t v(\lambda) d\lambda$$

# The End