

Question 1

For the circuit shown in Fig. 1,

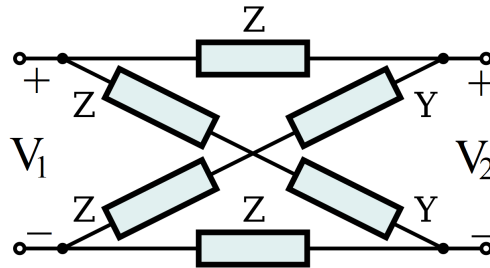


Figure 1: Lattice network.

(a) Find the network function $H(j\omega) = \frac{V_2(j\omega)}{V_1(j\omega)}$, where $Z(j\omega)$ and $Y(j\omega)$ denote impedance and admittance of the diagonal single-port passive networks.

(b) Let $Z(j\omega) = j\omega + \frac{1}{j\omega}$ and $Y(j\omega) = j\omega + \frac{1}{j\omega}$ be a series and a parallel LC network, respectively. Find the simplified transfer function $H(j\omega) = \frac{V_2(j\omega)}{V_1(j\omega)}$ and the corresponding amplitude and phase responses.

(c) Plot the amplitude and phase response of $H(j\omega)$ calculated in part (b).

Question 2

Calculate the Thevenin and Norton equivalent circuits seen from port ab in Fig. 2,

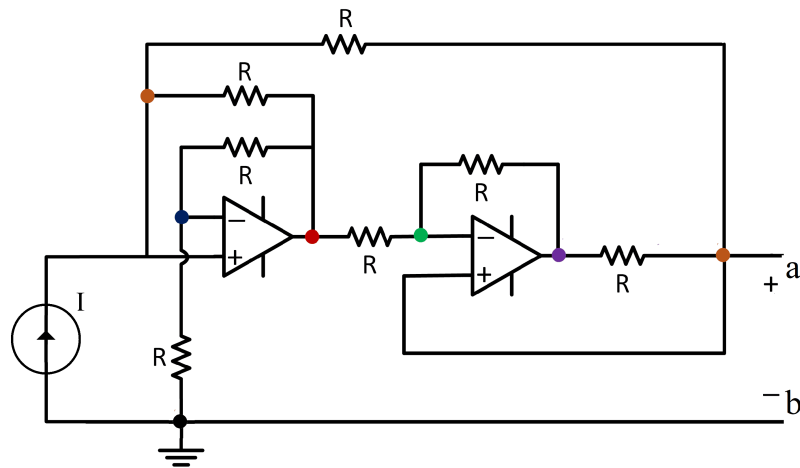


Figure 2: An op-amp circuit.

Question 3

The zero-state response of an LTI circuit to the input $x(t) = (e^{-t} - \cos(t) + \sin(t))u(t)$ is $y(t) = 2 \sin(t)u(t)$. Find the impulse response, step response, and zero-state response to the input $x_1(t) = e^{-2t} \sin(3t)u(t)$.

Question 4

The one ports \mathcal{N}_1 and \mathcal{N}_2 in Fig. 3 are in sinusoidal steady state. When the one-ports are connected as Fig. 3(a), $V_{aa'} = \sqrt{2}/\underline{-45^\circ}$, $I_{ab} = 1/\underline{0^\circ}$ while $V_{aa'} = \sqrt{2}/\underline{45^\circ}$, $I_{ab'} = 3/\underline{0^\circ}$ when the one-ports are connected as Fig. 3(b).

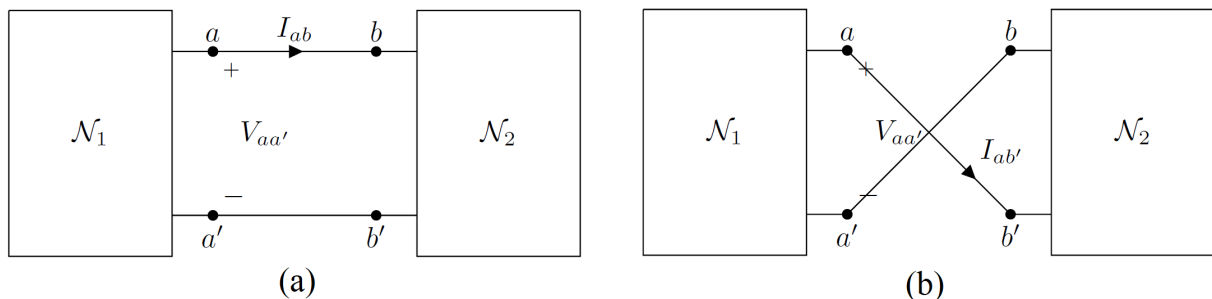


Figure 3: Two one-ports in sinusoidal steady state.

(a) Find the Thevenin equivalent circuits of the two one-ports.

(b) Find the resistance of the resistive load R_L connected between a and a' in Fig. 3(a) that absorbs the maximum average power.

(c) Find the maximum power absorbed by the resistive load R_L calculated in the previous part.

Question 5

Let $R_1 = 3\Omega$, $R_2 = 6\Omega$, and $L = \frac{2}{3}\text{H}$ in the first order RL circuit shown in Fig. 4.

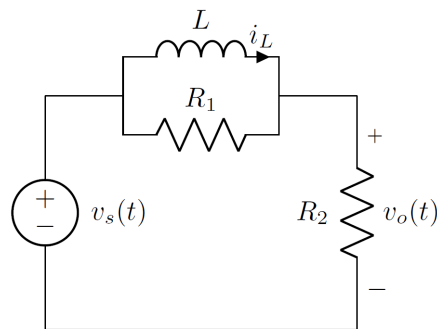


Figure 4: An RL circuit.

(a) Assume that $v_s(t) = e^{-\frac{9}{2}t}u(t)$. Calculate the initial current I_0 of the inductor such that $v_o(t) = 0, t > 0$.

(b) Assume that $v_s(t) = 8 \cos(\sqrt{3}t + \phi)u(t)$ V and let the inductor initial current $i_L(0) = I_0 = 1$ A. Calculate the phase ϕ such that no transient response appears in $i_L(t), t > 0$.