

# First-order Circuits

Mohammad Hadi

*mohammad.hadi@sharif.edu*

*@MohammadHadiDastgerdi*

Spring 2022

# Overview

- 1 First-order Circuits
- 2 First-order LTI RC Circuit
- 3 First-order LTI Circuit
- 4 First-order NTV Circuit

# First-order Circuits

# Circuit Types

## Statement (Linear Circuit)

*A linear circuit is a circuit that includes linear elements and/or independent sources.*

## Statement (LTI Circuit)

*An LTI circuit is a circuit that includes LTI elements and/or independent sources.*

## Statement (First-order Circuit)

*A first-order circuit is a circuit that has one independent energy-storage element.*

## Statement (First-order LTI Circuit)

*A first-order LTI circuit is an LTI circuit that has one independent energy-storage element.*

- Capacitors and inductors are **energy-storage elements**.

# Circuit Analysis

## Definition (Circuit Inputs)

Independent sources are called circuit inputs.

## Definition (Circuit Initial Conditions)

The initial voltage of the capacitors and initial currents of the inductors are referred to as circuit initial conditions.

## Definition (Circuit Response)

The circuit response is the voltage or current of a desired element of the circuit.

# Circuit Responses

## Definition (Zero-input response)

Zero-input response is defined as the response of a circuit when its inputs are identically zero.

## Definition (Zero-state response)

Zero-state response is defined as the response of a circuit when its initial conditions are zero.

## Definition (Complete response)

Complete response is defined as the response of a circuit to both inputs and initial states.

# Circuit Responses

## Definition (Impulse Response)

The zero-state response of the LTI circuit to the impulse input is called impulse response.

## Definition (Step Response)

The zero-state response of the LTI circuit to the unit step input is called step response.

# Circuit Responses

## Definition (Transient Response)

Transient response is the part of the circuit response that damps as time proceeds.

## Definition (Steady-state response)

Steady-state response is the part of the circuit response that remains as time proceeds.

# Linear Circuits

## Statement (Zero-input response)

*In a linear circuit, the zero-input response is a linear function of the initial conditions.*

## Statement (Zero-state response)

*In a linear circuit, the zero-state response is a linear function of the inputs.*

## Statement (Complete response)

*In a linear circuit, the complete response is the sum of zero-input and zero-state responses.*

- Homogeneity property of a linear function:

$$i_s(t) \rightarrow y(t) \Rightarrow K i_s(t) \rightarrow K y(t)$$

- Additivity property of a linear function:

$$i_{s1}(t) \rightarrow y_1(t), i_{s2}(t) \rightarrow y_2(t) \Rightarrow i_{s1}(t) + i_{s2}(t) \rightarrow y_1(t) + y_2(t)$$

## Statement (Input Shift Property)

*In an LTI circuit, the zero-state response to a shifted input experiences the same shift.*

- **Shift property:**  $i_s(t), y(0^-) = 0 \rightarrow y(t), t > 0 \Rightarrow i_s(t - t_0), y(t_0^-) = 0 \rightarrow y(t - t_0), t > t_0$

## Statement (Input Derivative Property)

*In an LTI circuit, the zero-state response to the derivative of an input equals the derivative of the zero-state response to the input.*

- **Derivative property:**

$$i_s(t), y(0^-) = 0 \rightarrow y(t), t > 0 \Rightarrow \frac{di_s(t)}{dt}, y(0^-) = 0 \rightarrow \frac{dy(t)}{dt}, t > 0$$

# First-order LTI RC Circuit

# Series RC Circuit


## Example (Zero-input response for series RC circuit)

The zero-input response of capacitor voltage in the series RC circuit has exponential form.

$$v_c(0^-) = V_0 \Rightarrow v_c(0^+) = V_0 \Rightarrow v_c(0) = V_0$$

$$\begin{aligned} i_R(t) - i_c(t) &= 0 \Rightarrow \frac{v_R(t)}{R} - C \frac{dv_c(t)}{dt} = 0 \\ -\frac{v_c(t)}{R} - C \frac{dv_c(t)}{dt} &= 0 \Rightarrow \frac{dv_c(t)}{dt} + \frac{1}{\tau} v_c(t) = 0, \tau = RC \end{aligned}$$
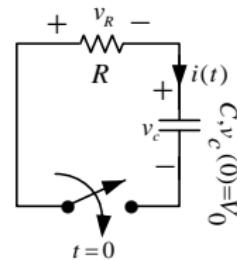
$$\begin{aligned} v_c(t) &= Ke^{-\frac{t}{\tau}}, v_c(0) = K = V_0 \\ \Rightarrow v_c(t) &= V_0 e^{-\frac{t}{\tau}}, t > 0 \end{aligned}$$



# Series RC Circuit

## Example (Zero-state response for series RC circuit)

The DC-driven zero-state response of capacitor voltage in the series RC circuit has exponential form.

$$v_c(0^-) = 0 \Rightarrow v_c(0^+) = 0 \Rightarrow v_c(0) = 0$$


$$v_R(t) + v_c(t) - v_s(t) = 0$$

$$\Rightarrow R i_R(t) + v_c(t) = R i_C(t) + v_c(t) = v_s(t)$$

$$\Rightarrow R C \frac{dv_C(t)}{dt} + v_c(t) = v_s(t)$$

$$\Rightarrow \frac{dv_C(t)}{dt} + \frac{1}{\tau} v_c(t) = \frac{v_s(t)}{\tau}, \quad \tau = RC$$
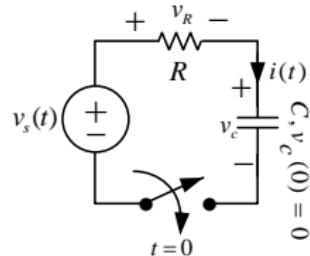
$$\Rightarrow \frac{dv_C(t)}{dt} + \frac{1}{\tau} v_c(t) = \frac{V_s}{\tau}$$



$$v_c(t) = K e^{-\frac{t}{\tau}} + V_s, v_c(0) = K + V_s = 0 \Rightarrow K = -V_s$$

$$\Rightarrow v_c(t) = V_s(1 - e^{-\frac{t}{\tau}}), t > 0$$

# Series RC Circuit

## Example (Complete response for series RC circuit)

The DC-driven complete response of capacitor voltage in the series RC circuit has exponential form.

$$v_c(0^-) = V_0 \Rightarrow v_c(0^+) = V_0 \Rightarrow v_c(0) = V_0$$


$$v_R(t) + v_c(t) - v_s(t) = 0$$

$$\Rightarrow R i_R(t) + v_c(t) = R i_C(t) + v_c(t) = v_s(t)$$

$$\Rightarrow R C \frac{dv_C(t)}{dt} + v_c(t) = v_s(t)$$

$$\Rightarrow \frac{dv_C(t)}{dt} + \frac{1}{\tau} v_c(t) = \frac{v_s(t)}{\tau}, \quad \tau = RC$$
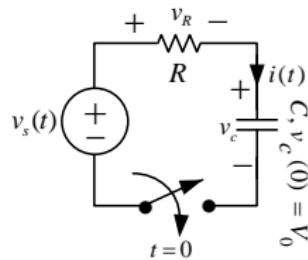
$$\Rightarrow \frac{dv_C(t)}{dt} + \frac{1}{\tau} v_c(t) = \frac{V_s}{\tau}$$



$$v_c(t) = K e^{-\frac{t}{\tau}} + V_s, \quad v_c(0) = K + V_s = V_0 \Rightarrow K = V_0 - V_s$$

$$\Rightarrow v_c(t) = (V_0 - V_s) e^{-\frac{t}{\tau}} + V_s, \quad t > 0$$


# Series RC Circuit

## Example (Complete response for series RC circuit)

The complete response is the sum of the zero-input and zero-state responses in the DC-driven series RC circuit.

$$v_c(t) = (V_0 - V_s)e^{-\frac{t}{\tau}} + V_s, t > 0$$
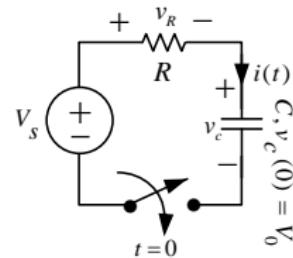
$$v_c(t) = V_0 e^{-\frac{t}{\tau}} + V_s(1 - e^{-\frac{t}{\tau}}), t > 0$$




# Series RC Circuit

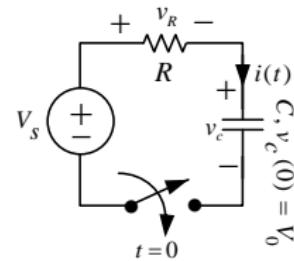Example (Transient and steady state responses for series RC circuit)

The DC-driven series RC circuit with  $\tau > 0$  has a damping exponential transient response and a constant steady state response.

$$v_c(t) = (V_0 - V_s)e^{-\frac{t}{\tau}} + V_s, t > 0$$



# Series RC Circuit


## Example (Current response for series RC circuit)

The current response experiences a discontinuity at  $t = 0$  in the series RC circuit.

$$i(0^-) = 0, i(0^+) = \frac{V_s - V_0}{R}$$

$$v_c(t) = (V_0 - V_s)e^{-\frac{t}{\tau}} + V_s, t > 0$$
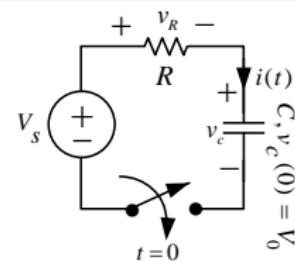
$$i(t) = C \frac{dv_c(t)}{dt} = \frac{V_s - V_0}{R} e^{-\frac{t}{\tau}}$$



# Series RC Circuit

## Example (Stored energy for series RC circuit)


$\frac{1}{2}CV_s^2$  of electrical energy is stored in the zero-state DC-driven series RC circuit.

$$v_c(t) = V_s(1 - e^{-\frac{t}{\tau}}), t > 0$$

$$i(t) = \frac{V_s}{R}e^{-\frac{t}{\tau}}$$

$$p(t) = \frac{V_s^2}{R}e^{-\frac{t}{\tau}}(1 - e^{-\frac{t}{\tau}})$$
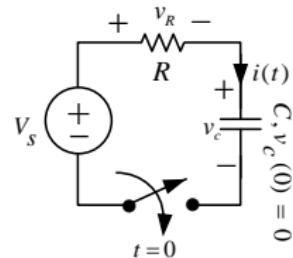
$$w(0, \infty) = \int_0^{\infty} p(t)dt = \frac{1}{2}CV_s^2$$



# Series RC Circuit

## Example (Step response)



Step response of the series RC circuit has exponential form.

$$v_c(0^-) = 0 \Rightarrow v_c(0^+) = 0$$

$$\frac{dv_c(t)}{dt} + \frac{1}{\tau} v_c(t) = \frac{1}{\tau}$$

$$\Rightarrow v_c(t) = 1 - e^{-\frac{t}{\tau}}, t > 0$$
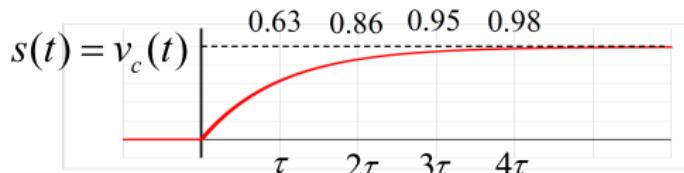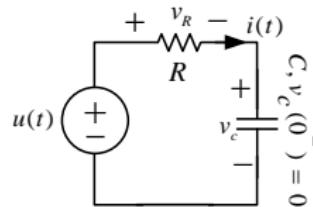
$$v_c(t) = s(t) = \begin{cases} 0, & t \leq 0 \\ 1 - e^{-\frac{t}{\tau}}, & t > 0 \end{cases} = (1 - e^{-\frac{t}{\tau}})u(t)$$



# Series RC Circuit

Example (Linearity and shift property of LTI circuits)


Zero-state response to a complex input can be found using linearity and shift properties of an LTI circuit.

$$v_c(0^-) = 0, v_s(t) = \frac{u(t) - u(t-T)}{T}$$

$$\frac{dv_c(t)}{dt} + \frac{1}{\tau} v_c(t) = \frac{u(t) - u(t-T)}{T\tau}$$

$$\Rightarrow v_c(t) = \begin{cases} 0, & t \leq 0 \\ \frac{1-e^{-\frac{t}{\tau}}}{T}, & 0 \leq t < T \\ \frac{e^{-\frac{t-T}{\tau}} - e^{-\frac{t}{\tau}}}{T}, & t \geq T \end{cases}$$
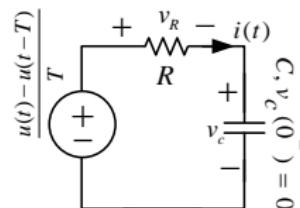
$$\Rightarrow v_c(t) = \frac{1}{T}(1 - e^{-\frac{t}{\tau}})u(t) - \frac{1}{T}(1 - e^{-\frac{t-T}{\tau}})u(t-T)$$



# Series RC Circuit

## Example (Impulse response)





Impulse response of the series RC circuit is the derivative of the step response.

$$v_c(0^-) = 0, \delta(t) = \lim_{T \rightarrow 0} \frac{u(t) - u(t - T)}{T}$$

$$\frac{dv_C(t)}{dt} + \frac{1}{\tau} v_c(t) = \frac{u(t) - u(t - T)}{T\tau}$$

$$\Rightarrow v_c(t) = \begin{cases} 0, & t \leq 0 \\ \frac{1-e^{-\frac{t}{\tau}}}{T}, & 0 \leq t < T \\ \frac{e^{-\frac{t-T}{\tau}}-e^{-\frac{t}{\tau}}}{T}, & t \geq T \end{cases}$$
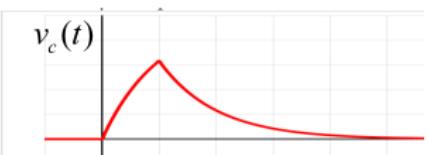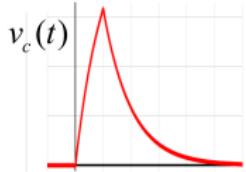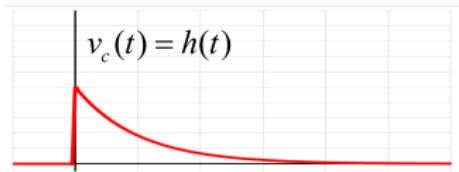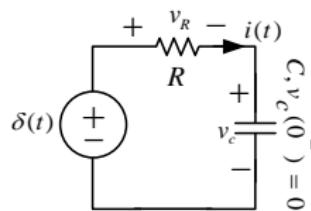
$$h(t) = \lim_{T \rightarrow 0} v_c(t) = \begin{cases} 0, & t \leq 0 \\ \frac{1}{\tau} e^{-\frac{t}{\tau}}, & t \geq 0 \end{cases} = \frac{1}{\tau} e^{-\frac{t}{\tau}} u(t) = \frac{ds(t)}{dt}$$



# Series RC Circuit

## Example (Impulse response (cont.))

Impulse response of the series RC circuit is the derivative of the step response.

$$\frac{dv_c(t)}{dt} + \frac{1}{\tau} v_c(t) = \frac{\delta(t)}{\tau}, v_c(0^-) = 0$$


$$\frac{dv_c(t)}{dt} + \frac{1}{\tau} v_c(t) = 0, t > 0, v_c(0^+) = ?$$

$$\int_{0^-}^{0^+} \left[ \frac{dv_c(t)}{dt} + \frac{1}{\tau} v_c(t) \right] dt = \int_{0^-}^{0^+} \frac{\delta(t)}{\tau} dt$$

$$(v_c(0^+) - v_c(0^-)) + 0 = \frac{1}{\tau} \Rightarrow v_c(0^+) = \frac{1}{\tau}$$

$$\frac{dv_c(t)}{dt} + \frac{1}{\tau} v_c(t) = 0, v_c(0^+) = \frac{1}{\tau}$$
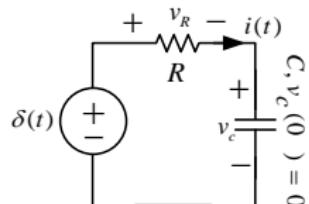
$$h(t) = \frac{1}{\tau} e^{-\frac{t}{\tau}} u(t) = \frac{ds(t)}{dt}$$



# Parallel RC Circuit

## Example (Complete response for parallel RC circuit)

The DC-driven complete response of capacitor voltage in the parallel RC circuit has exponential form.

$$v_c(0^-) = V_0 \Rightarrow v_c(0^+) = V_0 \Rightarrow v_c(0) = V_0$$

$$i_R(t) + i_c(t) - i_s(t) = 0$$

$$\Rightarrow \frac{v_c(t)}{R} + C \frac{dv_c(t)}{dt} = i_s(t)$$

$$\Rightarrow RC \frac{dv_c(t)}{dt} + v_c(t) = Ri_s(t)$$


$$\Rightarrow \frac{dv_c(t)}{dt} + \frac{1}{\tau} v_c(t) = \frac{i_s(t)}{C}, \quad \tau = RC$$

$$\Rightarrow \frac{dv_c(t)}{dt} + \frac{1}{\tau} v_c(t) = \frac{I_s}{C}, t > 0$$

$$\Rightarrow v_c(t) = Ke^{-\frac{t}{\tau}} + RI_s, v_c(0) = K + RI_s = V_0 \Rightarrow K = V_0 - RI_s$$

$$\Rightarrow v_c(t) = (V_0 - RI_s)e^{-\frac{t}{\tau}} + RI_s, t > 0$$
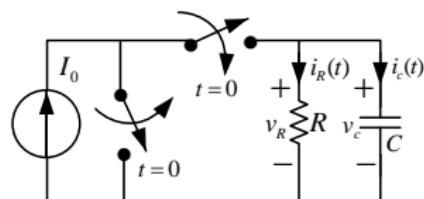
$$\Rightarrow v_c(t) = V_0 e^{-\frac{t}{\tau}} + RI_s(1 - e^{-\frac{t}{\tau}}), t > 0$$



# First-order LTI Circuit

# DC-driven RL Circuit

## Example (Complete response for an RL circuit)

The DC-driven complete response of inductor current in the RL circuit has exponential form.

$$i_L(0^-) = I_0 \Rightarrow i_L(0^+) = I_0 \Rightarrow i_L(0) = I_0$$

$$i_R(t) + i_L(t) - i_s(t) = 0$$

$$\Rightarrow \frac{v_L(t)}{R} + i_L(t) = i_s(t)$$

$$\Rightarrow \frac{L}{R} \frac{di_L(t)}{dt} + i_L(t) = i_s(t)$$


$$\Rightarrow \frac{di_L(t)}{dt} + \frac{1}{\tau} i_L(t) = \frac{i_s(t)}{\tau}, \quad \tau = \frac{L}{R}$$

$$\Rightarrow \frac{di_L(t)}{dt} + \frac{1}{\tau} i_L(t) = \frac{i_s}{\tau}, t > 0$$

$$\Rightarrow i_L(t) = K e^{-\frac{t}{\tau}} + I_s, i_L(0) = K + I_s = I_0 \Rightarrow K = I_0 - I_s$$

$$\Rightarrow i_L(t) = (I_0 - I_s) e^{-\frac{t}{\tau}} + I_s, t > 0$$
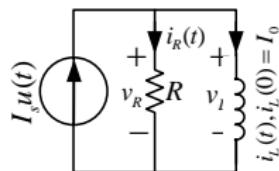
$$\Rightarrow i_L(t) = I_0 e^{-\frac{t}{\tau}} + I_s (1 - e^{-\frac{t}{\tau}}), t > 0$$



# DC-driven Complete Response

## Statement (DC-driven First Order LTI Circuit Describing Equation)

A DC-driven first-order LTI circuit is described by the constant-coefficient linear differential equation  $\frac{df(t)}{dt} + \frac{1}{\tau}f(t) = F_s$ ,  $f(t_0^+) = F_0$ ,  $t > t_0$ , where  $F_0$  is a suitably calculated initial value at  $t = t_0$ .



## Statement (DC-driven First Order LTI Circuit Complete Response)

A DC-driven first-order LTI circuit achieving steady state situation has the complete response  $f(t) = f(\infty) + [f(t_0^+) - f(\infty)]e^{-\frac{t-t_0}{\tau}}$ ,  $t > t_0$ , where  $\tau = R_{eq}C$  or  $\tau = \frac{L}{R_{eq}}$  and  $R_{eq}$  is the equivalent resistance seen from the energy-storage element in the in-rest circuit.  $f(t_0^+)$  is a suitably calculated initial value at  $t = t_0$  and  $f(\infty)$  is the steady state value when the energy-storage element acts like short or open circuit.

# DC-driven LTI First-order Circuit

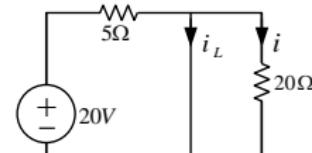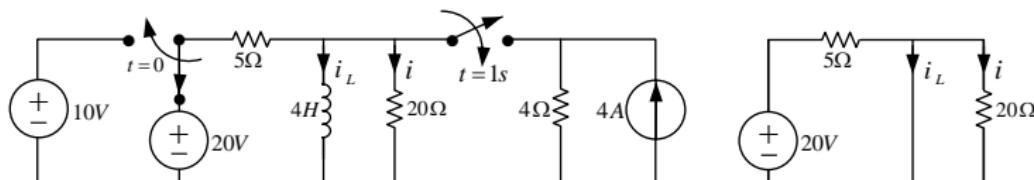Example (LTI first-order circuit with two time constants)

Switching may change the time constant of an LTI first-order circuit.




$$i(t) = 0, t < 0 \Rightarrow i_L(t) = \frac{20}{5} = 4, t < 0$$

$$i(0^-) = 0, i_L(0^-) = 4$$

# DC-driven LTI First-order Circuit

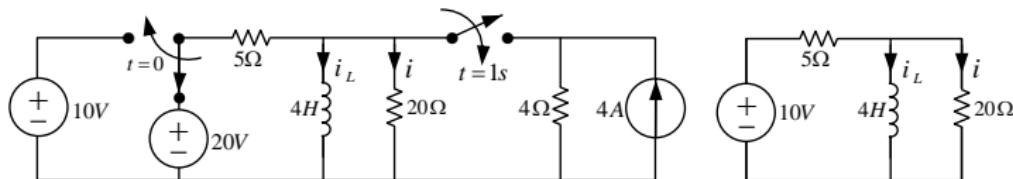Example (LTI first-order circuit with two time constants (cont.))

Switching may change the time constant of an LTI first-order circuit.



$$i_L(0^+) = i_L(0^-) = 4 \Rightarrow -10 + 5(i(0^+) + i_L(0^+)) + 20i(0^+) = 0 \Rightarrow i(0^+) = -0.4$$

$$i(\infty) = 0 \Rightarrow i_L(\infty) = \frac{10}{5} = 2$$

$$R_{eq} = 20||5 = 4 \Rightarrow \tau = \frac{L}{R_{eq}} = 1$$

$$i_L(t) = [i_L(0^+) - i_L(\infty)]e^{-\frac{t}{\tau}} + i_L(\infty) = 2 + 2e^{-t}, 0 < t < 1$$


$$i(t) = [i(0^+) - i(\infty)]e^{-\frac{t}{\tau}} + i(\infty) = -0.4e^{-t} = \frac{v_L(t)}{20} = \frac{4}{20} \frac{di_L(t)}{dt}, 0 < t < 1$$

$$i_L(1^-) = 2 + 2e^{-1} \approx 2.74$$

# DC-driven LTI First-order Circuit

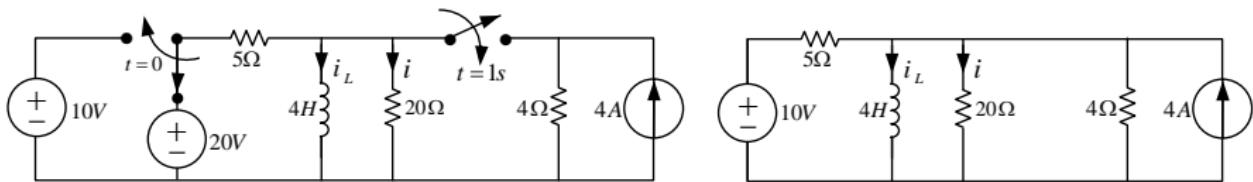Example (LTI first-order circuit with two time constants (cont.))

Switching may change the time constant of an LTI first-order circuit.



$$i_L(1^+) = i_L(1^-) = 2.74 \Rightarrow -10 + 5(i(1^+) + i_L(1^+)) + \frac{20i(1^+)}{4} - 4 + 20i(1^+) = 0 \Rightarrow i(1^+) = -0.33$$

$$i(\infty) = 0 \Rightarrow i_L(\infty) = \frac{10}{5} + 4 = 6$$

$$R_{eq} = 20||5||4 = 2 \Rightarrow \tau = \frac{L}{R_{eq}} = 2$$


$$i_L(t) = [i_L(1^+) - i_L(\infty)]e^{-\frac{t-1}{\tau}} + i_L(\infty) = 6 - 3.2e^{-\frac{t-1}{2}}, t > 1$$

$$i(t) = [i(1^+) - i(\infty)]e^{-\frac{t-1}{\tau}} + i(\infty) = -0.33e^{-\frac{t-1}{2}} = \frac{v_L(t)}{20} = \frac{4}{20} \frac{di_L(t)}{dt}, t > 1$$

# DC-driven LTI First-order Circuit

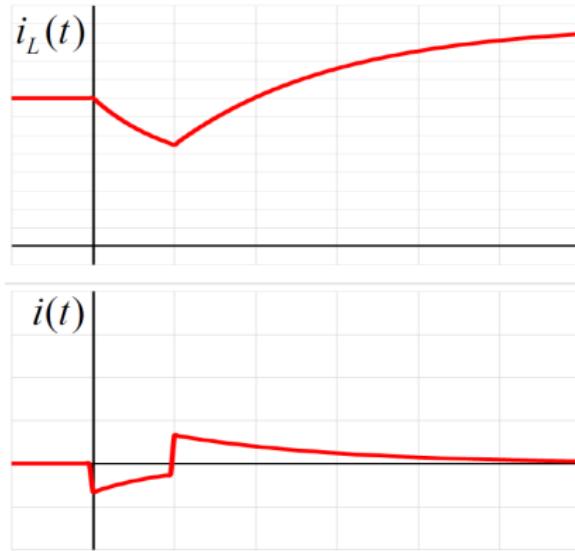Example (LTI first-order circuit with two time constants (cont.))

Switching may change the time constant of an LTI first-order circuit.



# DC-driven LTI First-order Circuit

## Example (Step response calculation)

Step response can be found using various methods.


$$-v_s(t) + 5i(t) + v_C(t) = 0, \quad i(t) = \frac{1}{2} \frac{v_C(t)}{dt} + \frac{v_C(t)}{20}$$

$$\frac{dv_C(t)}{dt} + \frac{1}{2} v_C(t) = \frac{2}{5} v_s(t)$$

$$\frac{dv_C(t)}{dt} + \frac{1}{2} v_C(t) = \frac{2}{5} u(t), v_C(0^-) = 0$$

$$\frac{dv_C(t)}{dt} + \frac{1}{2} v_C(t) = \frac{2}{5}, t > 0, v_C(0^+) = 0$$
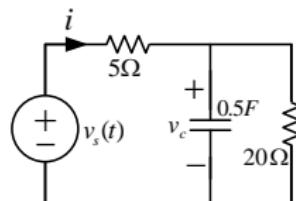
$$v_C(t) = \frac{4}{5}(1 - e^{-\frac{t}{2}}), t > 0, \quad s_v(t) = \frac{4}{5}(1 - e^{-\frac{t}{2}})u(t)$$



$$s_v(t) = \begin{cases} 0, & t < 0 \\ [v_C(0^+) - v_C(\infty)]e^{-\frac{t}{\tau}} + v_C(\infty), & t > 0 \end{cases} = \frac{4}{5}(1 - e^{-\frac{t}{2}})u(t)$$

# DC-driven LTI First-order Circuit

## Example (Step response calculation (cont.))

Step response can be found using various methods.

$$-v_s(t) + 5i(t) + v_C(t) = 0, \quad i(t) = \frac{1}{2} \frac{v_C(t)}{dt} + \frac{v_C(t)}{20}$$

$$\frac{di(t)}{dt} + \frac{1}{2}i(t) = \frac{1}{50}v_s(t) + \frac{1}{5} \frac{dv_s(t)}{dt}$$


$$\frac{di(t)}{dt} + \frac{1}{2}i(t) = \frac{1}{50}u(t) + \frac{1}{5}\delta(t), i(0^-) = 0$$

$$\int_{0^-}^{0^+} \frac{di(t)}{dt} dt + \frac{1}{2} \int_{0^-}^{0^+} i(t) dt = \frac{1}{50} \int_{0^-}^{0^+} u(t) dt + \frac{1}{5} \int_{0^-}^{0^+} \delta(t) dt$$

$$(i(0^+) - i(0^-)) + 0 = 0 + \frac{1}{5} \Rightarrow i(0^+) = \frac{1}{5}$$

$$\frac{di(t)}{dt} + \frac{1}{2}i(t) = \frac{1}{50}, i(0^+) = \frac{1}{5}$$
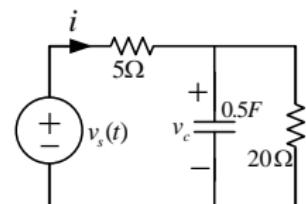
$$i(t) = \frac{4}{25}e^{-\frac{t}{2}} + \frac{1}{25}, t > 0, \quad s_i(t) = \left[ \frac{4}{25}e^{-\frac{t}{2}} + \frac{1}{25} \right] u(t)$$




# DC-driven LTI First-order Circuit

## Example (Step response calculation (cont.))

Step response can be found using various methods.

$$i(t) = \frac{v_s(t) - v_c(t)}{5} \Rightarrow s_i(t) = \frac{u(t) - s_v(t)}{5} = \left[ \frac{4}{25} e^{-\frac{t}{2}} + \frac{1}{25} \right] u(t)$$
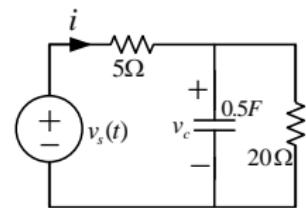
$$s_i(t) = \begin{cases} 0, & t < 0 \\ [i(0^+) - i(\infty)]e^{-\frac{t}{\tau}} + i(\infty), & t > 0 \end{cases} = \left[ \frac{4}{25} e^{-\frac{t}{2}} + \frac{1}{25} \right] u(t)$$



# DC-driven LTI First-order Circuit

## Example (Impulse response calculation)

Impulse response can be found using various methods.

$$-v_s(t) + 5i(t) + v_C(t) = 0, \quad i(t) = \frac{1}{2} \frac{dv_C(t)}{dt} + \frac{v_C(t)}{20}$$

$$\frac{dv_C(t)}{dt} + \frac{1}{2}v_C(t) = \frac{2}{5}v_s(t)$$


$$\frac{dv_C(t)}{dt} + \frac{1}{2}v_C(t) = \frac{2}{5}\delta(t), v_C(0^-) = 0$$

$$\int_{0^-}^{0^+} \frac{dv_C(t)}{dt} dt + \frac{1}{2} \int_{0^-}^{0^+} v_C(t) dt = \frac{2}{5} \int_{0^-}^{0^+} \delta(t) dt$$

$$(v_C(0^+) - v_C(0^-)) + 0 = 0 + \frac{2}{5} \Rightarrow v_C(0^+) = \frac{2}{5}$$

$$\frac{dv_C(t)}{dt} + \frac{1}{2}v_C(t) = 0, v_C(0^+) = \frac{2}{5}$$
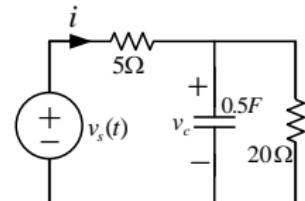
$$v_C(t) = \frac{2}{5}e^{-\frac{t}{2}} t > 0, \quad h_v(t) = \frac{2}{5}e^{-\frac{t}{2}} u(t)$$



$$h_v(t) = \frac{ds_v(t)}{dt} = \frac{d}{dt} [(1 - e^{-\frac{t}{2}})u(t)] = \frac{2}{5}e^{-\frac{t}{2}}u(t)$$

# DC-driven LTI First-order Circuit

## Example (Impulse response calculation (cont.))


Impulse response can be found using various methods.

$$h_i(t) = \frac{ds_i(t)}{dt} = \frac{d}{dt} \left[ \left( \frac{4}{25} e^{-\frac{t}{2}} + \frac{1}{25} \right) u(t) \right] = \frac{-2}{25} e^{-\frac{t}{2}} u(t) + \frac{1}{5} \delta(t)$$

$$i(t) = \frac{v_s(t) - v_c(t)}{5} \Rightarrow h_i(t) = \frac{\delta(t) - h_v(t)}{5} = \frac{-2}{25} e^{-\frac{t}{2}} u(t) + \frac{1}{5} \delta(t)$$

$$\frac{di(t)}{dt} + \frac{1}{2} i(t) = \frac{1}{50} \delta(t) + \frac{1}{5} \delta'(t), i(0^-) = 0$$

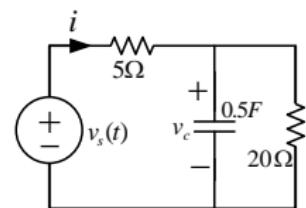
$$h_i(t) = \frac{-2}{25} e^{-\frac{t}{2}} u(t) + \frac{1}{5} \delta(t)$$



# DC-driven LTI First-order Circuit
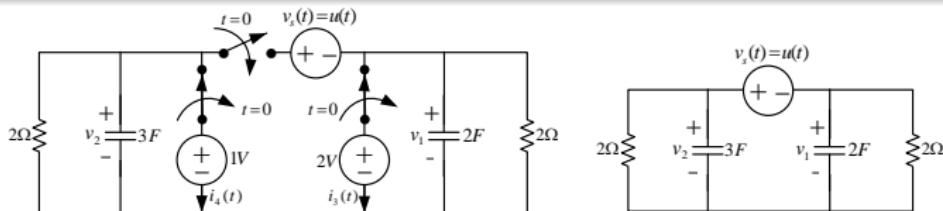
## Example (LTI first-order circuit with two capacitors)

Each capacitive loop decrements the number of independent capacitors.



$$v_1(0^-) = 2, \quad v_2(0^-) = 1$$

$$\begin{cases} -v_2(t) + u(t) + v_1(t) = 0 \\ \frac{v_2(t)}{2} + 3\frac{dv_2(t)}{dt} + i_4(t) + i_3(t) + 2\frac{dv_1(t)}{dt} + \frac{v_1(t)}{2} = 0, \quad i_4(t) = i_3(t) = 0 \end{cases}, t > 0$$

$$\begin{cases} -v_2(0^+) + u(0^+) + v_1(0^+) = 0 \\ 0 + 3(v_2(0^+) - v_2(0^-)) + 0 + 0 + 2(v_1(0^+) - v_1(0^-)) + 0 = 0 \end{cases} \Rightarrow \begin{cases} v_1(0^+) = 0.8 \\ v_2(0^+) = 1.8 \end{cases}$$


$$\frac{dv_2(t)}{dt} + \frac{1}{5}v_2(t) = 0.1u(t) + 0.4\delta(t), v_2(0^+) = 1.8$$

$$v_2(t) = 0.5 + 1.3e^{-\frac{t}{5}}, t > 0$$

# DC-driven LTI First-order Circuit

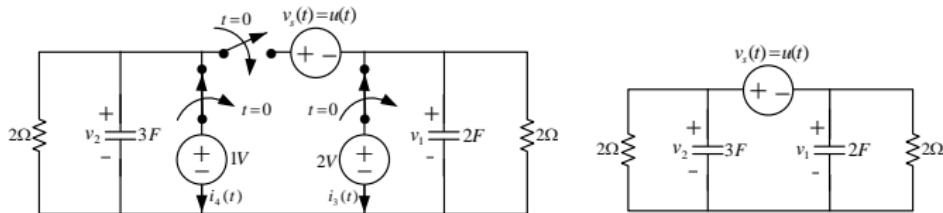Example (LTI first-order circuit with two capacitors (cont.))

Each capacitive loop decrements the number of independent capacitors.



$$v_1(0^-) = 2, \quad v_2(0^-) = 1 \Rightarrow v_1(0^+) = 0.8, \quad v_2(0^+) = 1.8$$

$$v_1(\infty) = -0.5, \quad v_2(\infty) = 0.5$$

$$R_{eq} = 2||2 = 1, \quad C_{eq} = 2 + 3 = 5 \Rightarrow \tau = R_{eq} C_{eq} = 5$$


$$v_1(t) = (v_1(0^+) - v_1(\infty))e^{-\frac{t}{\tau}} + v_1(\infty) = -0.5 + 1.3e^{-\frac{t}{5}}$$

$$v_2(t) = (v_2(0^+) - v_2(\infty))e^{-\frac{t}{\tau}} + v_2(\infty) = 0.5 + 1.3e^{-\frac{t}{5}}$$

# DC-driven LTI First-order Circuit

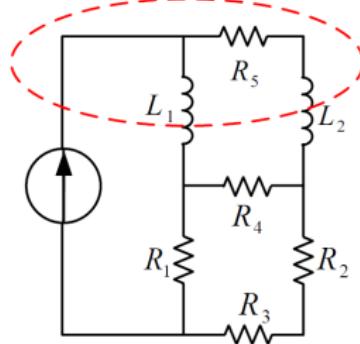Example (LTI first-order circuit with two inductors)

Each inductive Gaussian surface decrements the number of independent inductors.



$$R_{eq} = R_5 + (R_4 \parallel (R_1 + R_2 + R_3)), \quad L_{eq} = L_1 + L_2 \Rightarrow \tau = \frac{L_{eq}}{R_{eq}}$$

# Exponentially-driven LTI First-order Circuit

## Example (Exponential input)

In the circuit below with  $R = 1 \Omega$ ,  $c = 0.5 F$ ,  $v_C(0^+) = 2 V$ , and  $i_s(t) = 5e^{-t}$ , the capacitor voltage has no steady state response.

$$\frac{dv_C(t)}{dt} + 2v_C(t) = 2i_s(t), v_C(0^+) = 2$$

$$\frac{dv_C(t)}{dt} + 2v_C(t) = 10e^{-t}, v_C(0^+) = 2$$


$$v_C(t) = Ke^{-2t} + Ae^{-t}$$

$$d[Ae^{-t}] + 2Ae^{-t} = 10e^{-t} \Rightarrow A = 10$$

$$v_C(0^+) = K + 10 = 2 \Rightarrow K = -8$$

$$v_C(t) = -8e^{-2t} + 10e^{-t}, t > 0$$

$$v_C(t \rightarrow \infty) = 0$$

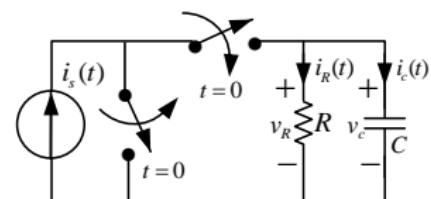

# Exponentially-driven LTI First-order Circuit

## Example (Sinusoidal input)

In the circuit below with  $R = 1 \Omega$ ,  $c = 0.5 F$ ,  $v_C(0^+) = 2 V$ , and  $i_s(t) = 5 \cos(t)$ , the capacitor voltage has sinusoidal steady state response.

$$\frac{dv_C(t)}{dt} + 2v_C(t) = 2i_s(t), v_C(0^+) = 2$$

$$\frac{dv_C(t)}{dt} + 2v_C(t) = 10 \cos(t), v_C(0^+) = 2$$

$$v_C(t) = Ke^{-2t} + A \cos(t) + B \sin(t)$$

$$\frac{d[A \cos(t) + B \sin(t)]}{dt} + 2[A \cos(t) + B \sin(t)] = 10 \cos(t)$$

$$(2A + B) \cos(t) + (2B - A) \sin(t) = 10 \cos(t)$$


$$\begin{cases} 2A + B = 10 \\ 2B - A = 0 \end{cases} \Rightarrow A = 4, B = 2$$

$$v_C(0^+) = K + 4 = 2 \Rightarrow K = -2$$

$$v_C(t) = -2e^{-2t} + 4 \cos(t) + 2 \sin(t), t > 0$$

$$v_C(t) = -2e^{-2t} + 2\sqrt{5} \cos(t - \tan^{-1}(0.5)), t > 0$$
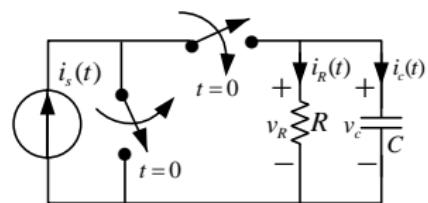
$$v_C(t \rightarrow \infty) = 2\sqrt{5} \cos(t - \tan^{-1}(0.5))$$



# First-order NTV Circuit

# First-order NTV Circuit

## Example (First-order LTV circuit)

Generally, a first-order LTV circuit is not described by constant coefficient linear differential equation.

$$R(t) = \frac{1}{1 + 0.5 \cos(t)}, v_C(0) = 2$$


$$i_C(t) + i_R(t) = 0 \Rightarrow \frac{dv_C(t)}{dt} + (1 + 0.5 \cos(t))v_C(t) = 0, t > 0$$

$$\frac{dv_C}{v_C} = -(1 + 0.5 \cos(t))dt, t > 0$$

$$\int_{v_C(0)}^{v_C(t)} \frac{dv_C}{v_C} = - \int_0^t (1 + 0.5 \cos(t))dt$$

$$\ln(v_C(t)) - \ln(v_C(0)) = -t - 0.5 \sin(t), t > 0$$
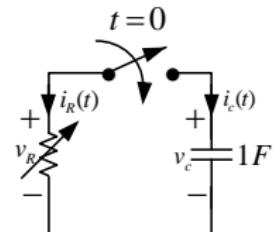
$$v_C(t) = 2e^{-t - 0.5 \sin(t)}, t > 0$$



# First-order NTV Circuit

## Example (First-order NTI circuit)

Generally, a first-order NTI circuit is not described by constant coefficient linear differential equation.

$$i_R(t) = v_R^2(t), v_C(0) = 2$$


$$i_C(t) + i_R(t) = 0 \Rightarrow \frac{dv_C(t)}{dt} + v_C^2(t) = 0, t > 0$$

$$\frac{dv_C}{v_C^2} = -dt, t > 0$$

$$\int_{v_C(0)}^{v_C(t)} \frac{dv_C}{v_C^2} = - \int_0^t dt$$

$$-\frac{1}{v_C(t)} + \frac{1}{v_C(0)} = -t, t > 0$$


$$v_C(t) = \frac{1}{t + 0.5}, t > 0$$

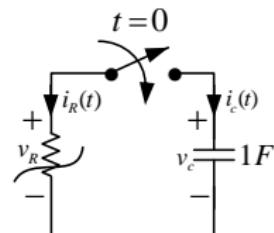

# First-order NTV Circuit
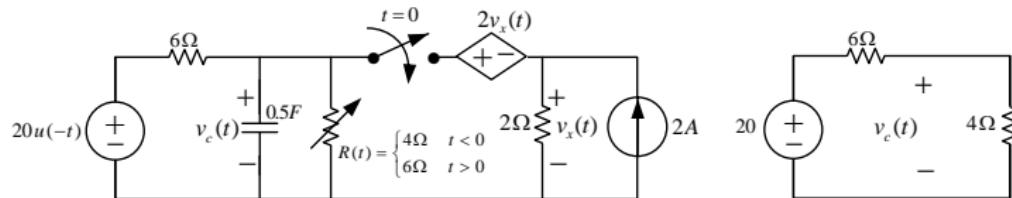
## Example (First-order LTV circuit)

A first-order LTV circuit may be treated as an LTI circuit in different time intervals.




$$v_C(t) = \frac{4}{4+6} 20 = 8, t < 0 \Rightarrow v_C(0^-) = 8$$

# First-order NTV Circuit
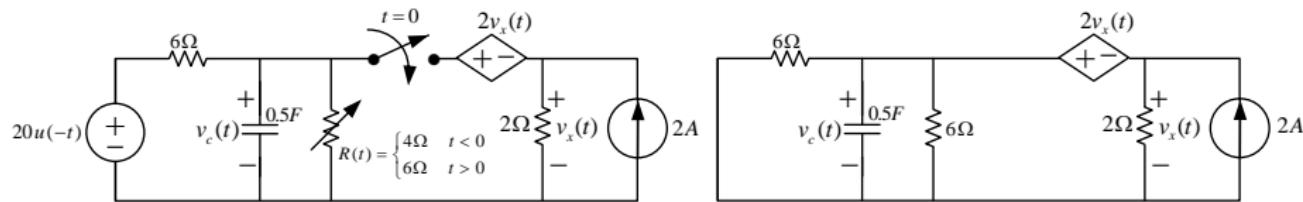
## Example (First-order LTV circuit (cont.))

Generally, a first-order LTV circuit may be treated as an LTI circuit in different time intervals.




$$v_C(t) = [v_C(0^+) - v_C(\infty)]e^{-\frac{t}{\tau}} + v_C(\infty), \quad t > 0$$

$$v_C(0^+) = v_C(0^-) = 8$$

# First-order NTV Circuit
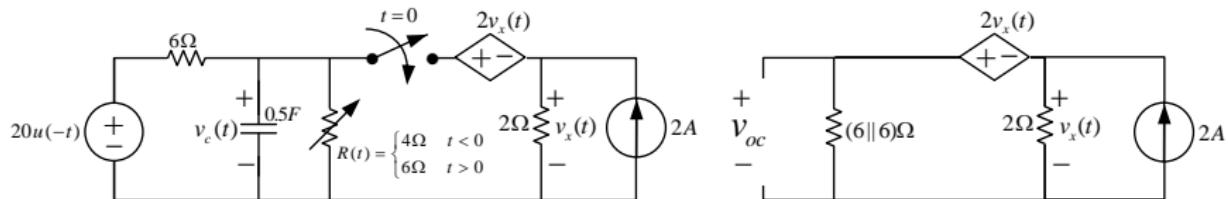
## Example (First-order LTV circuit (cont.))

Generally, a first-order LTV circuit may be treated as an LTI circuit in different time intervals.




$$v_C(t) = [v_C(0^+) - v_C(\infty)]e^{-\frac{t}{\tau}} + v_C(\infty), \quad t > 0$$
$$v_C(\infty) = v_{oc} = 4$$

# First-order NTV Circuit
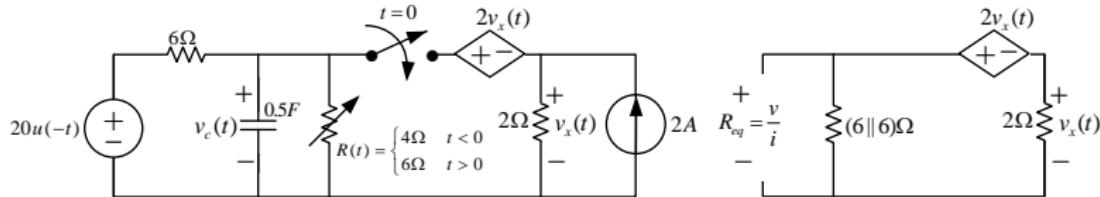
## Example (First-order LTV circuit (cont.))

Generally, a first-order LTV circuit may be treated as an LTI circuit in different time intervals.



$$v_C(t) = [v_C(0^+) - v_C(\infty)]e^{-\frac{t}{\tau}} + v_C(\infty) = 4 + 4e^{-t}, t > 0$$

$$R_{eq} = 2 \Rightarrow \tau = R_{eq} C = 1$$

# The End