

Operational Amplifiers

Mohammad Hadi

mohammad.hadi@sharif.edu

@MohammadHadiDastgerdi

Spring 2022



- 1 Operational Amplifiers
- 2 Well-known Op-Amp Circuits
- 3 Op-Amp Circuits
- 4 Amplifiers

Operational Amplifiers

Definition (Op-Amp)



An operational amplifier is a multi-terminal element characterized as
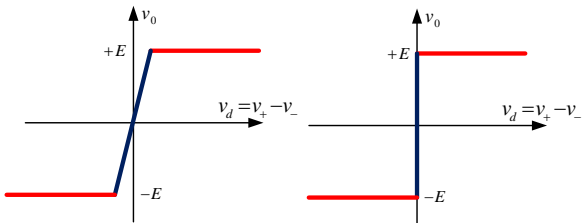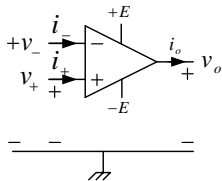
$$v_o = \begin{cases} +E & v_d = v_+ - v_- > 0 \\ \in (-E, +E) & v_d = v_+ - v_- = 0 \approx E \operatorname{sgn}(v_d) \\ -E & v_d = v_+ - v_- < 0 \end{cases}$$



Statement (Linear and Nonlinear Behaviors of Op-Amp)

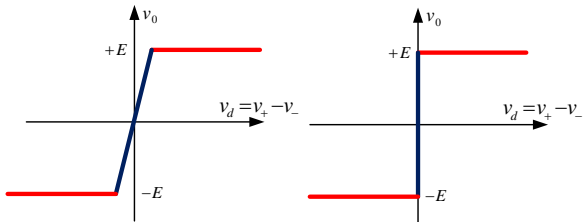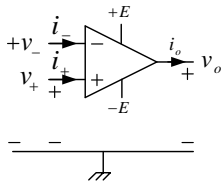
An operational amplifier can be considered as a nonlinear analog comparator or can be considered as a linear amplifier with infinite gain $A \approx \infty$ for $v_o \in (-E, +E)$.



Linear Amplification

Example (Linear behavior of op-amp)

If an ideal op-amp has negative feedback, it can work as an amplifier provided that $|v_o| < V_{sat} \approx E$ and $|i_o| \lesssim I_{sat}$.

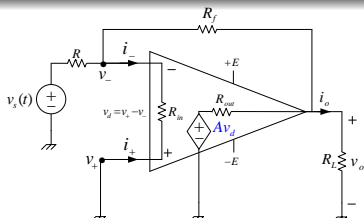

$$\frac{v_- - v_s}{R} + \frac{v_- - v_o}{R_f} + \frac{v_- - 0}{R_{in}} = 0, \quad \frac{v_o - v_-}{R_f} + \frac{v_o - Av_d}{R_{out}} + \frac{v_o - 0}{R_L} = 0$$


$$G = \frac{v_o}{v_s} = \frac{-A + \frac{R_{out}}{R_f}}{\frac{R}{R_f} \left(1 + A + \frac{R_{out}}{R_{in}} + \frac{R_{out}}{R_L}\right) + \left(1 + \frac{R_{out}}{R_L}\right) \left(1 + \frac{R}{R_{in}}\right) + \frac{R_{out}}{R_f}} \Rightarrow \lim_{\substack{A \rightarrow \infty \\ R_{in} \rightarrow \infty \\ R_{out} \rightarrow 0}} G = -\frac{R_f}{R}$$

$$v_d = v_+ - v_- = -v_s \frac{RR_{in}G + R_f R_{in}}{R_f R_{in} + RR_{in} + RR_f} \Rightarrow \lim_{\substack{A \rightarrow \infty \\ R_{in} \rightarrow \infty \\ R_{out} \rightarrow 0}} v_d = 0 \Rightarrow \lim_{\substack{A \rightarrow \infty \\ R_{in} \rightarrow \infty \\ R_{out} \rightarrow 0}} i_R = 0$$

Linear Amplification

Example (Linear model of op-amp)

When an ideal op-amp is used as an amplifier, it can be modeled by a dependent voltage source with the implicit assumptions $|v_o| < V_{sat} \approx E$ and $|i_o| \lesssim I_{sat}$.

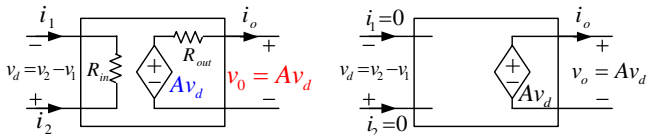

$$A = \infty, R_{in} = \infty, R_{out} = 0 \Rightarrow v_d = 0, \Rightarrow v_- = v_+$$




$$A = \infty, R_{in} = \infty, R_{out} = 0 \Rightarrow i_R = 0 \Rightarrow i_+ = 0, -i_- = 0$$

$$|v_o| < V_{sat} \approx E, \quad |i_o| \lesssim I_{sat}$$

Feedback

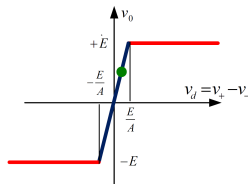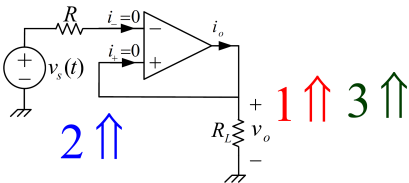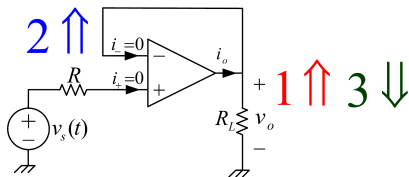Example (Negative and positive feedback)


Negative feedback makes the circuit stable while the circuit will be unstable when the feedback is positive.



Well-known Op-Amp Circuits

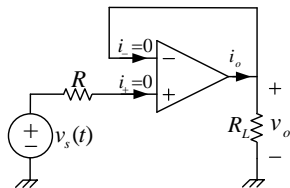Example (Buffer)

A buffer can be implemented using op-amps.



$$v_o(t) = v_-(t) = v_+(t) = v_s(t)$$


$$i_o(t) = \frac{v_o(t)}{R_L}$$

$$|i_o(t)| < I_{sat}, \quad |v_o(t)| < V_{sat} \approx E$$

Inverting Amplifier

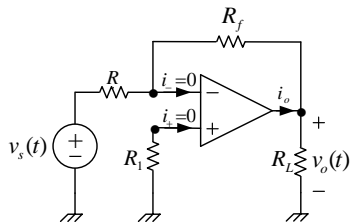Example (Inverting amplifier)

An inverting amplifier can be implemented using op-amps.



$$i_+ = 0 \Rightarrow v_+ = 0 \Rightarrow v_- = 0$$

$$\frac{0 - v_s(t)}{R} + \frac{0 - v_o(t)}{R_f} = 0 \Rightarrow v_o(t) = -\frac{R_f}{R} v_s(t)$$


$$i_o(t) = \frac{v_o(t) - 0}{R_f} + \frac{v_o(t)}{R_L}$$

$$|i_o(t)| < I_{sat}, \quad |v_o(t)| < V_{sat} \approx E$$

Non-inverting Amplifier

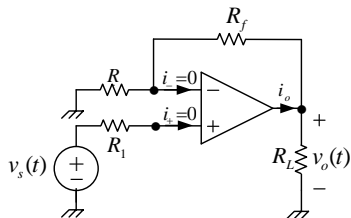Example (Non-inverting amplifier)

A non-inverting amplifier can be implemented using op-amps.



$$i_+ = 0 \Rightarrow v_+ = v_s(t) \Rightarrow v_- = v_s(t)$$

$$\frac{v_s(t) - 0}{R} + \frac{v_s(t) - v_o(t)}{R_f} = 0 \Rightarrow v_o(t) = \left(1 + \frac{R_f}{R}\right)v_s(t)$$


$$i_o(t) = \frac{v_o(t) - v_s(t)}{R_f} + \frac{v_o(t)}{R_L}$$

$$|i_o(t)| < I_{sat}, \quad |v_o(t)| < V_{sat} \approx E$$

Negative Adder

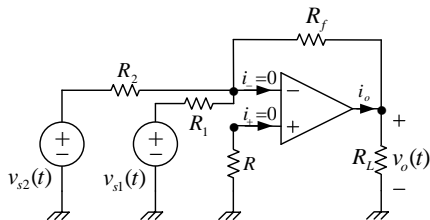Example (Negative adder)

A negative adder can be implemented using op-amps.



$$i_+ = 0 \Rightarrow v_+ = 0 \Rightarrow v_- = 0$$

$$\frac{0 - v_{s1}(t)}{R_1} + \frac{0 - v_{s2}(t)}{R_2} + \frac{0 - v_o(t)}{R_f} = 0 \Rightarrow v_o(t) = -\frac{R_f}{R_1} v_{s1}(t) - \frac{R_f}{R_2} v_{s2}(t)$$


$$i_o(t) = \frac{v_o(t)}{R_f} + \frac{v_o(t)}{R_L}$$

$$|i_o(t)| < I_{sat}, \quad |v_o(t)| < V_{sat} \approx E$$

Positive Adder

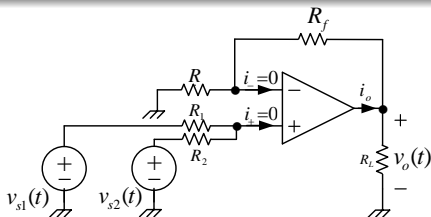Example (Positive adder)

A positive adder can be implemented using op-amps.



$$i_+ = 0 \Rightarrow v_+ = \frac{R_2}{R_1 + R_2} v_{s1}(t) + \frac{R_1}{R_1 + R_2} v_{s2}(t) \Rightarrow v_- = v_+$$

$$\frac{v_-(t) - 0}{R} + \frac{v_-(t) - v_o(t)}{R_f} = 0 \Rightarrow v_o(t) = \left(1 + \frac{R_f}{R}\right) v_-(t)$$


$$v_o(t) = \left(1 + \frac{R_f}{R}\right) \left[\frac{R_2}{R_1 + R_2} v_{s1}(t) + \frac{R_1}{R_1 + R_2} v_{s2}(t) \right]$$

$$i_o(t) = \frac{v_o(t) - v_-(t)}{R_f} + \frac{v_o(t)}{R_L}$$

$$|i_o(t)| < I_{sat}, \quad |v_o(t)| < V_{sat} \approx E$$

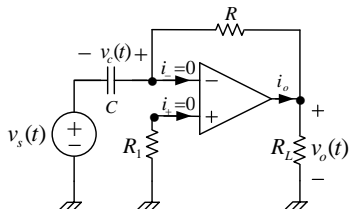Example (Differentiator)

A differentiator can be implemented using op-amps.



$$i_+ = 0 \Rightarrow v_+ = 0 \Rightarrow v_- = 0 \Rightarrow v_c(t) + v_s(t) = 0$$


$$C \frac{dv_c}{dt} + \frac{0 - v_o(t)}{R} = 0 \Rightarrow v_o(t) = -RC \frac{dv_s(t)}{dt}$$

$$i_o(t) = \frac{v_o(t)}{R} + \frac{v_o(t)}{R_L}$$

$$|i_o(t)| < I_{sat}, \quad |v_o(t)| < V_{sat} \approx E$$

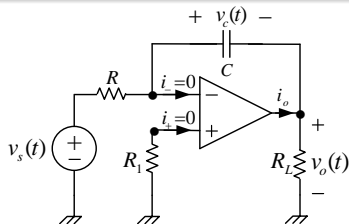Example (Integrator)

An integrator can be implemented using op-amps.



$$i_+ = 0 \Rightarrow v_+ = 0 \Rightarrow v_- = 0 \Rightarrow v_c(t) + v_o(t) = 0$$

$$C \frac{dv_c}{dt} + \frac{0 - v_s(t)}{R} = 0 \Rightarrow C \frac{dv_o}{dt} = -\frac{v_s(t)}{R} \Rightarrow v_o(t) = v_o(0) - \frac{1}{RC} \int_0^t v_s(\lambda) d\lambda$$


$$i_o(t) = \frac{-v_s(t)}{R} + \frac{v_o(t)}{R_L}$$

$$|i_o(t)| < I_{sat}, \quad |v_o(t)| < V_{sat} \approx E$$

Op-Amp Circuits

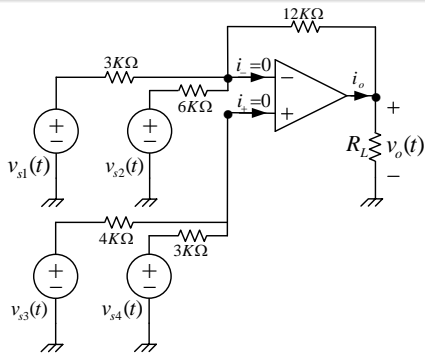Example (Linear voltage combiner)

A linear voltage combiner can be implemented using op-amps.



$$v_-(t) = v_+(t) = \frac{3}{3+4} v_{s3}(t) + \frac{4}{3+4} v_{s4}(t)$$


$$\frac{v_-(t) - v_{s1}(t)}{3} + \frac{v_-(t) - v_{s2}(t)}{6} + \frac{v_-(t) - v_o(t)}{12} = 0$$

$$v_o(t) = -4v_{s1}(t) - 2v_{s2}(t) + 3v_{s3}(t) + 4v_{s4}(t)$$

Op-Amp Circuits

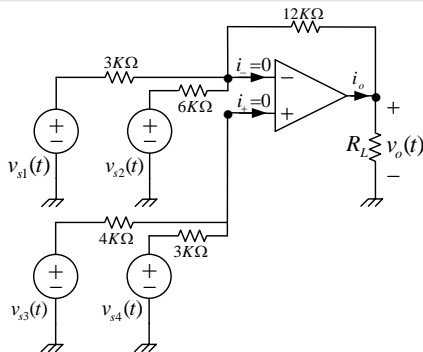Example (Linear voltage combiner (cont.))

A linear voltage combiner can be implemented using op-amps.




$$v_{s1} = 1, v_{s2} = 2, v_{s3} = 3, V_{sat} = 15, I_{sat} = 0.002$$

$$\Rightarrow |v_o| = |-4 \times 1 - 2 \times 2 + 3 \times 3 + 4v_{s4}| < 15 \Rightarrow -4 < v_{s4}(t) < 3.5$$

$$v_{s4} = 3 \in [-4, 3.5] \Rightarrow i_o(t) = \frac{v_o(t) - v_-(t)}{12} + \frac{v_o(t)}{R_L} = \frac{10}{12} + \frac{13}{R_L} < 2 \Rightarrow R_L > 11.143 \text{ k}\Omega$$

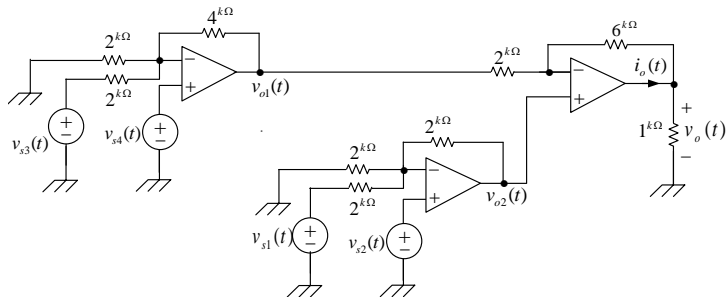Example (Circuit with multiple op-amps)

Op-amp circuits can be interconnected to create complex circuits.



$$\frac{v_{s4}}{2} + \frac{v_{s4} - v_{s3}}{2} + \frac{v_{s4} - v_{o1}}{4} = 0, \quad \frac{v_{s2}}{2} + \frac{v_{s2} - v_{s1}}{2} + \frac{v_{s2} - v_{o2}}{2} = 0$$


$$\frac{v_{o2} - v_{o1}}{2} + \frac{v_{o2} - v_o}{6} = 0, \quad i_o = \frac{v_o - v_{o2}}{6} + \frac{v_o}{1}$$

$$v_o = -4v_{s1} + 12v_{s2} + 6v_{s3} - 15v_{s4}, \quad i_o = -4.5v_{s1} + 13.5v_{s2} + 7v_{s3} - 17.5v_{s4}$$

Op-Amp Circuits

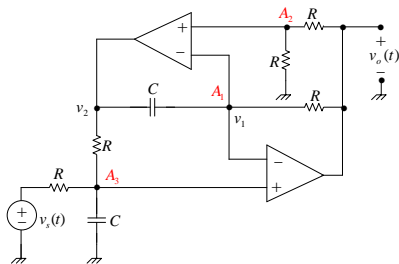Example (Circuit with multiple op-amps)

The step response of the op-amp circuit below has sinusoidal form for $RC = 0.5$.




$$\begin{cases} \frac{v_1(t) - v_o(t)}{R} + C \frac{d(v_1(t) - v_2(t))}{dt} = 0 \\ \frac{v_1(t)}{R} + \frac{v_1(t) - v_o(t)}{R} = 0 \\ \frac{v_1(t) - v_2(t)}{R} + \frac{v_1(t) - v_s(t)}{R} + C \frac{dv_1(t)}{dt} = 0 \end{cases}$$

$$\frac{d^2 v_o(t)}{dt^2} + 2 \frac{dv_o(t)}{dt} + 4v_o(t) = 4 \frac{dv_s}{dt} \Rightarrow s(t) = v_o(t) = \frac{4\sqrt{3}}{3} e^{-t} \sin(\sqrt{3}t) u(t)$$

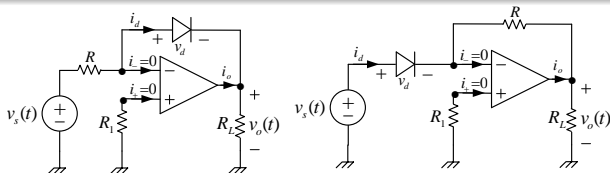Example (Exponential and logarithmic amplifiers)

Exponential and logarithmic amplifiers can be implemented using op-amps.



$$\frac{0 - v_s(t)}{R} + i_d(t) = -\frac{v_s(t)}{R} + I_s \left(e^{\frac{v_d(t)}{V_T}} - 1 \right) \approx -\frac{v_s(t)}{R} + I_s e^{\frac{v_d(t)}{V_T}} = -\frac{v_s(t)}{R} + I_s e^{-\frac{v_o(t)}{V_T}} = 0$$

$$\Rightarrow v_o(t) = -V_T \ln\left(\frac{v_s(t)}{R I_s}\right)$$


$$\frac{0 - v_o(t)}{R} - i_d(t) = -\frac{v_o(t)}{R} - I_s \left(e^{\frac{v_d(t)}{V_T}} - 1 \right) \approx -\frac{v_o(t)}{R} - I_s e^{\frac{v_d(t)}{V_T}} = -\frac{v_o(t)}{R} - I_s e^{\frac{v_s(t)}{V_T}} = 0$$

$$\Rightarrow v_o(t) = -R I_s e^{\frac{v_s(t)}{V_T}}$$

Op-Amp Circuit Synthesis

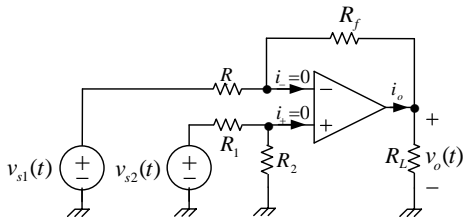Example (Op-Amp Circuit Synthesis)

The op-amp circuit below can implement the equation $v_o = -4v_{s1} + 3v_{s2}$.



$$v_o(t) = -\frac{R_f}{R} v_{s1}(t) + \left(1 + \frac{R_f}{R}\right) \frac{R_2}{R_1 + R_2} v_{s2}(t)$$


$$\frac{R_f}{R} = 4, \quad \left(1 + \frac{R_f}{R}\right) \frac{R_2}{R_1 + R_2} = 3$$

$$R_f = 4R \Rightarrow \frac{R_2}{R_1 + R_2} = \frac{3}{5} \Rightarrow R_2 = 3R, R_1 = 2R$$

Op-Amp Circuit Synthesis

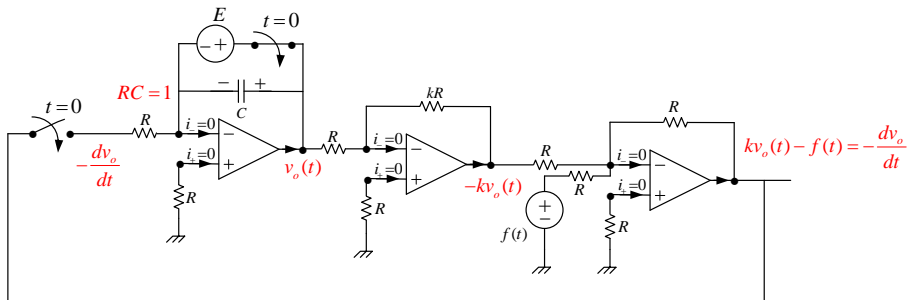Example (Op-Amp Circuit Synthesis)

The op-amp circuit below can solve the differential equation $\frac{dv_o}{dt} + kv_o = f(t)$, $t > 0$; $v_o(0^+) = E$.







$$\frac{dv_o}{dt} + kv_o = f(t) \Rightarrow -\frac{dv_o}{dt} = kv_o - f(t)$$

Negative and Positive Feedback

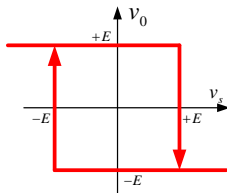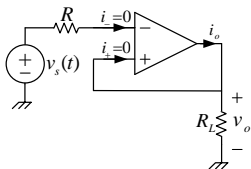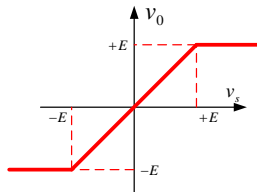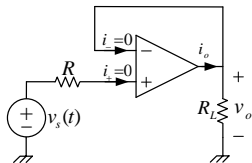Example (Buffer with negative and positive feedback)





Negative and positive feedback lead to completely different behavior in a buffer circuit.



Negative and Positive Feedback

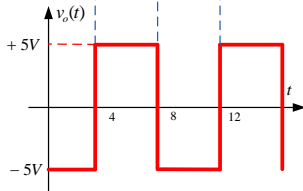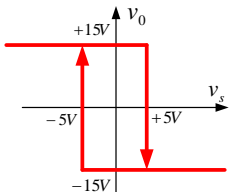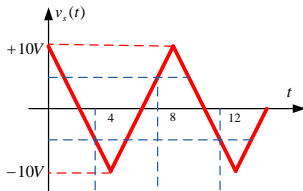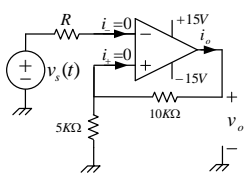Example (Schmitt Trigger)


A Schmitt trigger circuit can be implemented using an op-amp with positive feedback.



Negative and Positive Feedback

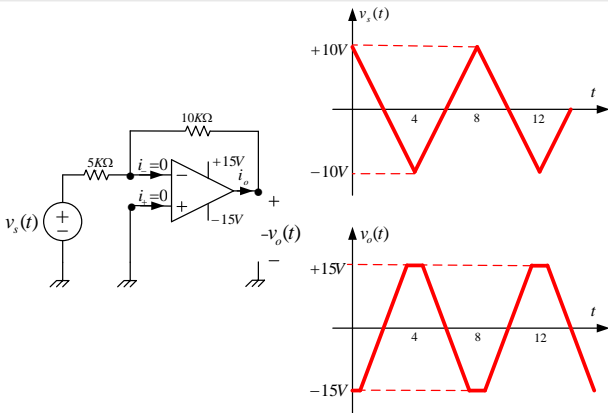Example (Saturated inverting amplifier)

An inverting op-amp amplifier is saturated if the input voltage amplitude is unacceptably high.




$$v_o = -2v_s \Rightarrow |v_o| = 2|v_s| < 15 \Rightarrow |v_s| < 7.5$$

Negative and Positive Feedback

Example (Op-amp without feedback)


An op-amp circuit may have no feedback.

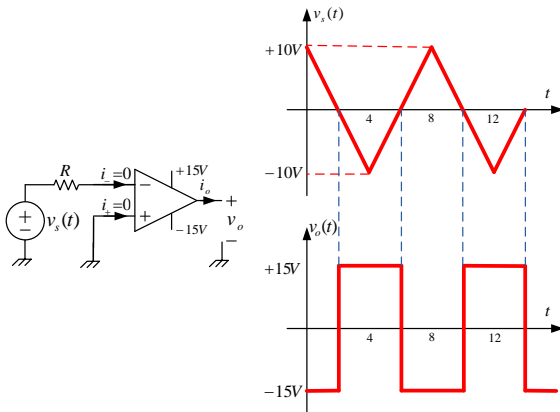

Negative and Positive Feedback

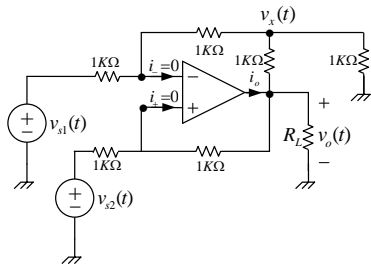Example (Op-amp with negative and positive feedback)

For an op-amp circuit with both positive and negative feedback, the negative feedback is usually assumed dominant.




$$\begin{cases} \frac{v_-(t) - v_{s1}(t)}{1} + \frac{v_-(t) - v_x(t)}{1} = 0 \\ \frac{v_+(t) - v_{s2}(t)}{1} + \frac{v_+(t) - v_o(t)}{1} = 0 \\ \frac{v_x(t) - v_-(t)}{1} + \frac{v_x(t) - v_o(t)}{1} + \frac{v_x(t) - 0}{1} = 0 \\ v_+(t) = v_-(t) \end{cases} \Rightarrow v_o(t) = 2v_{s1}(t) - \frac{5}{3}v_{s2}(t)$$

Amplifiers

Statement (Amplifier Types)


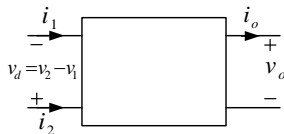
An amplifier can be modeled as a two-port and may have one of the four main types including voltage/voltage, voltage/current, current/voltage, and current/current amplifier.



$$G_{vv} = \frac{v_o}{v_d}, \quad G_{vi} = \frac{i_o}{v_d}, \quad G_{iv} = \frac{v_o}{i_1}, \quad G_{ii} = \frac{i_o}{i_1}$$


Statement (Amplifier Models)

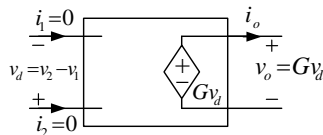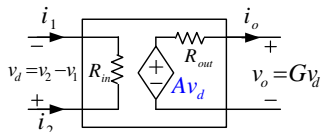An amplifier can be described by its total gain, internal gain, input resistance, and output resistance.



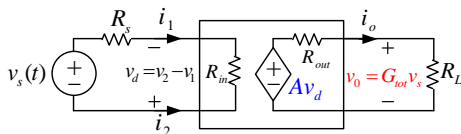Example (Ideal amplifier)

Input and output resistance degrade the amplifier performance.




$$v_o = \frac{R_L}{R_L + R_{out}} A v_d(t) = \frac{R_L}{R_L + R_{out}} A \frac{-R_{in}}{R_{in} + R_s} v_s \Rightarrow G_{tot} = \frac{v_o}{v_s} = - \frac{R_L}{R_L + R_{out}} \frac{R_{in}}{R_{in} + R_s} A$$

$$R_{in} \rightarrow \infty, R_o \rightarrow 0 \Rightarrow G_{tot} = -A$$

Amplifier Feedback

Statement (Negative Feedback)

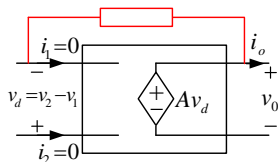Negative feedback can be used to stabilize the total gain for an amplifier with high internal gain, high input resistance, and low output resistance.



$$A \rightarrow \infty, R_{in} \rightarrow \infty, R_o \rightarrow 0$$

The End