

Question 1

A capacitor is described by the characteristic curve $\ln(v^2) + \sinh^{-1}(\frac{q}{v^2}) = 0$.

(a) *Is the capacitor linear?*

(b) *Is the capacitor time-invariant?*

(c) *Is the capacitor voltage-controlled?*

(d) *Is the capacitor charge-controlled?*

(e) *Is the capacitor passive?*

(f) *Find the voltage-current equation of the capacitor.*

(g) *Calculate the absorbed power of the capacitor.*

(h) *Calculate the absorbed energy of the capacitor during the time interval $[0, t]$.*