

### Question 1

Consider the circuit shown in Fig. 1, where  $i_s(t)$  is a positive-value bounded signal and diode is ideal.

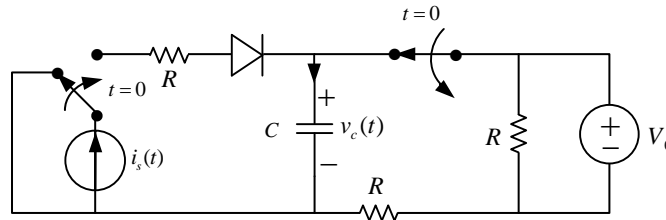


Figure 1: A circuit with a capacitor.

(a) Find an expression for the capacitor voltage  $v_c(t)$  valid for all time  $t$ .

(b) Find the steady state response of  $v_c(t)$  when  $i_s(t) = 1$ .

(c) Find the steady state response of  $v_c(t)$  when  $i_s(t) = e^{-t}$ .

### Question 2

Find an expression for  $i_C(t), t > 1$  in Fig. 2, where

1. The resistor is LTV with the resistance  $R(t) = t$ .
2. The inductor is LTV with the inductance  $L(t) = t^2$ .
3. The capacitor is LTI with the capacitance  $C = 1$ .
4. The voltage source is  $v_s(t) = t, t > 1$ .
5. The initial conditions are  $v_C(1^+) = 0$  and  $i_L(1^+) = 0$ .

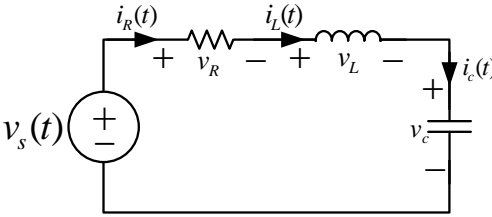


Figure 2: A second-order circuit.



Mohammad Hadi