

Question 1

Consider the circuit shown in Fig. 1, where $i_s(t)$ is a positive-value bounded signal and diode is ideal.

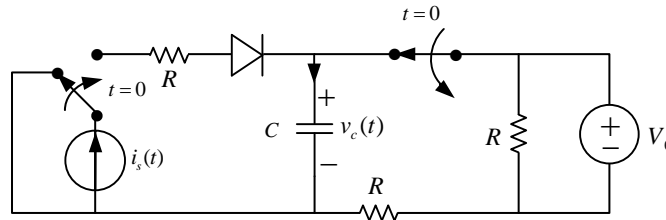


Figure 1: A circuit with a capacitor.

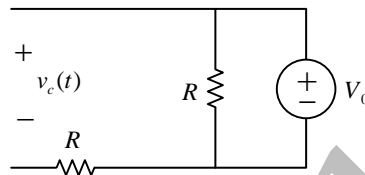


Figure 2: The circuit of Fig. 1 for $t < 0$.

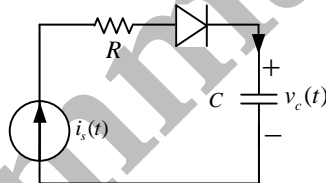


Figure 3: The circuit of Fig. 1 for $t > 0$.

(a) Find an expression for the capacitor voltage $v_c(t)$ valid for all time t .

For $t < 0$, the capacitor is fully charged by the DC voltage source and gets the voltage $v_c(t) = V_0, t < 0$, as shown in Fig. 2. Clearly, $v_c(0^-) = V_0$. The circuit for $t > 0$ is shown in Fig. 3. A discontinuity in the capacitor voltage at $t = 0$ leads to an impulse in the capacitor current and cannot be supplied by the bounded signal $i_s(t)$. So, $v_c(0^+) = v_c(0^-) = V_0$. Now, for $t > 0$,

$$v_c(t) = v_c(0^+) + \frac{1}{C} \int_{0^+}^t i_s(\lambda) d\lambda = V_0 + \frac{1}{C} \int_0^t i_s(\lambda) d\lambda$$

Note that the diode acts like a short circuit as long as $i_s(t) > 0$.

(b) Find the steady state response of $v_c(t)$ when $i_s(t) = 1$.

We have,

$$v_c(t) = V_0 + \frac{1}{C} \int_{0^+}^t i_s(\lambda) d\lambda = V_0 + \frac{1}{C} \int_{0^+}^t d\lambda = V_0 + \frac{t}{C}$$

Clearly, $v_c(t)$ has no steady state response since $v_c(\infty) = \infty$.

(c) Find the steady state response of $v_c(t)$ when $i_s(t) = e^{-t}$.

We have,

$$v_c(t) = V_0 + \frac{1}{C} \int_{0^+}^t i_s(\lambda) d\lambda = V_0 + \frac{1}{C} \int_{0^+}^t e^{-\lambda} d\lambda = V_0 + \frac{1 - e^{-t}}{C}$$

Clearly, $v_c(t)$ approaches the steady state constant value of $V_0 + \frac{1}{C}$ as time proceeds.

Question 2

Find an expression for $i_C(t), t > 1$ in Fig. 4, where

1. The resistor is LTV with the resistance $R(t) = t$.
2. The inductor is LTV with the inductance $L(t) = t^2$.
3. The capacitor is LTI with the capacitance $C = 1$.
4. The voltage source is $v_s(t) = t, t > 1$.
5. The initial conditions are $v_C(1^+) = 0$ and $i_L(1^+) = 0$.

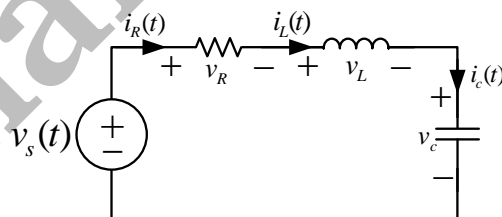


Figure 4: A second-order circuit.

Writing a KVL for the circuit loop,

$$v_R(t) + v_L(t) + v_C(t) = R(t)i_R(t) + L(t)\frac{di_L(t)}{dt} + i_L(t)\frac{dL(t)}{dt} + v_C(1^+) + \frac{1}{C} \int_{1^+}^t i_C(\lambda) d\lambda = v_s(t)$$

Since $i_R(t) = i_L(t) = i_C(t)$,

$$ti_C(t) + t^2 \frac{di_C(t)}{dt} + 2ti_C(t) + v_C(1^+) + \int_{1^+}^t i_C(\lambda) d\lambda = t, t > 1$$

Taking the time derivative of the equation,

$$i_C(t) + t \frac{di_C(t)}{dt} + 2t \frac{di_C(t)}{dt} + t^2 \frac{d^2i_C(t)}{dt^2} + 2i_C(t) + 2t \frac{di_C(t)}{dt} + i_C(t) = 1, t > 1$$

$$t^2 \frac{d^2i_C(t)}{dt^2} + 5t \frac{di_C(t)}{dt} + 4i_C(t) = 1, t > 1$$

This is a non-homogeneous Euler differential equation with the characteristic equation

$$m^2 + (5 - 1)m + 4 = 0 \Rightarrow m = -2, -2$$

The solution is of the form

$$i_C(t) = K_1 t^{-2} + K_2 t^{-2} \ln(t) + \frac{1}{4}, t > 1$$

Initial conditions give $i_C(1^+) = i_L(1^+) = 0$ and

$$i_C(1^+) + \frac{di_C(t)}{dt} \Big|_{t=1^+} + 2i_C(1^+) + v_C(1^+) + \int_{1^+}^{1^+} i_C(\lambda) d\lambda = 1 \Rightarrow \frac{di_C(t)}{dt} \Big|_{t=1^+} = 1$$

So,

$$i_C(1^+) = K_1 + \frac{1}{4} = 0 \Rightarrow K_1 = -\frac{1}{4} \Rightarrow i_C(t) = -\frac{1}{4} t^{-2} + K_2 t^{-2} \ln(t) + \frac{1}{4},$$

$$i'_C(t) = \frac{1}{2} t^{-3} - 2K_2 t^{-3} \ln(t) + K_2 t^{-2} \frac{1}{t} \Rightarrow i'_C(1^+) = K_2 + \frac{1}{2} = 1 \Rightarrow K_2 = \frac{1}{2}$$

Finally,

$$i_C(t) = -\frac{1}{4} t^{-2} + \frac{1}{2} t^{-2} \ln(t) + \frac{1}{4}, t > 1$$