

Question 1

Calculate the steady state average power consumed by the resistor in the series RC circuit shown in Fig. 1.

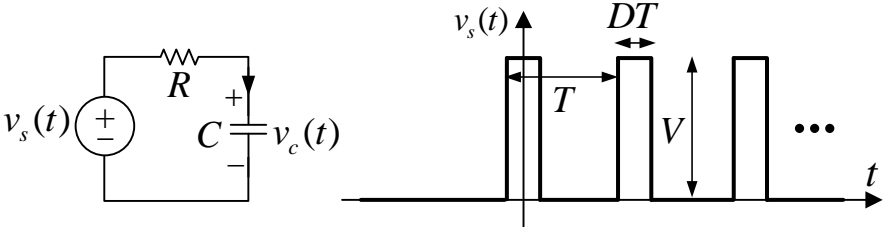


Figure 1: A series RC circuit.

Mohammad Hadi