

### Question 1

Calculate the steady state average power consumed by the resistor in the series RC circuit shown in Fig. 1.

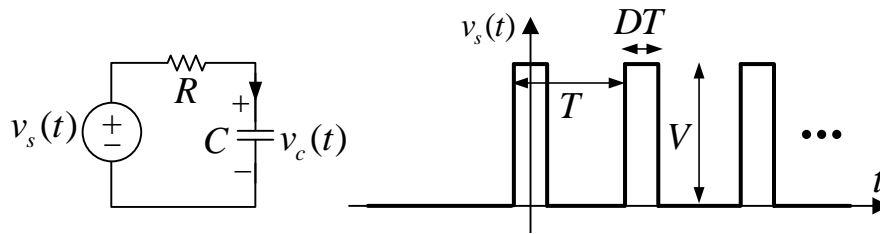


Figure 1: A series RC circuit.

The circuit is derived with  $v_s(t) = v_p(t)u(t)$ , where  $v_p(t)$  is an even periodic pulse having the Fourier series

$$v_p(t) = a_0 + \sum_{n=1}^{\infty} a_n \cos(n\frac{2\pi}{T}t) = AD + \sum_{n=1}^{\infty} \frac{2A}{n\pi} \sin(n\pi D) \cos(n\frac{2\pi}{T}t)$$

So, the circuit is derived with a linear combination of the sinusoidal signals with different frequencies. For a sinusoidal signal  $v_{sin}(t)$  with the frequency  $\omega$ ,

$$H(j\omega) = \frac{V_R}{V_{sin}} = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega RC}{j\omega RC + 1}$$

Because the circuit is LTI, the resistor voltage equals

$$v_R(t) = a_0 |H(j0)| \cos(0t + \angle H(j0)) + \sum_{n=1}^{\infty} a_n |H(jn\frac{2\pi}{T})| \cos(n\frac{2\pi}{T}t + \angle H(jn\frac{2\pi}{T}))$$

Since the sinusoidal components in the resistor voltage have different frequencies, the average power can be found using superposition as

$$P_{avR} = \frac{a_0^2 |H(j0)|^2 \cos^2(\angle H(j0))}{R} + \sum_{n=1}^{\infty} \frac{a_n^2 |H(jn\frac{2\pi}{T})|^2}{2R}$$

$$P_{avR} = 0 + \sum_{n=1}^{\infty} \frac{a_n^2}{2R} \frac{R^2 C^2 (n\frac{2\pi}{T})^2}{1 + R^2 C^2 (n\frac{2\pi}{T})^2} = \sum_{n=1}^{\infty} \frac{8A^2 RC^2 \sin^2(n\pi D)}{T^2 + 4R^2 C^2 n^2 \pi^2}$$