

Simple Circuits

Mohammad Hadi

mohammad.hadi@sharif.edu

@MohammadHadiDastgerdi

Spring 2022

Overview

- 1 Simple Circuits
- 2 Interconnection Conversion
- 3 Voltage/Current Divider
- 4 Source Transformation
- 5 Circuit Symmetry
- 6 Node/Mesh Analysis
- 7 Thevenin/Norton Equivalent Circuits
- 8 Superposition
- 9 Small Signal Analysis
- 10 Circuits with Ideal Diodes

Simple Circuits

Circuit Types

Statement (Linear Circuit)

A linear circuit is a circuit that includes linear elements and/or independent sources.

Statement (LTI Circuit)

An LTI circuit is a circuit that includes LTI elements and/or independent sources.

Statement (Simple Circuit)

A simple circuit is a circuit that includes LTI resistors, linear dependent sources, and independent sources.

- Linear resistors, linear capacitors, linear inductors, linear dependent sources, ... are **linear elements**.

Definition (Circuit Variables)

Branch currents and branch voltages in a given circuit are called circuit variables.

Definition (Circuit Analysis)


The circuit analysis problem is to determine all or part of the circuit variables for a circuit.

Interconnection Conversion

Interconnection Conversion

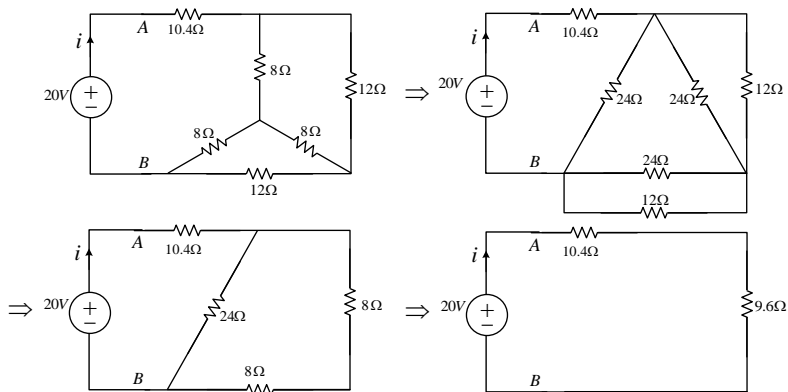Example (Δ/Y /series/parallel conversions)

Interconnection conversions can be used to demonstrate that $i = 1$ A in the circuit below.



Voltage/Current Divider

Voltage/Current Divider

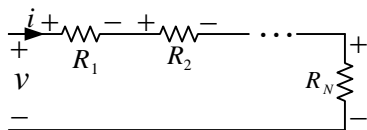


Figure: Resistive voltage divider circuit.

$$v_k = R_k i_k = R_k i = R_k \frac{v}{\sum_{k=1}^N R_k} = \frac{R_k}{\sum_{k=1}^N R_k} v$$

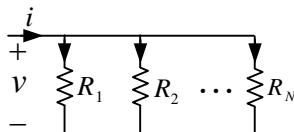



Figure: Resistive current divider circuit.

$$i_k = G_k v_k = G_k v = G_k \frac{i}{\sum_{k=1}^N G_k} = \frac{G_k}{\sum_{k=1}^N G_k} i$$

Maximum Power Transfer

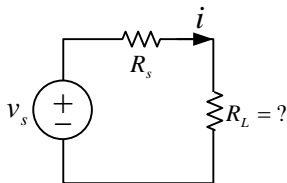Example (Maximum power transfer)

In the resistive circuit below, the maximum power is delivered to the load if $R_L = R_s$.



$$v_L = \frac{R_L}{R_s + R_L} v_s \Rightarrow P_L = \frac{v_L^2}{R_L} = \frac{R_L}{(R_s + R_L)^2} v_s^2$$

$$\frac{dP_L}{dR_L} = 0 \Rightarrow R_L = R_s, P_{L_{max}} = \frac{v_s^2}{4R_s}$$

Source Transformation

Source Transformation

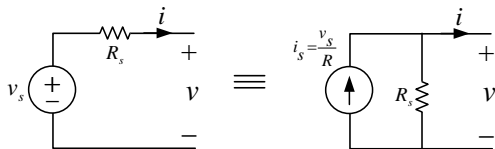


Figure: Independent **source transformation**.

$$v = v_s - Ri \Rightarrow i = \frac{v_s}{R} - \frac{v}{R}$$

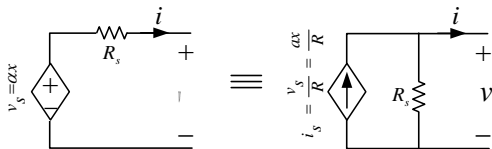



Figure: Dependent **source transformation**.

$$v = v_s - Ri \Rightarrow i = \alpha x - Ri \Rightarrow i = \frac{v_s}{R} - \frac{\alpha x}{R} = \frac{v_s}{R} - \frac{v_s}{R}$$

Maximum Power Transfer

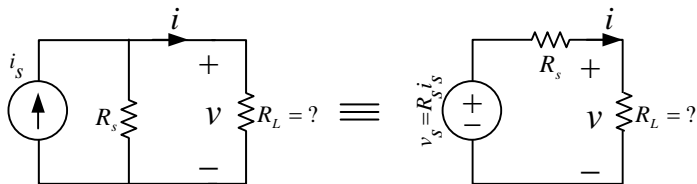Example (Maximum power transfer)

In the resistive circuit below, the maximum power is delivered to the load if $R_L = R_S$.




Circuit Symmetry

Circuit Symmetry

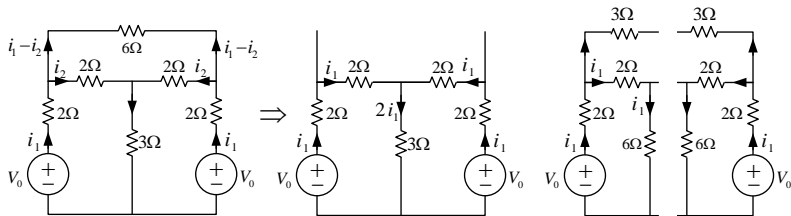Example (Positive Circuit Symmetry)

Circuit symmetry can facilitate circuit analysis.




$$i_1 = \frac{V_0}{2 + 2 + 6} = \frac{V_0}{10}$$

Circuit Symmetry

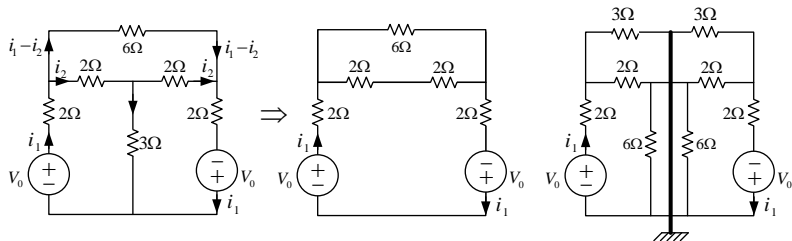Example (Negative Circuit Symmetry)

Circuit symmetry can facilitate circuit analysis.




$$i_1 = \frac{V_0}{2 + 2 \parallel 3} = \frac{V_0}{3.2}$$

Circuit Symmetry

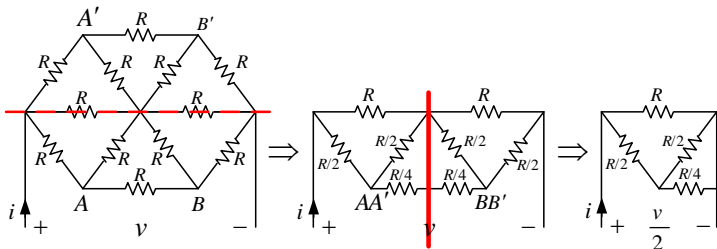Example (Circuit Symmetry)

Circuit symmetry can facilitate circuit analysis.



$$\frac{v/2}{i} = \left(\frac{R}{4} \parallel \frac{R}{2} + \frac{R}{2} \right) \parallel R = \frac{2}{5}R \Rightarrow R_{in} = \frac{v}{i} = \frac{4}{5}R$$


Node/Mesh Analysis

Node Analysis

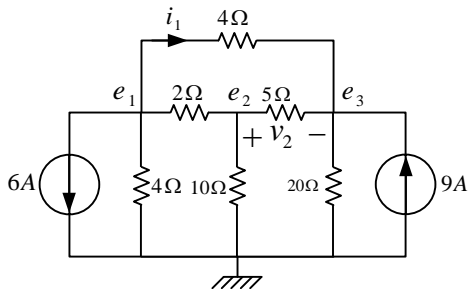Example (Simple node analysis)

In the circuit below, $v_2 = -15$ V and $i_1 = -4.825$ A.

$$\begin{cases} 6 + \frac{e_1}{4} + \frac{e_1 - e_2}{2} + \frac{e_1 - e_3}{4} = 0 \\ \frac{e_2 - e_1}{2} + \frac{e_2}{10} + \frac{e_2 - e_3}{5} = 0 \\ \frac{e_3 - e_1}{4} + \frac{e_3 - e_2}{5} + \frac{e_3}{20} - 9 = 0 \end{cases}$$
$$\Rightarrow \begin{bmatrix} 1 & -0.5 & -0.25 \\ -0.5 & 0.8 & -0.2 \\ -0.25 & -0.2 & 0.5 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix} = \begin{bmatrix} -6 \\ 0 \\ 9 \end{bmatrix}$$
$$\Rightarrow \begin{cases} e_1 = 4 \\ e_2 = 8.3 \\ e_3 = 23.3 \end{cases}$$
$$\Rightarrow \begin{cases} i_1 = \frac{e_1 - e_3}{4} = -4.825 \\ v_2 = e_2 - e_3 = -15 \end{cases}$$




Node Analysis

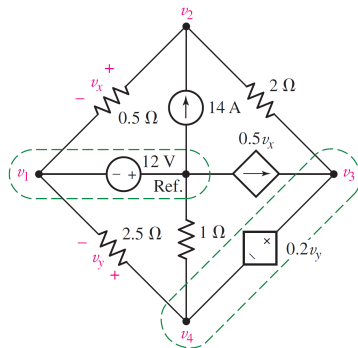Example (Node analysis with supernode)

In the circuit below, $v_1 = -12$ V, $v_2 = -4$ V, $v_3 = 0$ V, and $v_4 = -2$ V.

$$\Rightarrow \left\{ \begin{array}{l} v_1 = -12 \\ v_3 - v_4 = 0.2v_y \\ \frac{v_1 - v_2}{0.5} + \frac{v_3 - v_2}{2} + 14 = 0 \\ \frac{v_1 - v_4}{2.5} + \frac{-v_4}{1} + \frac{v_2 - v_3}{2} + 0.5v_x = 0 \end{array} \right.$$
$$\Rightarrow \left\{ \begin{array}{l} v_1 = -12 \\ v_3 - v_4 = 0.2v_4 - 0.2v_1 \\ \frac{v_1 - v_2}{0.5} + \frac{v_3 - v_2}{2} + 14 = 0 \\ \frac{v_1 - v_4}{2.5} + \frac{-v_4}{1} + \frac{v_2 - v_3}{2} + 0.5(v_2 - v_1) = 0 \end{array} \right.$$



Nodal Analysis


Example (Node analysis with supernode (cont.))

In the circuit below, $v_1 = -12$ V, $v_2 = -4$ V, $v_3 = 0$ V, and $v_4 = -2$ V.

$$\Rightarrow \begin{cases} -2v_1 + 2.5v_2 - 0.5v_3 & = 14 \\ 0.1v_1 - v_2 + 0.5v_3 + 1.4v_4 & = 0 \\ v_1 & = -12 \\ 0.2v_1 + v_3 - 1.2v_4 & = 0 \end{cases}$$

$$\Rightarrow \begin{bmatrix} -2 & 2.5 & -0.5 & 0 \\ 0.1 & -1 & 0.5 & 1.4 \\ 1 & 0 & 0 & 0 \\ 0.2 & 0 & 1 & -1.2 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} 14 \\ 0 \\ -12 \\ 0 \end{bmatrix}$$
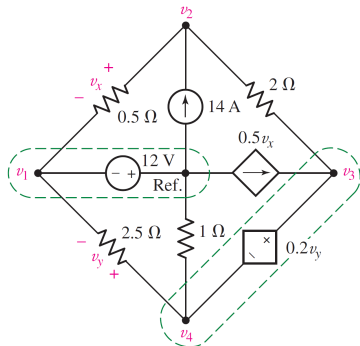
$$\Rightarrow v_2 = \frac{\begin{vmatrix} -2 & 14 & -0.5 & 0 \\ 0.1 & 0 & 0.5 & 1.4 \\ 1 & -12 & 0 & 0 \\ 0.2 & 0 & 1 & -1.2 \end{vmatrix}}{\begin{vmatrix} -2 & 2.5 & -0.5 & 0 \\ 0.1 & -1 & 0.5 & 1.4 \\ 1 & 0 & 0 & 0 \\ 0.2 & 0 & 1 & -1.2 \end{vmatrix}} = -4$$



Node Analysis

Node analysis procedures:

- 1 Count the number of nodes (N nodes).
 - 2 Designate a **reference node** (usually, a **high-degree node**).
 - 3 **Label** the nodal voltages ($N - 1$ labels).
 - 4 Form a **supernode** about each voltage source and relate its voltage to nodal voltages.
 - 5 Write a **KCL equation** for each nonreference node and for each supernode that does not contain the reference node. Use **element equations** to express the currents in terms of nodal voltages.
 - 6 Express any additional unknowns in terms of appropriate nodal voltages (occurs for **dependent sources**).
 - 7 **Organize** the equations.
 - 8 Solve the system of equations for the nodal voltages ($N - 1$ equations).
- ✓ **Handy** node analysis: appropriate the circuits with a **low number of nodes**.

Mesh Analysis

Example (Simple mesh analysis)


In the circuit below, $i_x = 0$ A and $v_y = 1$ V.

$$\begin{cases} -7 + 1(i_1 - i_2) + 6 + 2(i_1 - i_3) = 0 \\ 1(i_2 - i_1) + 2(i_2) + 3(i_2 - i_3) = 0 \\ 2(i_3 - i_1) - 6 + 3(i_3 - i_2) + 1(i_3) = 0 \end{cases}$$

$$\Rightarrow \begin{bmatrix} 3 & -1 & -2 \\ -1 & 6 & -3 \\ -2 & -3 & 6 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \\ 6 \end{bmatrix}$$

$$\Rightarrow \begin{cases} i_1 = 3 \\ i_2 = 2 \\ i_3 = 3 \end{cases}$$
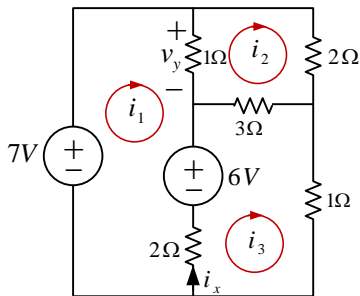
$$\Rightarrow \begin{cases} i_x = i_3 - i_1 = 0 \\ v_y = 1(i_1 - i_2) = 1 \end{cases}$$



Mesh Analysis

Example (Mesh analysis with supermesh)


In the circuit below, $i_1 = 9$ A, $i_2 = 2.5$ A, and $i_3 = 2$ A.

$$\begin{cases} i_1 - i_3 = 7 \\ (i_2 - i_1) + 2i_2 + 3(i_2 - i_3) = 0 \\ (i_1 - i_2) + 3(i_3 - i_2) + (i_3) - 7 = 0 \end{cases}$$

$$\Rightarrow \begin{cases} i_1 - i_3 = 7 \\ -i_1 + 6i_2 - 3i_3 = 0 \\ i_1 - 4i_2 + 4i_3 = 7 \end{cases}$$

$$\Rightarrow \begin{bmatrix} 1 & 0 & -1 \\ -1 & 6 & -3 \\ 1 & -4 & 4 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 7 \\ 0 \\ 7 \end{bmatrix}$$
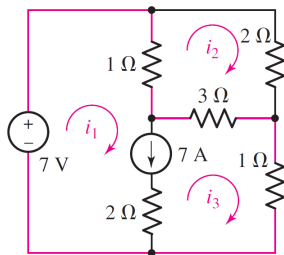
$$\Rightarrow i_2 = \frac{\begin{vmatrix} 1 & 7 & -1 \\ -1 & 0 & -3 \\ 1 & 7 & 4 \end{vmatrix}}{\begin{vmatrix} 1 & 0 & -1 \\ -1 & 6 & -3 \\ 1 & -4 & 4 \end{vmatrix}} = 2.5$$



Mesh analysis procedures:

- 1 Make sure that the circuit is **planar**.
 - 2 Count the number of meshes (M meshes).
 - 3 **Label** the mesh currents (M labels).
 - 4 Form a **supermesh** to enclose the meshes shares a current source and relate its current to mesh currents.
 - 5 Write a **KVL** equation around each mesh and supermesh. Use **element equations** to express the voltages in terms of mesh currents.
 - 6 Express any additional unknowns in terms of appropriate mesh currents (occurs for **dependent sources**).
 - 7 **Organize** the equations.
 - 8 **Solve** the system of equations for the mesh currents (M equations).
- ✓ **Handy** mesh analysis: appropriate the for the **planar** circuits with a **low number of meshes**.

Thevenin/Norton Equivalent Circuits

Thevenin/Norton Equivalent Circuits

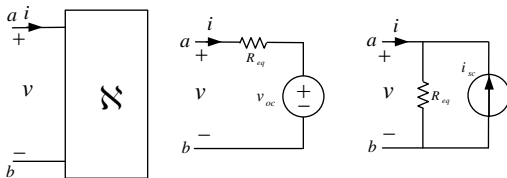


Figure: Any linear one-port can be replaced with its equivalent Thevenin or Norton one-port.

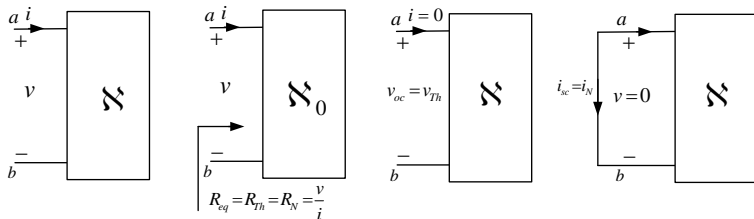


Figure: Open circuit voltage, short circuit current, and equivalent resistor are related by $v_{oc} = R_{eq} i_{sc}$.


Thevenin/Norton Equivalent Circuits

Example (Thevenin/Norton equivalent circuits)

In the circuit below, $v_{oc} = 4\text{ V}$, $i_{sc} = \frac{4}{3}\text{ A}$, and $R_{eq} = 3\ \Omega$.

$$2(3 - i_1) = -40 + 2i_1 \Rightarrow i_1 = \frac{23}{2}$$

$$v_{oc} = -2(4) - 5 - 2i_1 + 40 = 4$$

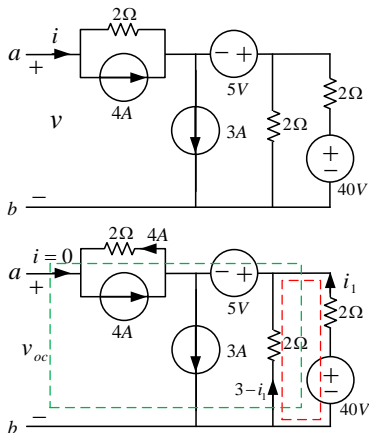



Thevenin/Norton Equivalent Circuits

Example (Thevenin/Norton equivalent circuits (cont.))

In the circuit below, $v_{oc} = 4\text{ V}$, $i_{sc} = \frac{4}{3}\text{ A}$, and $R_{eq} = 3\ \Omega$.

$$\begin{cases} 2(3 - i_1 - i) = -40 + 2i_1 \Rightarrow i_1 = \frac{23}{2} \\ -2(4 - i) - 5 - 2i_1 + 40 = 0 \end{cases}$$

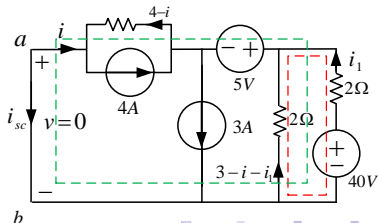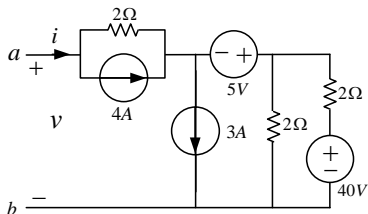
$$\Rightarrow i = -\frac{4}{3} \Rightarrow i_{sc} = \frac{4}{3}$$




Thevenin/Norton Equivalent Circuits

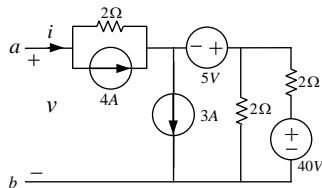Example (Thevenin/Norton equivalent circuits (cont.))

In the circuit below, $v_{oc} = 4\text{ V}$, $i_{sc} = \frac{4}{3}\text{ A}$, and $R_{eq} = 3\ \Omega$.



$$R_{eq} = 2 + (2||2) = 3$$

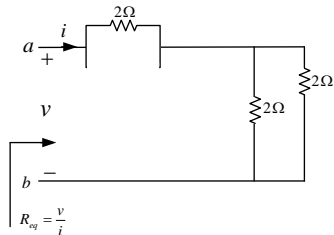

Thevenin/Norton Equivalent Circuits



Example (Thevenin/Norton equivalent circuits (cont.))

In the circuit below, $v_{oc} = 4\text{ V}$, $i_{sc} = \frac{4}{3}\text{ A}$, and $R_{eq} = 3\ \Omega$.

$$v_{oc} = 4$$

$$i_{sc} = \frac{4}{3}$$

$$R_{eq} = 3$$

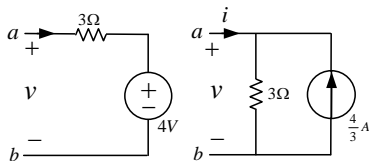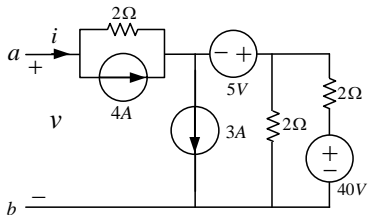

Thevenin/Norton Equivalent Circuits


Example (Thevenin/Norton equivalent circuits)

In the circuit below, $v_{oc} = 4\text{ V}$, $i_{sc} = \frac{4}{3}\text{ A}$, and $R_{eq} = 3\ \Omega$.

$$2(3 - i_1 - i) = -40 + 2i_1 \Rightarrow i_1 = \frac{23 - i}{2}$$

$$v = -2(4 - i) - 5 - 2i_1 + 40 = 3i + 4$$

$$i = \frac{1}{3}v - \frac{4}{3}$$

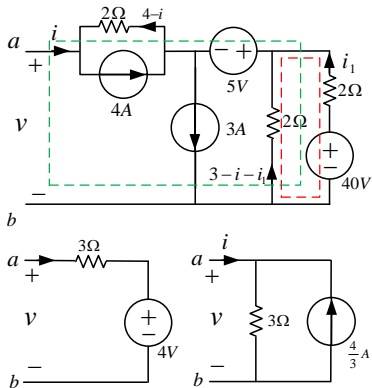


Thevenin/Norton Equivalent Circuits

Example (Thevenin/Norton equivalent circuits)

In the circuit below, $v_{oc} = \frac{10}{3}$ V, $i_{sc} = 20$ A, and $R_{eq} = \frac{1}{6}$ Ω .

$$i_1 + i_1 = 20 \Rightarrow i_1 = 10$$
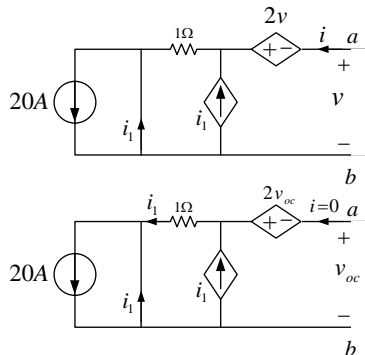
$$v_{oc} = -2v_{oc} + i_1 + 0 \Rightarrow v_{oc} = \frac{10}{3}$$



Thevenin/Norton Equivalent Circuits


Example (Thevenin/Norton equivalent circuits (cont.))

In the circuit below, $v_{oc} = \frac{10}{3}$ V, $i_{sc} = 20$ A, and $R_{eq} = \frac{1}{6}$ Ω .

$$i_1 = 20 \Rightarrow i_{sc} = i_1 = 20$$

$$i_1 + i_1 + i = 0 \Rightarrow i_1 = \frac{i}{2}$$

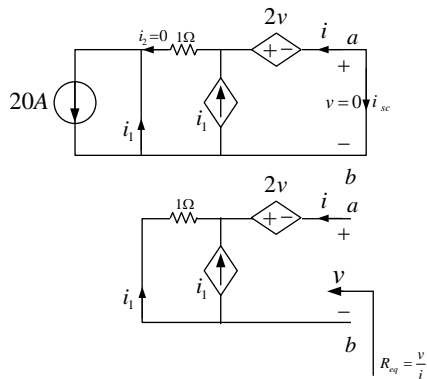
$$v = -2v - i_1 = -2v + \frac{i}{2} \Rightarrow R_{eq} = \frac{v}{i} = \frac{1}{6}$$



Thevenin/Norton Equivalent Circuits

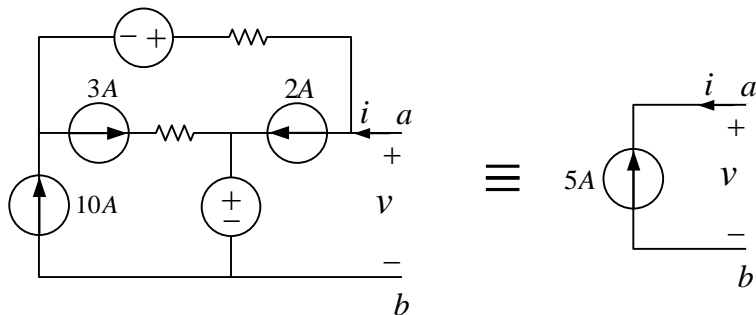Example (Norton equivalent circuits)


For the circuit below, $i_{sc} = 5 \text{ A}$ and $R_{eq} = \infty \Omega$ and therefore, only Norton equivalent circuit exists.



Thevenin/Norton Equivalent Circuits

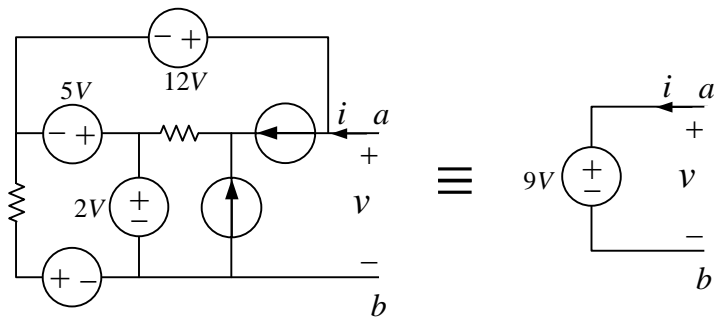Example (Thevenin equivalent circuits)


For the circuit below, $v_{oc} = 9\text{ V}$ and $R_{eq} = 0\ \Omega$ and therefore, only Thevenin equivalent circuit exists.



Thevenin/Norton Equivalent Circuits

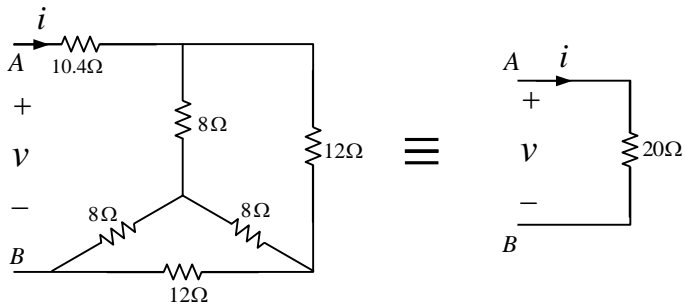Example (Thevenin equivalent circuits)

For the circuit below, $R_{eq} = 20 \Omega$ and therefore, the Thevenin/Norton equivalent circuit includes only a resistor.



Superposition

Superposition

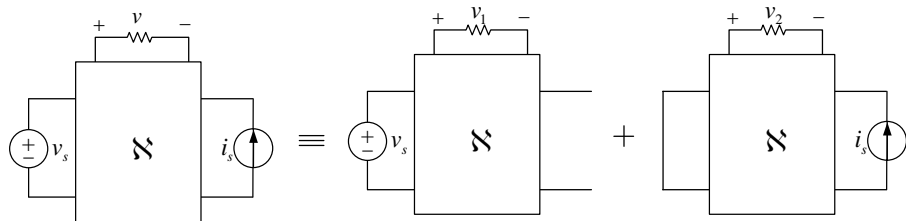


Figure: For any **linear circuit**, the **voltage across** or the **current through** any element may be calculated by **adding** algebraically all the **individual voltages** or **currents** caused by the **separate independent sources** acting alone, with all other **independent voltage sources** replaced by **short circuits** and all other **independent current sources** replaced by **open circuits**.

Superposition

Example (Superposition)





Superposition can facilitate circuit analysis.

$$v_1 = \frac{6 \parallel 6}{6 \parallel 6 + 6} 18 = 6$$

$$iv_2 = 6 \frac{1/6}{1/6 + 1/6 + 1/6} 30 = 60$$

$$v_3 = \frac{6 \parallel 6}{6 \parallel 6 + 6} 27 = 9$$

$$v = v_1 + v_2 + v_3 = 75$$

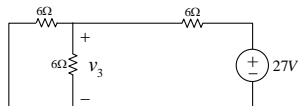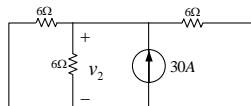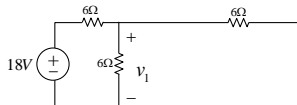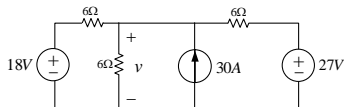


Small Signal Analysis

Operating Point

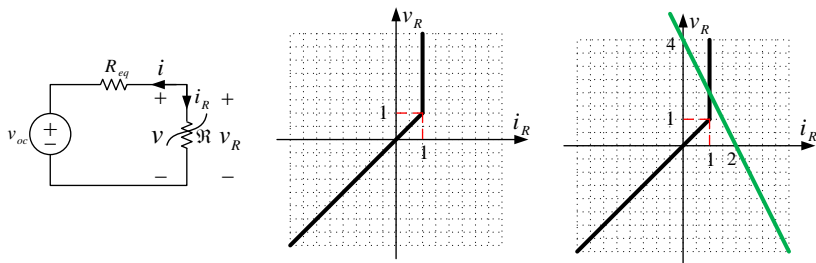Example (Operating Point)

Thevenin equivalent circuit can facilitate analysis of a circuit with a single nonlinear element.



$$v_{oc} = 4, R_{eq} = 2 \Rightarrow v = V_{oc} + R_{eq}i = 4 + 2i$$

$$v = 2i + 4 \Rightarrow v_R = -2i_R + 4 \Rightarrow i_R = 1, v_R = 2$$

Small-signal Analysis


Example (Small-signal analysis)

Circuits with nonlinear elements can be investigated using small-signal analysis.

$$|v_s(t)| \ll E$$

$$\begin{cases} v(t) = -R_s i(t) + E \\ i(t) = f(v(t)) \end{cases}$$
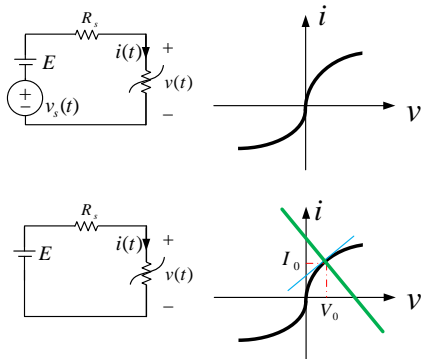
$$\Rightarrow \begin{cases} v(t) = V_0 = -R_s I_0 + E \\ i(t) = I_0 = f(V_0) \end{cases}$$



Small-signal Analysis

Example (Small-signal analysis (cont.))

Circuits with nonlinear elements can be investigated using small-signal analysis.





$$|v_s(t)| \ll E$$

$$\begin{cases} V_0 + v_1(t) = -R_s(i_0 + i_1(t)) + E + v_s(t) \\ i_0 + i_1(t) = f(V_0 + v_1(t)) \end{cases}$$

$$\Rightarrow \begin{cases} V_0 + v_1(t) = -R_s(i_0 + i_1(t)) + E + v_s(t) \\ i_0 + i_1(t) \approx f(V_0) + \left. \frac{df}{dv} \right|_{(V_0, I_0)} v_1(t) \end{cases}$$

$$\Rightarrow \begin{cases} v_1(t) = -R_s i_1(t) + v_s(t) \\ i_1(t) \approx \frac{1}{R_0} v_1(t) \end{cases}$$

$$\Rightarrow \begin{cases} v_1(t) = -R_s i_1(t) + v_s(t) \\ i_1(t) \approx \frac{1}{R_0} v_1(t), G_0 = \frac{1}{R_0} = \left. \frac{df}{dv} \right|_{(V_0, I_0)} \end{cases}$$

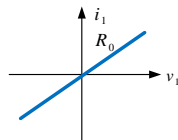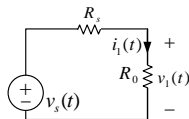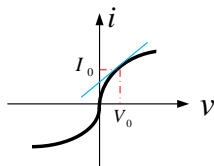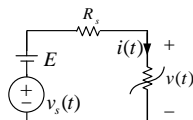

Circuits with Ideal Diodes

Circuits with Ideal Diodes


Example (Circuits with ideal diodes)

In circuits with ideal diodes, the circuit should be analyzed for various configurations of diodes.

$$i = 0$$

$$v_{D_1} = v - 2 \leq 0 \Rightarrow v \leq 2$$
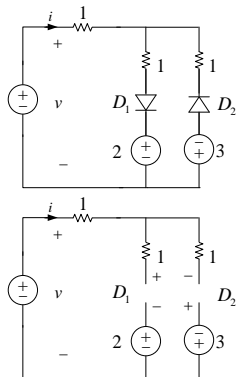
$$v_{D_2} = -v - 3 \leq 0 \Rightarrow v \geq -3$$



Circuits with Ideal Diodes



Example (Circuits with ideal diodes (cont.))

In circuits with ideal diodes, the circuit should be analyzed for various configurations of diodes.

$$i = \frac{v - 2}{2}$$

$$i_{D_1} = i \geq 0 \Rightarrow v \geq 2$$
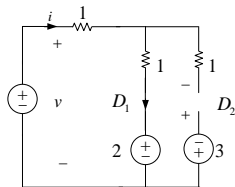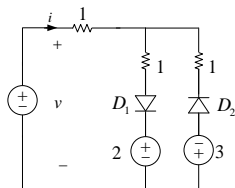
$$v_{D_2} = -v - 3 + \frac{v - 2}{2} \leq 0 \Rightarrow v \geq -8$$



Circuits with Ideal Diodes



Example (Circuits with ideal diodes (cont.))

In circuits with ideal diodes, the circuit should be analyzed for various configurations of diodes.

$$i = \frac{v + 3}{2}$$

$$v_{D_1} = v - 2 - \frac{v + 3}{2} \leq 0 \Rightarrow v \leq 7$$
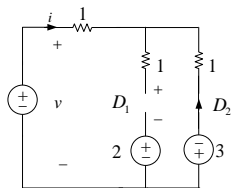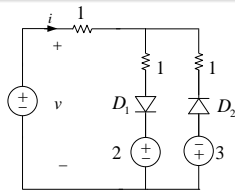
$$i_{D_2} = -i \geq 0 \Rightarrow v \leq -3$$



Circuits with Ideal Diodes

Example (Circuits with ideal diodes (cont.))


In circuits with ideal diodes, the circuit should be analyzed for various configurations of diodes.

$$\frac{e-v}{1} + \frac{e-2}{1} + \frac{e+3}{1} = 0 \Rightarrow e = \frac{v-1}{3}$$

$$i = \frac{v-e}{1} = \frac{2v+1}{3}$$

$$i_{D_1} = e - 2 = \frac{v-7}{3} \geq 0 \Rightarrow v \geq 7$$
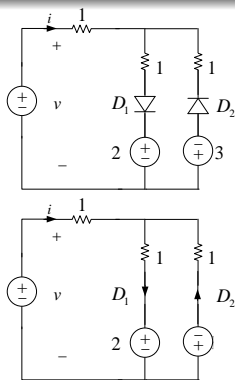
$$i_{D_2} = -(e+3) = -\frac{v+8}{3} \geq 0 \Rightarrow v \leq -8$$





Circuits with Ideal Diodes

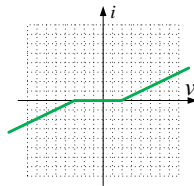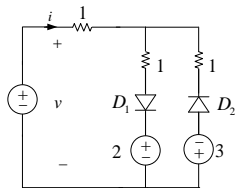Example (Circuits with ideal diodes (cont.))

In circuits with ideal diodes, the circuit should be analyzed for various configurations of diodes.

$$i = \begin{cases} \frac{v+3}{2}, & v \leq -3 \\ 0, & -3 < v \leq 2 \\ \frac{v-2}{2}, & v > 2 \end{cases}$$



The End