

Sinusoidal Steady State Analysis

Mohammad Hadi

mohammad.hadi@sharif.edu

@MohammadHadiDastgerdi

Spring 2022

Overview

- 1 Sinusoidal Steady State
- 2 Phasors
- 3 Impedance and Admittance
- 4 Sinusoidal Steady State Analysis
- 5 Sinusoidal Steady State Power
- 6 Network Function
- 7 Filters

Sinusoidal Steady State

Statement (Describing Differential Equation)

An LTI circuit with sinusoidal input is described by a non-homogeneous sinusoidally-driven constant-coefficient linear differential equation.

- **Single-input LTI circuit:** $\begin{cases} \sum_{i=0}^n a_i y^{(i)}(t) = \sum_{j=0}^m b_j w^{(j)}(t), t > 0^- \\ y(0^-), y'(0^-), \dots, y^{(n-1)}(0^-) \end{cases}$
- **Sinusoidal input:** $w(t) = A \cos(\omega t + \theta)u(t)$
- **Single-input sinusoidal LTI circuit:** $\begin{cases} \sum_{i=0}^n a_i y^{(i)}(t) = B \cos(\omega t + \phi), t > 0 \\ y(0^+), y'(0^+), \dots, y^{(n-1)}(0^+) \end{cases}$
- **Natural frequencies:** $\sum_{i=1}^n a_i s_i = 0$
- **Complete response:** $y(t) = y_h(t) + y_p(t) = y_{tr}(t) + y_{ss}(t)$
- **Homogeneous response:** $y_h(t) = \sum_{i=1}^n k_i e^{s_i t}, t > 0$
- **Particular response:** $y_p(t) = \begin{cases} C \cos(\omega t + D), & s_i \neq j\omega, \forall i \\ Ct \cos(\omega t + D), & s_i = j\omega, \exists i \end{cases}$

Natural Frequency

Definition (Natural Frequencies)

The roots of the characteristic equation of the LTI circuit differential equation are called natural frequencies.

- **Natural frequencies:** $F(s) = \sum_{i=1}^n a_i s_i = 0, a_i > 0$

Statement (Natural Frequencies)

Natural frequencies appear in real or complex conjugate forms.

- **Complex conjugate natural frequencies:** $F(s_i) = 0 \Rightarrow F(s_i^*) = 0$

Natural Frequency

Statement (Strictly Passive LTI Circuit)

Natural frequencies of a strictly passive LTI circuit fall within the LHS of the complex plane.

Statement (Passive LTI Circuit)

Natural frequencies of a passive LTI circuit fall within the LHS of the complex plane or are simple conjugate pure imaginary values on the $j\omega$ -axis.

Statement (Active LTI Circuit)

An active LTI circuit has at least one natural frequency on the RHS of the complex plane or one repeated natural frequency on the $j\omega$ axis.

Statement (Sinusoidal Steady State for Strictly Passive LTI Circuits)

A strictly passive LTI circuit with sinusoidal input achieves sinusoidal steady state.

- **Natural frequencies:** $\Re\{s_i\} < 0, \forall i$
- **Complete response:** $y(t) = \sum_{i=1}^n k_i e^{s_i t} + C \cos(\omega t + D), t > 0$
- **Sinusoidal steady state response:** $y_{ss}(t) = C \cos(\omega t + D), t > 0$

Statement (Steady State for Passive LTI Circuits)

A passive LTI circuit with sinusoidal input may achieve steady state.

- 1 Natural frequencies:** $s_{1,2} = \pm j\omega_0, \omega_0 \neq \omega; \quad \Re\{s_i\} < 0, i = 3, 4, \dots$
 - Complete response:**
$$y(t) = C_0 \cos(\omega_0 t + D_0) + \sum_{i=3}^n k_i e^{s_i t} + C \cos(\omega t + D), t > 0$$
 - Steady state response:** $y_{ss}(t) = C_0 \cos(\omega_0 t + D_0) + C \cos(\omega t + D), t > 0$
- 2 Natural frequencies:** $s_{1,2} = \pm j\omega_0, \omega_0 = \omega; \quad \Re\{s_i\} < 0, i = 3, 4, \dots$
 - Complete response:**
$$y(t) = C_0 \cos(\omega_0 t + D_0) + \sum_{i=3}^n k_i e^{s_i t} + Ct \cos(\omega t + D), t > 0$$

Statement (Active LTI Circuits)

An active LTI circuit doesn't have steady state.

- **Natural frequencies:** $\Re\{s_i\} > 0, \exists i$
- **Complete response:** $y(t) = \sum_{i=1}^n k_i e^{s_i t} + C \cos(\omega t + D), t > 0$

Sinusoidal Steady State

Example (Sinusoidal steady state for series RC circuit)

The series passive RC circuit achieves sinusoidal steady state.

$$\begin{cases} \frac{dv_c}{dt} + \frac{v_c(t)}{RC} = \frac{i_s(t)}{C} = \frac{A \cos(\omega t + \theta) u(t)}{C} \\ v_c(0^-) = V_0 \end{cases}$$

$$\begin{cases} \frac{dv_c}{dt} + \frac{v_c(t)}{RC} = \frac{A \cos(\omega t + \theta)}{C}, t > 0 \\ v_c(0^+) = v_c(0^-) = V_0 \end{cases}$$

$$v_c(t) = v_{ch}(t) + v_{cp}(t) = Ke^{-\frac{t}{RC}} + B \cos(\omega t + \phi), t > 0$$


$$-B\omega \sin(\omega t + \phi) + \frac{B \cos(\omega t + \phi)}{RC} = \frac{A \cos(\omega t + \theta)}{C}$$

$$\begin{cases} B = \frac{AR}{\sqrt{1+(RC\omega)^2}} \\ \phi = \theta - \tan^{-1}(RC\omega) \end{cases}$$

$$V_0 = Ke^0 + B \cos(\phi) \Rightarrow K = V_0 - B \cos(\phi)$$

$$v_c(t) = (V_0 - B \cos(\phi))e^{-\frac{t}{RC}} + B \cos(\omega t + \phi), t > 0$$
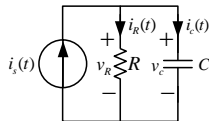
$$v_{ss}(t) = B \cos(\omega t + \phi), t > 0$$



Phasors

Definition (Phasors)

The phasor $X = Ae^{j\theta} = A/\underline{\theta}$ can fully describe the sinusoidal signal $x(t) = A \cos(\omega t + \theta) = \Re\{Xe^{j\omega t}\}$ with the known frequency ω .

- **Sinusoidal signal:** $A \cos(\omega t + \theta) \equiv Ae^{j\theta} = A/\underline{\theta}$
- **Phasor amplitude:** $|A|$
- **Phasor phase:** $\theta + \begin{cases} 0, & A \geq 0 \\ \pi, & A < 0 \end{cases}$
- **Sinusoidal signal:** $A \sin(\omega t + \theta) \equiv Ae^{j(\theta-90^\circ)} = A/\underline{\theta - 90^\circ}$
- **Sinusoidal signal:** $-A \sin(\omega t + \theta) \equiv Ae^{j(\theta+90^\circ)} = A/\underline{\theta + 90^\circ}$
- **Differentiation:** $\frac{d(Xe^{j\omega t})}{dt} = j\omega Xe^{j\omega t}$
- **Real-part and differentiation:** $\Re\left\{\frac{d(Xe^{j\omega t})}{dt}\right\} = \frac{d\Re\{Xe^{j\omega t}\}}{dt}$

Phasor Calculation

Example (Phasor calculation)

Phasor can facilitate calculations.

$$x(t) = A \cos(\omega t + \theta), \quad X = Ae^{j\theta}$$

$$y(t) = \sum_{k=0}^m a_k \frac{d^k x(t)}{dt^k} = B \cos(\omega t + \phi) \Rightarrow Y = Be^{j\phi} = \sum_{k=0}^m a_k (j\omega)^k X = Ae^{j\theta} \sum_{k=0}^m a_k (j\omega)^k$$

Example (Phasor calculation)

Phasor can facilitate calculations.

$$v(t) = 2 \cos(3t + \underline{30^\circ}) - 4 \sin(3t + \underline{45^\circ}) + 3 \sin(3t) - 10 \cos(3t)$$

$$\Re\{Ve^{j3t}\} = \Re\{2/\underline{30^\circ} e^{j3t}\} - \Re\{4/\underline{-90^\circ + 45^\circ} e^{j3t}\} + \Re\{3/\underline{-90^\circ} e^{j3t}\} - \Re\{10/\underline{0^\circ} e^{j3t}\}$$

$$V = (2/\underline{30^\circ}) - (4/\underline{-90^\circ + 45^\circ}) + (3/\underline{-90^\circ}) - (10/\underline{0^\circ})$$

$$V = (2 \cos(30^\circ) - 4 \cos(-45^\circ) + 0 - 10) + j(2 \sin(30^\circ) - 4 \sin(-45^\circ) - 3 - 0)$$

$$V = -11.096 + j0.83 = 11.127/\underline{175.72^\circ}$$

$$v(t) = 11.127 \cos(3t + 175.72^\circ)$$

Example (Phasor calculation)

Phasor can facilitate calculations.

$$\sum_{k=0}^n a_k \frac{d^k y}{dt^k} = \sum_{k=0}^m b_k \frac{d^k w}{dt^k}, \quad w(t) = A \cos(\omega t + \theta)$$

$$w(t) = \Re\{We^{j\omega t}\} = \Re\{Ae^{j\theta}e^{j\omega t}\}, \quad y_p(t) = \Re\{Y_p e^{j\omega t}\} = \Re\{Be^{j\phi}e^{j\omega t}\}$$

$$\sum_{k=0}^n a_k \frac{d^k}{dt^k} (\Re\{Y_p e^{j\omega t}\}) = \sum_{k=0}^m b_k \frac{d^k}{dt^k} (\Re\{We^{j\omega t}\})$$

$$\sum_{k=0}^n a_k \Re\left\{\frac{d^k}{dt^k} (Y_p e^{j\omega t})\right\} = \sum_{k=0}^m b_k \Re\left\{\frac{d^k}{dt^k} (We^{j\omega t})\right\}$$

$$\Re\left\{\sum_{k=0}^n a_k \frac{d^k}{dt^k} (Y_p e^{j\omega t})\right\} = \Re\left\{\sum_{k=0}^m b_k \frac{d^k}{dt^k} (We^{j\omega t})\right\}$$

$$\Re\left\{\left[\sum_{k=0}^n a_k (j\omega)^k Y_p\right] e^{j\omega t}\right\} = \Re\left\{\left[\sum_{k=0}^m b_k (j\omega)^k W\right] e^{j\omega t}\right\}$$

$$Y_p \sum_{k=0}^n a_k (j\omega)^k = W \sum_{k=0}^m b_k (j\omega)^k \Rightarrow Y_p = \frac{\sum_{k=0}^m b_k (j\omega)^k}{\sum_{k=0}^n a_k (j\omega)^k} W$$

Sinusoidal Steady State Analysis

Example (Sinusoidal steady state analysis using phasors)

Sinusoidal steady state can be found using phasor calculation.

$$v_s(t) = 2 \cos(2t)u(t), i_L(0^-) = 4, v_C(0^-) = 2$$

$$\frac{d^2 v_C}{dt^2} + 3 \frac{dv_C}{dt} + 2v_C(t) = 4 \cos(2t)u(t), v_C(0^-) = 2, i_L(0^-) = 4$$

$$\begin{cases} \frac{d^2 v_C}{dt^2} + 3 \frac{dv_C}{dt} + 2v_C(t) = 4 \cos(2t), t > 0 \\ v_C(0^+) = v_C(0^-) = 2, v'_C(0^+) = i_C(0^+) = i_L(0^+) = i_L(0^-) = 4 \end{cases}$$

$$v_C(t) = v_h + v_p = K_1 e^{-t} + K_2 e^{-2t} + B \cos(2t + \phi), t > 0$$


$$W = 2e^{j0}, w(t) = 2 \cos(2t), V_p = B e^{j\phi}, v_p(t) = B \cos(2t + \phi)$$

$$((j2)^2 + 3(j2) + 2)V_p = 2W = 4e^{j0} \Rightarrow V_p = \frac{4}{-2 + 6j} = 0.64e^{-j108.4^\circ}$$

$$\begin{cases} B = 0.64 \\ \phi = -108.4^\circ \end{cases} \Rightarrow v_p(t) = v_{CSS}(t) = 0.64 \cos(2t - 108.4^\circ)$$

$$\begin{cases} 2 = K_1 + K_2 + 0.64 \cos(-108.4^\circ) \\ 4 = -K_1 - 2K_2 - 1.28 \sin(-108.4^\circ) \end{cases}$$
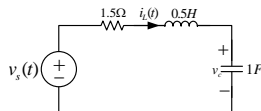
$$v_C(t) = 7.2e^{-t} - 5e^{-2t} + 0.64 \cos(2t - 108.4^\circ), t > 0$$



Impedance and Admittance

Impedance and Admittance

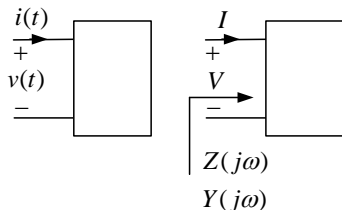


Figure: Impedance $Z(j\omega) = R(j\omega) + jX(j\omega) = \frac{V(j\omega)}{I(j\omega)}$ and admittance $Y(j\omega) = G(j\omega) + jB(j\omega) = \frac{I(j\omega)}{V(j\omega)} = \frac{1}{Z(j\omega)}$ for a one-port in-rest network. $R(j\omega)$, $X(j\omega)$, $G(j\omega)$, and $B(j\omega)$ stand for **resistance**, **reactance**, **conductance**, and **susceptance**. The impedance and admittance are not phasors and do not have equivalent time-domain signals.

- **Port voltage and current signals:** $v(t) = V_m \cos(\omega t + \theta)$, $i(t) = I_m \cos(\omega t + \phi)$
- **Port voltage and current phasors:** $V = V_m \angle \theta$, $I = I_m \angle \phi$
- **One-port impedance and admittance:** $Z(j\omega) = \frac{1}{Y(j\omega)} = \frac{V(j\omega)}{I(j\omega)}$

Resistor

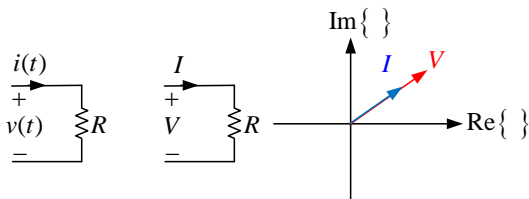


Figure: The current phasor I in an **LTI resistor** has no phase difference with voltage phasor V . An LTI resistor is described by the impedance $Z = R$ or admittance $Y = \frac{1}{R}$.

$$v(t) = V_m \cos(\omega t + \theta) = Ri(t) = RI_m \cos(\omega t + \phi)$$

$$V = V_m e^{j\theta} = RI_m e^{j\phi} = RI \Rightarrow \begin{cases} |V| = |RI| = |R||I| \\ \angle V = \angle I \end{cases}$$

Capacitor

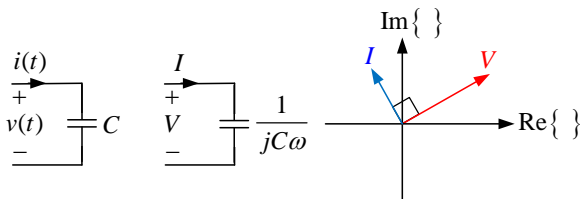


Figure: The current phasor I in an **LTI capacitor** leads the voltage phasor V by 90° . An LTI capacitor is described by the impedance $Z = \frac{1}{j\omega C}$ or admittance $Y = j\omega C$.

$$i(t) = C \frac{dv(t)}{dt} = C \frac{dV_m \cos(\omega t + \theta)}{dt} = -CV_m \omega \sin(\omega t + \theta) = CV_m \omega \cos(\omega t + \theta + 90^\circ)$$

$$I = I_m e^{j\phi} = CV_m \omega e^{j(\theta + 90^\circ)} = j\omega CV_m e^{j\theta} \Rightarrow \begin{cases} |V| = \left| \frac{I}{j\omega C} \right| = \frac{|I|}{|\omega C|} \\ \angle V = \angle I - 90^\circ \end{cases}$$

Inductor

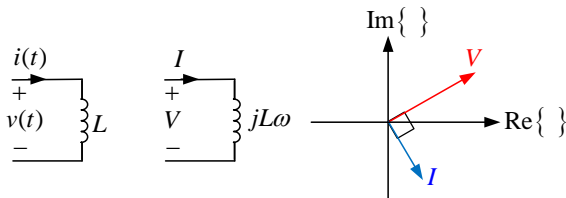


Figure: The current phasor I in an **LTI inductor** lags the voltage phasor V by 90° . An LTI inductor is described by the impedance $Z = j\omega L$ or admittance $Y = \frac{1}{j\omega L}$.

$$v(t) = V_m \cos(\omega t + \theta) = L \frac{di(t)}{dt} = -LI_m \omega \sin(\omega t + \phi) = LI_m \omega \cos(\omega t + \phi + 90^\circ)$$

$$V = V_m e^{j\theta} = LI_m \omega e^{j(\phi + 90^\circ)} = j\omega LI_m e^{j\theta} \Rightarrow \begin{cases} |V| = |j\omega L| = |I| |\omega L| \\ \angle V = \angle I + 90^\circ \end{cases}$$

Passive One-port

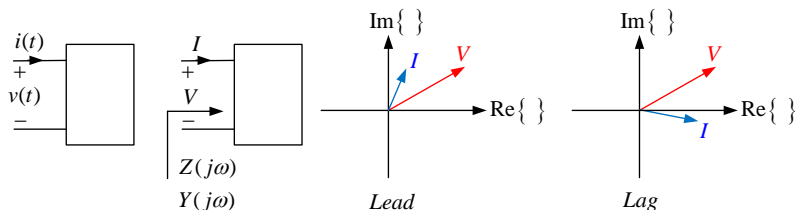


Figure: A passive one-port has the impedance $Z = R + jX = \frac{1}{Y}$, $R \geq 0$.

- **Passive load:** $Z = R + jX = |Z|e^{j\angle Z}$, $R = \Re\{Z\} \geq 0 \equiv -90^\circ \leq \angle Z \leq 90^\circ$
- **Resistive load:** $Z = R + jX = |Z|e^{j\angle Z}$, $X = 0 \equiv \angle Z = 0$
- **Inductive (lagging) load:** $Z = R + jX = |Z|e^{j\angle Z}$, $X > 0 \equiv 0 < \angle Z \leq 90^\circ$
- **Capacitive (leading) load:** $Z = R + jX = |Z|e^{j\angle Z}$, $X < 0 \equiv -90^\circ \leq \angle Z < 0$

Sinusoidal Steady State Analysis

- KCL in phasor-domain:** $\sum_k i_k(t) = \sum_k [i_{hk}(t) + i_{pk}(t)] = 0 \Rightarrow \sum_k i_{pk}(t) = 0, t \gg 0 \Rightarrow \sum_k \Re\{I_k e^{j\omega t}\} = 0 \Rightarrow \Re\{e^{j\omega t} \sum_k I_k\} = 0 \Rightarrow \sum_k I_k = 0$
- KVL in phasor-domain:** $\sum_k v_k(t) = \sum_k [v_{hk}(t) + v_{pk}(t)] = 0 \Rightarrow \sum_k v_{pk}(t) = 0, t \gg 0 \Rightarrow \sum_k \Re\{V_k e^{j\omega t}\} = 0 \Rightarrow \Re\{e^{j\omega t} \sum_k V_k\} = 0 \Rightarrow \sum_k V_k = 0$

Series and Parallel Connections

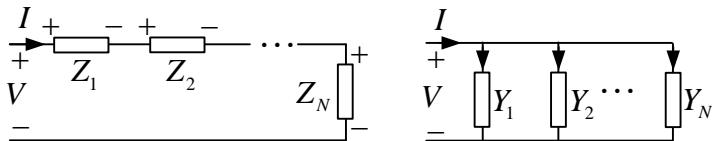


Figure: Series and parallel connection of impedances. The Delta-Wye conversion is also valid in phasor domain.

- **Series connection:** $V = \sum_k V_k = \sum_k Z_k I_k = I \sum_k Z_k \Rightarrow Z = \frac{V}{I} = \sum_k Z_k$
- **Parallel connection:** $I = \sum_k I_k = \sum_k Y_k V_k = V \sum_k Y_k \Rightarrow Y = \frac{I}{V} = \sum_k Y_k$

Source Transformation

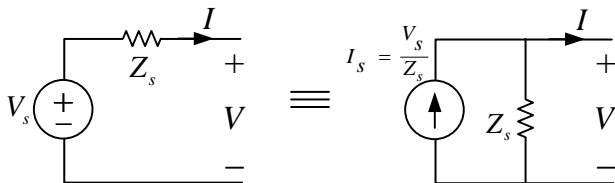


Figure: Source transformation.

$$V = V_s - Z_s I \Rightarrow I = \frac{V_s}{Z_s} - \frac{V}{Z_s}$$

Thevenin/Norton Equivalent Circuit

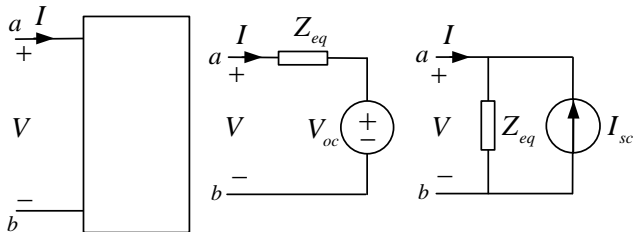


Figure: Phasor-domain Thevenin/Norton Equivalent Circuit for an LTI circuit.

$$V_{oc} = V|_{I=0}, \quad I_{sc} = -I|_{V=0}, \quad Z_{eq} = \frac{V}{I}|_{W=0}, \quad V_{oc} = Z_{eq}I_{sc}$$

Superposition


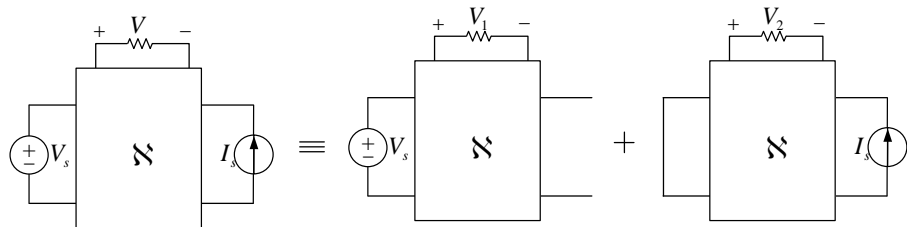
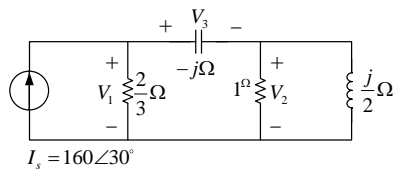


Figure: If the independent sources have the same frequency, the phasor-domain superposition for an LTI circuit yields $V = V_1 + V_2$.

Node Analysis

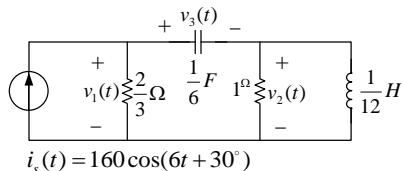Example (Phasor-domain node analysis)

Node analysis can be used in phasor domain.



$$\begin{cases} -\frac{160 \angle 30^\circ}{3} + \frac{V_1}{2} + \frac{V_1 - V_2}{-j} = 0 \\ \frac{V_2 - V_1}{-j} + \frac{V_2}{1} + \frac{V_2}{0.5j} = 0 \end{cases}$$



$$\Rightarrow \begin{bmatrix} 1.5 + j & j \\ j & 1 - j \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 160 \angle 30^\circ \\ 0 \end{bmatrix}$$

$$\Rightarrow V_1 = \frac{\begin{vmatrix} 160 \angle 30^\circ & j \\ 0 & 1 - j \end{vmatrix}}{\begin{vmatrix} 1.5 + j & j \\ j & 1 - j \end{vmatrix}} = 63.6 - 7.6j = 64 \angle -6.9^\circ \Rightarrow v_1(t) = 64 \cos(6t - 6.9^\circ)$$

Mesh Analysis

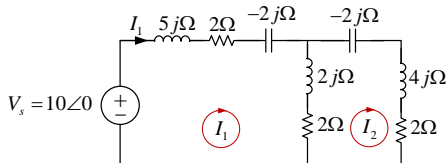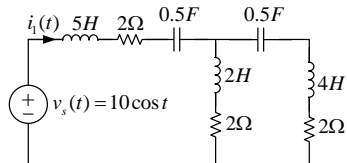Example (Phasor-domain mesh analysis)

Mesh analysis can be used in phasor domain.




$$\begin{cases} -10 + (5j + 2 - 2j)I_1 + (2j + 2)(I_1 - I_2) = 0 \\ (2j + 2)(I_2 - I_1) + (-2j + 4j + 2)I_2 = 0 \end{cases}$$

$$\Rightarrow \begin{bmatrix} 4 + 5j & -2 - 2j \\ -2 - 2j & 4 + 4j \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \end{bmatrix}$$

$$\Rightarrow I_1 = \frac{\begin{vmatrix} 10 & -2 - 2j \\ 0 & 4 + 4j \end{vmatrix}}{\begin{vmatrix} 4 + 5j & -2 - 2j \\ -2 - 2j & 4 + 4j \end{vmatrix}} = \frac{10}{3 + 4j} = 1.2 - 1.6j = 2\angle -53.1^\circ \Rightarrow i_1(t) = 2 \cos(t - 53.1^\circ)$$

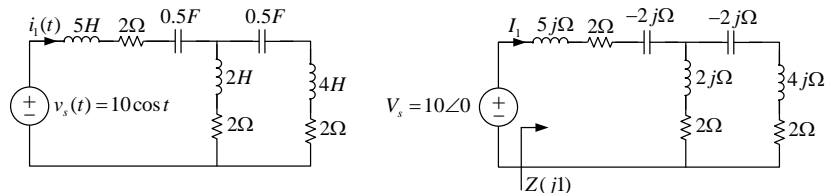Example (Input impedance)

Series and parallel connections can facilitate circuit analysis.





$$Z(j1) = (5j + 2 - 2j) + ((2j + 2) \parallel (-2j + 4j + 2)) = 3 + 4j$$

$$I_1 = \frac{V_s}{Z(j1)} = \frac{10}{3 + 4j} = 1.2 - 1.6j = 2\angle -53.1^\circ \Rightarrow i_1(t) = 2\cos(t - 53.1^\circ)$$

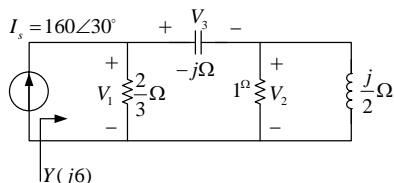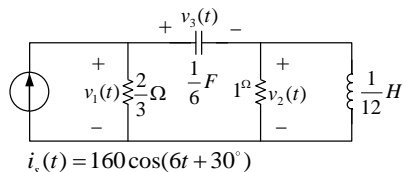Example (Input admittance)

Series and parallel connections can facilitate circuit analysis.




$$Y(j6) = \frac{3}{2} + \frac{1}{(-j) + (1 \parallel 0.5j)} = 2 + 1.5j = 2.5 \underline{36.9^\circ}$$

$$V_1 = \frac{I_s}{Y(j6)} = \frac{160 \underline{30^\circ}}{2.5 \underline{36.9^\circ}} = 64 \underline{-6.9^\circ} \Rightarrow v_1(t) = 64 \cos(6t - 6.9^\circ)$$

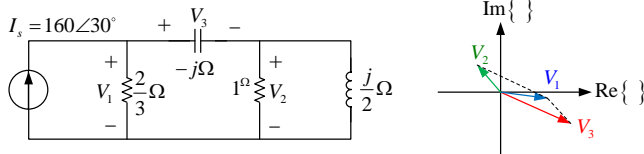Example (Voltage division)

Voltage and current division rules can facilitate circuit analysis.



$$i_s(t) = 160 \cos(6t + 30^\circ) \Rightarrow I_s = 160 \angle 30^\circ$$

$$V_1 = \frac{I_s}{\frac{3}{2} + \frac{1}{(-j) + (1 \parallel 0.5j)}} = 63.6 - 7.6j = 64 \angle -6.9^\circ \Rightarrow v_1(t) = 64 \cos(6t - 6.9^\circ)$$

$$V_2 = \frac{1 \parallel 0.5j}{(-j) + (1 \parallel 0.5j)} V_1 = -28 + 35.6j = 45.2 \angle 128^\circ \Rightarrow v_2(t) = 45.2 \cos(6t + 128^\circ)$$

$$V_3 = \frac{-jV_1}{(-j) + (1 \parallel 0.5j)} = V_1 - V_2 = 91.6 - 43.2j = 101.2 \angle -25.3^\circ \Rightarrow v_3(t) = 101.2 \cos(6t - 25.3^\circ)$$

Example (First-order circuit)

Sinusoidal steady state can be simply found using phasor analysis.


$$i_s(t) = A \cos(\omega t + \theta) \Rightarrow I_s = A/\theta$$

$$I_s = \frac{V_c}{R} + \frac{V_c}{\frac{1}{j\omega C}} = \left(\frac{1}{R} + j\omega C\right)V_c$$

$$\Rightarrow V_c = \frac{I_s}{\frac{1}{R} + j\omega C} = \frac{RA/\theta}{1 + j\omega RC}$$



$$\Rightarrow V_c = \frac{AR}{\sqrt{1 + (RC\omega)^2}} \angle \theta - \tan^{-1}(RC\omega)$$
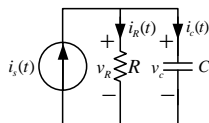
$$v_c(t) = \frac{AR}{\sqrt{1 + (RC\omega)^2}} \cos(\omega t + \theta - \tan^{-1}(RC\omega))$$



Example (Duality)

Duality can facilitate phasor analysis.

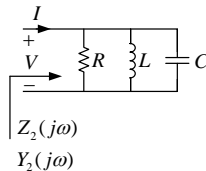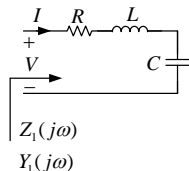

$$Z_1(j\omega) = R + j\omega L + \frac{1}{j\omega C} = R + j\left(L\omega - \frac{1}{C\omega}\right)$$

$$Y_1(j\omega) = \frac{1}{Z_1(j\omega)} = \frac{1}{R + j\left(L\omega - \frac{1}{C\omega}\right)} = \frac{R}{R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2} - j \frac{L\omega - \frac{1}{C\omega}}{R^2 + \left(L\omega - \frac{1}{C\omega}\right)^2}$$

$$Y_2(j\omega) = \frac{1}{R} + j\omega C + \frac{1}{j\omega L} = \frac{1}{R} + j\left(C\omega - \frac{1}{L\omega}\right)$$

$$Z_2(j\omega) = \frac{1}{Y_2(j\omega)} = \frac{1}{\frac{1}{R} + j\left(C\omega - \frac{1}{L\omega}\right)} = \frac{\frac{1}{R}}{\frac{1}{R^2} + \left(C\omega - \frac{1}{L\omega}\right)^2} - j \frac{C\omega - \frac{1}{L\omega}}{\frac{1}{R^2} + \left(C\omega - \frac{1}{L\omega}\right)^2}$$

Example (Thevenin/Norton equivalent circuits)

Thevenin/Norton equivalent circuits can be found using phasor analysis.


$$\begin{cases} V_1 = 2.5\angle 30^\circ \\ V_{oc} = -10V_1 = 25\angle -150^\circ \end{cases}$$

$$\begin{cases} 2.5\angle 30^\circ + 0.5I_2 = \frac{V_1}{1} \\ 15I_2 - 10V_1 + 40j(I_2 - 0.5I_2) = 0 \end{cases}$$

$$I_2 = -1.12\angle -33.5^\circ \Rightarrow I_{sc} = -I_2 = 1.12\angle -33.5^\circ$$


$$\begin{cases} 0.5I_2 = \frac{V_1}{1} \\ V_2 = 15I_2 - 10V_1 + 40j(I_2 - 0.5I_2) = 0 \end{cases}$$
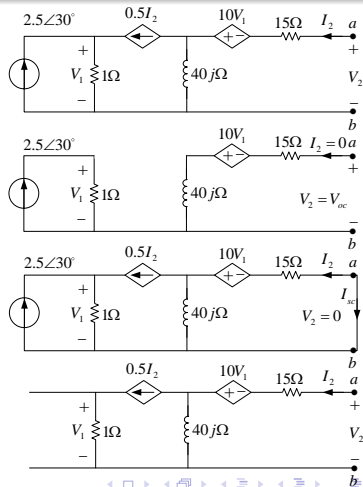
$$V_2 = (10 + 20j)I_2 \Rightarrow Z_{eq} = \frac{V_2}{I_2} = 10 + 20j$$



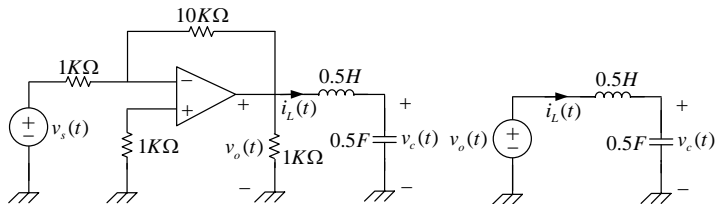Example (SSS analysis for op-amp circuits)

Phasor analysis can be used to determine sinusoidal steady state of op-amp circuits.





$$v_o(t) = -10v_s(t), v_s(t) = -0.1 \sin(t) \Rightarrow v_o(t) = \sin(t) \Rightarrow V_o = -j$$

$$V_c = \frac{-2j}{0.5j - 2j} V_o = -\frac{4}{3}j \Rightarrow v_c(t) = \frac{4}{3} \cos(t - 90^\circ) = \frac{4}{3} \sin(t)$$

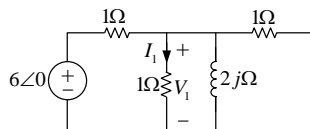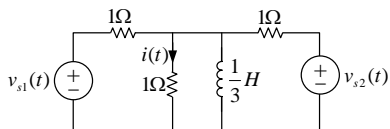Example (Superposition)

Phasor-domain superposition is valid if the sinusoidal sources have the same frequency.




$$v_{s1}(t) = 6 \cos(6t) + 60 \cos(3t - 30^\circ), \quad v_{s2}(t) = 60 \cos(3t + 60^\circ), \quad i(t) = i_1(t) + i_2(t)$$

$$I_1 = \frac{V_1}{1} = \frac{(1) \parallel (1) \parallel (2j)}{1 + (1) \parallel (1) \parallel (2j)} 6\angle 0^\circ = \frac{12j}{1 + 6j} = 1.97\angle 9.5^\circ \Rightarrow i_1(t) = 1.97 \cos(6t + 9.5^\circ)$$

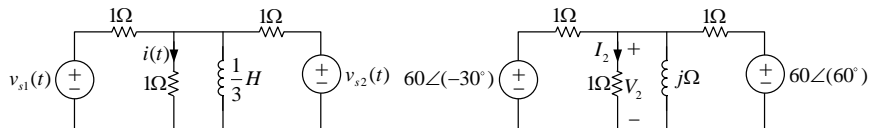Example (Superposition (cont.))

Phasor-domain superposition is valid if the sinusoidal sources have the same frequency.



$$I_2 = \frac{V_2}{1} = I_{21} + I_{22} = \frac{V_{21}}{1} + \frac{V_{22}}{1} = \frac{(1) \parallel (1) \parallel (j)}{1 + (1) \parallel (1) \parallel (j)} 60 \angle -30^\circ + \frac{(1) \parallel (1) \parallel (j)}{1 + (1) \parallel (1) \parallel (j)} 60 \angle 60^\circ$$

$$I_2 = \frac{j}{1 + 3j} 60 \sqrt{2} \angle 15^\circ = 26.83 \angle 33.7^\circ \Rightarrow i_2(t) = 26.83 \cos(3t + 33.7^\circ)$$

$$i(t) = i_1(t) + i_2(t) = 1.97 \cos(6t + 9.5^\circ) + 26.83 \cos(3t + 33.7^\circ)$$

Sinusoidal Steady State Power

Instantaneous Power

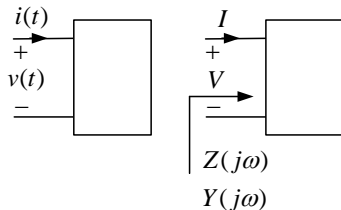


Figure: A **one-port** with sinusoidal voltage and currents.

- **Port voltage and current signals:** $v(t) = V_m \cos(\omega t + \theta)$, $i(t) = I_m \cos(\omega t + \phi)$
- **Port voltage and current phasors:** $V = V_m \angle \theta$, $I = I_m \angle \phi$
- **Absorbed instantaneous power:** $p(t) = v(t)i(t) = V_m \cos(\omega t + \theta) I_m \cos(\omega t + \phi)$
- **Absorbed instantaneous power:** $p(t) = \frac{V_m I_m}{2} \cos(2\omega t + \theta + \phi) + \frac{V_m I_m}{2} \cos(\theta - \phi)$

Average (Real) Power

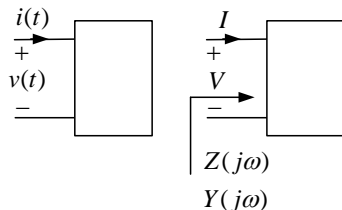


Figure: A **passive one-port** with sinusoidal voltage and currents.

- **Port voltage and current signals:** $v(t) = V_m \cos(\omega t + \theta)$, $i(t) = I_m \cos(\omega t + \phi)$
- **Port voltage and current phasors:** $V = V_m \angle \theta$, $I = I_m \angle \phi$
- **Absorbed instantaneous power:** $p(t) = \frac{V_m I_m}{2} \cos(2\omega t + \theta + \phi) + \frac{V_m I_m}{2} \cos(\theta - \phi)$
- **Average (real) power:** $P_{av} = \frac{1}{T} \int_0^T p(t) dt = \frac{V_m I_m}{2} \cos(\theta - \phi)$
- **Average (real) power:** $P_{av} = \frac{V_m I_m}{2} \cos(\angle V - \angle I) = \frac{V_m I_m}{2} \cos(\angle Z)$
- **Passive load average power:** $-90^\circ \leq \angle Z \leq 90^\circ \Rightarrow P_{av} \geq 0$

Resistive Load Average Power

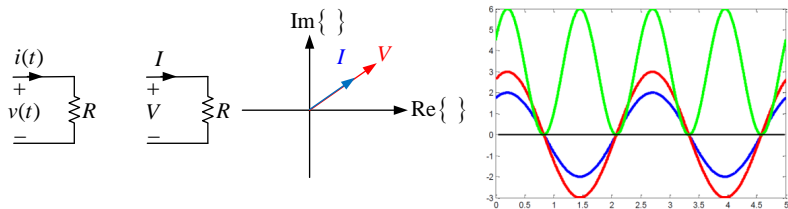


Figure: Average power for a **resistive passive load**.

- **Average (real) power:** $P_{av} = \frac{V_m I_m}{2} \cos(\angle V - \angle I) = \frac{V_m I_m}{2} \cos(\angle Z)$
- **Resistive load average power:** $P_{av} = \frac{V_m I_m}{2} \cos(0^\circ) = \frac{V_m I_m}{2} = \frac{1}{2} R I_m^2$

Capacitive Load Average Power

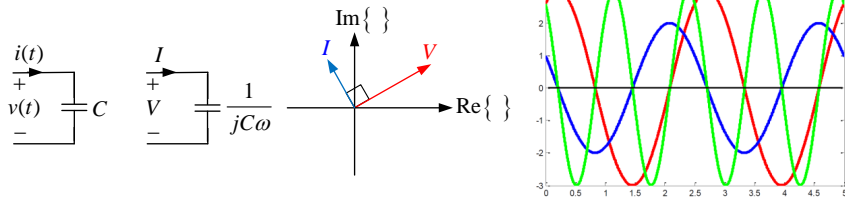


Figure: Average power for a **capacitive passive load**.

- **Average (real) power:** $P_{av} = \frac{V_m I_m}{2} \cos(\angle V - \angle I) = \frac{V_m I_m}{2} \cos(\angle Z)$
- **Capacitive load average power:** $P_{av} = \frac{V_m I_m}{2} \cos(-90^\circ) = 0$

Inductive Load Average Power

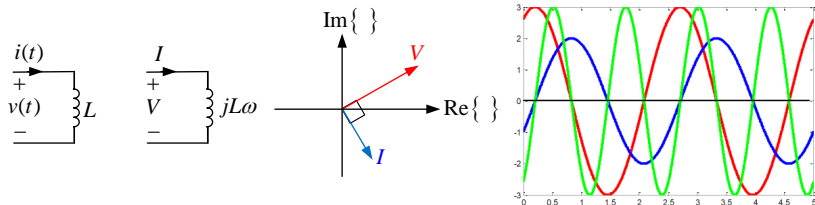


Figure: Average power for a **inductive passive load**.

- **Average (real) power:** $P_{av} = \frac{V_m I_m}{2} \cos(\angle V - \angle I) = \frac{V_m I_m}{2} \cos(\angle Z)$
- **Inductive load average power:** $P_{av} = \frac{V_m I_m}{2} \cos(90^\circ) = 0$

Complex Power

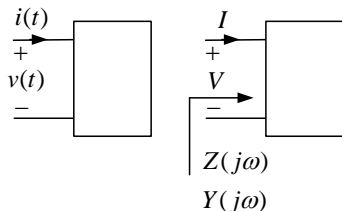


Figure: A **one-port** with sinusoidal voltage and currents.

- **Port voltage and current signals:** $v(t) = V_m \cos(\omega t + \theta)$, $i(t) = I_m \cos(\omega t + \phi)$
- **Port voltage and current phasors:** $V = V_m \angle \theta$, $I = I_m \angle \phi$
- **Apparent (complex) power (VA):** $P = \frac{1}{2} VI^* = \frac{1}{2} Z |I|^2 = \frac{1}{2} R |I|^2 + j \frac{1}{2} X |I|^2$
- **Apparent (complex) power (VA):**
$$P = \frac{V_m e^{j\theta} I_m e^{-j\phi}}{2} = \frac{V_m I_m}{2} [\cos(\theta - \phi) + j \sin(\theta - \phi)]$$
- **Apparent (complex) power (VA):** $P = P_{av} + jQ$

Reactive Power

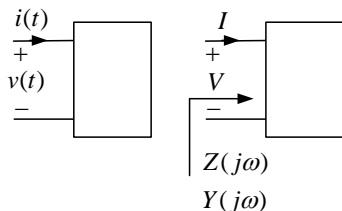


Figure: A **one-port** with sinusoidal voltage and currents.

- **Apparent (complex) power (VA):**

$$P = \frac{1}{2} VI^* = \frac{1}{2} Z |I|^2 = \frac{1}{2} R |I|^2 + j \frac{1}{2} X |I|^2 = P_{av} + jQ$$

- **Average (real) power (W):** $P_{av} = \Re\{P\} = \frac{V_m I_m}{2} \cos(\angle Z) = \frac{1}{2} R |I|^2$
- **Reactive (imaginary) power (VAR):** $Q = \Im\{P\} = \frac{V_m I_m}{2} \sin(\angle Z) = \frac{1}{2} X |I|^2$

Reactive Power


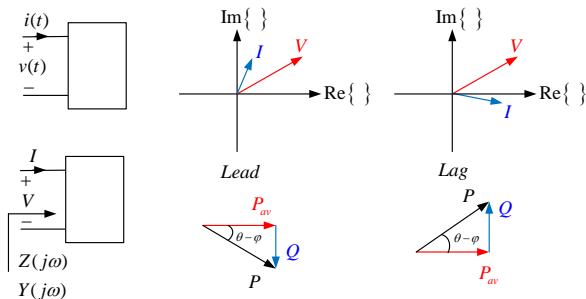


Figure: Power triangle.

- Apparent (complex) power (VA): $P = P_{av} + jQ$
- Power factor: $PF = \cos(\angle Z) = \cos(\angle V - \angle I), 0 \leq PF \leq 1$
- Resistive load: $X = 0 \equiv Q = 0 \equiv PF = 1$
- Capacitive (leading) load: $X < 0 \equiv Q < 0 \equiv 0 \leq PF < 1, lead$
- Inductive (lagging) load: $X > 0 \equiv Q > 0 \equiv 0 \leq PF < 1, lag$

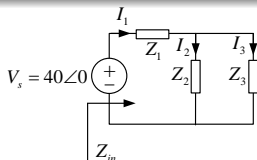Example (Power Conservation)

Sum of the absorbed complex (real, reactive) powers is zero.



$$Z_1 = 1.5\Omega, \quad Z_2 = j\Omega, \quad Z_3 = (1 - j2)\Omega$$

$$Z_{in} = 2 + 1.5j \Rightarrow I_1 = 16\angle-36.9^\circ, \quad I_2 = 25.3\angle-55.4^\circ, \quad I_3 = 11.3\angle98.1^\circ$$

$$P_1 = \frac{Z_1 |I_1|^2}{2} = (192 + 0j) \text{ VA} \Rightarrow P_{av1} = 192 \text{ W}, \quad Q_1 = 0 \text{ VAR}, \quad PF_1 = 1$$

$$P_2 = \frac{Z_2 |I_2|^2}{2} = (0 + 320j) \text{ VA} \Rightarrow P_{av2} = 0 \text{ W}, \quad Q_2 = 320 \text{ VAR}, \quad PF_2 = 0, \text{ lag}$$

$$P_3 = \frac{Z_3 |I_3|^2}{2} = (64 - 128j) \text{ VA} \Rightarrow P_{av3} = 64 \text{ W}, \quad Q_3 = -28 \text{ VAR}, \quad PF_3 = 0.45, \text{ lead}$$

$$P_s = -\frac{V_s I_1^*}{2} = (-256 - 192j) \text{ VA} \Rightarrow P_{avs} = -256 \text{ W}, \quad Q_s = -192 \text{ VAR}$$

$$\sum_k P_k = 0, \quad \sum_k P_{avk} = 0, \quad \sum_k Q_k = 0, \quad \sum_k |P_k| \neq 0$$

Example (Transmission line loss)

Loads with low power factor increase transmission line loss.

$$V_m = |V_L| = 300\text{V}, \quad P_{avL} = 900\text{W}, \quad PF_L = 1, \quad r = 1\Omega$$


$$P_{avL} = \frac{V_m I_m}{2} \cos(\angle Z) \Rightarrow 900 = \frac{300 I_m}{2} \times 1 \Rightarrow I_m = 6\text{A}$$

$$P_{avr} = \frac{1}{2} r I_m^2 = 18 \Rightarrow \eta = \frac{900}{900 + 18} = 98\%$$

$$V_m = |V_L| = 300\text{V}, \quad P_{avL} = 900\text{W}, \quad PF_L = 0.5, \quad r = 1\Omega$$

$$P_{avL} = \frac{V_m I_m}{2} \cos(\angle Z) \Rightarrow 900 = \frac{300 I_m}{2} \times 0.5 \Rightarrow I_m = 12\text{A}$$
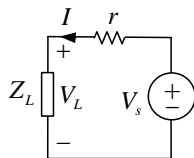
$$P_{avr} = \frac{1}{2} r I_m^2 = 72 \Rightarrow \eta = \frac{900}{900 + 72} = 93\%$$



Example (Maximum power transfer)


In a simple power transmission circuit with the transmission line impedance Z_s , the load $Z_L = Z_s^*$ absorbs the maximum power from the source.

$$I = \frac{V_s}{Z_s + Z_L} = \frac{V_s}{(R_s + R_L) + j(X_s + X_L)}$$

$$P_{avL} = \frac{\Re\{Z_L\}}{2} |I|^2 = \frac{1}{2} \frac{R_L}{(R_L + R_s)^2 + (X_L + X_s)^2} |V_s|^2$$

$$\begin{cases} \frac{\partial P_{avL}}{\partial R_L} = 0 \\ \frac{\partial P_{avL}}{\partial X_L} = 0 \end{cases} \Rightarrow \begin{cases} R_L = \sqrt{R_s^2 + (X_s + X_L)^2} \\ X_L = -X_s \end{cases}$$

$$\Rightarrow Z_L = Z_s^* = R_s - jX_s, \quad \max\{P_{avL}\} = \frac{|V_s|^2}{8R_L}$$

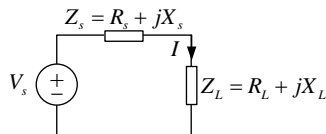

Average Power

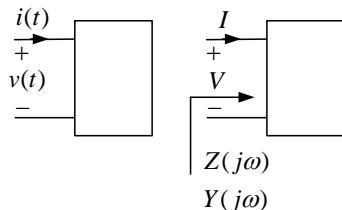


Figure: An LTI one-port with sinusoidal voltages and currents having a **same frequency**.

- **Port voltage:** $v(t) = v_1(t) + v_2(t) = V_{m1} \cos(\omega_1 t + \theta_1) + V_{m2} \cos(\omega_2 t + \theta_2), \omega_1 = \omega_2$
- **Port current:** $i(t) = i_1(t) + i_2(t) = I_{m1} \cos(\omega_1 t + \phi_1) + I_{m2} \cos(\omega_2 t + \phi_2), \omega_1 = \omega_2$
- **Overall port voltage:** $v(t) = V_m \cos(\omega_1 t + \theta)$
- **Overall port current:** $i(t) = I_m \cos(\omega_1 t + \phi)$
- **Instantaneous power:** $p(t) = \frac{V_m I_m}{2} \cos(2\omega t + \theta + \phi) + \frac{V_m I_m}{2} \cos(\theta - \phi)$
- **Average power:** $P_{av} = \frac{1}{T} \int_0^T p(t) dt = \frac{V_m I_m}{2} \cos(\theta - \phi)$

Additive Property of Average Power

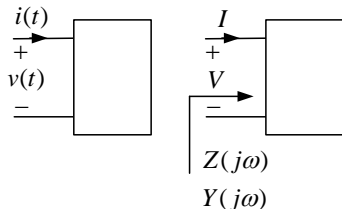


Figure: An LTI one-port with sinusoidal voltage and currents having different frequencies.

- **Port voltage:** $v(t) = v_1(t) + v_2(t) = V_{m1} \cos(\omega_1 t + \theta_1) + V_{m2} \cos(\omega_2 t + \theta_2), \omega_1 \neq \omega_2$
- **Port current:** $i(t) = i_1(t) + i_2(t) = I_{m1} \cos(\omega_1 t + \phi_1) + I_{m2} \cos(\omega_2 t + \phi_2), \omega_1 \neq \omega_2$
- **Instantaneous power:**


$$p(t) = \frac{V_{m1}I_{m1}}{2} \cos(2\omega_1 t + \theta_1 + \phi_1) + \frac{V_{m1}I_{m1}}{2} \cos(\theta_1 - \phi_1) + \frac{V_{m2}I_{m2}}{2} \cos(2\omega_2 t + \theta_2 + \phi_2) + \frac{V_{m2}I_{m2}}{2} \cos(\theta_2 - \phi_2) + \frac{V_{m1}I_{m2}}{2} \cos((\omega_1 + \omega_2)t + \theta_1 + \phi_2) + \frac{V_{m1}I_{m2}}{2} \cos((\omega_1 - \omega_2)t + \theta_1 - \phi_2) + \frac{V_{m2}I_{m1}}{2} \cos((\omega_2 + \omega_1)t + \theta_2 + \phi_1) + \frac{V_{m2}I_{m1}}{2} \cos((\omega_2 - \omega_1)t + \theta_2 - \phi_1)$$

- **Average power:** $P_{av} = \frac{1}{T} \int_0^T p(t) dt, \quad T = LCM(T_1, T_2)$
- **Average power:** $P_{av} = \frac{V_{m1}I_{m1}}{2} \cos(\theta_1 - \phi_1) + \frac{V_{m2}I_{m2}}{2} \cos(\theta_2 - \phi_2) = P_{av1} + P_{av2}$

Additive Property of Average Power

Example (Additive property of average power)

The average power is identical for the same and different frequency conditions in the circuit below provided that $\phi_1 - \phi_2 = \pm 90^\circ$, where $I_1 = |I_1|/\phi_1$ and $I_2 = |I_2|/\phi_2$.

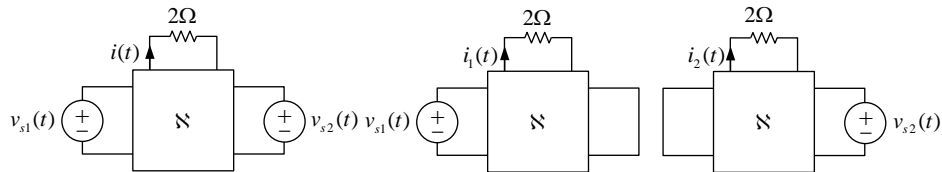

$$\omega_1 \neq \omega_2 \Rightarrow P_{av} = P_{av1} + P_{av2} = \frac{1}{2}R[|I_1|^2 + |I_2|^2]$$

$$\omega_1 = \omega_2 \Rightarrow P_{av} = \frac{1}{2}R|I|^2 = \frac{1}{2}R|I_1 + I_2|^2 = \frac{1}{2}R(I_1 + I_2)(I_1 + I_2)^* = \frac{1}{2}R[|I_1|^2 + |I_2|^2 + 2\Re\{I_1 I_2^*\}]$$

$$\omega_1 = \omega_2 \Rightarrow P_{av} = \frac{1}{2}R[|I_1|^2 + |I_2|^2 + 2I_1 I_2 \cos(\phi_1 - \phi_2)] \Rightarrow \phi_1 - \phi_2 = \pm 90^\circ$$

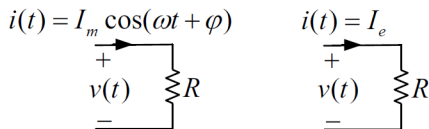


Figure: **Effective value** is equivalent to **root mean square (RMS) value**.

- **Average power:** $P_{av} = \frac{1}{T} \int_0^T p(t) dt = \frac{R}{T} \int_0^T i^2(t) dt = \frac{1}{2} R I_m^2$
- **Effective power:** $P = R I_e^2$
- **Effective current:** $P = P_{av} \Rightarrow I_e = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt} = \frac{I_m}{\sqrt{2}}$
- **Average power:** $P_{av} = \frac{1}{2} R I_m^2 = R I_e^2$

Example (Effective value of the sum of two sinusoidal voltages)

The effective value of the sum of two sinusoidal voltages depends on whether the voltages have equal or non-equal frequencies.

$$v(t) = V_{m1} \cos(\omega_1 t + \theta_1) + V_{m2} \cos(\omega_2 t + \theta_2), \quad T = \text{LCM}(T_1, T_2)$$

$$V_{av} = V_{dc} = \frac{1}{T} \int_0^T v(t) dt = 0$$

$$V_{rms} = V_e = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt} = \begin{cases} \frac{\sqrt{V_{m1}^2 + V_{m2}^2}}{\sqrt{2}}, & \omega_1 \neq \omega_2 \\ \frac{V_m}{\sqrt{2}} = \frac{\sqrt{V_{m1}^2 + V_{m2}^2 + 2V_{m1}V_{m2}\cos(\theta_1 - \theta_2)}}{\sqrt{2}}, & \omega_1 = \omega_2 \end{cases}$$

Network Function

Network Function

Definition (Network Function)

In a single input LTI circuit with sinusoidal steady state, the network function $H(j\omega) = \frac{Y(j\omega)}{W(j\omega)}$ is defined as the ratio of the phasor $Y(j\omega)$ of a desired response to the phasor $W(j\omega)$ of the sinusoidal input with the frequency ω .

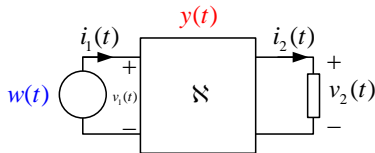


Figure: Definition of **network function** for a single input LTI circuit.

Types of Network Functions

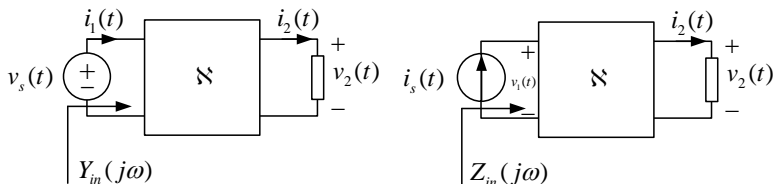


Figure: Different types of **network functions**.

- **Driving point impedance:** $H(j\omega) = \frac{V_1}{I_s}$
- **Driving point admittance:** $H(j\omega) = \frac{I_1}{V_s}$
- **Transfer impedance:** $H(j\omega) = \frac{V_2}{I_s}$
- **Transfer admittance:** $H(j\omega) = \frac{I_2}{V_s}$
- **Voltage gain:** $H(j\omega) = \frac{V_2}{V_s}$
- **Current gain:** $H(j\omega) = \frac{I_2}{I_s}$

Properties of Network Functions

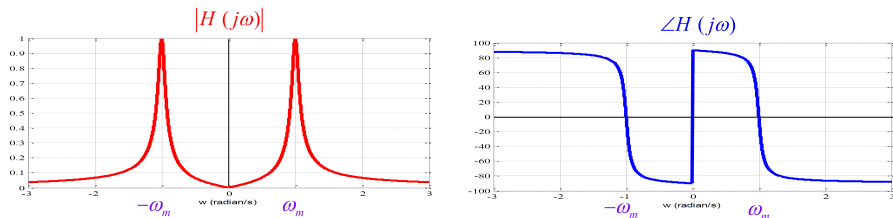



Figure: Due to Hermitian symmetry, the amplitude and phase of a network functions is usually plotted for $\omega \geq 0$. The amplitude is usually plotted in logarithmic scale.

- **Network function:** $H(j\omega) = |H(j\omega)| \underline{\angle H(j\omega)} = \Re\{H(j\omega)\} + j\Im\{H(j\omega)\}$
- **Hermitian symmetry:** $|H(-j\omega)| = |H(j\omega)|$, $\underline{\angle H(-j\omega)} = -\underline{\angle H(j\omega)}$
- **Hermitian symmetry:** $\Re\{H(-j\omega)\} = \Re\{H(j\omega)\}$, $\Im\{H(-j\omega)\} = -\Im\{H(j\omega)\}$
- **Output response:** $Y(j\omega) = H(j\omega)W(j\omega) \Rightarrow \begin{cases} |Y(j\omega)| = |H(j\omega)||W(j\omega)| \\ \underline{\angle Y(j\omega)} = \underline{\angle H(j\omega)} + \underline{\angle W(j\omega)} \end{cases}$
- **Output response:**

$$w(t) = \sum_k A_k \cos(\omega_k t + \theta_k) \Rightarrow y(t) = \sum_k A_k |H(j\omega_k)| \cos(\omega_k t + \theta_k + \underline{\angle H(j\omega_k)})$$

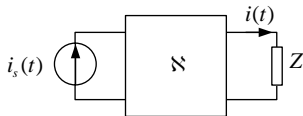Example (Network Function)

Network function can be used to calculate the circuit response to different sinusoidal inputs.



$$i_s(t) = 3 \cos(t) + \cos(2t + 20^\circ), \quad H(j\omega) = \frac{I}{I_s} = \frac{1 - j\omega}{1 + j\omega}, \quad Z = R = 2\Omega$$

$$i_{s1}(t) = 3 \cos(t) \equiv I_{s1} = 3\angle 0^\circ \Rightarrow I_1 = H(j1)I_{s1} = \frac{1 - j1}{1 + j1} 3\angle 0^\circ = 3\angle -90^\circ$$

$$i_{s2}(t) = \cos(2t + 20^\circ) \equiv I_{s2} = 1\angle 20^\circ \Rightarrow I_2 = H(j2)I_{s2} = \frac{1 - j2}{1 + j2} 1\angle 20^\circ = 1\angle -107^\circ$$


$$i(t) = i_1(t) + i_2(t) = 3 \sin(t) + \cos(2t - 107^\circ)$$

$$\omega_1 \neq \omega_2 \Rightarrow P_{av} = P_{av1} + P_{av2} = \frac{1}{2}R|I_1|^2 + \frac{1}{2}R|I_2|^2 = 3^2 + 1^2 = 10W$$

Network Function

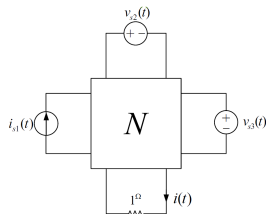Example (Network Function)

In a multi-input LTI circuit, the impact of each input on a desired response is described by a network function.



$$H_1(j\omega) = \frac{I}{I_{s1}} \Big|_{V_{s2}=0, V_{s3}=0} = \frac{2 + j\omega}{1 + j\omega}, \quad H_2(j\omega) = \frac{I}{V_{s2}} \Big|_{I_{s1}=0, V_{s3}=0} = \frac{3 - 2j\omega}{1 + j\omega}, \quad H_3(j\omega) = \frac{I}{V_{s3}} \Big|_{I_{s1}=0, V_{s2}=0} = \frac{4 + j\omega}{1 + j\omega}$$

$$i_{s1}(t) = \cos(t), \quad v_{s2}(t) = 2 \cos(t), \quad v_{s3}(t) = 3 \cos(t)$$

$$I_1 = H_1(j1)I_{s1} = \frac{2 + j1}{1 + j1} 1\angle 0^\circ, \quad I_2 = H_2(j1)V_{s2} = \frac{3 - j2}{1 + j1} 2\angle 0^\circ, \quad I_3 = H_3(j1)V_{s3} = \frac{4 + j1}{1 + j1} 3\angle 0^\circ$$



$$I = I_1 + I_2 + I_3 = 10 - 10j = 10\sqrt{2}\angle -45^\circ \Rightarrow i(t) = 10\sqrt{2} \cos(t - 45^\circ) = 10 \cos(t) + 10 \sin(t)$$

$$P_{av} = \frac{1}{2} R |I|^2 = 100$$

Network Function

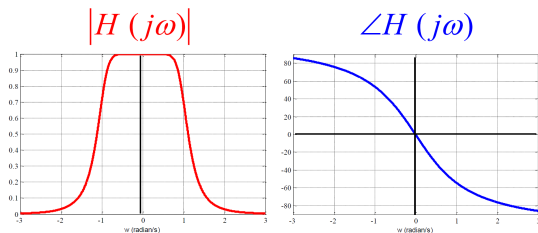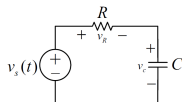Example (Network Function)

Phasor analysis can be used to determine network functions.




$$H(j\omega) = \frac{V_c}{V_s} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{1 + jRC\omega}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (RC\omega)^2}}, \quad \angle H(j\omega) = -\tan^{-1}(RC\omega)$$

Network Function

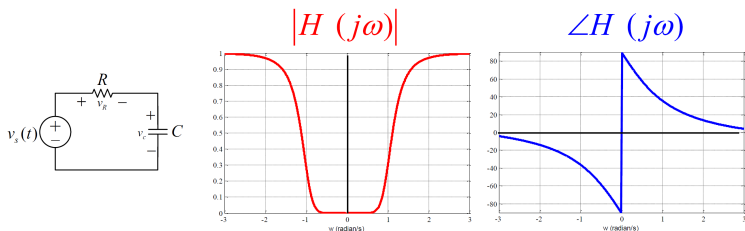Example (Network Function)

Phasor analysis can be used to determine network functions.



$$H(j\omega) = \frac{V_R}{V_s} = \frac{R}{R + \frac{1}{j\omega C}} = \frac{jRC\omega}{1 + jRC\omega}$$

$$|H(j\omega)| = \frac{RC|\omega|}{\sqrt{1 + (RC\omega)^2}}, \quad \angle H(j\omega) = \pm 90^\circ - \tan^{-1}(RC\omega)$$

Filters

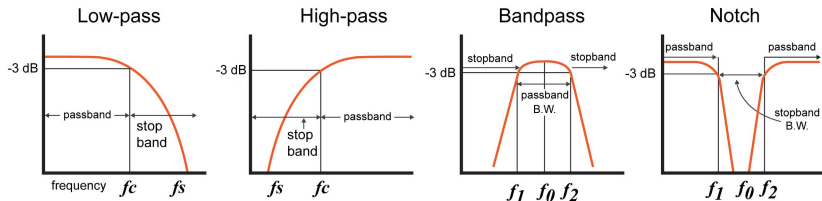


Figure: Frequency response of different filters. Note that the horizontal axis may be frequency $f = \frac{\omega}{2\pi}$ or angular frequency ω .

Filter types

- Lowpass filter (LPF)
- Highpass filter (HPF)
- Bandpass filter (BPF)
- Bandstop filter (Notch)

- 3-dB cut off frequency: $|H(j\omega_c)| = \frac{\max\{|H(j\omega)|\}}{\sqrt{2}}$

Parallel RLC Circuit

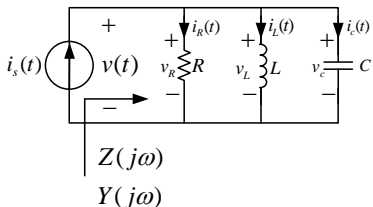


Figure: A Parallel RLC circuit with natural frequency $\omega_0 = \frac{1}{\sqrt{LC}}$, damping factor $\alpha = \frac{1}{2RC}$, and quality factor $Q = \frac{\omega_0}{2\alpha} = \frac{R\sqrt{C}}{\sqrt{L}}$ can act like a BPF.

- **Network function:** $H(j\omega) = \frac{V}{I_s} = Z(j\omega) = \frac{1}{\frac{1}{R} + j(c\omega - \frac{1}{L\omega})} = \frac{R}{1 + jQ(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega})}$
- **Frequency response:**
 $|H(j\omega)| = \frac{R}{\sqrt{1 + Q^2(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega})^2}}, \quad \angle H(j\omega) = -\tan^{-1}(Q(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}))$
- **Amplitude response:** $20 \log_{10}(|H(j\omega)|) = 20 \log_{10}\left(\frac{R}{\sqrt{1 + Q^2(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega})^2}}\right)$
- **Phase response:** $\angle H(j\omega) = -\tan^{-1}(Q(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}))$

Parallel RLC Circuit

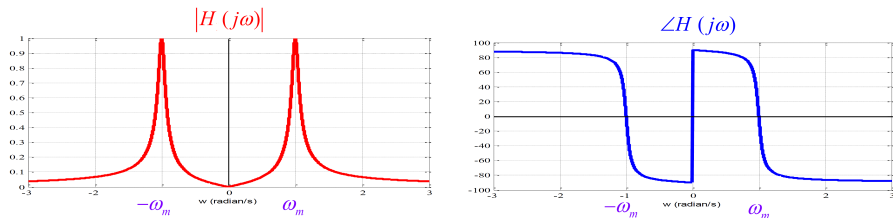


Figure: Typical frequency response of a parallel RLC circuit.

- 3-dB cut-off frequencies: $|H(j\omega)| = \frac{|H|_{max}}{\sqrt{2}} \Rightarrow \frac{R}{\sqrt{1+Q^2\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)^2}} = \frac{R}{\sqrt{2}}$
- 3-dB cut-off frequencies: $\omega_{1,2} = \omega_0\left(\frac{\pm 1}{2Q} + \sqrt{1 + \frac{1}{4Q^2}}\right)$
- 3-dB bandwidth: $\Delta\omega = |\omega_2 - \omega_1| = \frac{\omega_0}{Q} = 2\alpha$
- Quality factor: $Q = \frac{\omega_0}{2\alpha} = \frac{\omega_0}{\Delta\omega}$
- Central frequency: $\omega_0 = \sqrt{\omega_1\omega_2} = \frac{1}{\sqrt{LC}}$

Parallel RLC Circuit

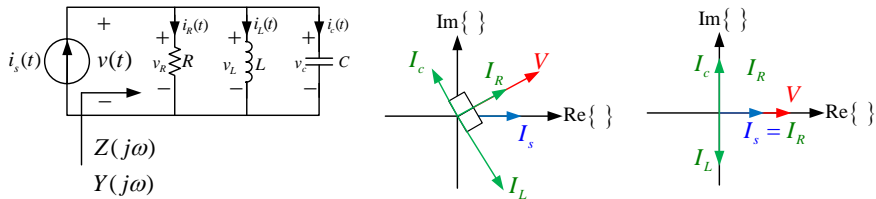



Figure: Resonance in a parallel RLC circuit.

- **Network function:** $H(j\omega) = \frac{1}{\frac{1}{R} + j\left(c\omega - \frac{1}{L\omega}\right)} = \frac{R}{1 + jQ\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)}$
- **Resonance frequency:** $c\omega - \frac{1}{L\omega} = 0 \Rightarrow \omega_r = \frac{1}{\sqrt{LC}}$

Filtering Response

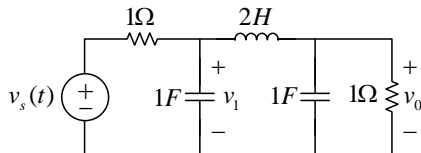Example (Third-order lowpass filter)

Filtering response can be investigated using phasor analysis.



$$\frac{V_1 - V_s}{1} + \frac{V_1}{1/j\omega} + \frac{V_1 - V_o}{j2\omega} = 0, \quad \frac{V_o}{1} + \frac{V_o}{1/j\omega} + \frac{V_o - V_1}{j2\omega} = 0$$

$$H(j\omega) = \frac{V_o}{V_s} = \frac{1}{2(1 - 2\omega^2) + j2\omega(\omega^2 - 2)}$$





$$|H(j\omega)| = \frac{1}{2\sqrt{1 + \omega^6}}, \quad \angle H(j\omega) = -\tan^{-1}\left(\frac{\omega(\omega^2 - 2)}{1 - 2\omega^2}\right)$$

$$|H(j\omega)| = \frac{1}{\sqrt{2}} \frac{1}{2} \Rightarrow \omega_c = 1$$

Filtering Response

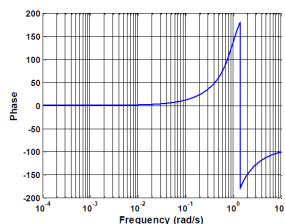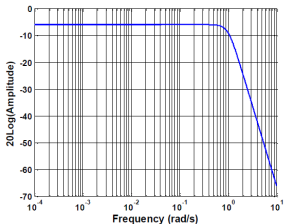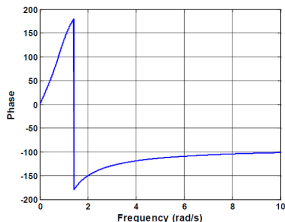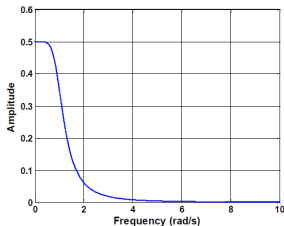Example (Third-order lowpass filter (cont.))

Filtering response can be investigated using phasor analysis.



Example (Third-order lowpass filter (cont.))

Filtering response can be investigated using phasor analysis.

$$v_s(t) = 2 + 4 \cos(t) - 6 \sin\left(\frac{\sqrt{2}}{2}t + 20^\circ\right) + 3 \cos(\sqrt{2}t - 40^\circ) + 8 \cos(10t + 30^\circ)$$

$$v_o(t) = 2|H(j0)| \cos(0t + \angle H(j0)) + 4|H(j1)| \cos(t + \angle H(j1)) \\ - 6|H(j\frac{\sqrt{2}}{2})| \sin\left(\frac{\sqrt{2}}{2}t + 20^\circ + \angle H(j\frac{\sqrt{2}}{2})\right) + 3|H(j\sqrt{2})| \cos(\sqrt{2}t - 40^\circ + \angle H(j\sqrt{2})) \\ + 8|H(j10)| \cos(10t + 30^\circ + \angle H(j10))$$

$$v_o(t) = 2\frac{1}{2} \cos(0t + 0^\circ) + 4\frac{1}{2\sqrt{2}} \cos\left(t + \frac{3\pi}{4}\right) - 6\frac{\sqrt{2}}{3} \sin\left(\frac{\sqrt{2}}{2}t + 20^\circ + \frac{\pi}{2}\right) \\ + 3\frac{1}{6} \cos(\sqrt{2}t - 40^\circ + \pi) + 8\frac{1}{2000} \cos(10t + 30^\circ - 91.2^\circ)$$

The End