

## MATHEMATICAL QUESTIONS

### Question 1

Consider the triangle periodic signal shown in Fig. 1.

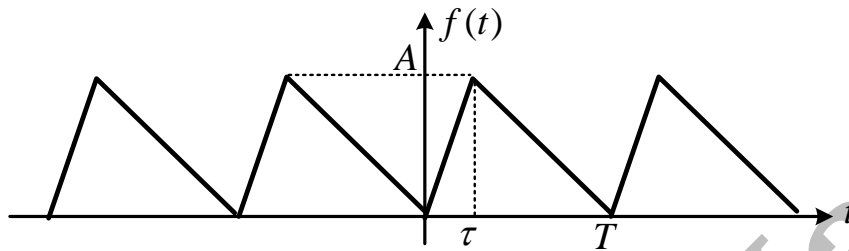


Figure 1: Triangle periodic signal.

(a) Express the periodic signal  $f(t)$  in terms of elementary signals for  $0 \leq t < T$ .

For  $0 \leq t \leq \tau$ , we have

$$f(t) = \frac{A}{\tau}t$$

For  $\tau < t \leq T$ , we have,

$$f(t) = A - \frac{A}{T-\tau}(t-\tau)$$

So,

$$f(t) = \frac{A}{\tau}t(u(t) - u(t-\tau)) + (A - \frac{A}{T-\tau}(t-\tau))(u(t-\tau) - u(t-T))$$

$$f(t) = \frac{A}{\tau}r(t) - \frac{AT}{\tau(T-\tau)}r(t-\tau) + \frac{A}{T-\tau}r(t-T)$$


(b) Find the average and RMS values of  $f(t)$ .

$$f_{average} = \frac{1}{T} \int_0^T f(t)dt = \frac{1}{T} \int_0^{\tau} \frac{A}{\tau}t dt + \frac{1}{T} \int_{\tau}^T (A - \frac{A}{T-\tau}(t-\tau))dt = \frac{A}{2}$$

$$f_{rms} = \sqrt{\frac{1}{T} \int_0^T f^2(t)dt} = \sqrt{\frac{1}{T} \int_0^{\tau} (\frac{A}{\tau}t)^2 dt + \frac{1}{T} \int_{\tau}^T (A - \frac{A}{T-\tau}(t-\tau))^2 dt} = \frac{A}{\sqrt{3}}$$

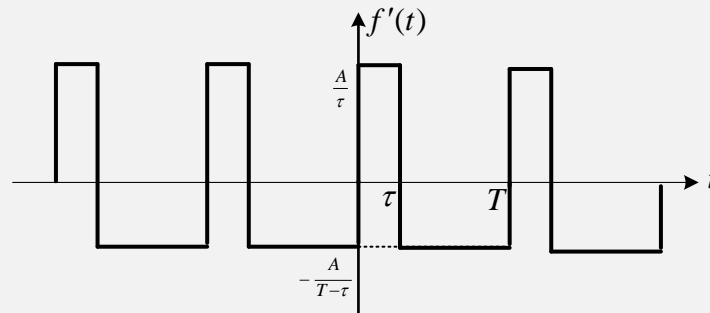(c) Plot  $f'(t)$ , the derivative of  $f(t)$ .

The derivative  $f'(t) = \frac{A}{\tau}u(t) - \frac{AT}{\tau(T-\tau)}u(t-\tau) + \frac{A}{T-\tau}u(t-T)$  is plotted as



(d) Let  $g(t) = B + f(t)$ , where  $B$  is a real number. Find the average and RMS values of  $g(t)$ .

$$g_{av} = \frac{1}{T} \int_0^T (f(t) + B) dt = \frac{1}{T} \int_0^T B dt + \frac{1}{T} \int_0^T f(t) dt = f_{average} + B = \frac{A}{2} + B$$

$$g_{rms} = \sqrt{\frac{1}{T} \int_0^T (f(t) + B)^2 dt} = \sqrt{\frac{1}{T} \int_0^T f^2(t) dt + \frac{1}{T} \int_0^T B^2 dt + \frac{1}{T} \int_0^T 2Bf(t) dt}$$

$$= \sqrt{f_{rms}^2 + B^2 + 2Bf_{av}} = \sqrt{\frac{A^2}{3} + B^2 + BA}$$

## Question 2

Calculate the delivered power and voltage of the dependent source in Fig. 2.

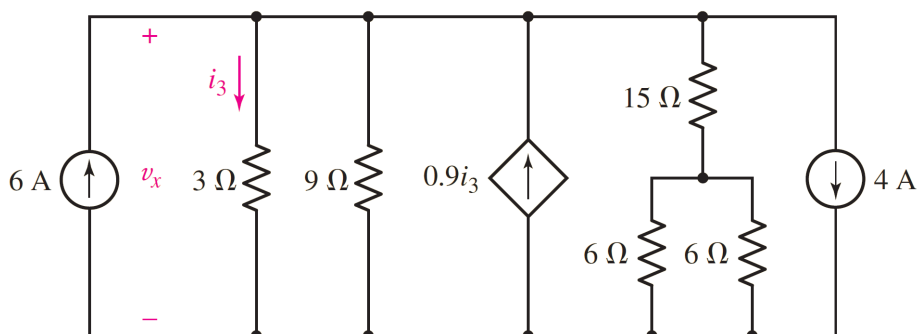


Figure 2: A circuit with dependent source.

$$i_3 = \frac{v_x}{3} \rightarrow v_x = 3i_3$$

$$KCL : -6 + \frac{v_x}{3} + \frac{v_x}{9} - 0.9i_3 + \frac{v_x}{15 + (6||6)} + 4 = 0$$

Hence,

$$-6 + i_3 + \frac{i_3}{3} - 0.9i_3 + \frac{i_3}{6} + 4 = 0 \rightarrow i_3 = \frac{10}{3} \rightarrow v_x = 10$$

So, the delivered power is

$$p = (0.9i_3)(v_x) = (0.9i_3)(3i_3) = (3)(10) = 30$$

### Question 3

Consider the linear time-variant capacitor of Fig. 3 with the capacitance  $C(t) = C_0 + C_1 \cos(\omega_1 t)$ .

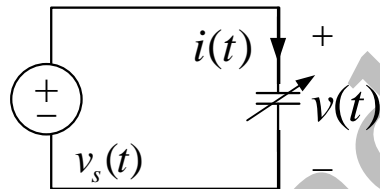


Figure 3: A linear time-variant capacitor with capacitance  $C(t) = C_0 + C_1 \cos(\omega_1 t)$ .

(a) Find the capacitor current if  $v_s(t) = A \cos(\omega_2 t)$ . Further, calculate the energy stored in the capacitor during the interval  $[0, t]$ .

$$i(t) = \frac{d}{dt}(C(t)v(t)), \quad v(t) = v_s(t) = A \cos(\omega_2 t)$$

$$\Rightarrow i(t) = \frac{d}{dt}[(c_0 + c_1 \cos(\omega_1 t))(A \cos(\omega_2 t))] = \frac{d}{dt}[c_0 A \cos(\omega_2 t) + c_1 A \cos(\omega_1 t) \cos(\omega_2 t)]$$

$$= -c_0 A \omega_2 \sin(\omega_2 t) - c_1 A \omega_1 \sin(\omega_1 t) \cos(\omega_2 t) - c_1 A \omega_2 \sin(\omega_2 t) \cos(\omega_1 t)$$

$$w(0, t) = \int_0^t v(x)i(x)dx = \int_0^t -c_0 A^2 \omega_2 \sin(\omega_2 x) \cos(\omega_2 x) dx$$

$$+ \int_0^t -c_1 A^2 \omega_1 \sin(\omega_1 x) \cos^2(\omega_2 x) dx + \int_0^t -c_1 A^2 \omega_2 \sin(\omega_2 x) \cos(\omega_1 x) \cos(\omega_2 x) dx =$$

$$= \frac{c_0 A^2}{4} [\cos(2\omega_2 t) - 1] + c_1 A^2 \omega_1 \left[ \frac{\cos((2\omega_2 + \omega_1)t) - 1}{4(2\omega_2 + \omega_1)} + \frac{1 - \cos((2\omega_2 - \omega_1)t)}{4(2\omega_2 - \omega_1)} + \frac{\cos(\omega_1 t) - 1}{2\omega_1} \right] + c_1 A^2 \omega_2 \left[ \frac{\cos((2\omega_2 + \omega_1)t) - 1}{4(2\omega_2 + \omega_1)} + \frac{\cos((2\omega_2 - \omega_1)t) - 1}{4(2\omega_2 - \omega_1)} \right]$$

(b) Find the capacitor current if  $v_s(t) = A$ . Further, calculate the energy stored in the capacitor during the interval  $[0, t]$ . Does the capacitor act like open circuit as  $t \rightarrow \infty$ ?

$$i(t) = \frac{d}{dt}(C(t)v(t)), \quad v(t) = v_s(t) = A$$

$$\Rightarrow i(t) = \frac{d}{dt}[A(c_0 + c_1 \cos(\omega_1 t))] = -c_1 A \omega_1 \sin(\omega_1 t)$$

$$w(0, t) = \int_0^t v(x)i(x)dx = \int_0^t -c_1 A^2 \omega_1 \sin(\omega_1 x) dx = c_1 A^2 (\cos(\omega_1 t) - 1)$$

Capacitor doesn't act like open circuit as  $t \rightarrow \infty$  since the current doesn't converge to zero as  $t \rightarrow \infty$ .

(c) Find the capacitor current if  $v_s(t) = A$  and  $C_1 = 0$ . Does the capacitor act like open circuit as  $t \rightarrow \infty$ ?

$$i(t) = \frac{d}{dt}(C(t)v(t)), \quad v(t) = v_s(t) = A$$

$$\Rightarrow i(t) = \frac{d}{dt}[Ac_0] = 0$$

Capacitor acts like open circuit as  $t \rightarrow \infty$  since the current is always zeros and therefore, converges to zero as  $t \rightarrow \infty$ .

## Question 4

In the circuit shown in Fig. 4,  $v_s(t) = A \cos(\omega t)u(t)$  and  $i_s(t) = B(1 - e^{-\alpha t})u(t)$ . Calculate  $v_L(t)$  and  $i_C(t)$ . Is  $v_L(t)$  continuous? How about  $i_C(t)$ ?

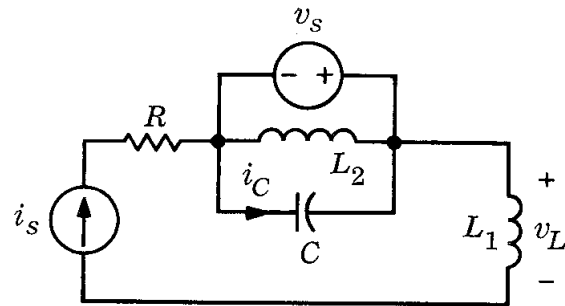


Figure 4: A circuit with LTI elements.

$$i_C = C \frac{dv_C}{dt}, \quad v_C = -v_s = -A \cos(\omega t)u(t)$$

$$\rightarrow i_C(t) = AC[\omega \sin(\omega t)u(t) - \delta(t)]$$

$$v_L = L_1 \frac{di_{L_1}}{dt}, \quad i_{L_1} = i_s = B(1 - e^{-\alpha t})u(t)$$

$$\rightarrow v_L(t) = L_1 B \alpha e^{-\alpha t} u(t) + L_1 B (1 - e^{-\alpha t}) \delta(t) = L_1 B \alpha e^{-\alpha t} u(t)$$

$v_L(t)$  is not continuous due to function  $u(t)$  which creates a discontinuity at  $t = 0$   
 $i_C(t)$  is not continuous due to function  $\delta(t)$  which creates a discontinuity at  $t = 0$ .

---

## SOFTWARE QUESTIONS

---

### Question 5

Write a simple MATLAB program that calculates the average and RMS values of a given periodic signal  $f(t)$ . The function  $f(t)$  is represented by a function handle in its fundamental period  $t \in [0, T]$ .

Here is a sample MATLAB implementation of the desired function.

```
1 function [avg, rms] = avg_rms_cal(f, T)
2
3 % average
4 avg = integral(f,0,T)/T;
```

```

5
6 % rms
7 fsqr = @(t) f(t).^2;
8 rms = sqrt(integral(fsqr,0,T)/T);
9
10 end

```

You may use the following mfile to call the developed function and see its results.

```

1 clear all
2 clc
3
4 % sample average and rms calculation
5 [avg, rms] = avg_rms_cal(@sin, 2*pi);
6 avg
7 rms
8
9 % sample average and rms calculation
10 f = @(t) t;
11 [avg, rms] = avg_rms_cal(f, 1);
12 avg
13 rms

```

The mfile prints the average values of  $-1.6289 \times 10^{-17}$  and 0.5000 and the RMS values of 0.7071 and 0.5774 for the periodic functions  $f(t) = \sin(t)$ ,  $0 \leq t \leq 2\pi$  and  $f(t) = t$ ,  $0 \leq t \leq 1$ , respectively.

## BONUS QUESTIONS

### Question 6

Find the RMS and average values of the real periodic signal  $f(t) = a_0 + \sum_{k=1}^{\infty} [a_k \cos(\frac{2\pi k}{T}t) + b_k \sin(\frac{2\pi k}{T}t)]$  expanded in its Fourier series form.

Before answering the main problem, let us express a lemma.

**Lemma:** For integer numbers  $n$  and  $m$ ,

$$\int_0^T \cos\left(\frac{2\pi m}{T}t\right) \cos\left(\frac{2\pi n}{T}t\right) dt = \begin{cases} T/2 & m = n \neq 0 \\ T/2 & m = -n \neq 0 \\ T & m = n = 0 \\ 0 & |m| \neq |n| \end{cases} \quad (1)$$

$$\int_0^T \sin\left(\frac{2\pi m}{T}t\right) \sin\left(\frac{2\pi n}{T}t\right) dt = \begin{cases} T/2 & m = n \neq 0 \\ -T/2 & m = -n \neq 0 \\ 0 & m = n = 0 \\ 0 & |m| \neq |n| \end{cases} \quad (2)$$

$$\int_0^T \sin\left(\frac{2\pi m}{T}t\right) \cos\left(\frac{2\pi n}{T}t\right) dt = 0 \quad (3)$$

Proving the lemma is straightforward and it is suggested to do it yourself.

**Average:**

We know that integral of a sinusoidal signal on a period is zero (check it!). So,

$$f_{av} = \frac{1}{T} \int_0^T f(t) dt = \frac{1}{T} \int_0^T a_0 dt + \frac{1}{T} \int_0^T \underbrace{\sum_{k=1}^{\infty} [a_k \cos(\frac{2\pi k}{T}t) + b_k \sin(\frac{2\pi k}{T}t)]}_{y(t)} dt$$

$$= a_0 + y_{av} = a_0 + \frac{1}{T} \sum_{k=1}^{\infty} \underbrace{\int_0^T [a_k \cos(\frac{2\pi k}{T}t) + b_k \sin(\frac{2\pi k}{T}t)] dt}_0 = a_0$$

Note that  $y_{av} = 0$ .

**RMS:**

The signal  $f(t)$  consists of a DC term  $a_0$  and an AC term  $y(t)$  with zero average  $y_{av} = 0$  as

$$f(t) = a_0 + \underbrace{\sum_{k=1}^{\infty} [a_k \cos(\frac{2\pi k}{T}t) + b_k \sin(\frac{2\pi k}{T}t)]}_{y(t)}$$

So,

$$f_{rms} = \sqrt{\frac{1}{T} \int_0^T f^2(t) dt} = \sqrt{a_0^2 + y_{rms}^2 + 2a_0 y_{av}} = \sqrt{a_0^2 + y_{rms}^2}$$

, where

$$y_{rms} = \sqrt{\frac{1}{T} \int_0^T y^2(t) dt}$$

Note that all the terms of  $y(t)$  are periodic with the period  $T$ . First, we should compute  $y^2(t)$ :

$$y^2(t) = \left( \sum_{i=1}^{\infty} [a_i \cos(\frac{2\pi i}{T}t) + b_i \sin(\frac{2\pi i}{T}t)] \right) \left( \sum_{j=1}^{\infty} [a_j \cos(\frac{2\pi j}{T}t) + b_j \sin(\frac{2\pi j}{T}t)] \right)$$

$$= \sum_{i=1}^{\infty} \sum_{j=1}^{\infty} a_i a_j \cos(\frac{2\pi i}{T}t) \cos(\frac{2\pi j}{T}t) + \sum_{i=1}^{\infty} \sum_{j=1}^{\infty} b_i b_j \sin(\frac{2\pi i}{T}t) \sin(\frac{2\pi j}{T}t)$$

$$+ \sum_{i=1}^{\infty} \sum_{j=1}^{\infty} a_i b_j \cos(\frac{2\pi i}{T}t) \sin(\frac{2\pi j}{T}t) + \sum_{i=1}^{\infty} \sum_{j=1}^{\infty} b_i a_j \sin(\frac{2\pi i}{T}t) \cos(\frac{2\pi j}{T}t)$$

Next, we should compute  $\int_0^T y^2(t) dt$  which means putting an integral before each of above terms (don't be afraid of these long terms, it is just an expansion).

$$\int_0^T y^2(t) dt = \sum_{i=1}^{\infty} \sum_{j=1}^{\infty} a_i a_j \int_0^T \cos(\frac{2\pi i}{T}t) \cos(\frac{2\pi j}{T}t) dt + \sum_{i=1}^{\infty} \sum_{j=1}^{\infty} b_i b_j \int_0^T \sin(\frac{2\pi i}{T}t) \sin(\frac{2\pi j}{T}t) dt$$

$$+ \sum_{i=1}^{\infty} \sum_{j=1}^{\infty} a_i b_j \int_0^T \cos(\frac{2\pi i}{T}t) \sin(\frac{2\pi j}{T}t) dt + \sum_{i=1}^{\infty} \sum_{j=1}^{\infty} b_i a_j \int_0^T \sin(\frac{2\pi i}{T}t) \cos(\frac{2\pi j}{T}t) dt$$

Now, we use the lemma. Last two terms are zero because they are made of the product of sines and cosines which are orthogonal in a period as given in (3). From first two terms, only the same-frequency sines and cosines remain as can be interpreted from (1) and (2). So,

$$\begin{aligned}\int_0^T y^2(t)dt &= \sum_{i=1}^{\infty} a_i^2 \frac{T}{2} + \sum_{i=1}^{\infty} b_i^2 \frac{T}{2} \\ &= \frac{T}{2} \sum_{i=1}^{\infty} (a_i^2 + b_i^2)\end{aligned}$$

So far, we have proven the Parseval's theorem which is a famous theorem and you will learn its details in the engineering mathematics course. Rest of the solution is quite simple.

$$\begin{aligned}\frac{1}{T} \int_0^T y^2(t)dt &= \frac{1}{2} \sum_{i=1}^{\infty} (a_i^2 + b_i^2) \\ \Rightarrow y_{\text{rms}} &= \sqrt{\frac{1}{T} \int_0^T y^2(t)dt} = \frac{\sqrt{\sum_{i=1}^{\infty} (a_i^2 + b_i^2)}}{\sqrt{2}}\end{aligned}$$

Hence

$$f_{\text{rms}} = \sqrt{a_0^2 + \frac{1}{2} \sum_{i=1}^{\infty} (a_i^2 + b_i^2)}$$

## Question 7

Return your answers by filling the  $\LaTeX$  template of the assignment.

---

## EXTRA QUESTIONS

---

## Question 8

Feel free to solve the following questions from the book "*Basic Circuit Theory*" by C. Desoer and E. Kuh.

1. Chapter 2, question 2.
2. Chapter 2, question 7.
3. Chapter 2, question 8.
4. Chapter 2, question 10.
5. Chapter 2, question 15.



- 6. Chapter 2, question 16.**
- 7. Chapter 2, question 17.**
- 8. Chapter 2, question 18.**

Mohammad Hadi