

## MATHEMATICAL QUESTIONS

### Question 1

Find the step and impulse responses of the current  $i(t)$  in Fig. 1.

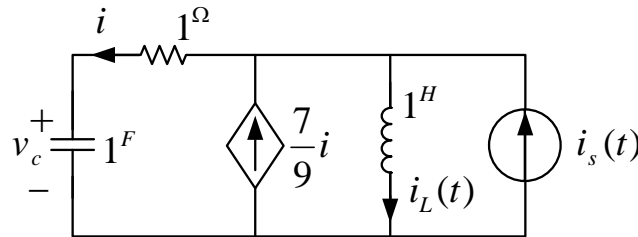


Figure 1: An LTI RLC circuit with dependent source.

**Differential equation:**

$$i = 1 \cdot \frac{dv_c}{dt}, \quad v_L = 1 \cdot \frac{di_L}{dt}$$

$$\begin{cases} \text{KCL: } -i - i_L + i_s + \frac{7}{9}i = 0 \Rightarrow i_L + \frac{2}{9}i = i_s \Rightarrow v_L + \frac{2}{9}\frac{di}{dt} = \frac{di_s}{dt} \\ \text{KVL: } v_L - v_c - i = 0 \end{cases}$$

$$\frac{2}{9} \frac{d^2 v_c}{dt^2} + \frac{dv_c}{dt} + v_c = \frac{di_s}{dt}$$

**Step Response:**

$$i_s(t) = u(t) \Rightarrow \frac{d^2 v_c}{dt^2} + \frac{9}{2} \frac{dv_c}{dt} + \frac{9}{2} v_c = \frac{9}{2} \frac{du(t)}{dt} = \frac{9}{2} \delta(t), t > 0^-$$

$$\frac{d^2 v_c}{dt^2} + \frac{9}{2} \frac{dv_c}{dt} + \frac{9}{2} v_c = 0, t > 0^+$$

$$s^2 + \frac{9}{2}s + \frac{9}{2} = 0 \Rightarrow s_{1,2} = \frac{-3}{2}, -3 \Rightarrow v_c = K_1 e^{-3t} + K_2 e^{-\frac{3}{2}t}$$

$$v_c(0^-) = v_c(0^+) = 0, \quad i_L(0^-) = i_L(0^+) = 0, \quad v'_c(0^+) = \frac{9}{2} i_s(0^+) - \frac{9}{2} i_L(0^+) = \frac{9}{2}$$

$$\Rightarrow K_1 = -3, K_2 = 3 \Rightarrow v_c(t) = 3(e^{-\frac{3}{2}t} - e^{-3t})u(t)$$

$$\Rightarrow s(t) = i(t) = \frac{dv_c(t)}{dt} = 9(e^{-3t} - \frac{1}{2}e^{-\frac{3}{2}t})u(t)$$

**Impulse Response:**

$$\Rightarrow h(t) = \frac{ds(t)}{dt} = 27\left(\frac{1}{4}e^{-\frac{3}{2}t} - e^{-3t}\right)u(t) + \frac{9}{2}\delta(t)$$

## Question 2

Find an expression for the zero-input response of  $v_1(t)$  in Fig. 2 valid for  $t > 0$  if  $v_1(0^+) = V_1$  and  $v_2(0^+) = V_2$ .

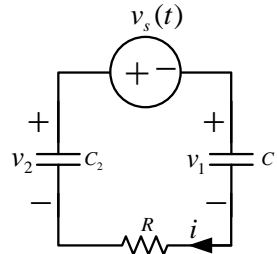


Figure 2: A circuit with two capacitors.

KVL yields

$$v_1(t) + Ri(t) - v_2(t) + v_s(t) = 0$$

while the KCL gives

$$C_1 \frac{dv_1}{dt} = i, \quad C_2 \frac{dv_2}{dt} = -i$$

The capacitor voltages should be continuous at  $t = 0$ . In fact, if the capacitor voltages experience a discontinuity at  $t = 0$ , the resistor current and voltage experience an impulse, which can not be supplied by the circuit. So,

$$v_1(0^-) = v_1(0^+) = V_1, \quad v_2(0^-) = v_2(0^+) = V_2.$$

If

$$i = C_1 \frac{dv_1}{dt} = -C_2 \frac{dv_2}{dt}$$

is integrated as  $\int_{0^+}^t$ ,

$$C_1(v_1(t) - v_1(0^+)) = -C_2(v_2(t) - v_2(0^+)) \Rightarrow v_2(t) = \frac{C_1 V_1 + C_2 V_2}{C_2} - \frac{C_1}{C_2} v_1(t)$$

From the KVL,

$$\begin{aligned} v_1 + RC_1 \frac{dv_1}{dt} + \frac{C_1}{C_2} v_1 - \frac{C_1 V_1 + C_2 V_2}{C_2} + v_s &= 0 \\ \Rightarrow \frac{dv_1}{dt} + \left( \frac{1}{RC_2} + \frac{1}{RC_1} \right) v_1 &= \frac{C_1 V_1 + C_2 V_2}{RC_1 C_2} - \frac{v_s}{RC_1} \\ \Rightarrow \frac{dv_1}{dt} + \frac{1}{RC_{eq}} v_1 &= \frac{C_1 V_1 + C_2 V_2}{RC_1 C_2} - \frac{v_s}{RC_1}, \quad C_{eq} = \frac{C_1 C_2}{C_1 + C_2} \end{aligned}$$

In the zero-input situation,

$$\frac{dv_1}{dt} + \frac{1}{RC_{eq}}v_1 = \frac{C_1V_1 + C_2V_2}{RC_1C_2}, \quad C_{eq} = \frac{C_1C_2}{C_1 + C_2}$$

Solving the differential equation yields

$$v_1(t) = A + Be^{-\frac{t}{RC_{eq}}}$$

The particular solution  $A$  satisfies the differential equation. So,

$$A = \frac{\frac{C_1V_1 + C_2V_2}{RC_1C_2}}{\frac{1}{RC_{eq}}} = \frac{C_1V_1 + C_2V_2}{RC_1C_2} R \frac{C_1C_2}{C_1 + C_2} = \frac{C_1V_1 + C_2V_2}{C_1 + C_2}$$

Further, using the initial condition,

$$V_1 = A + B \Rightarrow B = V_1 - A$$

Finally,

$$v_1(t) = A + (V_1 - A)e^{-\frac{t}{RC_{eq}}} = \frac{C_1V_1 + C_2V_2}{C_1 + C_2} - \frac{C_2(V_2 - V_1)}{C_1 + C_2} e^{-\frac{t}{RC_{eq}}}, t > 0$$

### Question 3

Calculate  $i_L(t), t > 0$  in Fig. 3, where

$$R(t) = \begin{cases} 2, & t < 0 \\ 1, & 0 < t < 2 \\ 3, & t > 2 \end{cases}$$


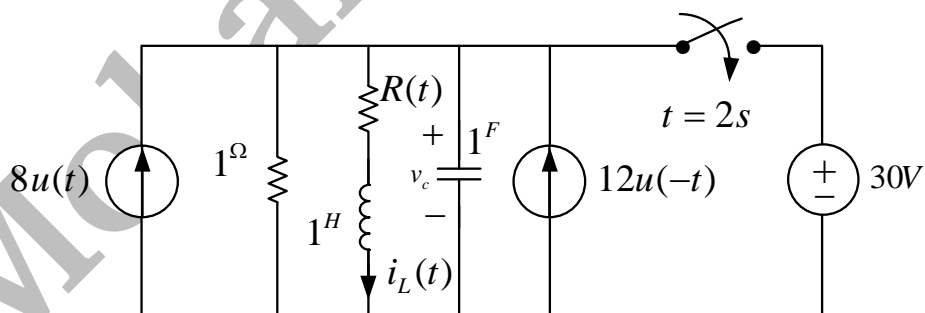


Figure 3: A second-order time-variant circuit.


The circuit should be analyzed in different time intervals:

**For  $t < 0$ :**

The circuit has been shown below,

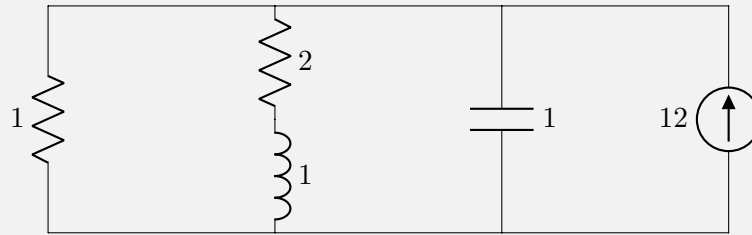

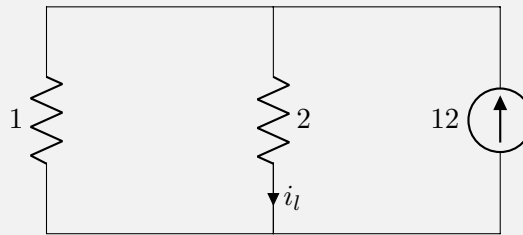The capacitor is open circuit and inductor is short circuit in  $t = 0^-$ , so the circuit is as shown below




$$i_L(t) = 12 \times \frac{1}{3} = 4 \quad v_c(t) = R_2 i_l = 2 \times 4 = 8$$

Clearly,

$$i_L(0^-) = 12 \times \frac{1}{3} = 4 \quad v_c(0^-) = R_2 i_l = 2 \times 4 = 8$$

**For  $0 < t < 2$ :**

The circuit has been shown below

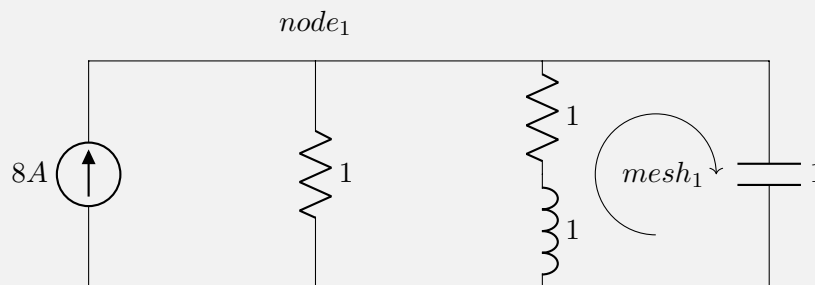

By writing KCL in  $node_1$

$$-8 + v_c + i_L + \frac{dv_c}{dt} = 0$$

By writing KVL in  $mesh_1$ ,

$$v_c = i_L + \frac{di_L}{dt}$$

Combining the written KCL and KVL equations and noting the continuity of  $i_L(t)$ ,

$$\frac{d^2 i_L}{dt^2} + 2 \frac{di_L}{dt} + 2 i_L = 8$$

The continuity of the inductor current results in

$$i_L(0^-) = i_L(0^+) = 4$$

By writing KVL in  $mesh_1$ ,

$$v_c(0^+) = i_L(0^+) + \frac{di_L(0^+)}{dt}, i_L(0^+) = 4, v_c(0^-) = v_c(0^+) = 8 \Rightarrow \frac{di_L(0^+)}{dt} = 4$$

Overall, the differential equation of the circuit is

$$\frac{d^2i_L}{dt^2} + 2\frac{di_L}{dt} + 2i_L = 8 \quad i_L(0^+) = 4 \quad \frac{di_L(0^+)}{dt} = 4$$

with the homogeneous solution

$$s^2 + 2s + 2 = 0 \Rightarrow s = -1 + i, -1 - i \Rightarrow i_{L_h} = Ae^{-t} \sin(t) + Be^{-t} \cos(t)$$

, the particular solution

$$i_{L_p} = K$$

, and the complete solution

$$i_L = Ae^{-t} \sin(t) + Be^{-t} \cos(t) + K$$

To find  $A$ ,  $B$ , and  $K$ , we use initial conditions and substitute the complete solution in differential equation.


$$\begin{cases} 2K = 8 \\ i_L(0^+) = 4 = B + 4 \\ \frac{di_L(0^+)}{dt} = 4 = A - B \end{cases} \Rightarrow K = 4, A = 4, B = 0$$

Finally,

$$i_L(t) = 4e^{-t} \sin(t) + 4$$

**For  $t > 2$ :**

The circuit has been shown below

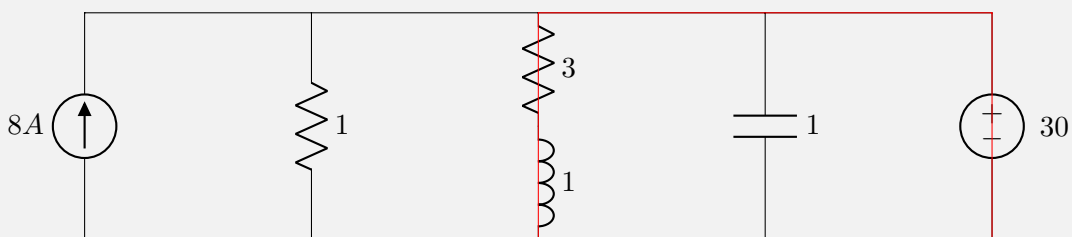

The describing differential equation is obtained by writing KVL in red loop as

$$\frac{di_L}{dt} + 3i_L = 30$$

with the initial condition

$$i_L(2^-) = 4e^{(-2)} + 4 = 4.5 = i_L(2^+)$$

, the homogeneous solution

$$s + 3 = 0 \Rightarrow s = -3 \Rightarrow i_{L_h} = Ae^{-3(t-2)}$$

, the particular solution

$$i_{Lp} = B$$

, and the complete solution

$$i_L = Ae^{-3(t-2)} + B$$

To find  $A$  and  $B$ , we use initial conditions and substitute the complete solution in differential equation.

$$\begin{cases} 3B = 30 \\ i_L(2^+) = 4.5 = A + B \end{cases} \Rightarrow A = -5.5, B = 10$$

So,

$$i_L(t) = -5.5e^{-3(t-2)} + 10$$

**Overall response:**

$$i_L(t) = \begin{cases} 4 & t < 0 \\ 4e^{-t} \sin(t) + 4 & 0 \leq t < 2 \\ -5.5e^{-3(t-2)} + 10 & t \geq 2 \end{cases}$$

### Question 4

Let  $v_c(0^-) = 2 \text{ V}$  and  $i_L(0^-) = 1 \text{ A}$  and find  $v_c(t), t > 0$  in Fig. 4.

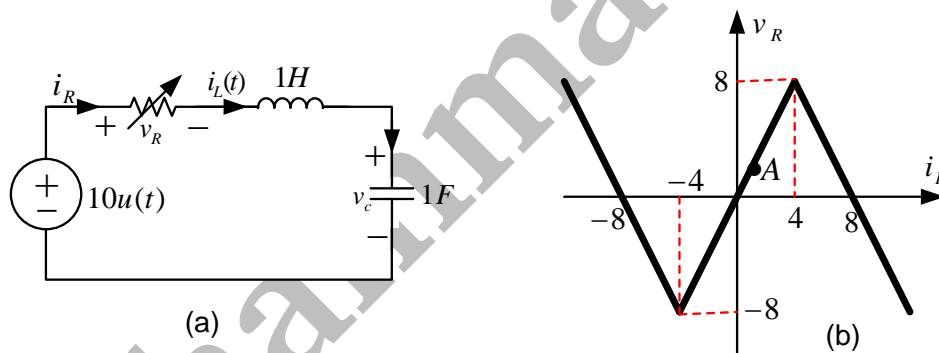


Figure 4: A nonlinear second-order circuit.

The nonlinear resistor is described by

$$v_R = \begin{cases} -2i_R + 16 & 4 \leq i_R \\ 2i_R & -4 \leq i_R \leq 4 \\ -2i_R - 16 & i_R \leq -4 \end{cases} \quad (1)$$

$$\begin{cases} i_L(0^-) = 1 \\ i_R = i_L = i_C \end{cases} \Rightarrow i_R(0^-) = 1 \Rightarrow v_R(0^-) = 2$$

KVL for  $t = 0^-$  gives

$$v_R(0^-) + v_L(0^-) + v_C(0^-) = 0 \Rightarrow 2 + \frac{di_L}{dt} + 2 = 0 \Rightarrow i'_L(0^-) = -4$$

$i_L(t)$  and  $v_C(t)$  can't jump at  $t = 0$ . So, we have,  $v_C(0^-) = v_C(0^+) = 2$  and  $i_L(0^-) = i_L(0^+) = 1$ . Hence,

$$v_R(0^+) + v_L(0^+) + v_C(0^+) = 10u(0^+) \Rightarrow 2 + \frac{di_L}{dt} + 2 = 10 \Rightarrow i'_L(0^+) = 6$$

For  $-4 < i_L(t) < 4$  and  $t > 0$ , we have

$$v_R(t) + v_L(t) + v_C(t) = 100$$

$$\frac{d(2i_L + \frac{di_L}{dt} + v_C(t))}{dt} = 0$$

$$\frac{d^2i_L}{dt^2} + 2\frac{di_L}{dt} + i = 0$$

$$\Rightarrow r^2 + 2r + 1 = 0 \Rightarrow r_1 = -1, r_2 = -1$$

$$\Rightarrow i_L(t) = A_1te^{-t} + A_0e^{-t}$$

According to initial conditions  $i_L(0^+) = 1$  and  $i'_L(0^+) = 6$ , we get  $A_0 = 1$  and  $A_1 = 7$ . Hence,

$$i_L(t) = e^{-t} + 7te^{-t}, t > 0$$

Now, we find the minimum and the maximum of  $i_L(t)$  to check whether  $-4 < i_L(t) = i_R(t) < 4$  is true or not.

**Minimum of  $i_L(t)$ :**

$$\frac{di_L(t)}{dt} = (6 - 7t)e^{-t}, t > 0$$

Clearly, for  $t > \frac{6}{7}$ ,  $\frac{di_L(t)}{dt} < 0$ . Therefore,  $\frac{6}{7} < t$ , the inductor current  $i_L(t)$  is descending while for  $0^+ < t < \frac{6}{7}$ , the inductor current is ascending. So, the minimum is either at  $t = \infty$  or  $t = 0^+$  and equals  $\min\{i_L(0^+), i(\infty)\} = 0$ . Hence,  $i_L(t) > -4, t > 0$ .

**Maximum of  $i_L(t)$ :**

$$\frac{di_L(t)}{dt} = (6 - 7t)e^{-t} = 0 \Rightarrow t = \frac{6}{7}$$

So, the maximum inductor current is  $i_L(\frac{6}{7}) \approx 2.97 < 4$ . Hence,  $i_L(t) < 4, t > 0$ .

Now, for  $t > 0$ , we get

$$\begin{aligned} v_C(t) &= v_C(0^+) + \frac{1}{C} \int_0^t i_C(t)dt \\ &= 2 + \int_0^t i_C(t)dt \\ &= 2 + \int_0^t (e^{-t} + 7te^{-t})dt \\ &= -7te^{-t} - 8e^{-t} + 10 \end{aligned}$$

---

## SOFTWARE QUESTIONS

---

### Question 5

Consider the parallel RLC circuit shown in Fig. 5. Use PSpice transient simulation to plot the step responses of  $v_c(t)$ ,  $i_L(t)$ ,  $i_R(t)$ , and  $i_c(t)$  for  $L = 1$ ,  $C = 1$ , and  $R = 0.25, 0.5, 1, 1000$ .

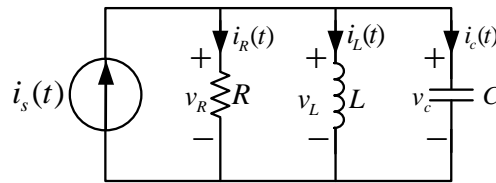


Figure 5: A parallel RLC circuit.

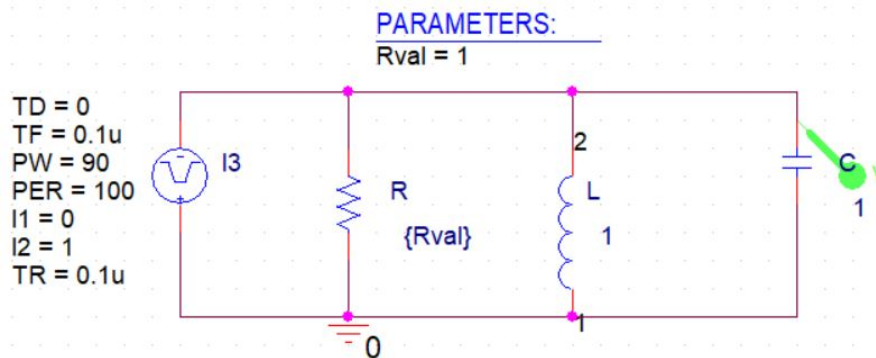


Figure 6: Schematic of the parallel RLC circuit in Capture environment.



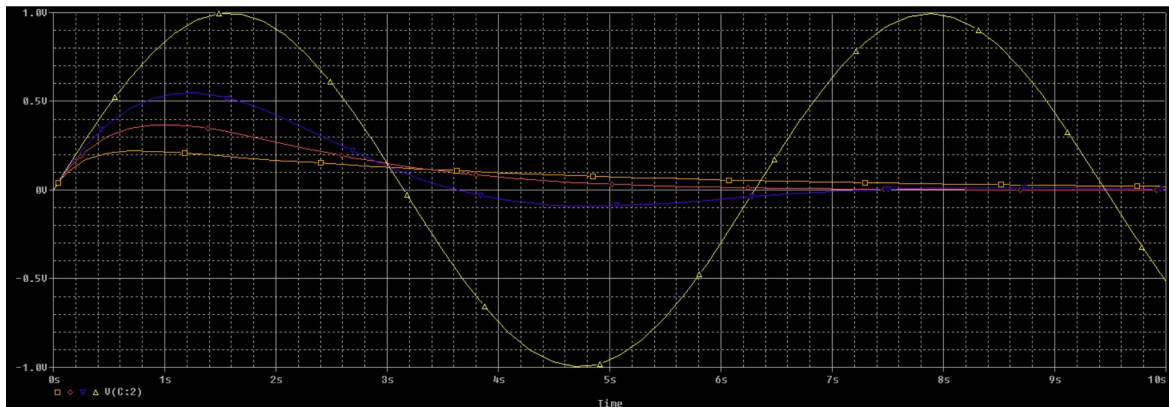


Figure 7: Capacitor voltage step response for  $R = 0.25, 0.5, 1, 1000$ .

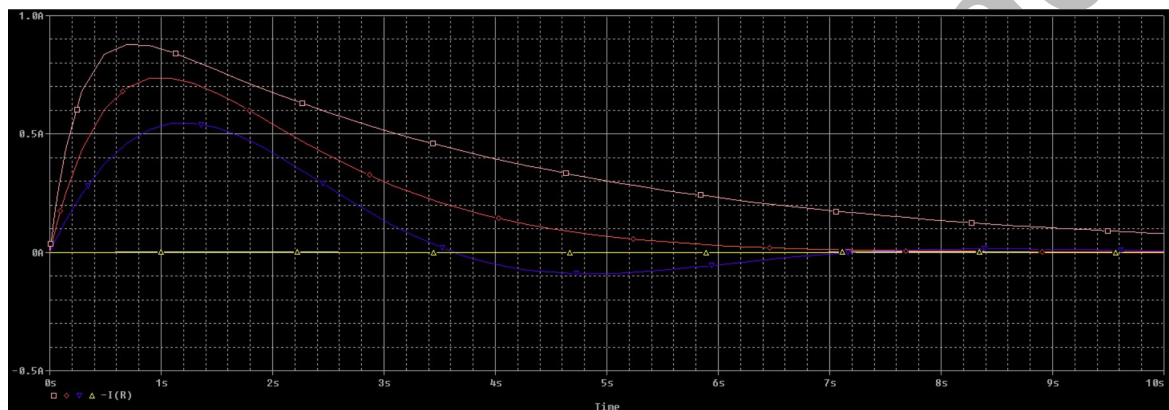


Figure 8: Resistor current step response for  $R = 0.25, 0.5, 1, 1000$ .

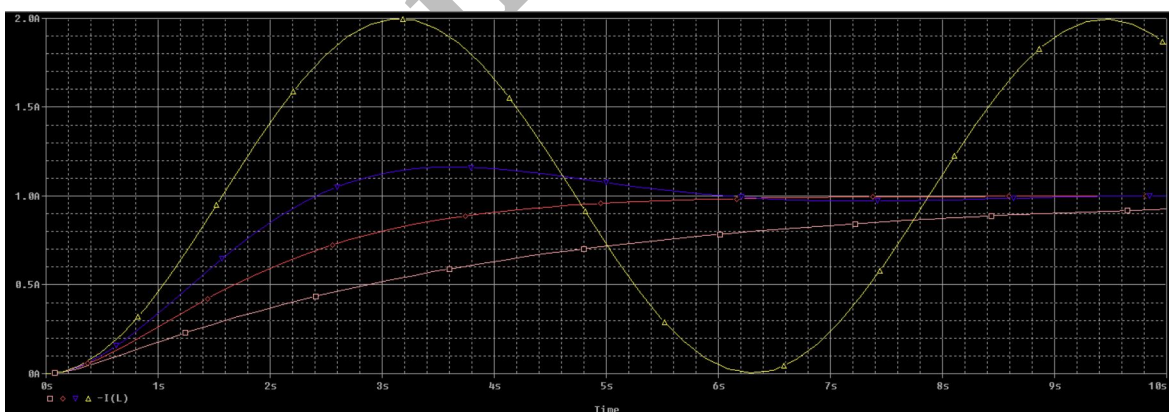


Figure 9: Inductor current step response for  $R = 0.25, 0.5, 1, 1000$ .

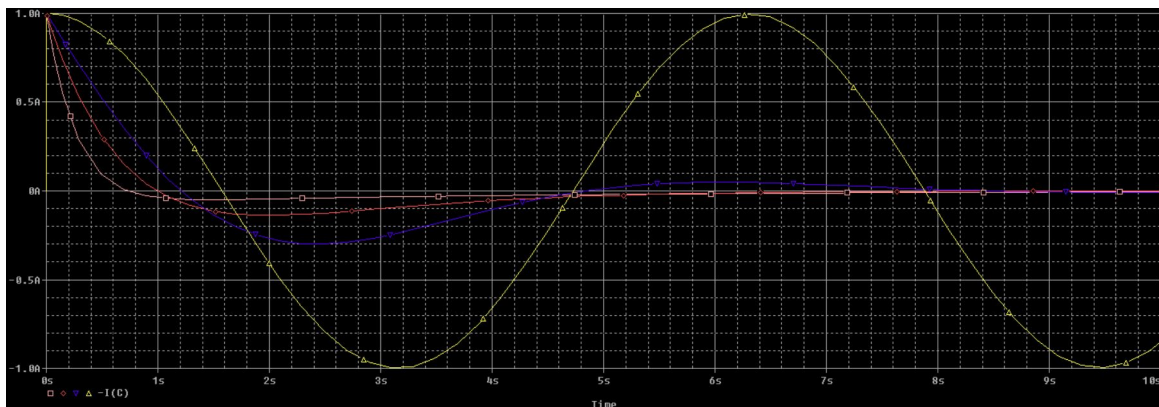


Figure 10: Capacitor current step response for  $R = 0.25, 0.5, 1, 1000$ .

Fig. 6 shows the schematic of the circuit in PSpice while Figs. 7-10 show the step responses of  $v_c(t)$ ,  $i_R(t)$ ,  $i_L(t)$ , and  $i_c(t)$  for  $R = 0.25, 0.5, 1, 1000$ . The step responses have overdamped, critically damped, underdamped, and lossless form for  $R = 0.25, 0.5, 1, 1000$ , respectively.

---

## BONUS QUESTIONS

---

### Question 6

Return your answers by filling the  $\LaTeX$  template of the assignment.

---

## EXTRA QUESTIONS

---

### Question 7

Feel free to solve the following questions from the book *“Engineering Circuit Analysis”* by W. Hayt, J. Kemmerly, and S. Durbin.

1. Chapter 9, question 13.
2. Chapter 9, question 14.
3. Chapter 9, question 20.
4. Chapter 9, question 26.

5. Chapter 9, question 35.
6. Chapter 9, question 37.
7. Chapter 9, question 39.
8. Chapter 9, question 48.
9. Chapter 9, question 50.
10. Chapter 9, question 51.
11. Chapter 9, question 53.
12. Chapter 9, question 61.
13. Chapter 9, question 65.

Mohammad Hadi