

Summary

Mohammad Hadi

mohammad.hadi@sharif.edu

@MohammadHadiDastgerdi

Spring 2022

Overview

- 1 Lumped Circuits
- 2 Circuit Elements
- 3 Circuit Analysis
- 4 Linear and Time-invariant Circuits
- 5 Sinusoidal Steady-state Analysis

Lumped Circuits

Maxwell and Kirchhoff Equations

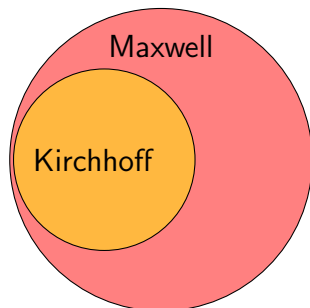


Figure: Maxwell and Kirchhoff equations.

- **Maxwell's equation:** Sophisticated **vector** quantities $\vec{E}, \vec{H}, \vec{D}, \vec{B}$
- **Kirchhoff's equations:** Simplified **scalar** quantities v, i, q, ϕ
- **Lumped condition:** $\max\{\text{circuit dimension}\} \ll \min\{\text{circuit wavelength}\}$

Example (Lump condition)

Intel Core i7-4702HQ processor with the package size $37.5\text{mm} \times 32\text{mm} \times 1.6\text{mm}$ and the maximum frequency 3.2 GHz is not a lumped circuit since its maximum dimension $d \approx \sqrt{37.5^2 + 32^2 + 1.6^2} = 49.32\text{ mm}$ is in the order of minimum operating wavelength $\lambda \approx 3 \times 10^{11} / (3.2 \times 10^9) = 93.72\text{ mm}$.

Example (Lump condition)

The power transmission system is a lumped circuit over Tehran city since the maximum transmission distance $d \approx 50\text{ km}$ is much less than the operating wavelength $\lambda \approx 3 \times 10^5 / 50 = 6000\text{ km}$.

Circuit Element

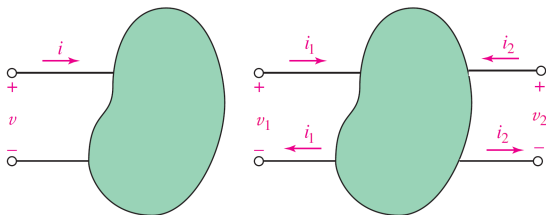


Figure: Passive sign convention in one-port and two-port circuit elements.

- **Circuit element**: an entity with voltage and current ports.
- **One-port element**: an element with two connection terminals.
- **Passive sign convention**: the current flows to the plus terminal.
- **Absorbed power**: assuming passive sign convention, $p = vi$.

Circuit Laws


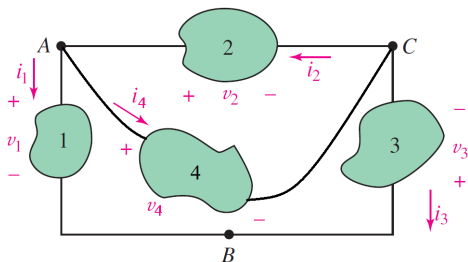


Figure: Kirchhoff's circuit laws for a sample circuit.

- **Circuit**: an interconnection of elements under an arbitrary topology.
- **KCL**: for the entering (exiting) currents at each node, $\sum_k i_k = 0$.
- **KVL**: for the aligned voltages around each closed path, $\sum_k v_k = 0$.
- **Tellegen**: for all branches, $\sum_k v_k i_k = 0$.

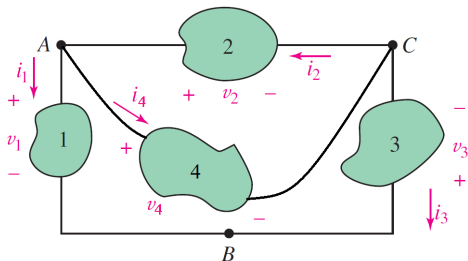Example (Circuit laws)

In the shown circuit, KCL at node A gives $i_1 + i_4 - i_2 = 0$ and KVL around loop ABC yields $v_1 + v_3 - v_2 = 0$. Elements 1 and 3 absorb the power $p_1 = v_1 i_1$ and $p_4 = -v_3 i_3$, respectively. Further, according to Tellegen's theorem, $v_1 i_1 - v_2 i_2 - v_3 i_3 + v_4 i_4 = 0$.



Circuit Elements

Basic One-port Elements

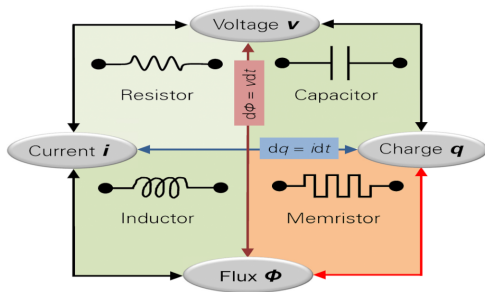


Figure: Basic one-port circuit elements.

- **Characteristic curve:** $f(y, x, t) = 0$, $x, y \in \{v, i, \phi, q\}$.
- **Linear element:** $f(y, x, t) = 0$ is an explicit linear function.
- **Time-invariant element:** $f(y, x) = 0$ is independent of t .

Basic One-port Elements

Element	LTI	LTV	NTI	NTV
Resistor	$v = Ri$	$v = R(t)i$	$f(v, i) = 0$	$f(v, i, t) = 0$
Capacitor	$q = Cv$	$q = C(t)v$	$f(q, v) = 0$	$f(q, v, t) = 0$
Inductor	$\phi = Li$	$\phi = L(t)i$	$f(\phi, v) = 0$	$f(\phi, v, t) = 0$

Table: Basic one-port circuit elements. L, N, TI, and TV stand for Linear, Nonlinear, Time-Invariant, Time-Variant, respectively.

- 1 **x-controlled element:** $f(y, x, t) = 0 \Rightarrow y = g(x, t)$.
- 2 **x-controlled element:** $f(y, x) = 0 \Rightarrow y = g(x)$.
- 3 **Voltage-flux relation:** $v = d\phi/dt$.
- 4 **Current-charge relation:** $i = dq/dt$.
- 5 **Absorbed power:** $p = vi$.
- 6 **Absorbed energy** over interval $[t_0, t]$: $w(t_0, t) = \int_{t_0}^t p dt'$.
- 7 **Passive element:** $\forall [t_0, t], W(t_0, t) \geq 0$.
- 8 **Active element:** $\exists [t_0, t], W(t_0, t) < 0$.

Basic One-port Elements

Example (Diode)

A diode with the following typical characteristic curve is an NTI voltage-controlled (current-controlled) passive resistor.

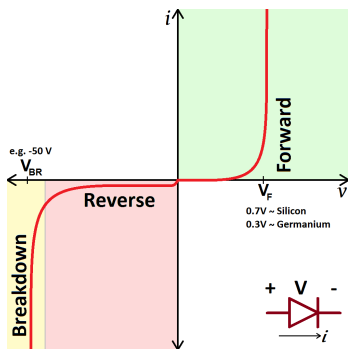


Figure: Typical characteristic curve of a diode.

Basic LTI Elements

Element	Characteristic Equation	Voltage Equation	Current Equation
Resistor	$v(t) = Ri(t)$	$v(t) = Ri(t)$	$i(t) = \frac{v(t)}{R}$
Capacitor	$q(t) = Cv(t)$	$v(t) = v(t_0) + \frac{\int_{t_0}^t i(t')dt'}{C}$	$i(t) = C \frac{dv(t)}{dt}$
Inductor	$\phi(t) = Li(t)$	$v(t) = L \frac{di(t)}{dt}$	$i(t) = i(t_0) + \frac{\int_{t_0}^t v(t')dt'}{L}$

Table: Basic LTI circuit elements.

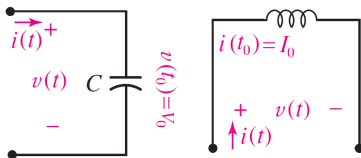


Figure: For complete description of capacitors and inductors, an **initial condition** is required.

Basic LTI Elements

Element	Characteristic Equation	Energy	Passivity
Resistor	$v(t) = Ri(t)$	$\mathcal{E}_H(t) = R \int_0^t i^2(t') dt'$	$R \geq 0$
Capacitor	$q(t) = Cv(t)$	$\mathcal{E}_E(t) = \frac{1}{2} Cv^2(t)$	$C \geq 0$
Inductor	$\phi(t) = Li(t)$	$\mathcal{E}_M(t) = \frac{1}{2} Li^2(t)$	$L \geq 0$

Table: Energy for basic LTI circuit elements. The initial energy at the reference time t_0 is assumed to be zero.

- 1 **Resistors**: the absorbed energy is **dissipated** as **heat energy**.
- 2 **Capacitors**: the absorbed energy is **stored** as **electrical energy**.
- 3 **Inductors**: the absorbed energy is **stored** as **magnetic energy**.

Basic Active Elements

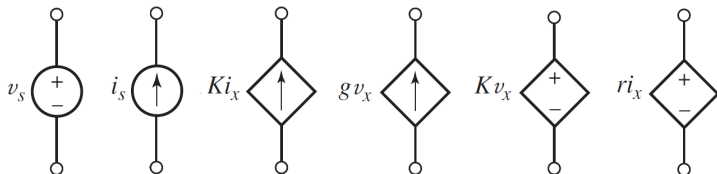


Figure: Basic active circuit elements. From left to right, independent voltage source, independent current source, **LTI** dependent current-controlled current source, **LTI** dependent voltage-controlled current source, **LTI** dependent voltage-controlled voltage source, and **LTI** dependent current-controlled voltage source.

- 1 **Sources:** a subset of (nonlinear) resistors.
- 2 **Dependent sources:** a subset of **two-port elements**.
- 3 **LTI dependent sources:** a subset of **LTI elements**.

Example (Initial condition modeling)

Initial conditions can be modeled by independent sources.

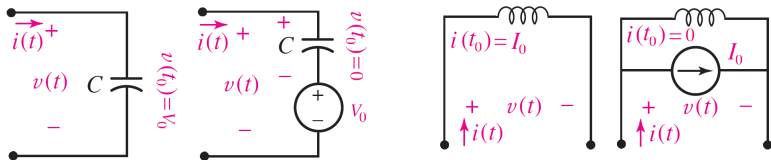


Figure: For complete description of capacitors and inductors, an **initial condition** is required. Initial conditions can be replaced with **independent sources**.

Example (Short and open circuit)

A voltage source set to zero acts like a short circuit (zero resistor) while a current source set to zero acts like an open circuit (infinite resistor).

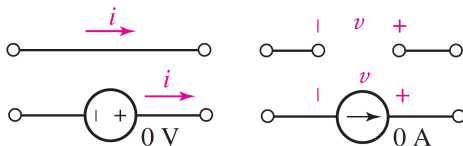


Figure: Zero-voltage and zero-current independent sources.

Parallel and Series Connections

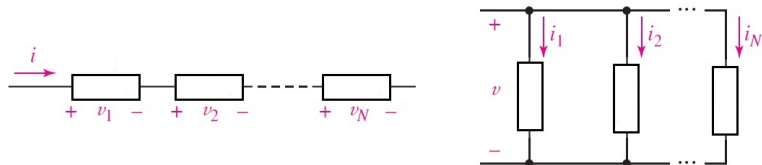


Figure: Parallel and series connection. **Series (parallel) elements have the same current (voltage).**

Element	Series Connection	Parallel Connection
Resistor	$R = \sum_i R_i$	$G = \sum_i G_i$
Capacitor	$S = \sum_i S_i$	$C = \sum_i C_i$
Inductor	$L = \sum_i L_i$	$\Gamma = \sum_i \Gamma_i$

Table: Parallel and series connection of basic linear elements. R , G , C , S , L , and Γ denote **resistance**, **conductance**, **capacitance**, **elastance**, **inductance**, and **reciprocal inductance**, respectively. The **initial conditions** are assumed to be **zero**.

Delta-Wye Conversion

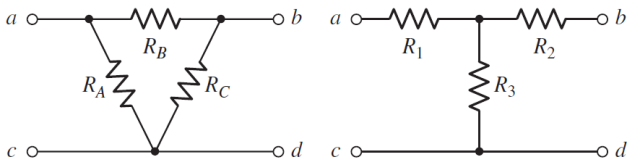


Figure: Resistive Δ (triangle, Π) and Y (star, T) networks. If the two networks are **equivalent**, then the port voltages and currents must be equal.

$$R_A = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2}$$

$$R_B = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_3}$$

$$R_C = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1}$$

$$R_1 = \frac{R_A R_B}{R_A + R_B + R_C}$$

$$R_2 = \frac{R_B R_C}{R_A + R_B + R_C}$$

$$R_3 = \frac{R_C R_A}{R_A + R_B + R_C}$$

Ideal Operational Amplifier

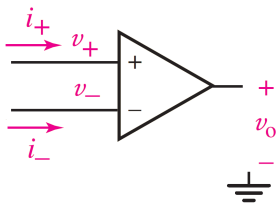


Figure: An ideal operational amplifier in which $i_- = 0$, $i_+ = 0$, and $v_- = v_+$.

- 1 No current at each input terminal.
- 2 No voltage difference between the input terminals.
- 3 Negative feedback for stability.
- 4 A member of LTI elements.

Circuit Analysis

Definition (Circuit Variables)

Branch currents and branch voltages in a given circuit are called circuit variables.

Definition (Circuit Analysis)

The circuit analysis problem is to determine all or part of the circuit variables for a circuit.

- 1 Basic circuit analysis procedures: nodal and mesh analysis
- 2 Nodal analysis: KCL-based analysis.
- 3 Mesh analysis: KVL-based analysis.

Nodal Analysis

Nodal analysis procedures:

- 1 Count the number of nodes (N nodes).
- 2 Designate a **reference node** (usually, a **high-degree node**).
- 3 **Label** the nodal voltages ($N - 1$ labels).
- 4 Form a **supernode** about each voltage source and relate its voltage to nodal voltages.
- 5 Write a **KCL equation** for each nonreference node and for each supernode that does not contain the reference node. Use **element equations** to express the currents in terms of nodal voltages.
- 6 Express any additional unknowns in terms of appropriate nodal voltages (occurs for **dependent sources**).
- 7 **Organize** the equations.
- 8 Solve the system of equations for the nodal voltages ($N - 1$ equations).


✓ **Handy** nodal analysis: appropriate the circuits with a **low number of nodes**.

Nodal Analysis

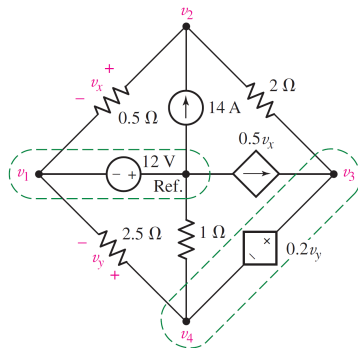Example (Nodal analysis)

In the circuit below, $v_1 = -12$ V, $v_2 = -4$ V, $v_3 = 0$ V, and $v_4 = -2$ V.

$$\Rightarrow \left\{ \begin{array}{l} v_1 = -12 \\ v_3 - v_4 = 0.2v_y \\ \frac{v_1 - v_2}{0.5} + \frac{v_3 - v_2}{2} + 14 = 0 \\ \frac{v_1 - v_4}{2.5} + \frac{-v_4}{1} + \frac{v_2 - v_3}{2} + 0.5v_x = 0 \end{array} \right.$$
$$\Rightarrow \left\{ \begin{array}{l} v_1 = -12 \\ v_3 - v_4 = 0.2v_4 - 0.2v_1 \\ \frac{v_1 - v_2}{0.5} + \frac{v_3 - v_2}{2} + 14 = 0 \\ \frac{v_1 - v_4}{2.5} + \frac{-v_4}{1} + \frac{v_2 - v_3}{2} + 0.5(v_2 - v_1) = 0 \end{array} \right.$$



Nodal Analysis


Example (Nodal analysis (cont.))

In the circuit below, $v_1 = -12$ V, $v_2 = -4$ V, $v_3 = 0$ V, and $v_4 = -2$ V.

$$\Rightarrow \begin{cases} -2v_1 + 2.5v_2 - 0.5v_3 & = 14 \\ 0.1v_1 - v_2 + 0.5v_3 + 1.4v_4 & = 0 \\ v_1 & = -12 \\ 0.2v_1 + v_3 - 1.2v_4 & = 0 \end{cases}$$

$$\Rightarrow \begin{bmatrix} -2 & 2.5 & -0.5 & 0 \\ 0.1 & -1 & 0.5 & 1.4 \\ 1 & 0 & 0 & 0 \\ 0.2 & 0 & 1 & -1.2 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} 14 \\ 0 \\ -12 \\ 0 \end{bmatrix}$$
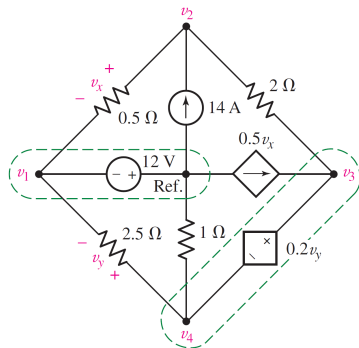
$$\Rightarrow v_2 = \frac{\begin{vmatrix} -2 & 14 & -0.5 & 0 \\ 0.1 & 0 & 0.5 & 1.4 \\ 1 & -12 & 0 & 0 \\ 0 & 0 & 1 & -1.2 \end{vmatrix}}{\begin{vmatrix} -2 & 2.5 & -0.5 & 0 \\ 0.1 & -1 & 0.5 & 1.4 \\ 1 & 0 & 0 & 0 \\ 0.2 & 0 & 1 & -1.2 \end{vmatrix}} = -4$$



Mesh analysis procedures:

- 1 Make sure that the circuit is **planar**.
- 2 Count the number of meshes (**M meshes**).
- 3 **Label** the mesh currents (**M labels**).
- 4 Form a **supermesh** to enclose the meshes shares a current source and relate its current to mesh currents.
- 5 Write a **KVL** equation around each mesh and supermesh. Use **element equations** to express the voltages in terms of mesh currents.
- 6 Express any additional unknowns in terms of appropriate mesh currents (occurs for **dependent sources**).
- 7 **Organize** the equations.
- 8 **Solve** the system of equations for the mesh currents (**M equations**).

✓ **Handy** mesh analysis: appropriate the for the **planar** circuits with a **low number of meshes**.

Mesh Analysis

Example (Mesh analysis)


In the circuit below, $i_1 = 9$ A, $i_2 = 2.5$ A, and $i_3 = 2$ A.

$$\begin{cases} i_1 - i_3 = 7 \\ (i_2 - i_1) + 2i_2 + 3(i_2 - i_3) = 0 \\ (i_1 - i_2) + 3(i_3 - i_2) + (i_3) - 7 = 0 \end{cases}$$

$$\Rightarrow \begin{cases} i_1 & - & i_3 = 7 \\ -i_1 + 6i_2 - 3i_3 = 0 \\ i_1 - 4i_2 + 4i_3 = 7 \end{cases}$$

$$\Rightarrow \begin{bmatrix} 1 & 0 & -1 \\ -1 & 6 & -3 \\ 1 & -4 & 4 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 7 \\ 0 \\ 7 \end{bmatrix}$$
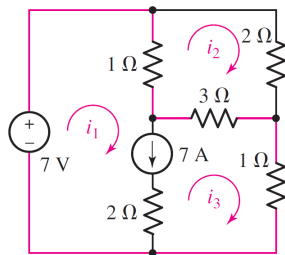
$$\Rightarrow i_2 = \frac{\begin{vmatrix} 1 & 7 & -1 \\ -1 & 0 & -3 \\ 1 & 7 & 4 \end{vmatrix}}{\begin{vmatrix} 1 & 0 & -1 \\ -1 & 6 & -3 \\ 1 & -4 & 4 \end{vmatrix}} = 2.5$$



Linear and Time-invariant Circuits

Input and Response

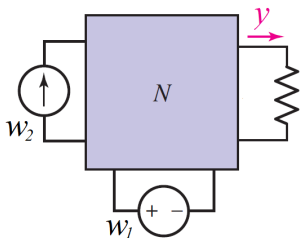


Figure: Inputs w_1 , w_2 and response y in a multi-input general circuit.

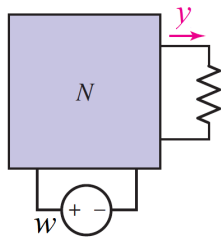


Figure: Input w and response y in a single-input general circuit.

- Each **input** corresponds to an **independent source**.
- Each **response** corresponds to a desired **circuit variable**.

Input and Response

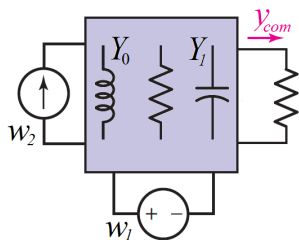


Figure: Complete response y_{com} .

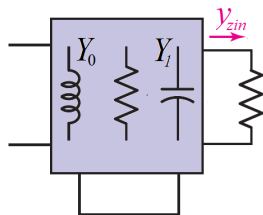


Figure: Zero-input response (natural) y_{zin} .

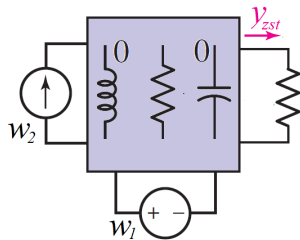


Figure: Zero-state response (forced) y_{zst} .

Circuit Classification

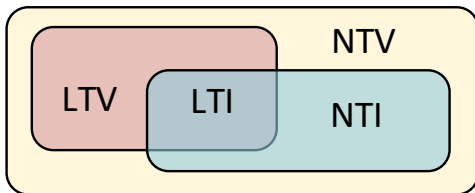


Figure: Common classification of circuits.

- **Linear circuit:** A circuit with only **linear elements or independent sources**.
- **Time-invariant circuit:** A circuit with only **time-invariant elements or independent sources**.
- **LTI circuit:** A circuit with only **LTI elements or independent sources**.

Theorem (Linear Circuits)

For linear circuits

- $y_{com} = y_{zin} + y_{zst}$.
- y_{zst} is a linear function (superposition) of the inputs $w = [w_1, w_2, \dots]$.
- y_{zin} is a linear function (superposition) of the initial state $Y = [Y_0, Y_1, \dots]$.

Theorem (LTI Circuits)

For each input-response pair in an LTI circuits,

- The complete response satisfies a linear differential equation with constant coefficients.
- The zero-state response to an arbitrary input $w(t)u(t)$ is $y_{zst}(t) = [w(t)u(t)] * h(t) = \int_0^t w(u)h(t-u)du$, where $h(t)$ is the causal impulse response.
- If $y_{zst}(t)$ is the zero-state response to the input $w(t)$, the zero-state response to the input $w(t-t_0)$ is $y_{zst}(t-t_0)$.
- The impulse and unit step responses relate together via $h(t) = \frac{ds(t)}{dt}$.

Theorem (Homogeneous Response)

The homogeneous response of the constant-coefficient linear differential equation

$$\sum_{i=0}^n a_i y^{(i)}(t) = 0, \quad y^{(i)}(0) = Y_i, i = 0, 1, \dots, n - 1$$

is of the form

$$y(t) = \sum_{k=1}^n A_k e^{s_k t}, t \geq 0$$

, where $s_k, k = 1, \dots, n$ are distinct roots of the characteristic equation $\sum_{k=0}^n a_k s^k = 0$. If a root has multiplicity, the corresponding exponential terms should be replaced by $e^{s_k t}, t e^{s_k t}, t^2 e^{s_k t}, \dots$. The constants A_k are obtained by substituting the initial conditions to the response.

Constant-coefficient Linear Differential Equations

Theorem (Impulse Response)

The impulse response $h(t)$ of the constant-coefficient linear differential equation

$$\sum_{i=0}^n a_i y^{(i)}(t) = \sum_{l=0}^m b_l w^{(l)}(t), \quad y^{(i)}(0) = 0, i = 0, 1, \dots, n-1$$

is of the form

$$h(t) = \begin{cases} u(t) \sum_{k=1}^n A_k e^{s_k t} & , \quad n > m \\ u(t) \sum_{k=1}^n A_k e^{s_k t} + \sum_{k=n-m}^0 A_k \delta^{(i)}(t) & , \quad n \leq m \end{cases}$$

, where $s_k, k = 1, \dots, n$ are distinct roots of the characteristic equation $\sum_{k=0}^n a_k s^k = 0$. If a root has multiplicity, the corresponding exponential terms should be replaced by $e^{s_k t}, t e^{s_k t}, t^2 e^{s_k t}, \dots$. The constants A_k are obtained by substituting $y(t) = h(t)$ and $w(t) = \delta(t)$ into the differential equation and equating its both sides.

First-order Circuits

Example (First-order circuit)

The complete response of a first-order circuit relates to the time constant τ .

$$i(t) = i_{zin}(t) + i_{zst}(t) = i_{zin}(t) + i_{zst1}(t) + i_{zst2}(t), t \geq 0$$


$$Ri_{zin}(t) + V_0 + \frac{1}{C} \int_0^t i_{zin}(u) du = 0, \quad i_{zin}(0) = -\frac{V_0}{R}$$

$$i'_{zin}(t) + \frac{1}{\tau} i_{zin}(t) = 0, \quad i_{zin}(0) = -\frac{V_0}{R}, \tau = RC$$

$$s + \frac{1}{\tau} = 0 \Rightarrow s = -\frac{1}{\tau} \Rightarrow i_{zin}(t) = Ae^{-\frac{t}{\tau}}$$

$$i_{zin}(0) = A = -\frac{V_0}{R}$$
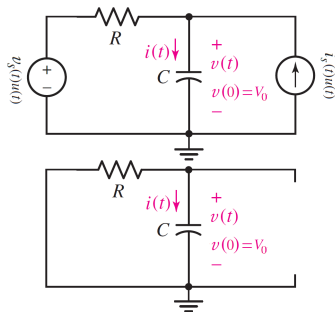
$$i_{zin}(t) = -\frac{V_0}{R} e^{-\frac{t}{\tau}}, t \geq 0$$



First-order Circuits

Example (First-order circuit (cont.))

The complete response of a first-order circuit relates to the time constant τ .

$$Rh_1(t) + \frac{1}{C} \int_0^t h_1(u) du - \delta(t) = 0, \quad h_1(0) = 0$$

$$h_1'(t) + \frac{1}{\tau} h_1(t) = \frac{1}{R} \delta'(t), \quad h_1(0) = 0, \tau = RC$$

$$s + \frac{1}{\tau} = 0 \Rightarrow s = -\frac{1}{\tau} \Rightarrow h_1(t) = A_1 e^{-\frac{t}{\tau}} u(t) + A_0 \delta(t)$$


$$-\frac{A_1}{\tau} e^{-\frac{t}{\tau}} u(t) + A_1 \delta(t) + A_0 \delta'(t) +$$

$$\frac{A_1}{\tau} e^{-\frac{t}{\tau}} u(t) + \frac{A_0}{\tau} \delta(t) = \frac{1}{R} \delta'(t)$$

$$A_0 = \frac{1}{R}, A_1 = -\frac{1}{R^2 C}$$

$$h_1(t) = -\frac{1}{R^2 C} e^{-\frac{t}{\tau}} u(t) + \frac{1}{R} \delta(t)$$
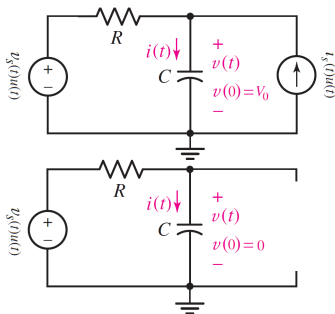
$$i_{zst1}(t) = h_1(t) * v_s(t) = u(t) \int_0^t v_s(u) h_1(t-u) du$$



First-order Circuits

Example (First-order circuit (cont.))

The complete response of a first-order circuit relates to the time constant τ .

$$\frac{1}{C} \int_0^t h_2(u) du + h_2(t) - \delta(t) = 0, \quad h_2(0) = 0$$

$$h_2'(t) + \frac{1}{\tau} h_2(t) = \delta'(t), \quad h_2(0) = 0, \tau = RC$$

$$s + \frac{1}{\tau} = 0 \Rightarrow s = -\frac{1}{\tau} \Rightarrow h_2(t) = A_1 e^{-\frac{t}{\tau}} u(t) + A_0 \delta(t)$$


$$-\frac{A_1}{\tau} e^{-\frac{t}{\tau}} u(t) + A_1 \delta(t) + A_0 \delta'(t) +$$

$$\frac{A_1}{\tau} e^{-\frac{t}{\tau}} u(t) + \frac{A_0}{\tau} \delta(t) = \delta'(t)$$

$$A_0 = 1, A_1 = -\frac{1}{RC}$$

$$h_2(t) = -\frac{1}{RC} e^{-\frac{t}{\tau}} u(t) + \delta(t)$$
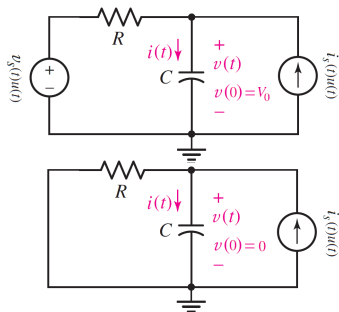
$$i_{zst2}(t) = h_2(t) * i_s(t) = u(t) \int_0^t i_s(u) h_2(t-u) du$$



Second-order Circuits

Example (Second-order circuit)


The natural voltage response in a second-order circuit depends on the damping factor α and resonance frequency ω_0 and takes one of possible forms overdamped, critically damped, and underdamped.

$$\begin{cases} \frac{v(t)}{R} + I_0 + \frac{\int_0^t v(u)du}{L} + Cv'(t) = 0 \\ v(0) = V_0, v'(0) = V_1 = \frac{1}{C}(-\frac{V_0}{R} - I_0) \end{cases}$$

$$v''(t) + 2\alpha v'(t) + \omega_0^2 v(t) = 0, \quad \alpha = \frac{1}{2RC}, \omega_0 = \frac{1}{\sqrt{LC}}$$

$$s^2 + 2\alpha s + \omega_0^2 = 0 \Rightarrow s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}, \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$
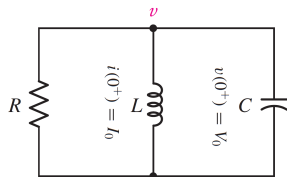
$$v(t) = \begin{cases} v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} & , \quad \alpha > \omega_0 \\ v(t) = e^{-\alpha t} (A_1 t + A_2) & , \quad \alpha = \omega_0 \\ v(t) = e^{-\alpha t} (B_1 \cos(\omega_d t) + B_2 \sin(\omega_d t)) & , \quad \alpha < \omega_0 \end{cases}$$



Thevenin and Norton Equivalency

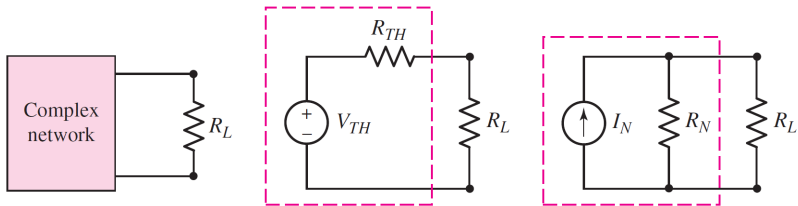


Figure: Thevenin and Norton equivalencies in resistive linear networks, where $R_{TH} = R_N$ and $V_{TH} = R_N I_N$.

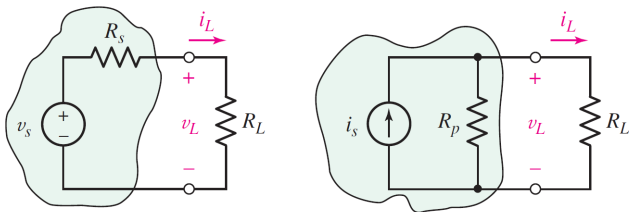


Figure: Source transformation in resistive linear networks, as a special case of Thevenin and Norton equivalencies, where $R_s = R_p$ and $v_s = R_p i_s$.

Dividers and Maximum Power Transfer

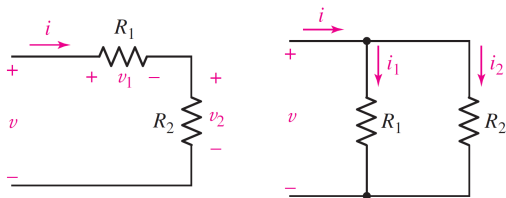


Figure: Resistive voltage divider, where $v_1 = \frac{R_1}{R_1+R_2} v$ and resistive current dividers, where $i_1 = \frac{R_2}{R_1+R_2} i$.

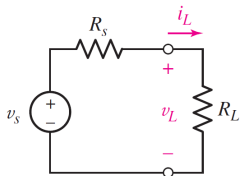


Figure: Maximum power transfer in a resistive network, where $R_s = R_L$.

Sinusoidal Steady-state Analysis

Constant-coefficient Linear Differential Equations

Theorem (Sinusoidal Response)

The sinusoidal response $y(t)$ of the constant-coefficient linear differential equation

$$\sum_{i=0}^n a_i y^{(i)}(t) = \sum_{l=0}^m b_l w^{(l)}(t), \quad y^{(i)}(0) = Y_i, \quad i = 0, 1, \dots, n-1$$

to the input $w(t) = |A| \cos(\omega t + \angle A) = \Re\{Ae^{j\omega t}\}$ is of the form

$$y(t) = y_h(t) + y_p(t) = \sum_{k=1}^n A_k e^{s_k t} + |B| \cos(\omega t + \angle B), \quad t \geq 0$$

, where the input phasor $A = |A|e^{j\angle A}$ and $s_k, k = 1, \dots, n$ are distinct roots of the characteristic equation $\sum_{k=0}^n a_k s^k = 0$. If a root has multiplicity, the corresponding exponential terms should be replaced by $e^{s_k t}, te^{s_k t}, t^2 e^{s_k t}, \dots$. The constants A_k are obtained by substituting the initial conditions into the differential equation while the steady-state response phasor $B = |B|e^{j\angle B}$ is the solution of the equation

$$B/A = H(j\omega) = \sum_{l=0}^m b_l (j\omega)^l / \sum_{i=0}^n a_i (j\omega)^i$$

, where $H(j\omega)$ is called frequency response or transfer function.

Constant-coefficient Linear Differential Equations

Theorem (Steady-state Sinusoidal Response)

If all the roots of the characteristic equation $\sum_{k=0}^n a_k s^k = 0$ corresponding to the differential equation

$$\sum_{i=0}^n a_i y^{(i)}(t) = \sum_{l=0}^m b_l w^{(l)}(t), \quad y^{(i)}(0) = Y_i, \quad i = 0, 1, \dots, n-1$$

are in the open left-hand complex plane, the steady-state sinusoidal response $y(t)$ to the input $w(t) = |A| \cos(\omega t + \angle A) = \Re\{Ae^{j\omega t}\}$ is of the form

$$y(t) = y_p(t) = |B| \cos(\omega t + \angle B), \quad t \geq 0$$

, where the input phasor $A = |A|e^{j\angle A}$. The steady-state response phasor $B = |B|e^{j\angle B}$ is the solution of the equation

$$B/A = H(j\omega) = \sum_{l=0}^m b_l (j\omega)^l / \sum_{i=0}^n a_i (j\omega)^i$$

, where $H(j\omega)$ is called frequency response or transfer function.

Sinusoidal Steady-state of LTI Circuits

Definition (Natural Frequencies of LTI Circuits)

Natural frequencies are the roots of the characteristic function of the constant-coefficient linear differential equation describing a desired input-response relationship in an LTI system.

Theorem (Sinusoidal Steady-state of LTI Circuits)

If the natural frequencies of an LTI circuit are in the open left-hand complex plane, then, irrespective of the initial state, as time proceeds, the circuit approaches a sinusoidal response, which can be obtained from phasor analysis.

- **Nodal** and **mesh** analysis can be used in phasor analysis.
- **Superposition** can be used for phasor analysis of a **multi-input linear circuits** whose sinusoidal inputs have the same frequency.
- **Thevenin and Norton equivalencies**, **source transformation**, **voltage and current division structures**, and **maximum power transfer condition** can be extended to phasor analysis of **linear circuits**.

Impedance and Admittance

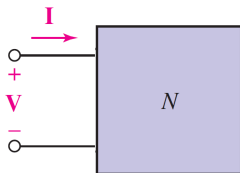


Figure: Impedance $Z = R + jX = \frac{V}{I}$ and admittance $Y = G + jB = \frac{I}{V} = \frac{1}{Z}$ for a one-port network. R , X , G , and B stand for **resistance**, **reactance**, **conductance**, and **susceptance**.

Element	Impedance $Z = \frac{V}{I}$	Admittance $Y = \frac{I}{V}$
Resistor	R	G
Capacitor	$\frac{1}{j\omega C}$	$j\omega C$
Inductor	$j\omega L$	$\frac{1}{j\omega L}$


Table: Impedance and admittance for basic LTI one-port circuit elements. **Series** and **parallel** combinations as well as **delta-why** conversion can be used for impedance and admittance.

Sinusoidal Steady-state Analysis

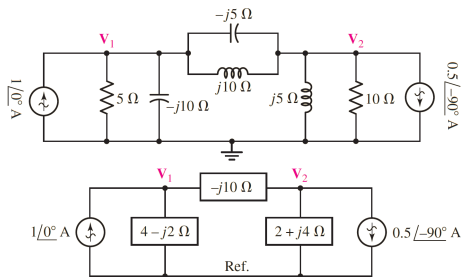Example (Sinusoidal Steady-state Analysis)

In the circuit below, $V_1 = 1 - j2$ V.

$$V_{11} = (4 - j2)(1\angle 0^\circ) \frac{-j10 + 2 + j4}{4 - j2 - j10 + 2 + j4}$$
$$V_{12} = (4 - j2)(-0.5\angle -90^\circ) \frac{2 + j4}{2 + j4 - j10 + 4 - j2}$$
$$V_1 = V_{11} + V_{12} = 1 - j2$$



Frequency Response Analysis

Example (Frequency response of series RLC circuit)

For a series RLC circuit with the frequency response $V(j\omega) = H(j\omega)I(j\omega) = I(j\omega)/[1/R + j(\omega C - 1/(\omega L))]$, the half-power bandwidth of $|V(j\omega)|$ is $B = \omega_0/Q_0$, where $\omega_0 = 1/\sqrt{LC}$ and $Q_0 = R\sqrt{C/L}$ are resonance frequency and quality factor, respectively.


$$V(j\omega) = Z(j\omega)I = \frac{I}{Y(j\omega)} = \frac{I}{\frac{1}{R} + j\omega C + \frac{1}{j\omega L}}$$

$$|V(j\omega)| = \frac{|I|}{\sqrt{\frac{1}{R^2} + (\omega C - \frac{1}{\omega L})^2}}$$

$$|V(j\omega_{3db})| = \max\{|V(j\omega)|\}/\sqrt{2} = R|I|/\sqrt{2}$$

$$\omega_{3db} = \omega_{1,2} = \omega_0 \left[\sqrt{1 + \left(\frac{1}{2Q_0}\right)^2} \pm \frac{1}{2Q_0} \right]$$

$$B = |\omega_2 - \omega_1| = \frac{\omega_0}{Q_0}$$

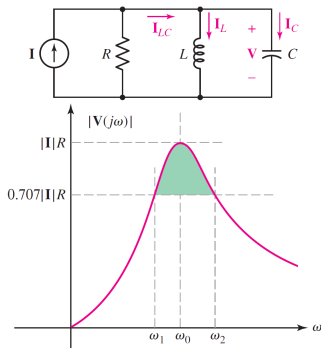

Power in Sinusoidal Steady-state

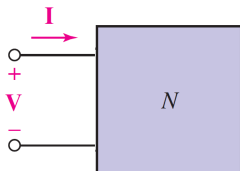


Figure: A one-port LTI network with the **voltage** $v(t) = |V| \cos(\omega t + \angle V)$ and **current** $i(t) = |I| \cos(\omega t + \angle I)$, the **phasors** $V = |V| \angle V$ and $I = |I| \angle I$, the **effective phasors** $V_e = V/\sqrt{2}$ and $I_e = I/\sqrt{2}$, and the **impedance** $Z = R + jX$.

- **Instantaneous power:** $p(t) = \frac{1}{2} |V| |I| [\cos(\angle V - \angle I) + \cos(2\omega t + \angle V + \angle I)]$
- **Complex power:** $S = \frac{1}{2} V I^* = \frac{1}{2} Z |I|^2 = \frac{1}{2} R |I|^2 + j \frac{1}{2} X |I|^2$
- **Average power:** $P = \lim_{T \rightarrow \infty} \frac{1}{2T} \int_{-T}^T p(t') dt' = \frac{1}{2} |V| |I| \cos(\angle V - \angle I)$
- **Average power:** $P = \Re\{S\} = \frac{1}{2} R |I|^2 = \frac{1}{2} |V| |I| \cos(\angle V - \angle I)$
- **Reactive power:** $Q = \Im\{S\} = \frac{1}{2} X |I|^2 = \frac{1}{2} |V| |I| \sin(\angle V - \angle I)$

Power in Sinusoidal Steady-state

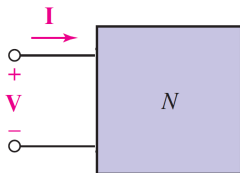


Figure: A one-port LTI network with the **voltage** $v(t) = |V| \cos(\omega t + \angle V)$ and **current** $i(t) = |I| \cos(\omega t + \angle I)$, the **phasors** $V = |V| \angle V$ and $I = |I| \angle I$, the **effective phasors** $V_e = V/\sqrt{2}$ and $I_e = I/\sqrt{2}$, and the **impedance** $Z = R + jX$.

- **Power factor:** $\text{PF} = \cos(\angle V - \angle I)$
- **Apparent (complex) power (VA):** $S = V_e I_e^* = Z |I_e|^2 = R |I_e|^2 + jX |I_e|^2$
- **Real (active, average) power (W):** $P = \Re\{S\} = R |I_e|^2 = |V_e| |I_e| \text{PF}$
- **Reactive power (VAR):** $Q = \Im\{S\} = X |I_e|^2 = |V_e| |I_e| \sin(\angle V - \angle I)$

Power in Sinusoidal Steady-state

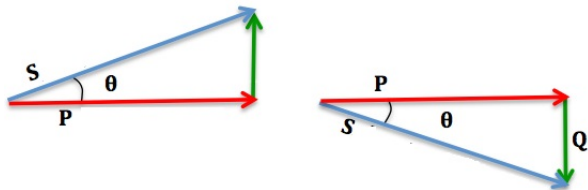


Figure: Power triangle for lagging and leading loads.

- **Power factor:** $PF = \cos(\angle V - \angle I) = \cos(\theta)$
- **Resistive load:** $\theta = 0 \equiv Q = 0$
- **Inductive (lagging) load:** $\theta > 0 \equiv Q > 0$
- **Capacitive (leading) load:** $\theta < 0 \equiv Q < 0$

Power in Sinusoidal Steady-state

Example (Sinusoidal Steady-state Power)

The power dissipated by the $10\ \Omega$ resistor in the circuit below is $10[79.23 \cos(5t - \angle 82.03^\circ) + 811.7 \cos(3t - \angle 76.86^\circ)]^2$.

$$i_1 = 2\angle 0^\circ \left[\frac{-j0.4}{10 - j - j0.4} \right] = 79.23\angle -82.03^\circ \text{ mA}$$


$$i_1(t) = 79.23 \cos(5t - 82.03^\circ) \text{ mA}$$

$$i_2 = 5\angle 0^\circ \left[\frac{-j1.667}{10 - j0.6667 - j1.667} \right] = 811.7\angle -76.86^\circ \text{ mA}$$

$$i_2(t) = 811.7 \cos(3t - 76.86^\circ) \text{ mA}$$

$$p(t) = 10[i_1(t) + i_2(t)]^2$$
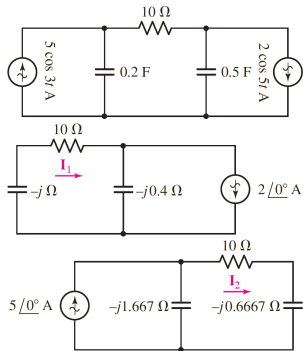
$$P = \frac{1}{2} \times 10 \times 79.23^2 + \frac{1}{2} \times 10 \times 811.7^2$$



Power in Sinusoidal Steady-state

Example (Maximum power transfer)

To transfer the maximum power to the load, $Z_{th} = Z_L^*$ in the circuit below.

$$I_L = \frac{V_{th}}{Z_{th} + Z_L} = \frac{V_{th}}{(R_{th} + R_L) + j(X_{th} + X_L)}$$

$$V_L = \frac{V_{th} Z_L}{Z_{th} + Z_L} = \frac{V_{th}(R_L + jX_L)}{(R_{th} + R_L) + j(X_{th} + X_L)}$$


$$P = \Re\{S\} = \Re\left\{\frac{1}{2} V_L I_L^*\right\}$$

$$P = \frac{1}{2} \frac{|V_{th}|^2 \sqrt{R_L^2 + X_L^2}}{(R_{th} + R_L)^2 + (X_{th} + X_L)^2} \cos(\tan^{-1}(\frac{X_L}{R_L}))$$

$$\frac{\partial P}{\partial R_{th}} = 0 \Rightarrow R_{th} = R_L$$

$$\frac{\partial P}{\partial X_{th}} = 0 \Rightarrow X_{th} = -X_L$$
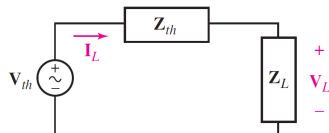
$$Z_{th} = R_{th} + jX_{th} = R_L - jX_L = Z_L^*$$



The End