

Class J Power Amplifiers





☐ Review

- Tuned Load Power Amplifiers (TLPAs)
- Harmonically Tuned Power Amplifiers (HTPAs)

☐ Second Harmonic Tuning Theory




☐ Class J Family

- Wide-Band Designs
- Dual-Band Designs
- Back-Off Efficiency Improvement

Tuned Load Power Amplifiers (TLPAs)



□ TLPAs: Class B, Class AB, ...

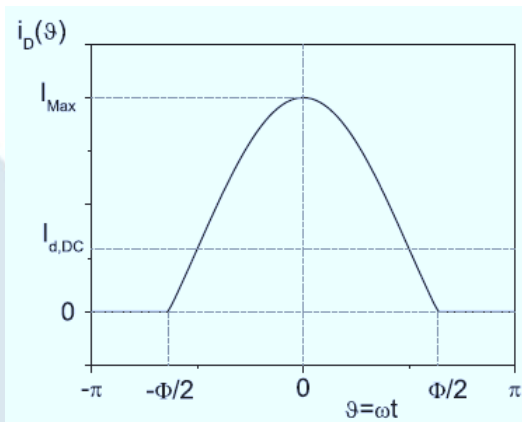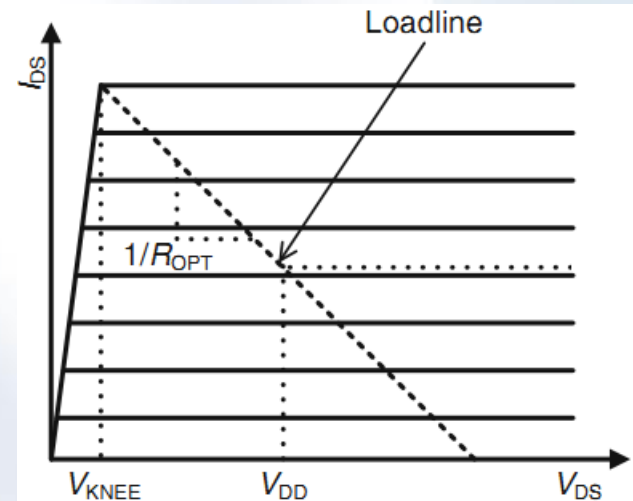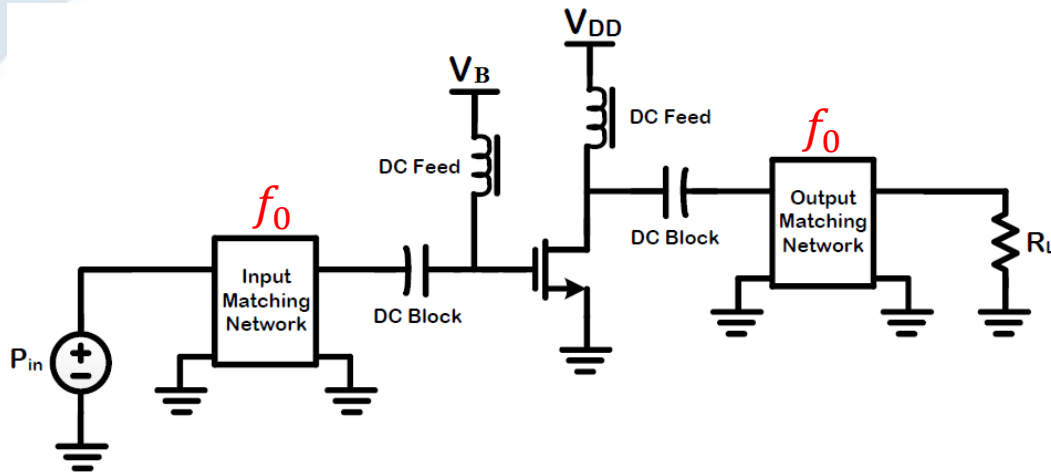


$$i_d(\theta) = \begin{cases} \frac{I_{max}}{1 - \cos \frac{\alpha}{2}} \left(\cos \theta - \cos \frac{\alpha}{2} \right) & -\frac{\alpha}{2} < \theta < \frac{\alpha}{2} \\ 0 & -\pi < \theta < \frac{\alpha}{2} ; \frac{\alpha}{2} < \theta < \pi \end{cases}$$

$$i_D(t) = I_0 + \sum_{n=1}^{\infty} I_n \cos(n\omega t + \xi_n)$$

$$v_{DS}(t) = V_{DD} - V_{TL} \cos \omega t$$
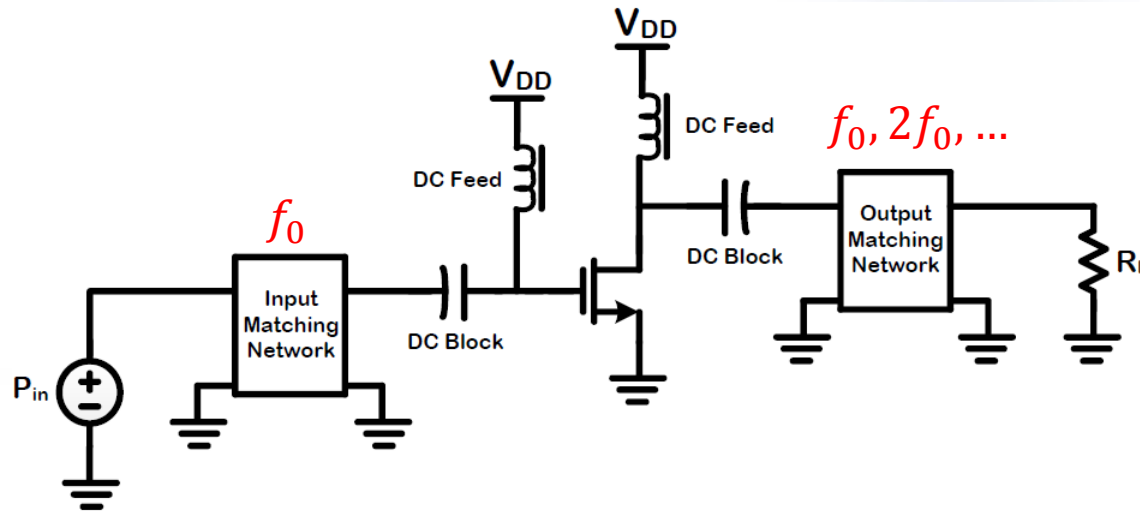
$$V_{TL} = \min[V_{DD} - V_{knee}, V_{BR} - V_{DD}]$$



$$i_D(t) = I_0 + \sum_{n=1}^{\infty} I_n \cos(n\omega t + \xi_n) \longrightarrow \text{Same as TL!}$$

$$v_{DS}(t) = V_{DD} - \sum_{n=1}^{\infty} V_n \cos(n\omega t + \psi_n) \longrightarrow V_{knee} \leq v_{DS}(t) \leq V_{BR}$$

$$P_{diss} = \frac{1}{T} \int_0^T v_{DS}(t) i_D(t) dt = V_{DD} I_0 - \frac{1}{2} \sum_{n=1}^{\infty} V_n I_n \cos(\phi_n)$$

$$P_{DC} = P_{diss} + P_{out_f} + \sum_{n=2}^{\infty} P_{out_{nf}}$$

$$\eta = \frac{P_{out_f}}{P_{DC}} = \frac{P_{out_f}}{P_{diss} + P_{out_f} + \sum_{n=2}^{\infty} P_{out_{nf}}}$$

$$P_{diss} + \sum_{n=2}^{\infty} P_{out_{nf}} = 0$$

\longrightarrow 100% Efficiency

$$Y_{L_n} = 0 \text{ or } Z_{L_n} = 0$$

$$\cos(\phi_n) = 0$$



❑ HTPAs: Class F, Class F⁻¹, J, and High Frequency Class E

❑ Only three harmonics could be controlled:

- Device parasitic capacitance
- Increased circuit complexity and matching losses

$$v_{DS}(t) = V_{DD} - V_1(\cos \omega t - k_2 \cos 2\omega t - k_3 \cos 3\omega t) \quad k_2 \equiv \frac{V_2}{V_1} \quad , \quad k_3 = \frac{V_3}{V_1}$$

$$v_{DS_{nor}}(\tau, k_2, k_3) = \frac{v_{DS}(\tau) - V_{DD}}{V_1} = -\cos \tau - k_2 \cos 2\tau - k_3 \cos 3\tau \quad \tau = \omega t$$

$$g(k_2, k_3) = \frac{V_1}{V_{TL}} \rightarrow \text{HT Gain}$$



$$p(k_2, k_3) = \frac{\max(v_{DS}(\tau)) - V_{DD}}{V_{DD} - V_{knee}} \rightarrow \text{HT Peaking}$$

$$\eta_{HT}(k_2, k_3) = g(k_2, k_3)\eta_{TL}$$

High Frequency 2nd HT PAs-Theory


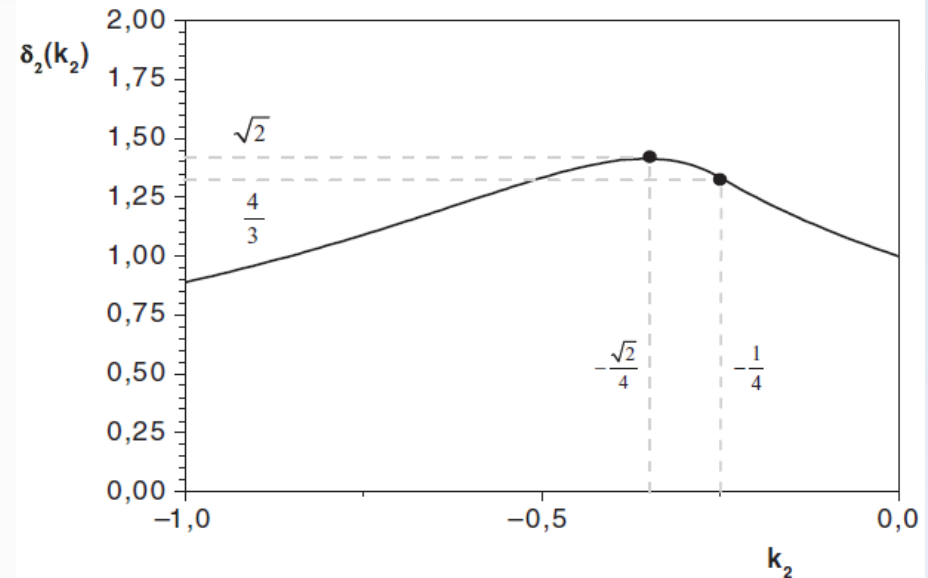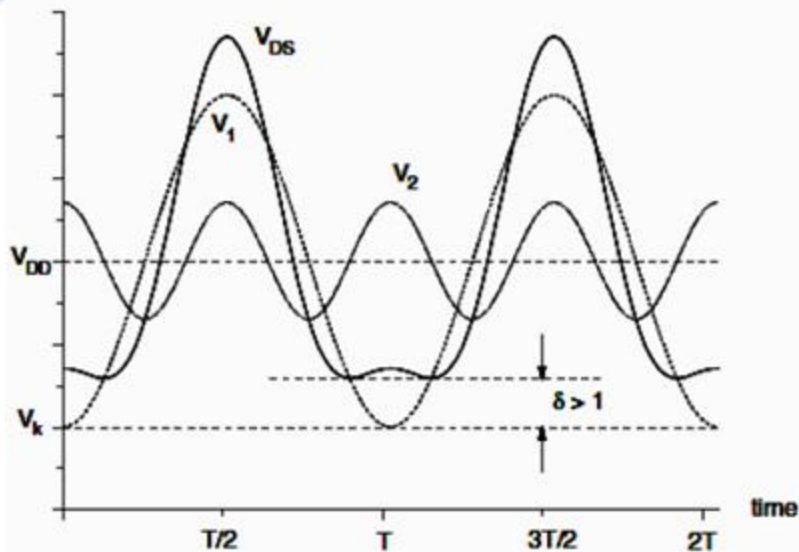
$$v_{DS_{nor}}(\tau, k_2, k_3) = -\cos \tau - k_2 \cos 2\tau$$



$$\frac{\partial v_{DS_{nor}}(\tau, k_2, k_3)}{\partial \tau} = \sin \tau + 2k_2 \sin 2\tau = 0$$

$$\tau_1 = 0 \quad , \quad \tau_2 = \pi \quad , \quad \tau_3 = \cos^{-1} \frac{-1}{4k_2}$$

$$g_2(k_2) \equiv g(k_2, k_3 = 0) = \begin{cases} \frac{-1}{k_2 + \frac{1}{8k_2}} & k_2 \leq -\frac{1}{4} \\ \frac{1}{1+k_2} & -\frac{1}{4} \leq k_2 \leq 0 \end{cases}$$

$$k_{2g} = -\frac{1}{2\sqrt{2}} \quad , \quad g_{2max} = \sqrt{2}$$

$$v_{ds}(\theta) = V_{DC} - (V_{DC} - V_{knee})(\sqrt{2} \cos \theta - 0.5 \cos 2\theta)$$

→ 111% Efficiency

High Frequency 2nd HT PAs-Peaking



$$v_{DS_{nor}}(\tau, k_2, k_3) = -\cos \tau - k_2 \cos 2\tau$$

$$\frac{\partial v_{DS_{nor}}(\tau, k_2, k_3)}{\partial \tau} = \sin \tau + 2k_2 \sin 2\tau = 0$$

$$\tau_1 = 0 \quad , \quad \tau_2 = \pi \quad , \quad \tau_3 = \cos^{-1} \frac{-1}{4k_2}$$

$$k_{2p} = -\frac{1}{2} \quad \text{,} \quad p_{2max} = 2$$



V_{DD} should be in order of $\frac{V_{BD}}{3}$

Lower Output Power

$$p_2(k_2) \equiv p(k_2, k_3 = 0) = \begin{cases} \frac{k_2 - 1}{k_2 + \frac{1}{8k_2}} & k_2 \leq -\frac{1}{4} \\ \frac{k_2 - 1}{k_2 + 1} & -\frac{1}{4} \leq k_2 \leq 0 \end{cases}$$


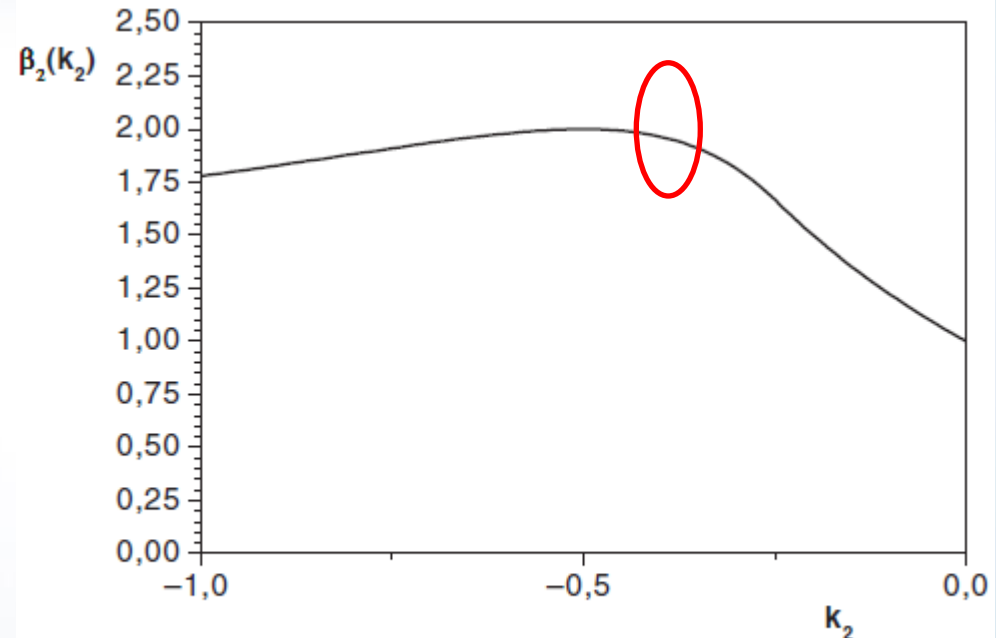


Figure Voltage overshoot function β_2 for different k_2 values.

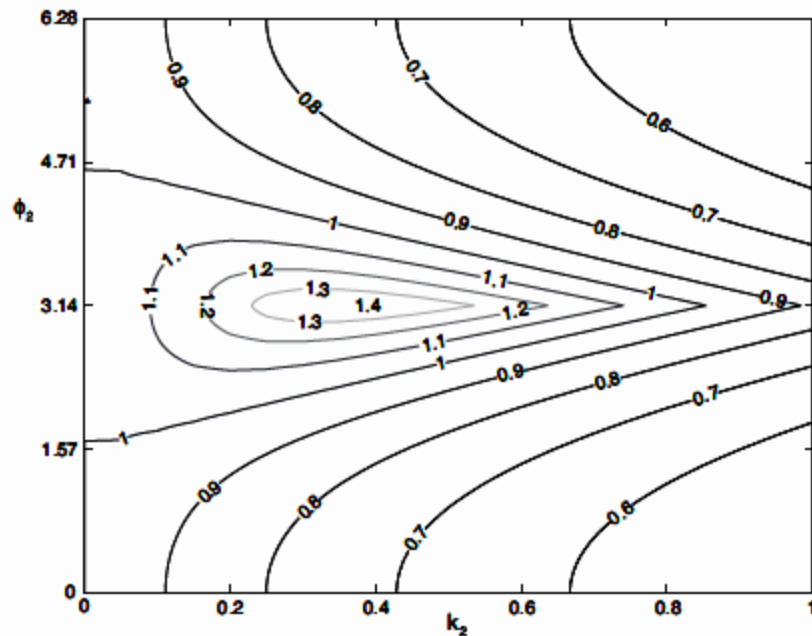
High Frequency 2nd HT PAs-Complex Termination




$$v_{DS}(t) = V_{DD} - V_1 \cos(\omega t) - V_2 \cos(2\omega t + \psi_2)$$



Gain

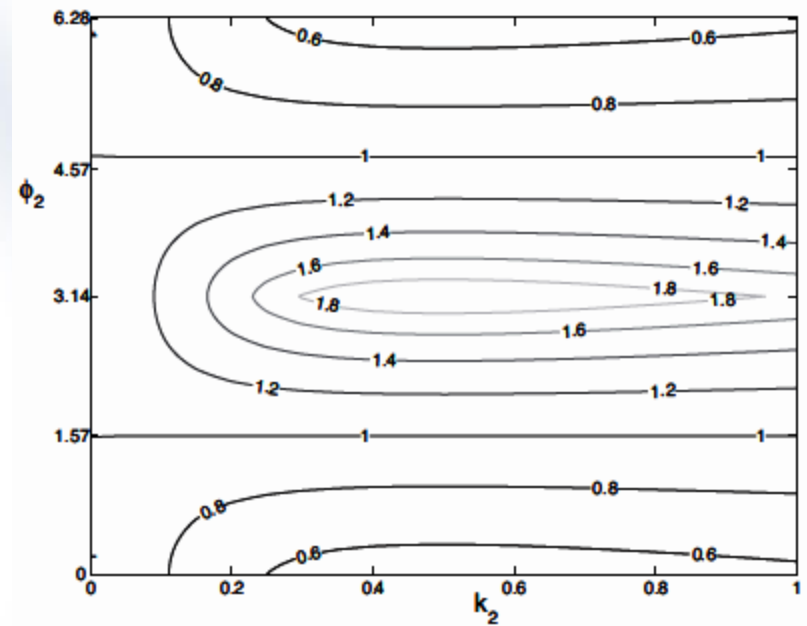

Peaking

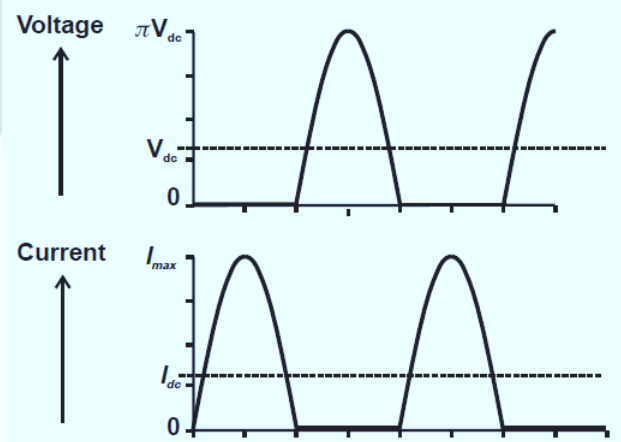

$$v_{ds}(\theta) = V_{DC} - (V_{DC} - V_{knee})(\sqrt{2} \cos \theta - 0.5 \cos 2\theta)$$



$$v_{DS}(t) = V_{DD} - V_1 \cos(\omega t + \psi_1) - V_2 \cos(2\omega t + \psi_2)$$

$$\alpha = \varphi = \frac{\pi}{2}:$$

$$i_D(\theta) = \frac{I_{Max}}{\pi} + \frac{I_{Max}}{2} \sin \theta - \frac{2I_{Max}}{3\pi} \cos 2\theta + \dots$$

$$v_D(\theta) = V_{DC} - \frac{\pi V_{DC}}{2} \sin(\theta + \delta) - \frac{2V_{DC}}{3} \cos 2(\theta + \delta) + \dots$$

$$Z_1 = \frac{\pi V_{DC}}{I_{Max}} \angle \delta, \quad Z_2 = \frac{\pi V_{DC}}{I_{Max}} \angle (2\delta - \pi) \rightarrow \frac{\pi}{4} < \delta < \frac{3\pi}{4}$$

$$\delta = \frac{\pi}{4}, \quad \delta = \frac{3\pi}{4}$$





Class J



Class J⁻¹

$$\eta_J = \sqrt{2} \eta_{TL} \cos\left(\frac{\pi}{4}\right) = \eta_{TL}$$

Class J Operation -Theory

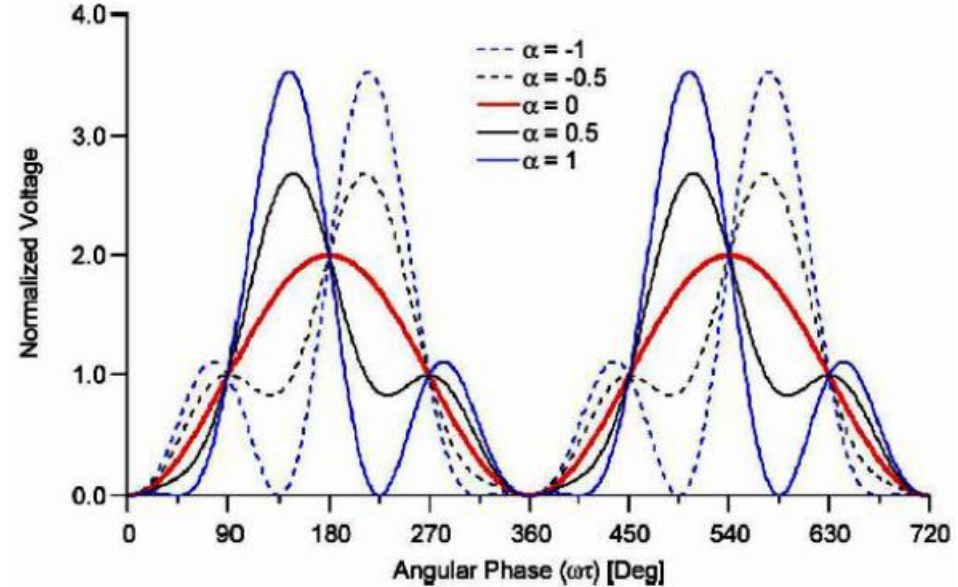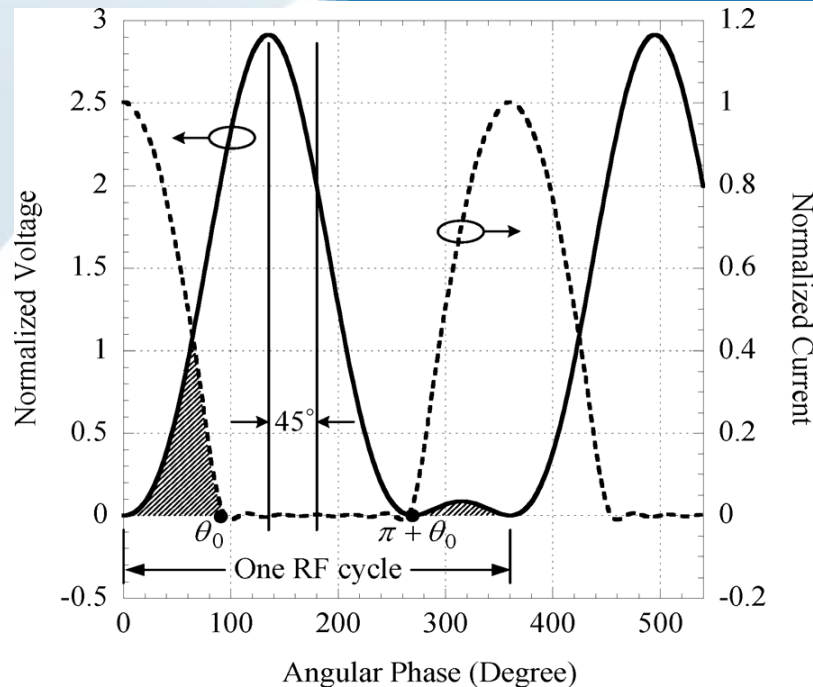

$$v_{DS}(\theta) = 1 - v_{1r} \cos \theta + v_{1q} \sin \theta + \sum_{n=2}^{\infty} v_{nq} \sin n\theta$$



$$v_{DS}(\theta) = 0 \quad , \quad v'_{DS}(\theta) = 0$$

$$v_{DS}(\theta) = (1 - \beta \cos \theta)(1 - \alpha \sin n\theta), \quad (-1 < \alpha < 1, 0 < \beta < 1)$$

$$v_{d_{1J}}(\theta) = V_{DC} - (V_{DC} - V_K)[\cos(\theta) - \sin(\theta) + 0.5 \sin(2\theta)]$$

$$Z_{L1}^J = -\frac{a_{v1} + jb_{v1}}{a_{i1} + jb_{i1}} = \frac{(V_{DC} - V_{knee})(1+j)}{\frac{I_{max}}{2}} = \frac{2(V_{DC} - V_{knee})}{I_{max}}(1+j)$$
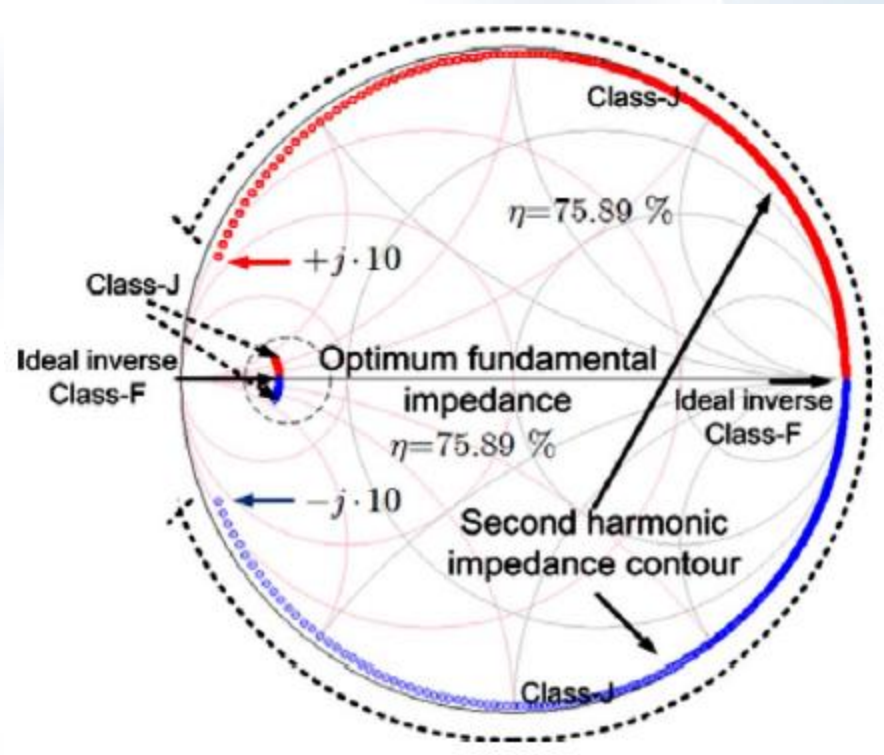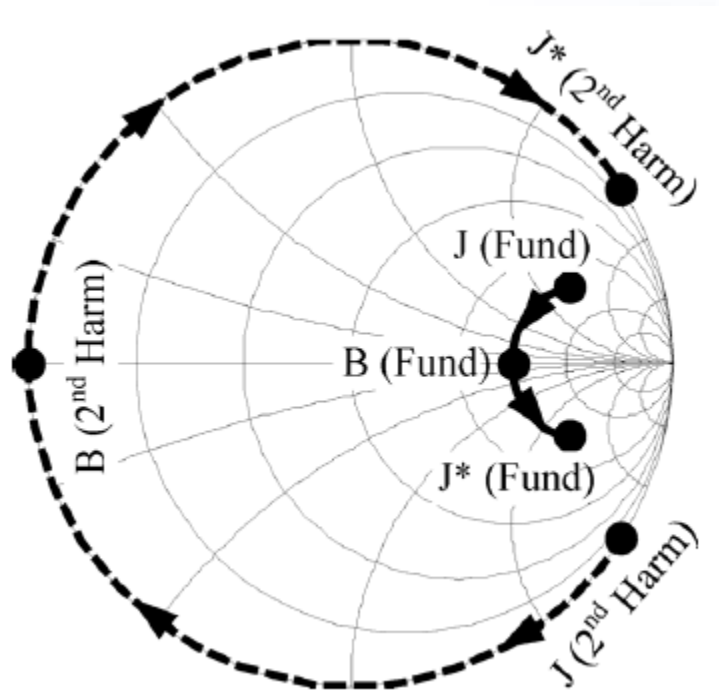
$$Z_{L2}^J = -\frac{a_{v2} + jb_{v2}}{a_{i2} + jb_{i2}} = \frac{-0.5(V_{DC} - V_{knee})j}{\frac{2I_{max}}{3\pi}} = -\left(\frac{3\pi}{8}\right) \frac{2(V_{DC} - V_{knee})}{I_{max}}j$$





- ❑ Simple Matching

- ❑ Wide-Band Designs

- ❑ Multi-Band/Multi-Standard Designs



- ❑ High Frequency Potential

- ❑ Lower Losses

- ❑ Peaking

- ❑ Lower Output Power

- ❑ Lower Efficiency Compared to Class F

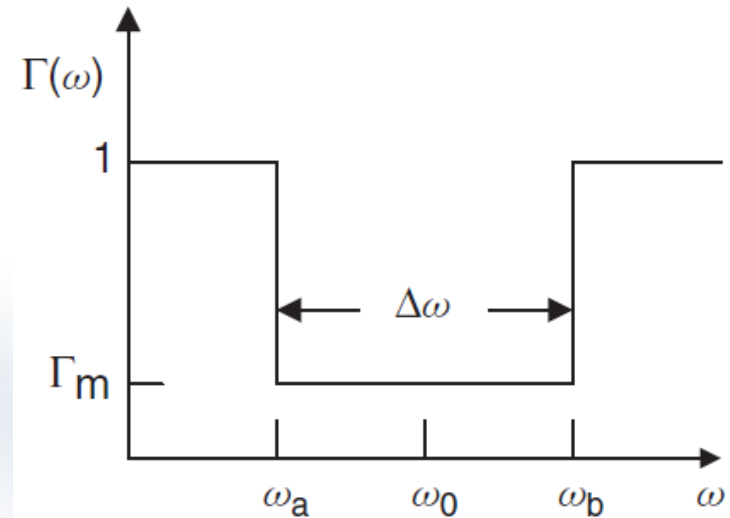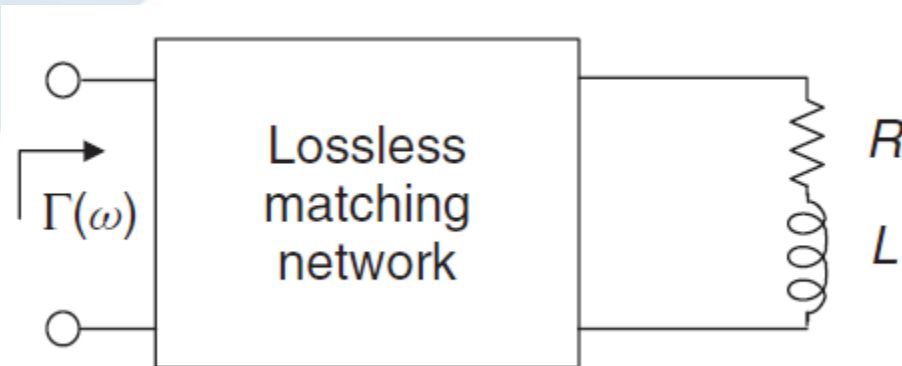

$$\Gamma(\omega) = \frac{Z_{in} - R_G}{Z_{in} + R_G} \quad , \quad \Delta\omega = \omega_b - \omega_a \quad , \quad Q_L = \frac{L\omega_0}{R} \quad , \quad Q_C = \frac{\omega_0}{\Delta\omega}$$

$$\int_0^{\infty} \ln \left| \frac{1}{\Gamma(\omega)} \right| d\omega \leq \frac{\pi R}{L} \quad \rightarrow \quad \Delta\omega \ln \left| \frac{1}{\Gamma_m} \right| = \frac{\pi R}{L} \quad \rightarrow \quad \frac{\Delta\omega}{\omega_0} = \frac{\pi}{Q_L \ln \left| \frac{1}{\Gamma_m} \right|}$$

For Class J Operation:


$$Z_{1_{opt}} = R_{opt} + jR_{opt} \rightarrow Q_L = 1$$

$$\text{For } \Gamma_m = 10 \text{ dB} \rightarrow \frac{\Delta\omega}{\omega_0} = 136 \%$$

Wide-Band Class J power Amplifier-Theory



Lopez, IEEE APM, 2004, 2005, and 2007

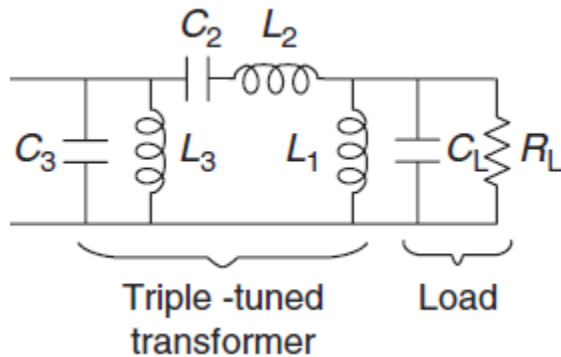

Coefficients a_n and b_n for Various Values of n

| n | a_n | b_n |
|----------|-------|-------|
| 1 | 1 | 1 |
| 2 | 2 | 1 |
| 3 | 2.413 | 0.678 |
| 4 | 2.628 | 0.474 |
| 5 | 2.755 | 0.347 |
| 6 | 2.838 | 0.264 |
| 7 | 2.896 | 0.209 |
| 8 | 2.937 | 0.160 |
| ∞ | π | 0 |





$$Q_L BW = \frac{1}{b_n \sinh \left[\frac{1}{a_n} \ln \left(\frac{1}{\Gamma} \right) \right] + \frac{1-b_n}{a_n} \ln \left(\frac{1}{\Gamma} \right)}$$

$$n = 1 : BW = \frac{1}{Q_L} \frac{2\Gamma_m}{1 - \Gamma_m^2} \rightarrow BW \cong 20 \%$$


$$n = 2 : BW = \frac{1}{Q_L} \frac{2\sqrt{\Gamma_m}}{1 - \Gamma_m} \rightarrow BW \cong 70 \%$$

$$n = 3 : \rightarrow BW \cong 95 \%$$

Class J Bandwidth- Clipping Contours

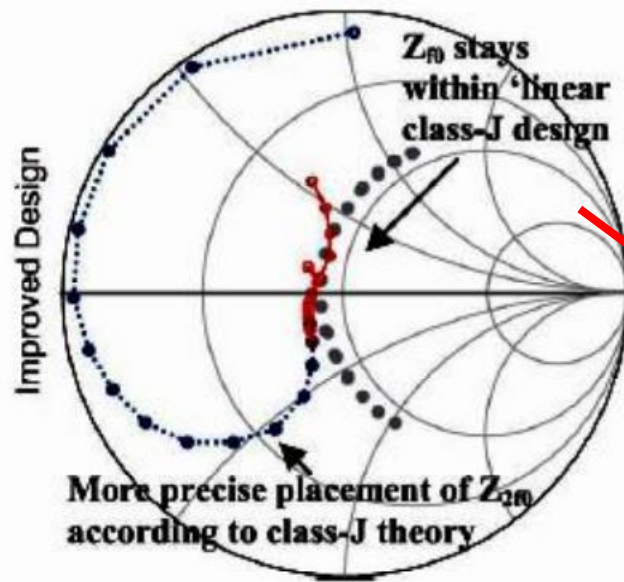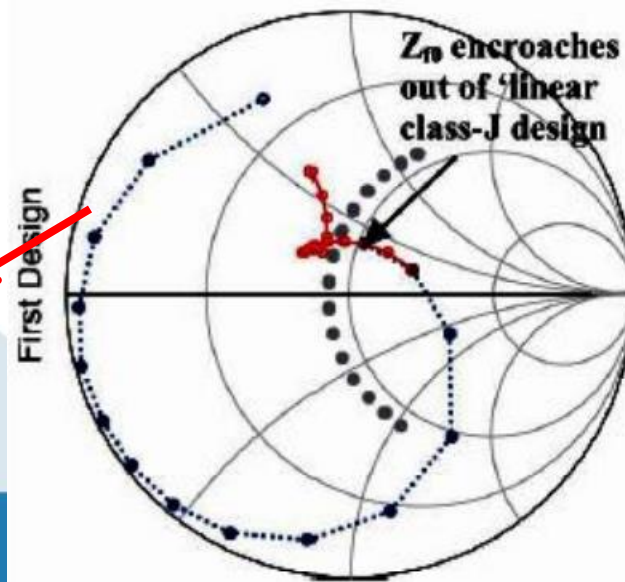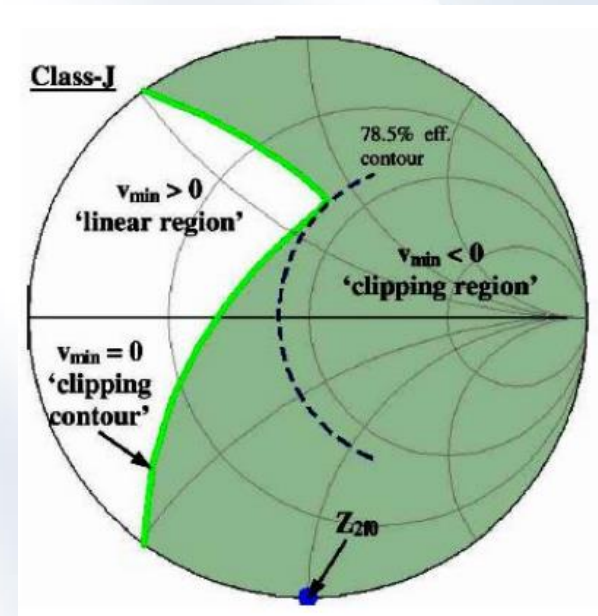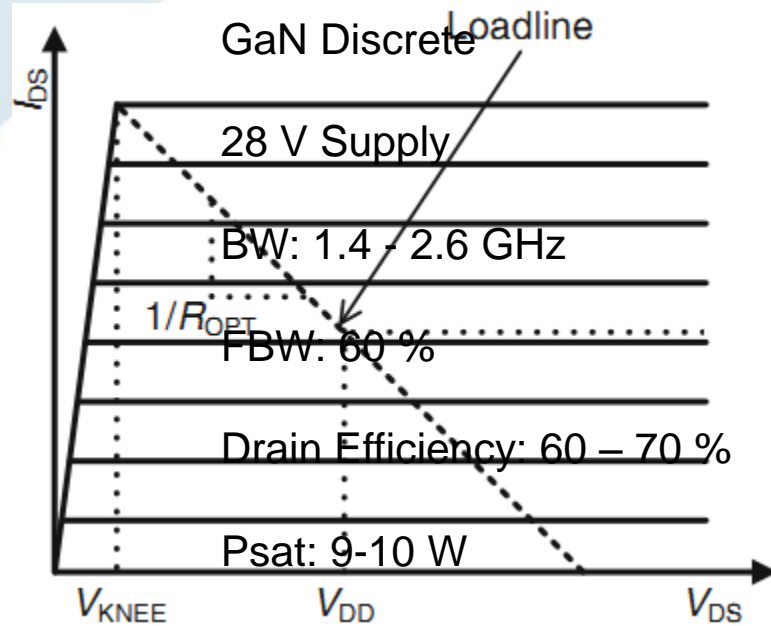

Class J Bandwidth- Matching Pool

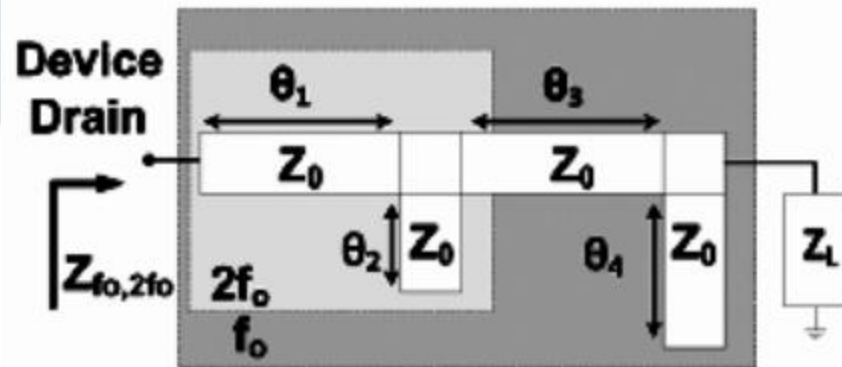

GaN Discrete


28 V Supply

BW: 1.6 - 2.2 GHz

FBW: 32 %

Drain Efficiency: 55 – 68 %

Psat: 10 W

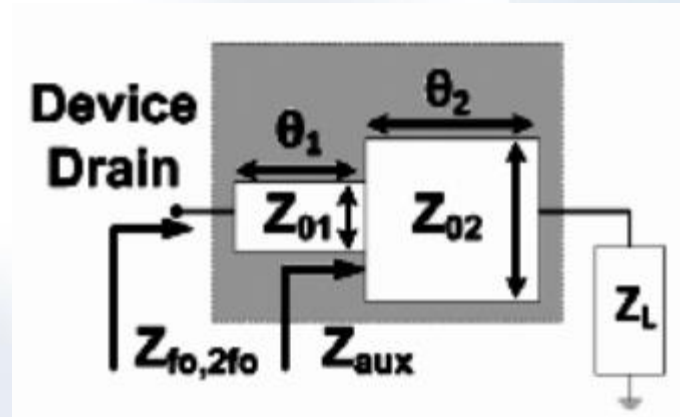

GaN Discrete

28 V Supply

BW: 0.5 – 1.8 GHz

FBW: 113%

Drain Efficiency: 50 – 69 %

Psat: 10 W

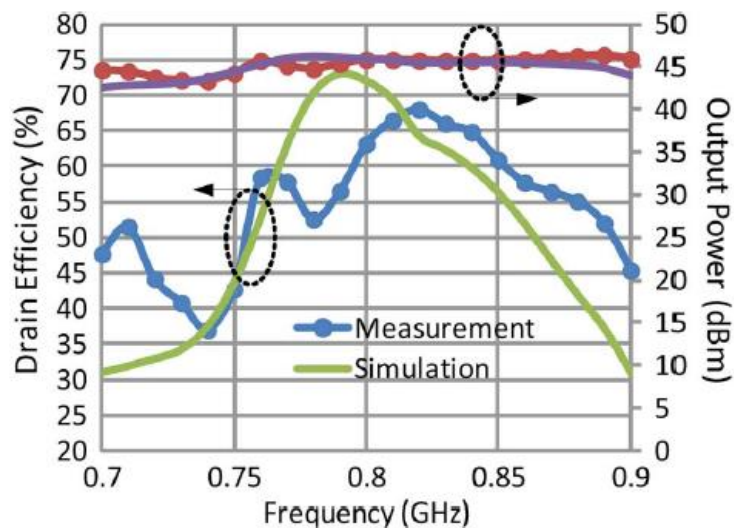


Fig. 19. Measurement and simulation results of output power and drain efficiency for the lower band.

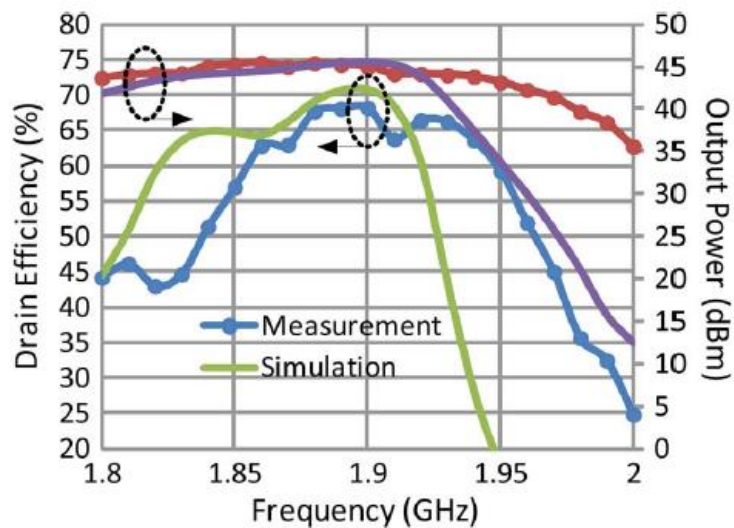


Fig. 20. Measurement and simulation results of output power and drain efficiency for the upper band.

TABLE I
TARGET FUNDAMENTAL IMPEDANCES

| Impedance | 0.8GHz | 1.9GHz |
|-------------|--------------|------------|
| Load side | $9.85+j4.8$ | $4+j2.4$ |
| Source side | $4.68+j3.66$ | $2.1-j2.7$ |


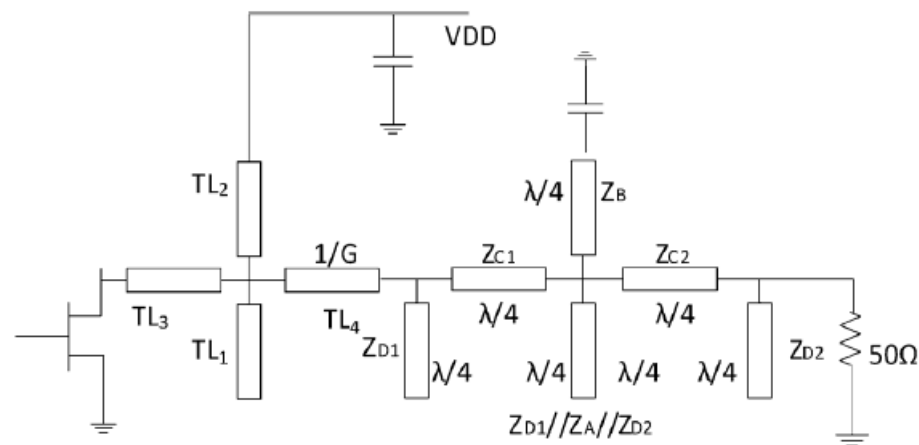


Fig. 14. Dual-band PA topology (load side).

Class J- High Back-Off Efficiency

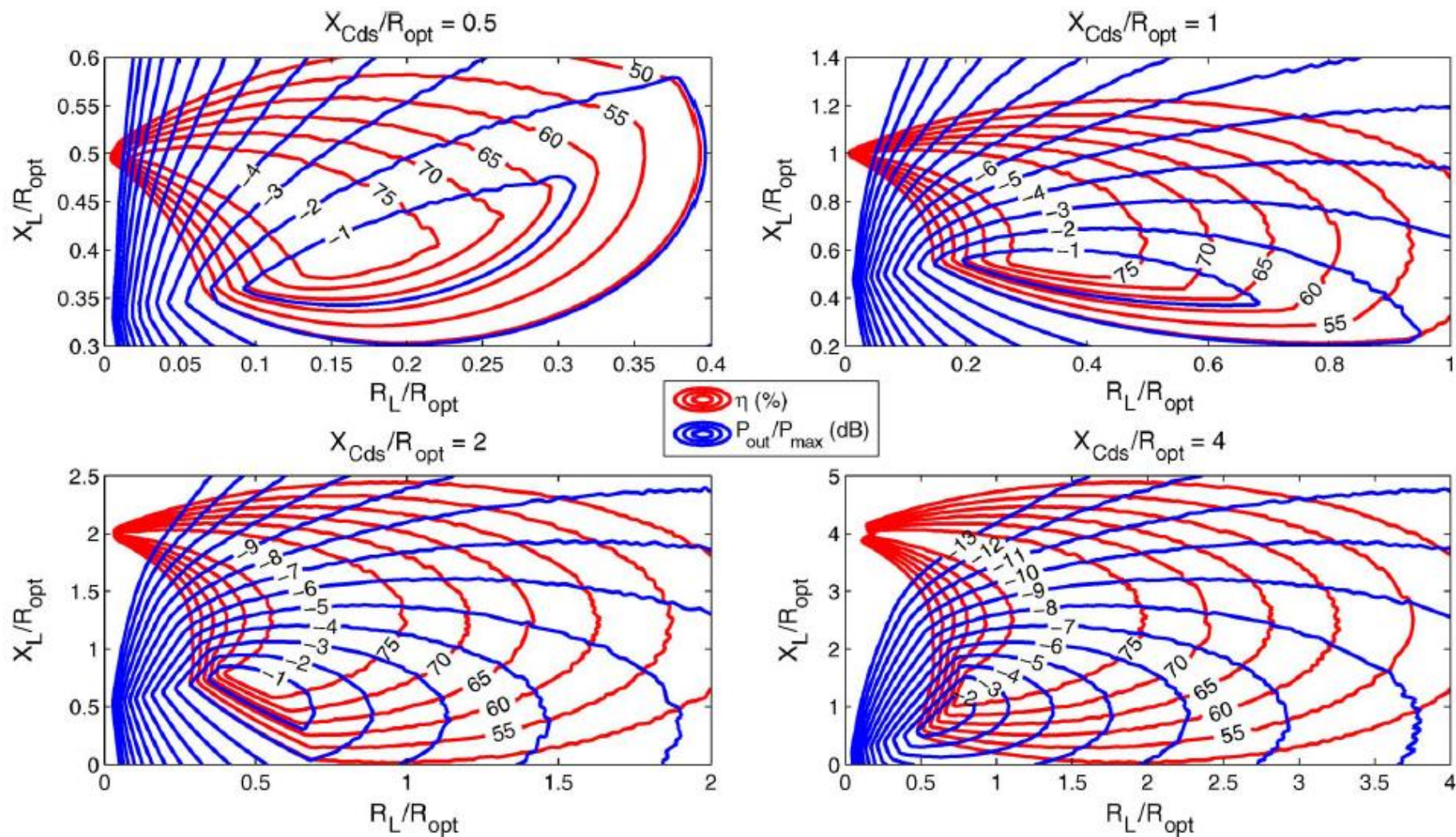



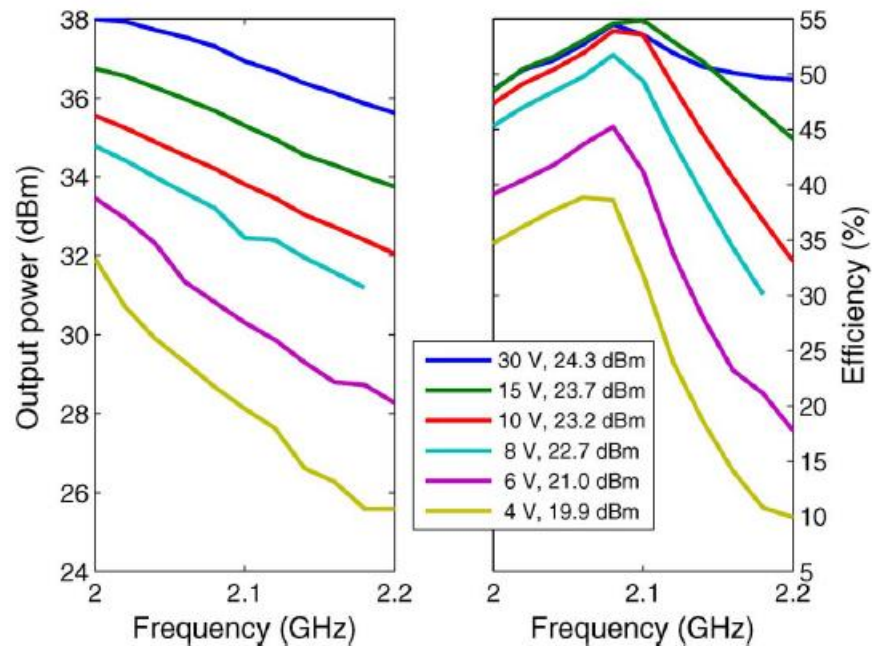
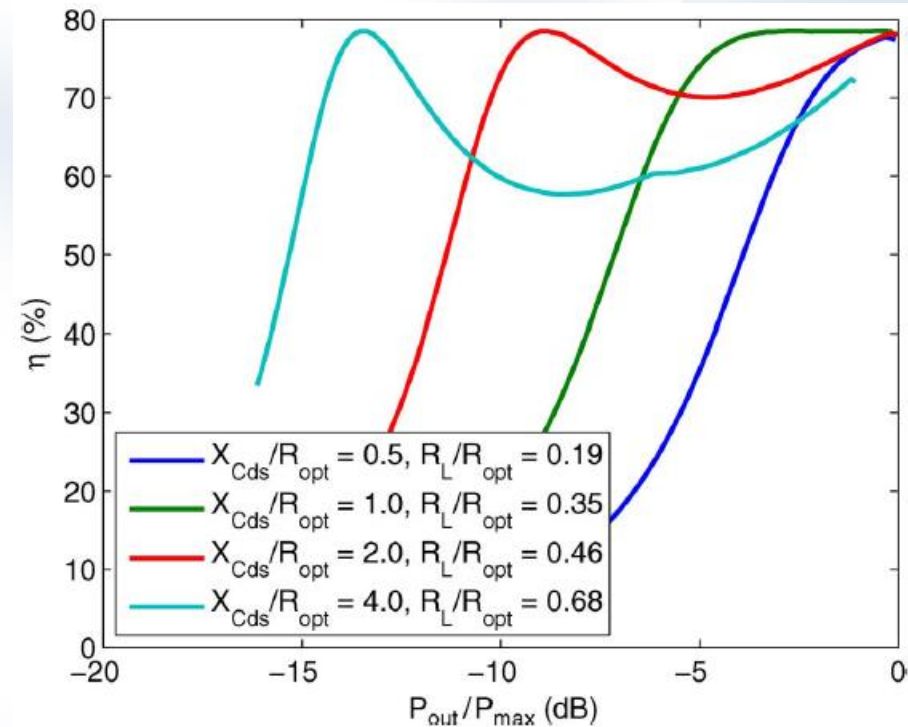
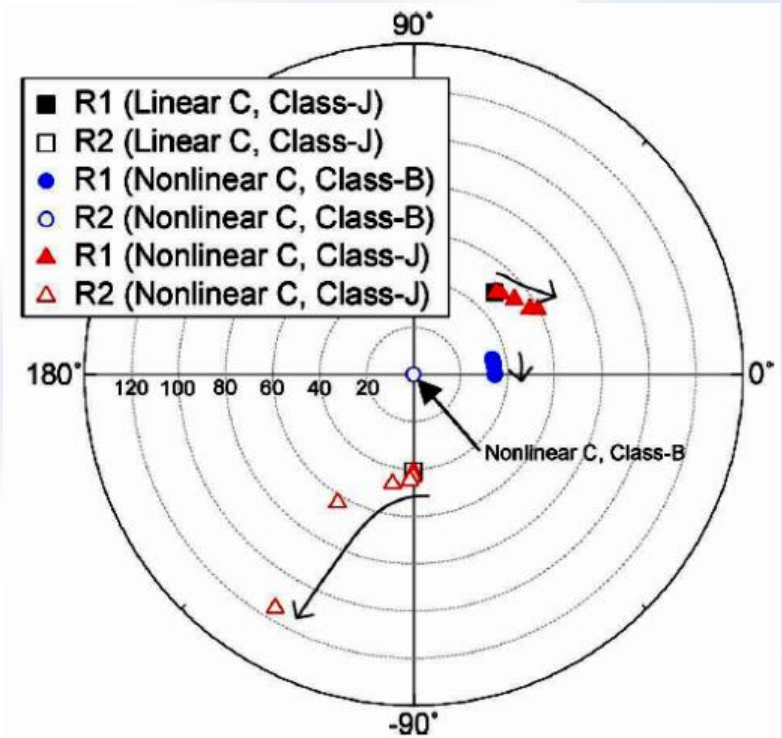


Fig. 11. Amplifier output power and efficiency versus frequency when following the optimum control function at 2.08 GHz, but backing off the input power by 2 dB.

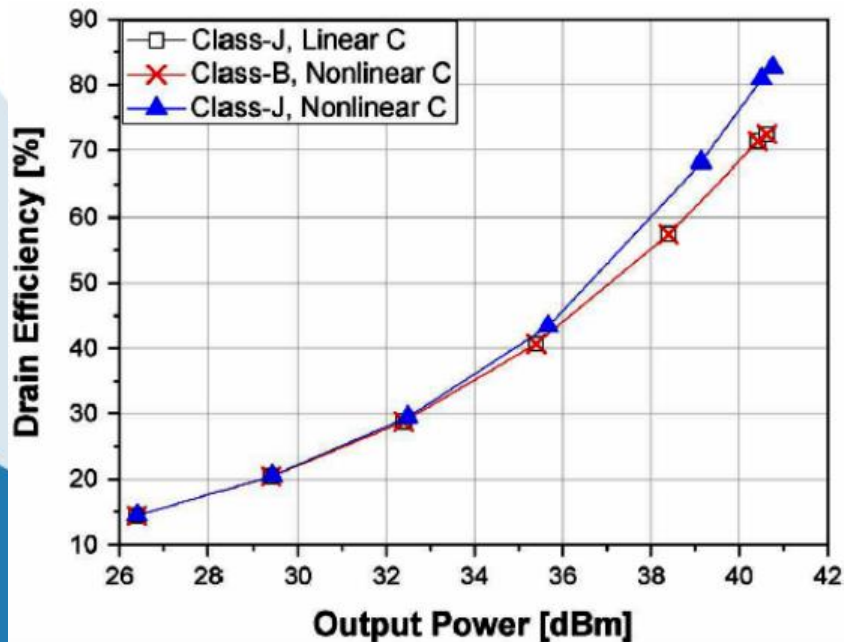

Class J Efficiency- Negative Resistance

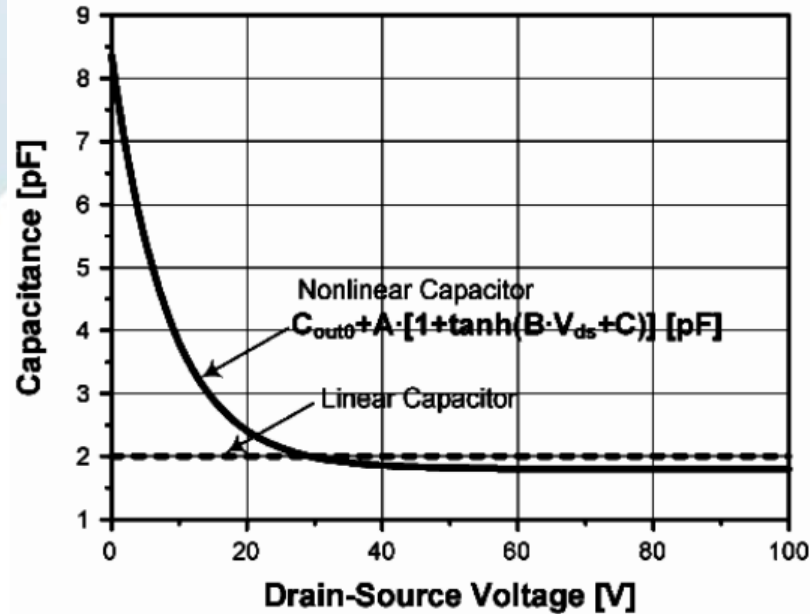

GaN Discrete

30 V Supply

f: 2.14 GHz


Drain Efficiency: 77%

Psat: 11.5 W

Class J Efficiency- Transistor Sizing



Rezaei, MTT, 2013

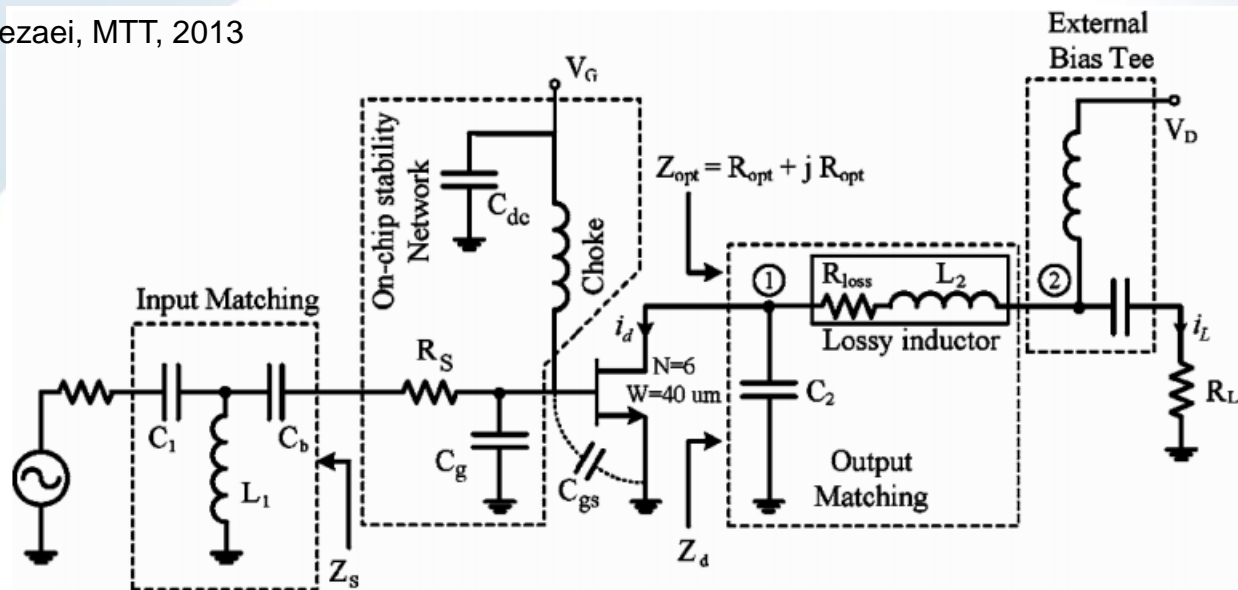

GaN Integrated

15 V Supply

f: 2.5 GHz

Drain Efficiency: 58%

Psat: 0.5 W

