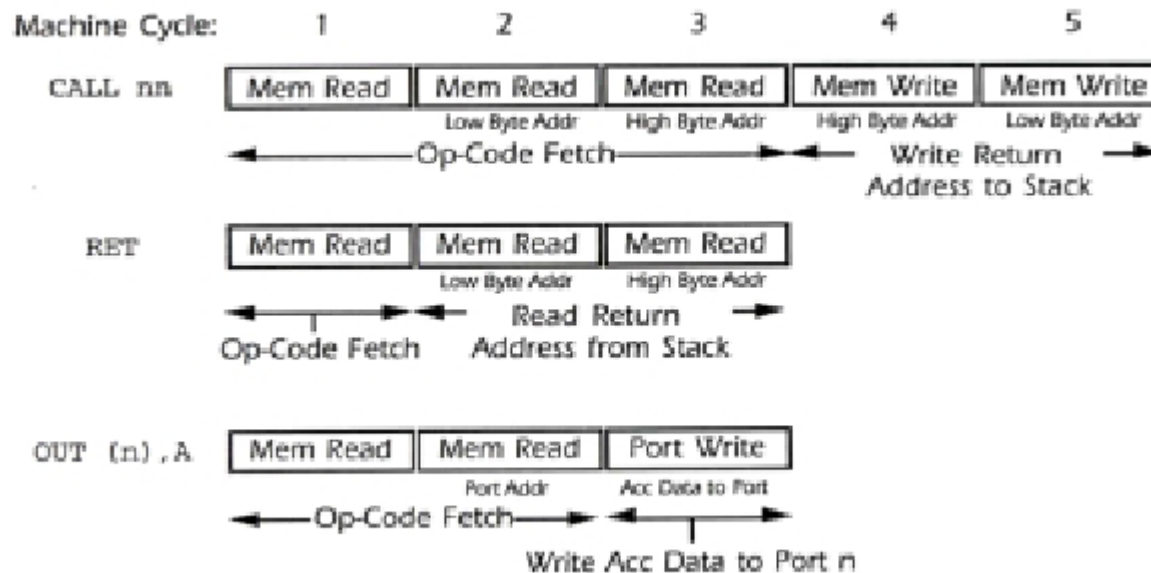


# Memory Interfacing

# Instruction Cycles and Machine Cycles


- Instruction cycle is the time taken to complete the execution of an instruction  $\Rightarrow$  1-6 machine operation cycles
- Machine cycle is defined as the time required to complete one operation of accessing memory, accessing IO, etc.



# T-States

- Machines cycles are divided up into system clock cycles called T-states ( $1T = 1C$  cycle)
- T-state =  $1T = 1/f_{Z80} = 1.75$  us for 4MHz
- Example: LD A, 09H
  - It is a 2-byte instruction with 2 machine cycles.  
(2 operations = M1 Opcode Fetch + Memory read(Operand))
  - The execution time =  $4T + 3T = 7T$ .
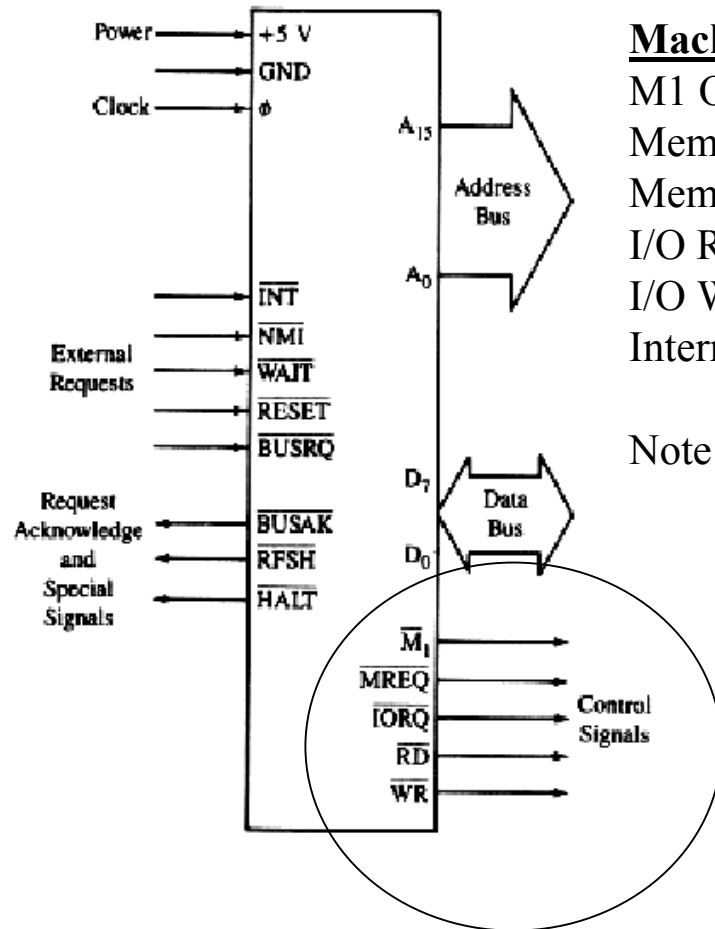
# The Z80 Machine Cycles and Control Signals




Machine Cycle	M1	MREQ	IORQ	RD	WR
M1 Opcode Fetch	0	0	1	0	1
Memory Read	1	0	1	0	1
Memory Write	1	0	1	1	0
I/O Read	1	1	0	0	1
I/O Write	1	1	0	1	0
Interrupt Ack	0	1	0	0	0


Note: Logic 0 = Active, Logic 1 = Inactive
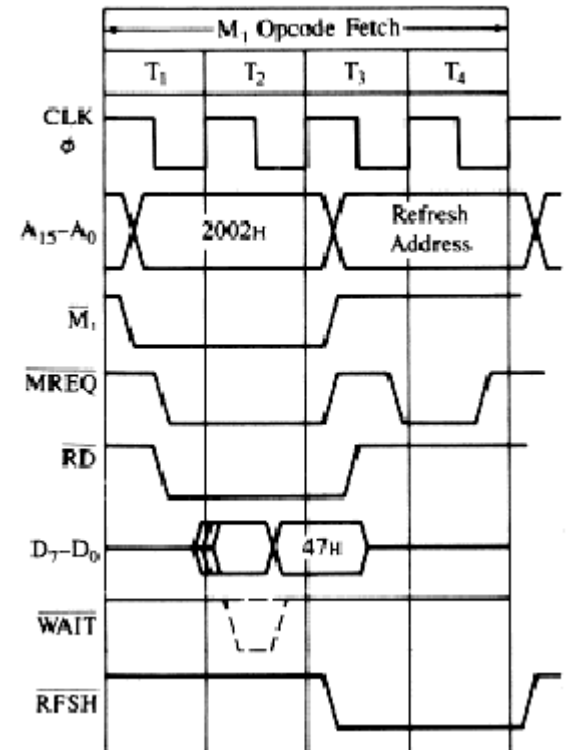
# M1 Opcode Fetch Cycle

- Used to differentiate with Memory Read(Operand) and used for Int Ack cycle
- Sequence of events(Initial condition PC=2002H)
  - M1 goes low at the beginning of T1.
  - Z80 places PC on address bus and increments PC by 1
  - After T1 falling edge, MREQ and RD are asserted.
  - External memory circuits decodes the address and 2002H is identified.
  - Data bus which was high impedance state is activated after leading edge of T2.
  - Memory places 47H on the data bus after falling edge of T2.
  - Data is read at the leading edge of T3 and signals become inactive
  - Between T3 and T4 the instruction decoder in the  $\mu$ P decodes and executes the opcode.




# M1 Refresh Cycle and Wait Signal

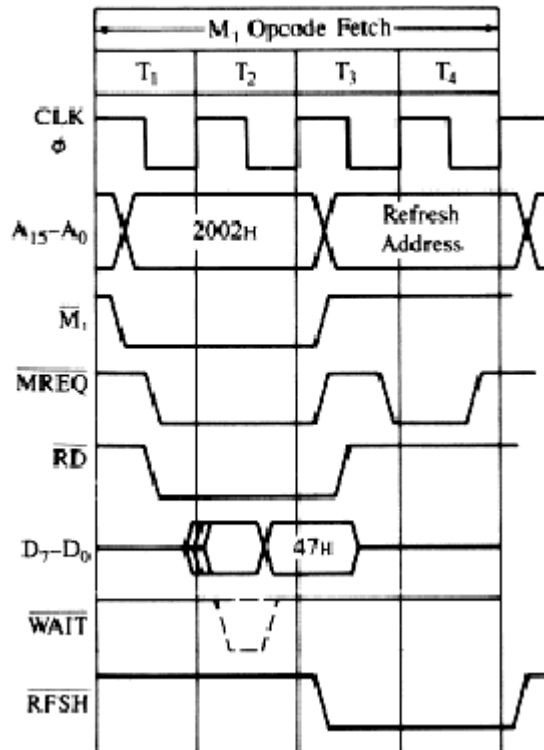

- Dynamic memory consists of MOS transistors, which store information as capacitive charges; each cell needs to be periodically refreshed.
- Wait signal : the Z80 samples the wait signal during T2 if low then Z80 adds wait states to extend the machine cycle - used to interface memories with slow response time.

# Memory Read Cycle

<u>Address</u>	<u>Opcode</u>	<u>Instruction</u>
2000	3E	LD A, 9FH
2001	9F	

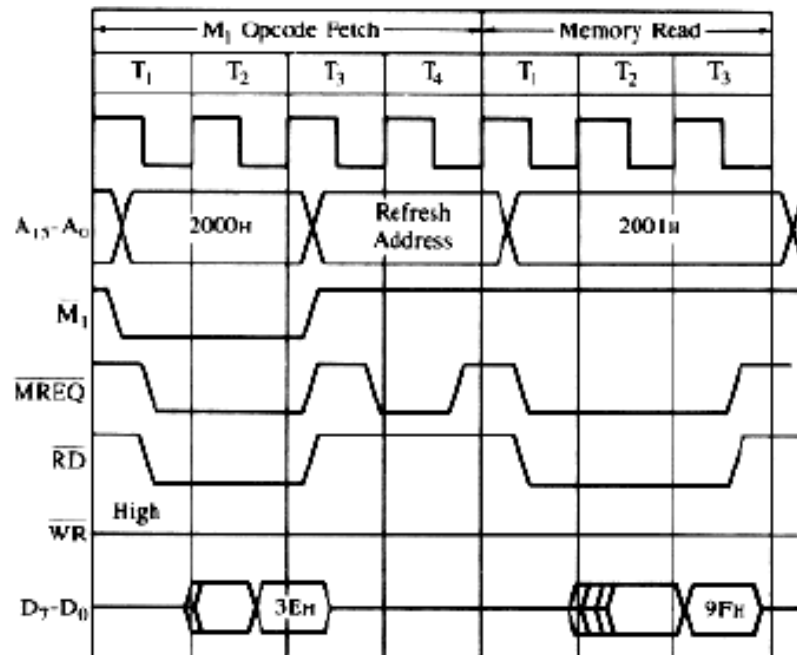

# Memory Write Cycle

Address

Opcode


Instruction

2003

77

LD (HL),A


(Assume HL = 2350H , A = 9FH)

 


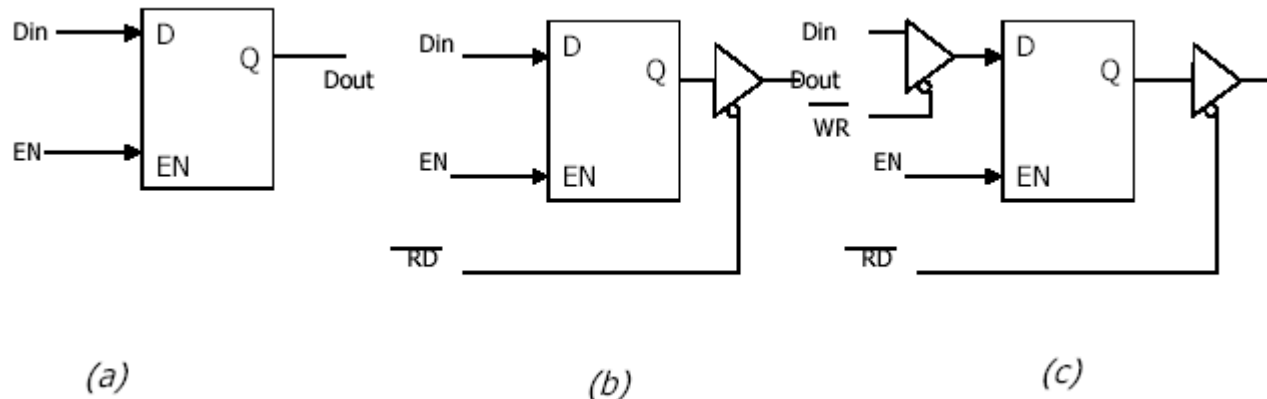
# Memories


- Memory cell : A latch that can store one binary bit
- Registers are made up of multiple memory cells.
- A simple latch with an input and enable bit(Figure a) : Stored bit is always available at output.
- Using tri-state buffer to the output of the the latch (Figure b) : Stored bit can be read only when buffer is enabled.
- Using a tri-state buffer on the input too (Figure c) : Write into it by enabling the input buffer and read from it by enabling the output buffer.



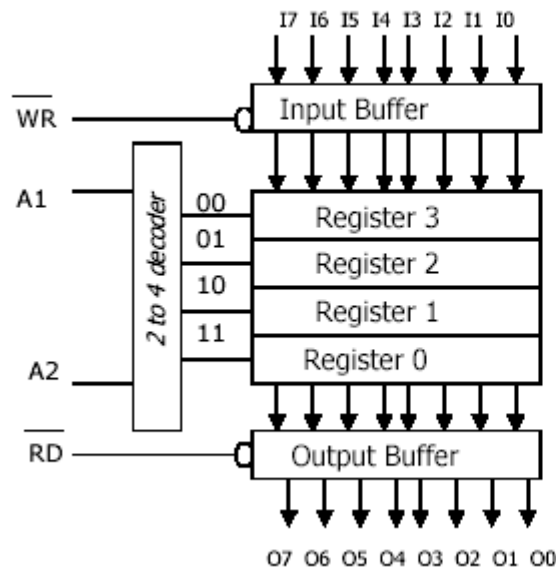
# Memories Continued

- Figure (a) shows a 4×8 bit memory(register).
- To write into or read from any one of the registers, a specific register should be identified. This is a simple decoding function; 2-to-4 decoder can perform that function.
- In this case two more input lines A1 and A0 called address lines are required by the decoder.

- Each combination (00, 01, 10, 11) can identify or enable one of the registers (R0-R3).
- If we have only 4 bit memory chips, we can combine two chips in parallel to make an 8-bit memory word as shown in Figure (b).




(a)

 

(b)



# Memory Chips

 

A typical 1K memory chip


- A0-A9 = Address lines to identify memory register, /CS (Chip Select) = signal to enable chip, /RD and /WR control signals to read from and write into memory.
- Number of address line is related to number of registers ( $2^n =$  number of registers, n is the number of address lines).
- /RD enables the output buffer. Data from the selected register are made available on the output lines.
- /WR enables the input buffer. Data on the input lines are written into memory cells.
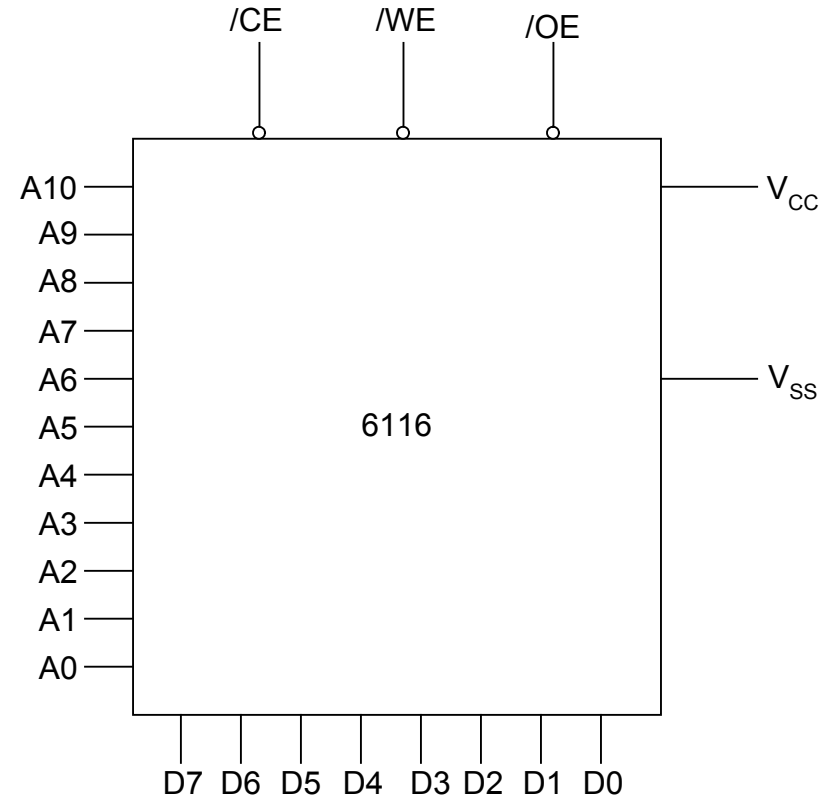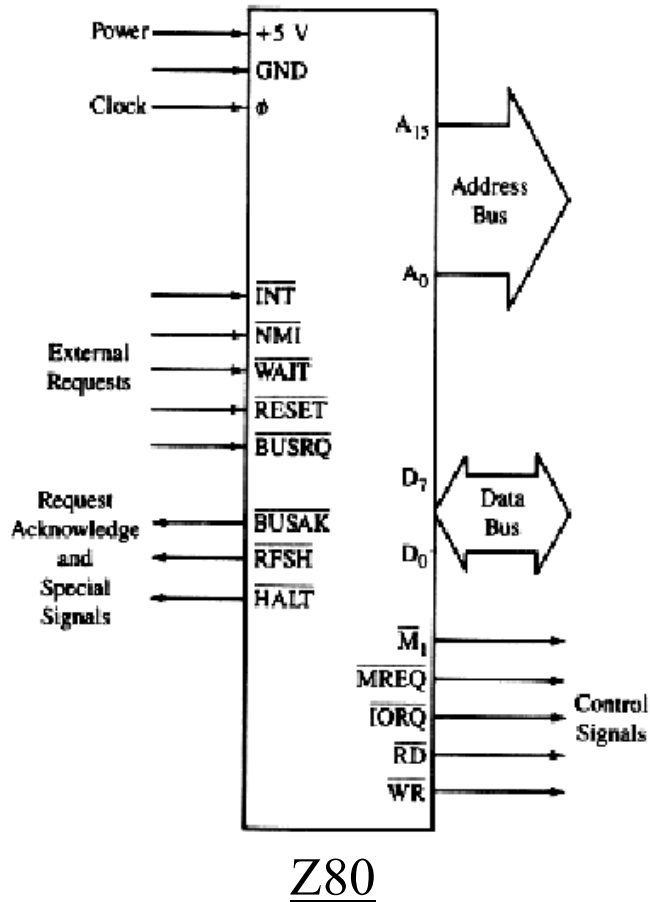
# Interfacing the Z80 with 6116 Memory Chip(2K x 8)



$\overline{\text{CE}}$  = Chip Enable  
 $\overline{\text{WE}}$  = Write Enable  
 $\overline{\text{OE}}$  = Output Enable  
 V<sub>CC</sub> = Power(+5 Volts)  
 V<sub>SS</sub> = Ground

# 6116 Interfacing Circuit

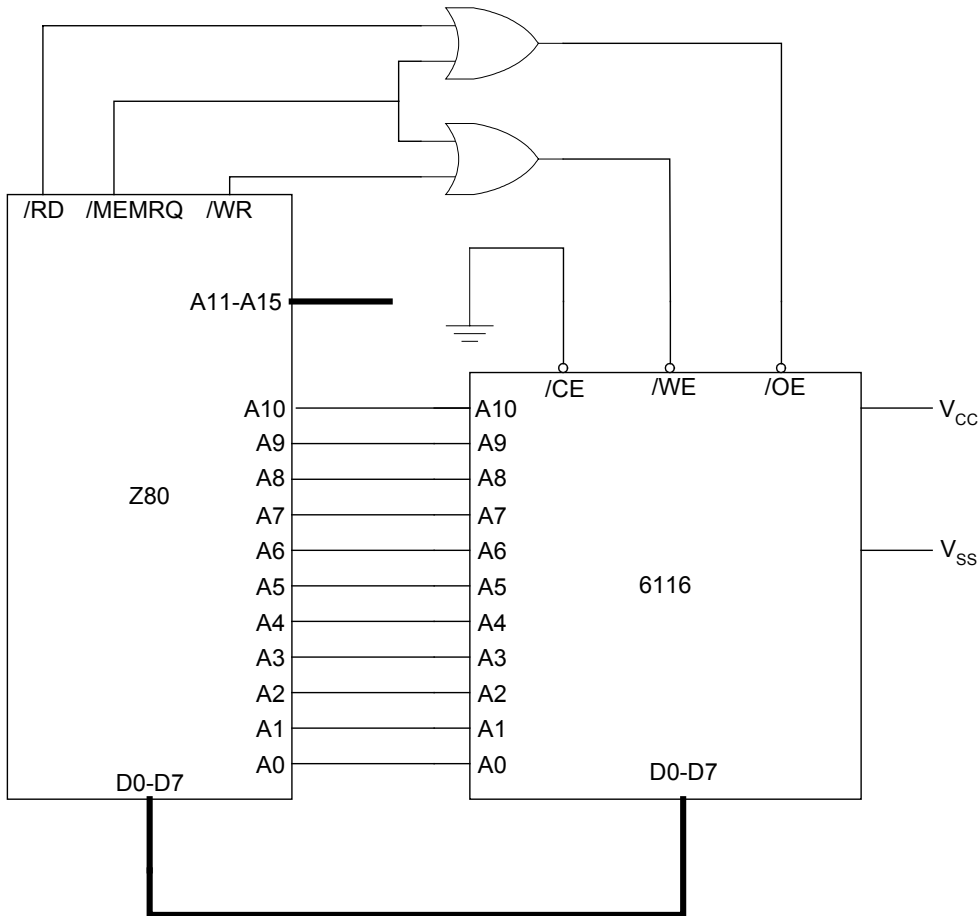

A15	A14	A13	A12	A11	A10	A9	A8	A7	A6	A5	A4	A3	A2	A1	A0
X	X	X	X	X	0	0	0	0	0	0	0	0	0	0	0
X	X	X	X	X	1	1	1	1	1	1	1	1	1	1	1

Address 0000H-07FFH =

Address 0800H-0FFFH =


Address 1000H-17FFH =

Address 1800H-1FFFH = ... =

Address 0F800H-0FFFFH

- Address 0000H is the same address on the 6116 chip as address 0800H, 1000H, 1800H, ..., 0F800H.


# 6116 Interfacing Circuit Continued

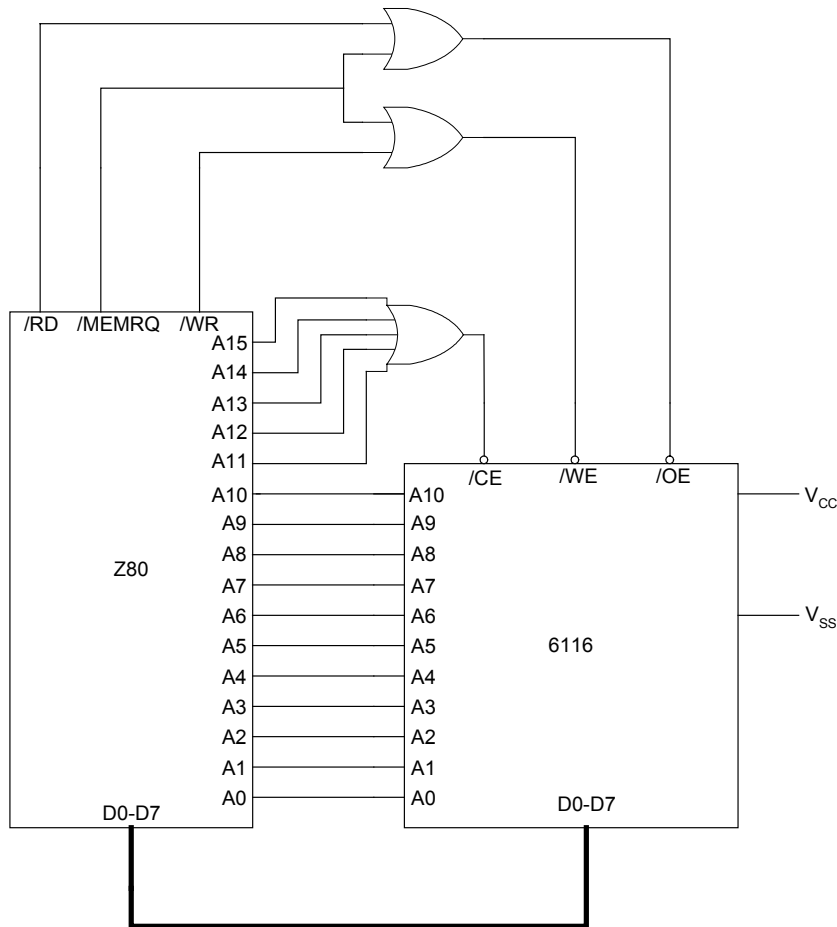

A15	A14	A13	A12	A11	A10	A9	A8	A7	A6	A5	A4	A3	A2	A1	A0
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
.	.	.	.	.	.	.	.	.	.	.	.	.	.	.	.
0	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1

- The memory range of the 6116 chip is 0000H-07FFH.

# 6116 Interfacing Circuit Continued

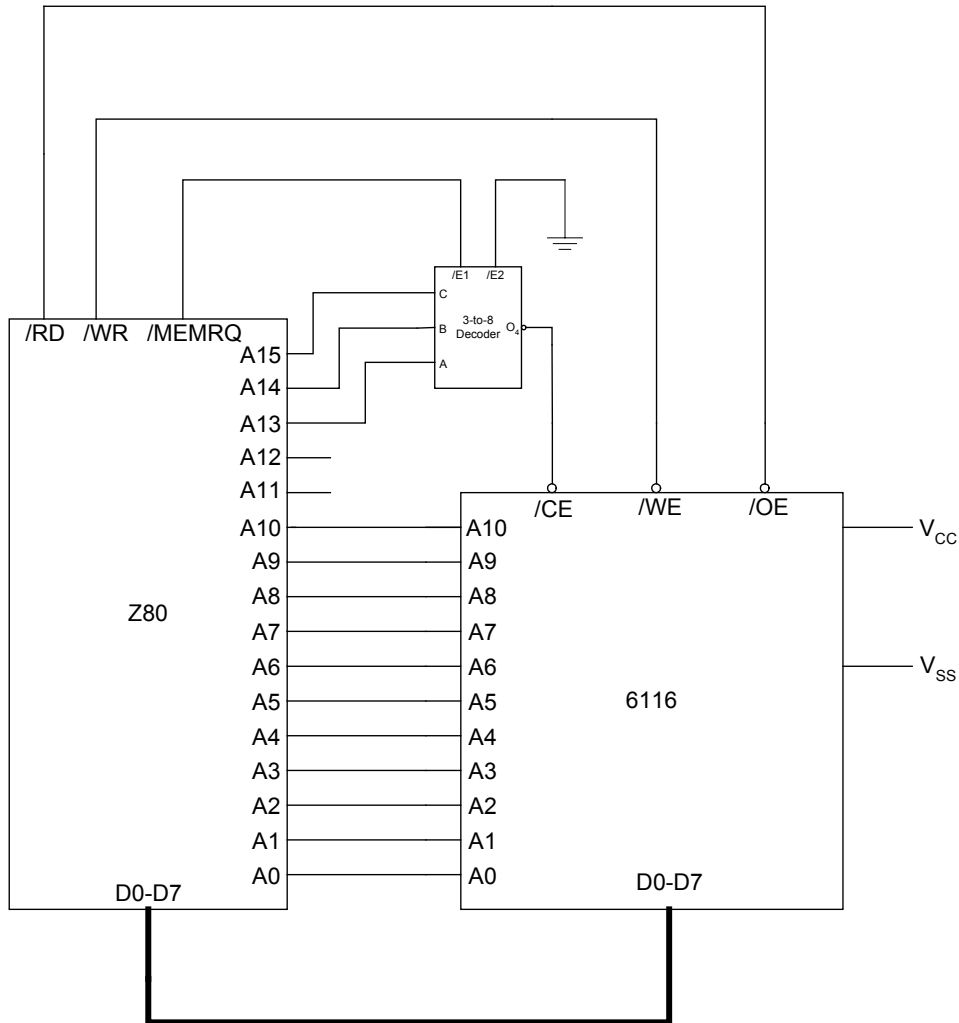


A15 A14 A13 A12 A11    A10 A9 A8 A7 A6 A5 A4 A3 A2 A1 A0

The memory range of the 6116 chip is

---
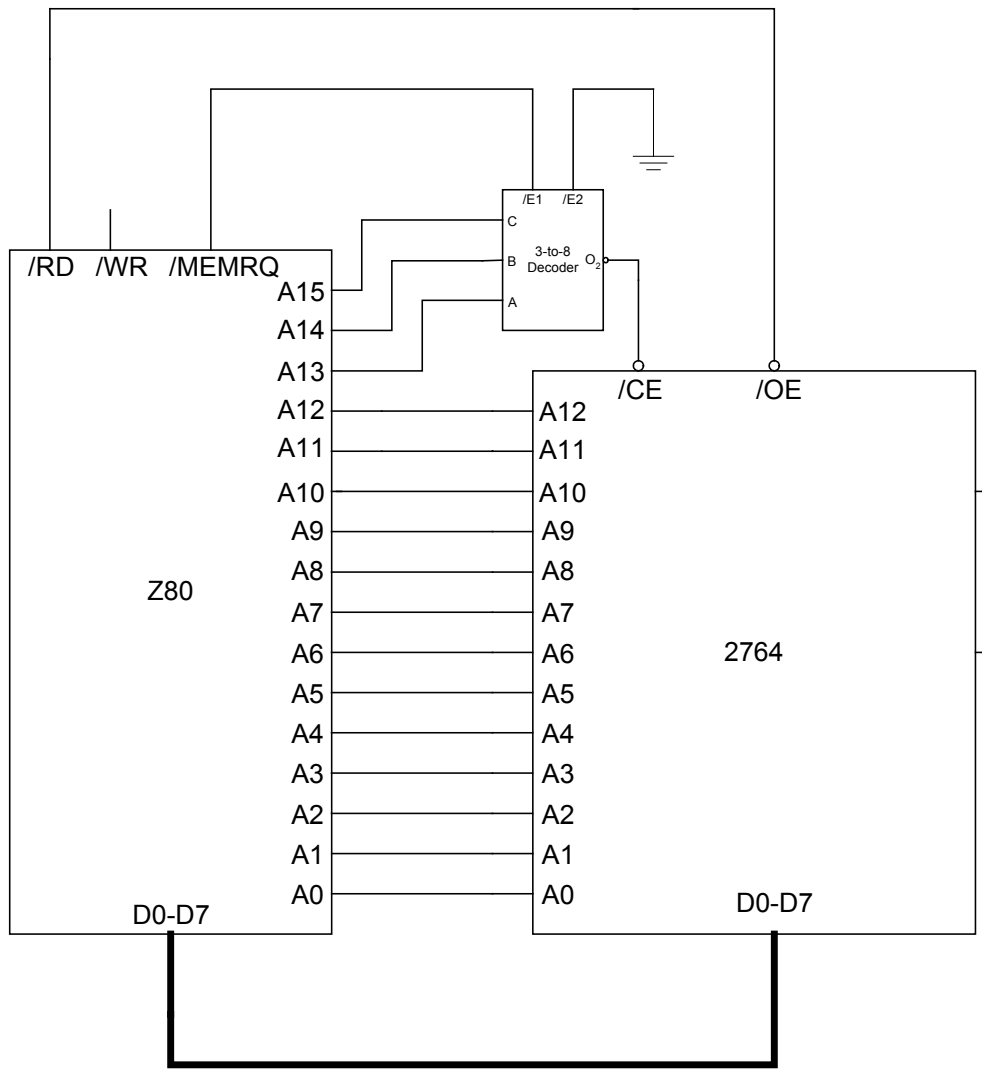
# Interfacing the Z80 with 2764 EPROM(8K x 8)



A15 A14 A13 A12 A11 A10 A9 A8 A7 A6 A5 A4 A3 A2 A1 A0


The memory range of the 2764 chip is

---


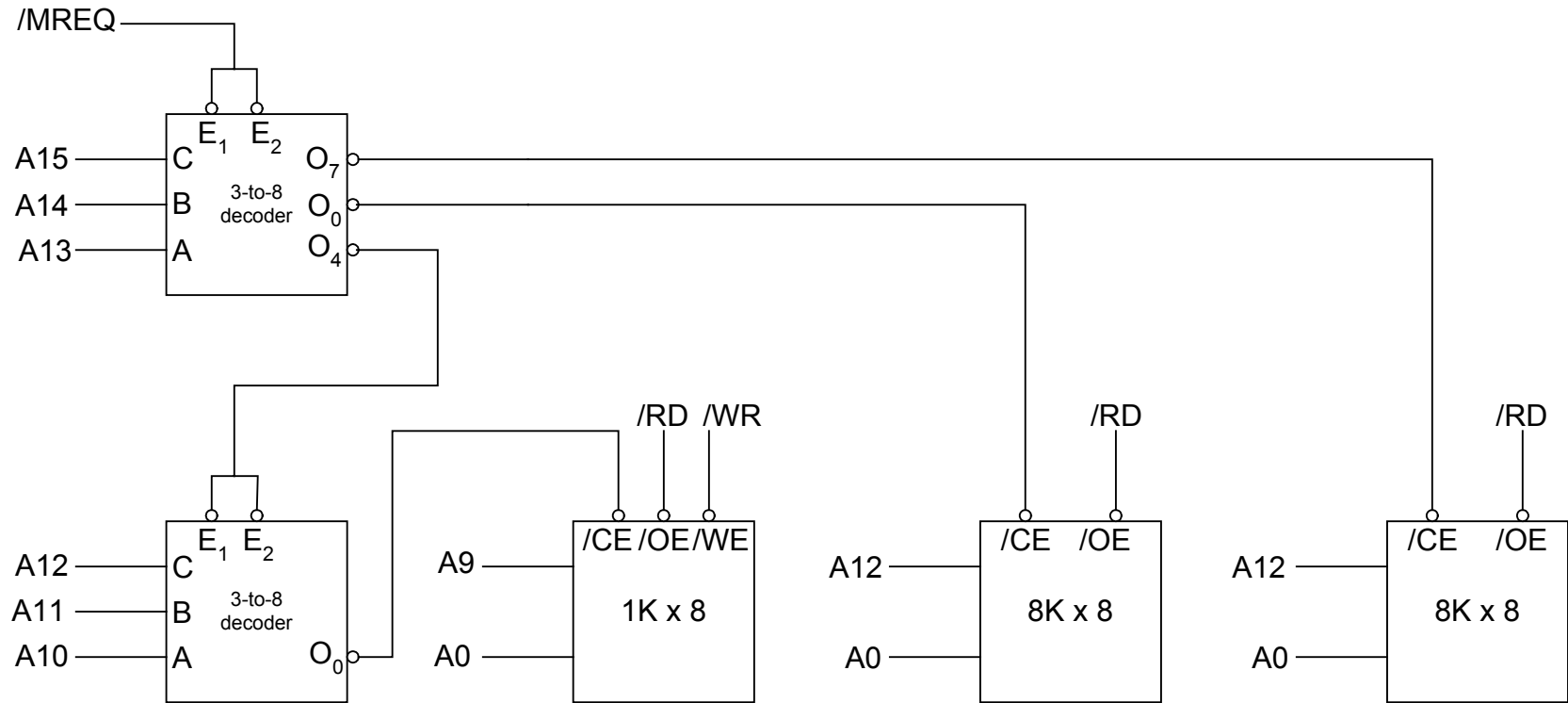
# Memory Map

- The Z80 has a 16-bit address bus which can access  $2^{16} = 2^6 \cdot 2^{10} = 65,536(64K)$  memory locations.
- Memory map(0000 to 0FFFFH) is a pictorial representation in which memory chips are located in the entire range of addresses.



# Memory Map Continued

