



Session5 Electronics1

Review OpAmp



Review Operational Amplifier

OP AMP is a differential amplifier

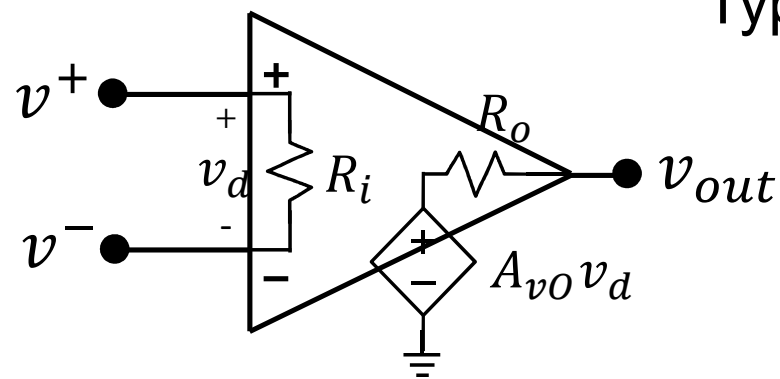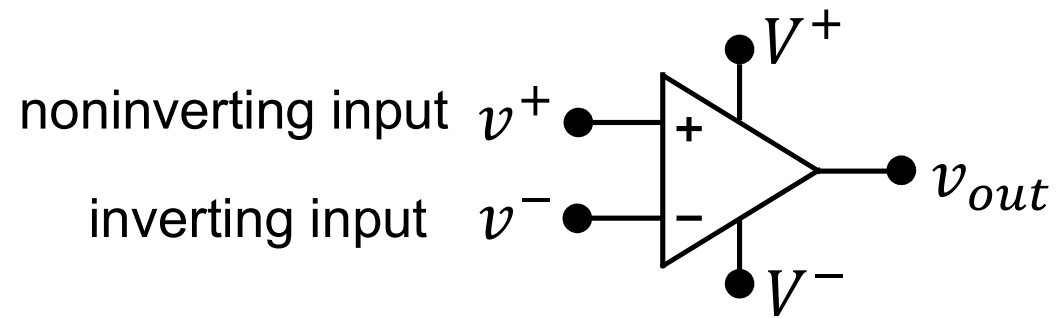


Typical values:

$R_i \sim 100 M\Omega$
 $R_o \sim 10 \Omega$
 $A_{v0} \sim 10^6$



ideal

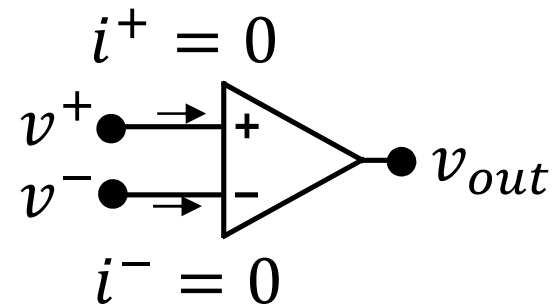$\rightarrow \infty$
 $\rightarrow 0$
 $\rightarrow \infty$





Regions: $\left\{ \begin{array}{l} \text{Linear: } v^- = v^+, v_0 = ?, \text{ when: } V^- < v_0 < V^+ \\ + \text{ Saturation : } v_0 = V^+, v^+, v^- = ?, \text{ when: } v^+ > v^- \\ - \text{ Saturation : } v_0 = V^-, v^+, v^- = ?, \text{ when: } v^+ < v^- \end{array} \right.$

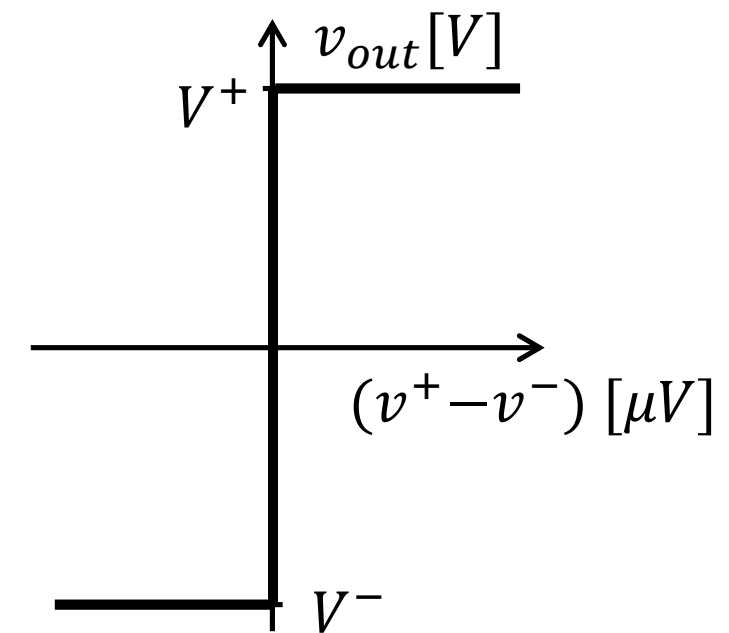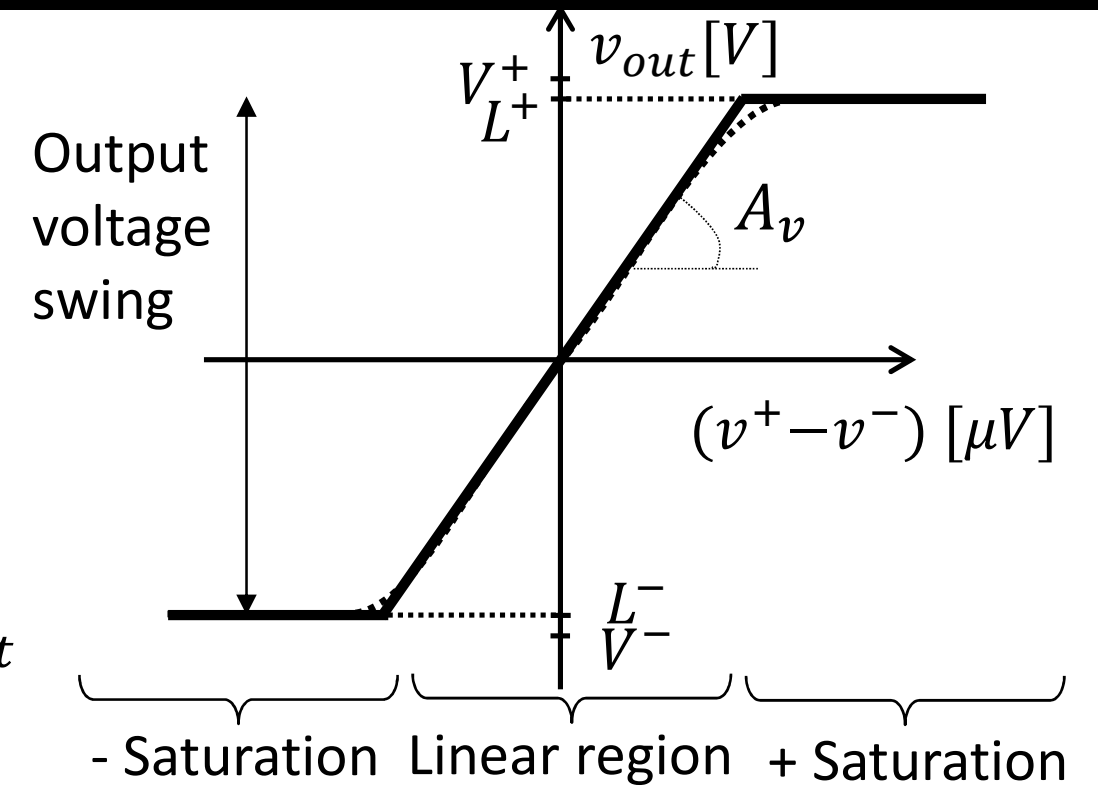Rules @ Linear: 1. $i^+ = i^- = 0$, 2. $v^- = v^+$



Noninverting OpAmp

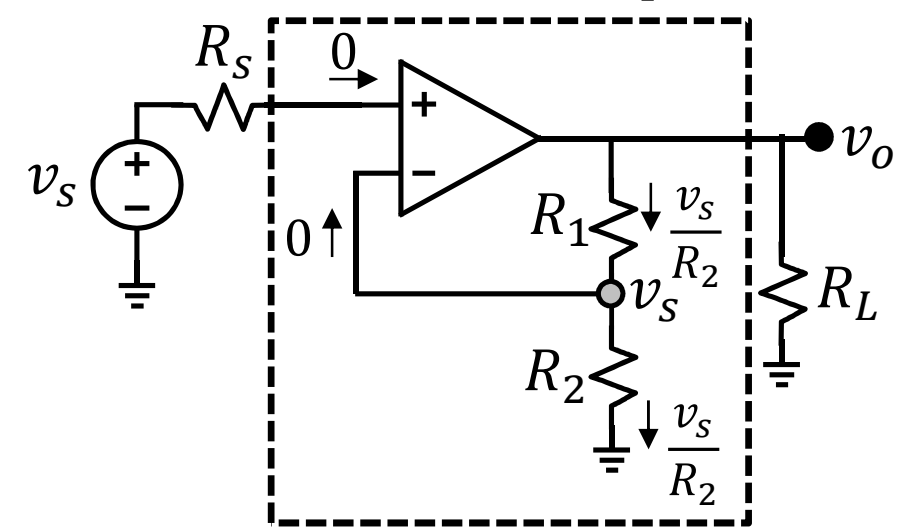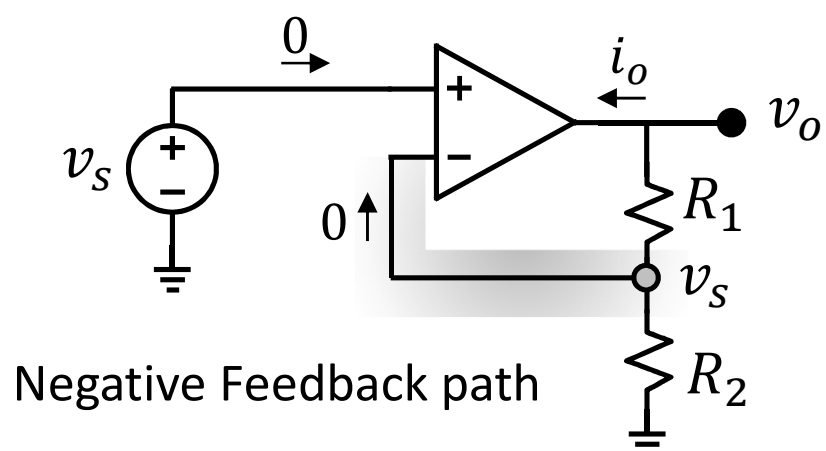1. $i^+ = i^- = 0$, @ Linear; 2. $v^- = v^+$





$$K = 1 + \frac{R_1}{R_2}$$

$$\frac{v_o}{v_s} = \frac{K}{\frac{K}{A_{vo}} \left[1 + \frac{R_o}{R_1 + R_2} \right] + 1}$$

$$\text{KCL: } \frac{v_o - v_s}{R_1} + \frac{0 - v_s}{R_2} = 0$$

$$\frac{v_o}{v_s} = A_v = 1 + \frac{R_1}{R_2}$$

$$i_o = -v_s/R_2$$

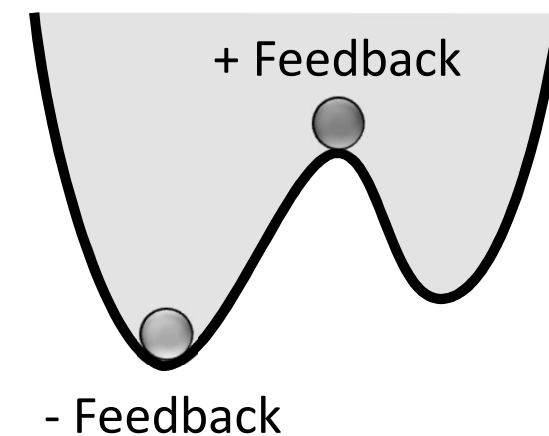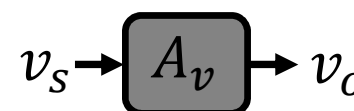


$$v_o = v_s + \frac{R_1 v_s}{R_2}$$

$$i_o = -\frac{v_s}{R_2} - \frac{v_o}{R_L}$$

$$\frac{v_o - v^-}{R_1} + \frac{0 - v^-}{R_2} = 0$$
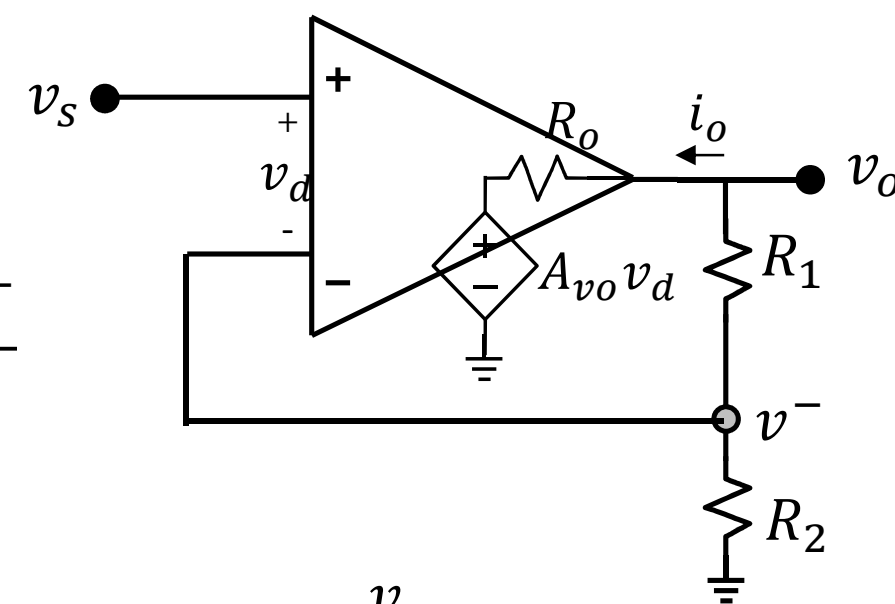
$$\frac{A_{vo}(v_s - v^-) - v_o}{R_o} = \frac{v_o - v^-}{R_1}$$






$$R_o \ll R_1 + R_2 \rightarrow R_o \sim 0 \rightarrow \frac{v_o}{v_s} = \frac{K}{\frac{K}{A_{vo}} + 1}$$



$$A_{vo} \gg K \rightarrow \frac{v_o}{v_s} = K$$




Noninverting OpAmp / Buffer

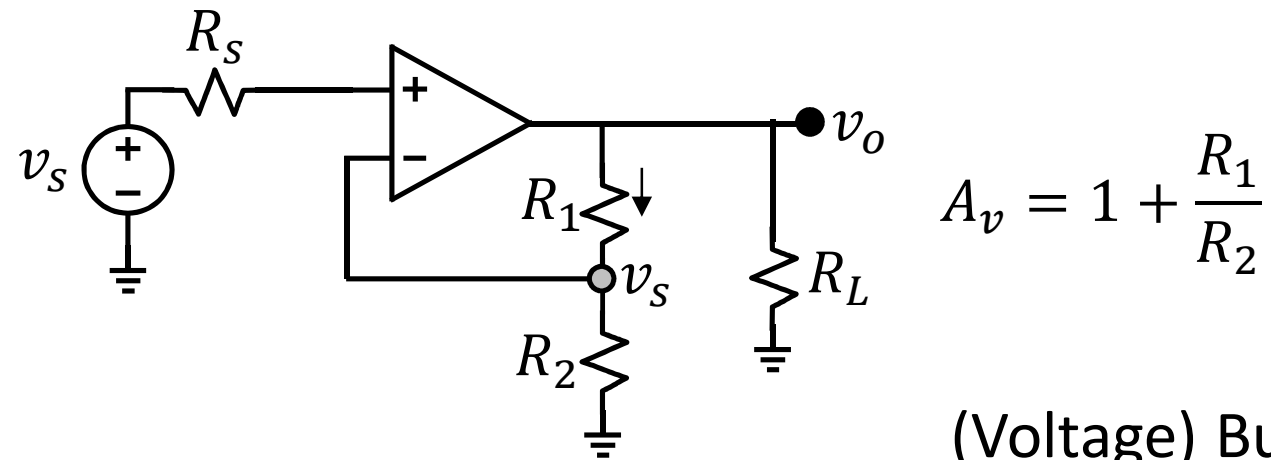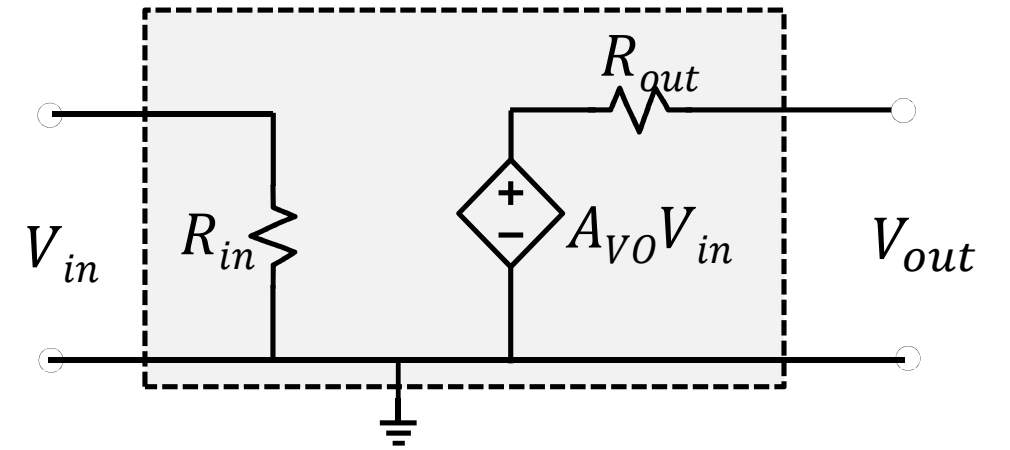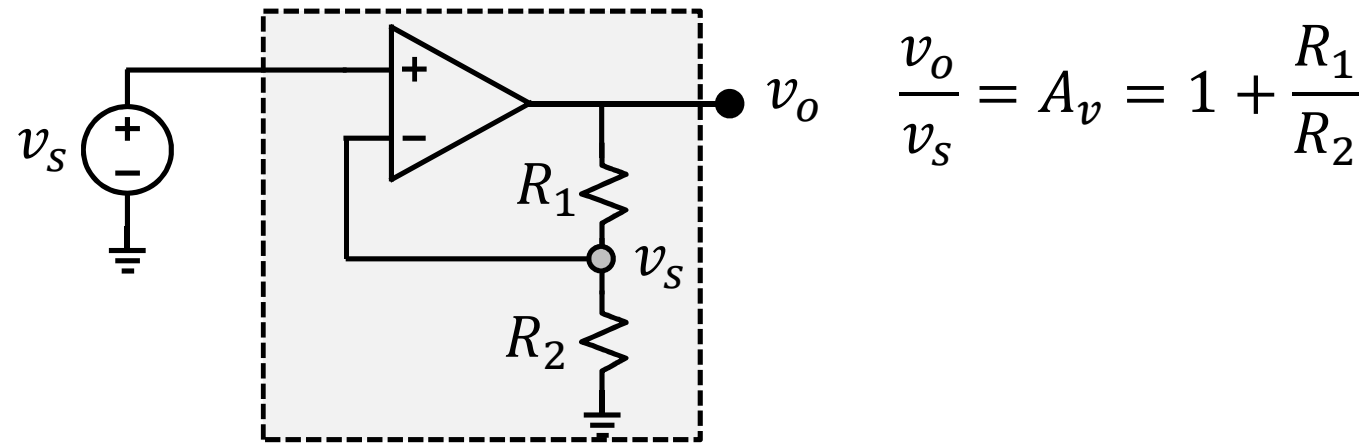

(Voltage) Buffer
Voltage follower

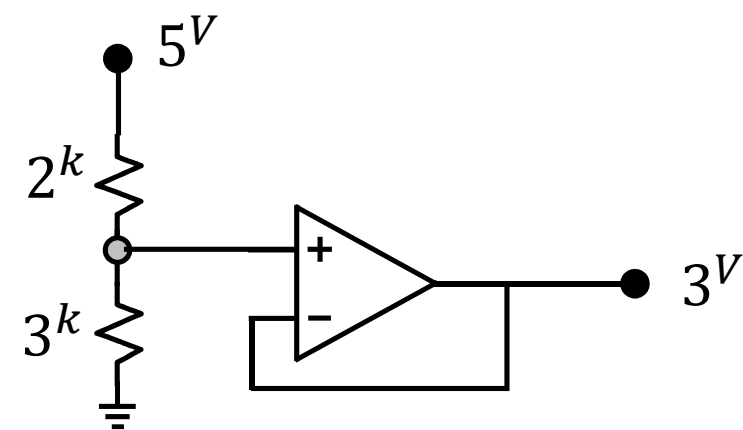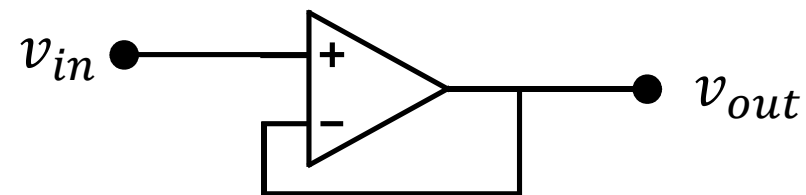


Inverting OpAmp

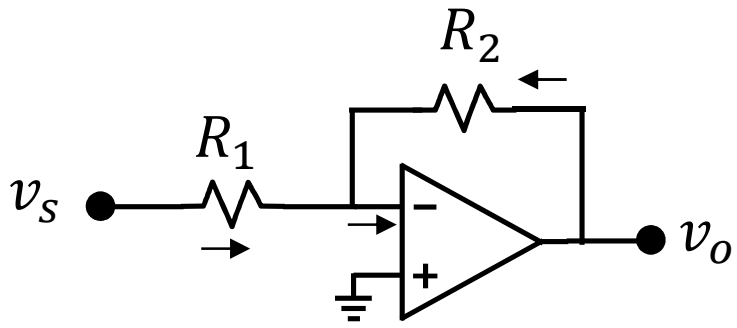

KCL: $\frac{v_s - v^-}{R_1} + \frac{v_o - v^-}{R_2} = i^-$

Virtual ground $v^- = 0$
 $i^- = 0$


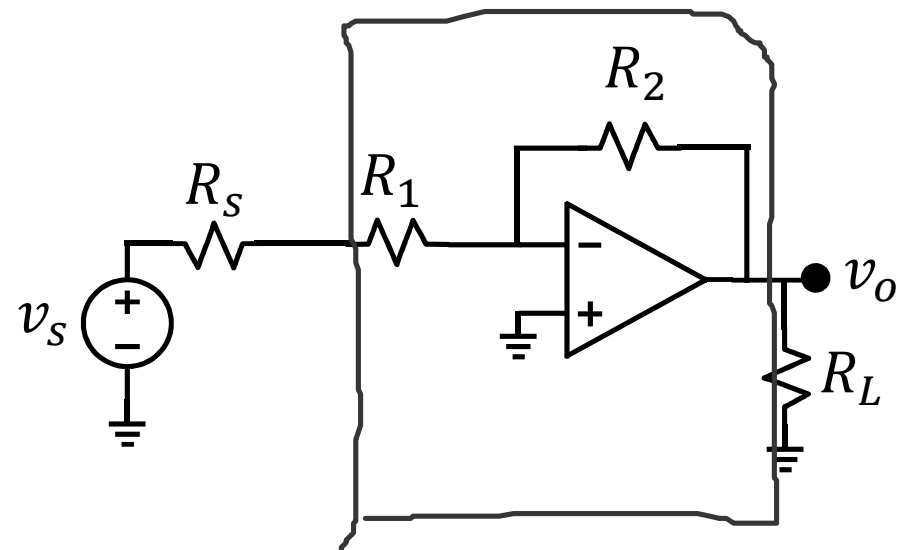
$\frac{v_o}{v_s} = A_V = -\frac{R_2}{R_1}$




$\frac{v_o}{v_s} = -\frac{R_2}{R_1 + R_s}$



IV VI

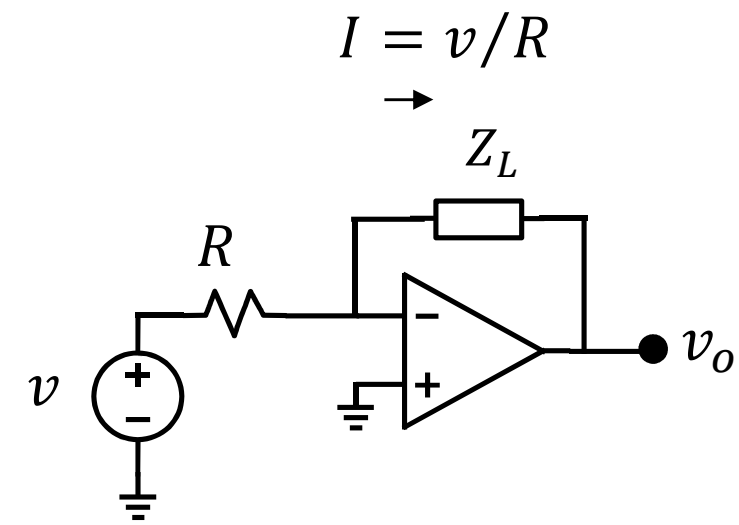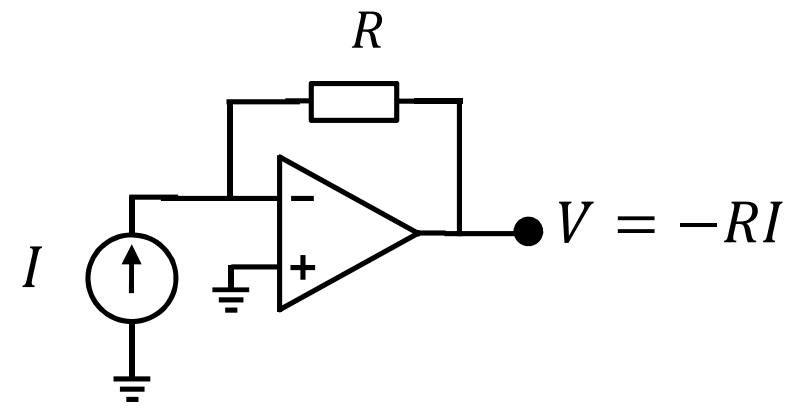



summing amplifier (adder)

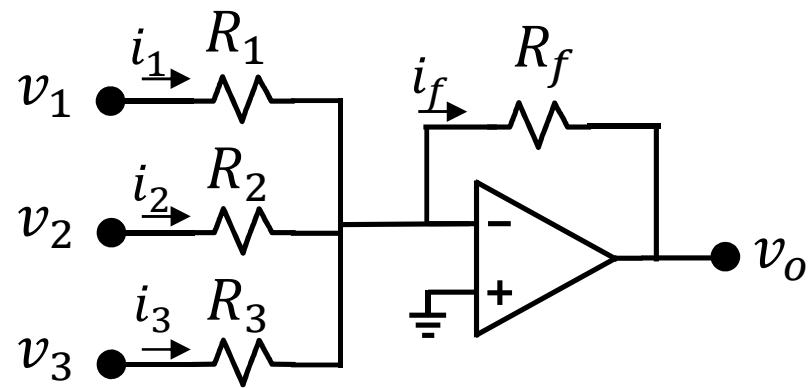

$$\text{KCL: } i_1 + i_2 + i_3 = i_f$$

$$\frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3} = \frac{-v_o}{R_f}$$
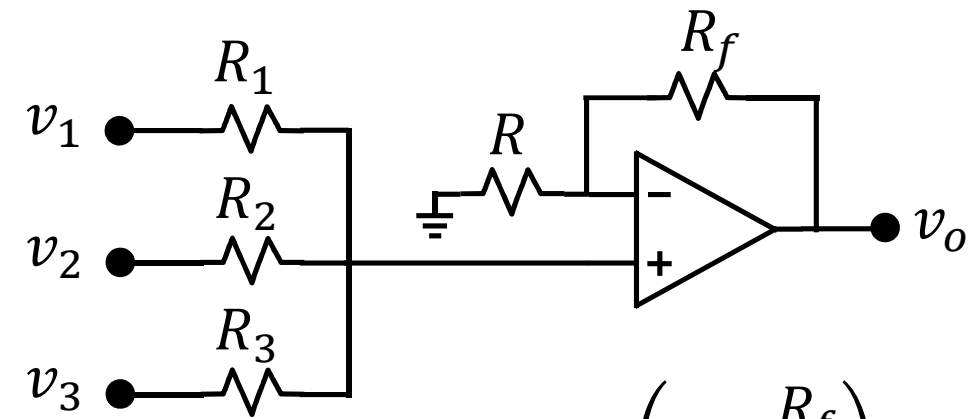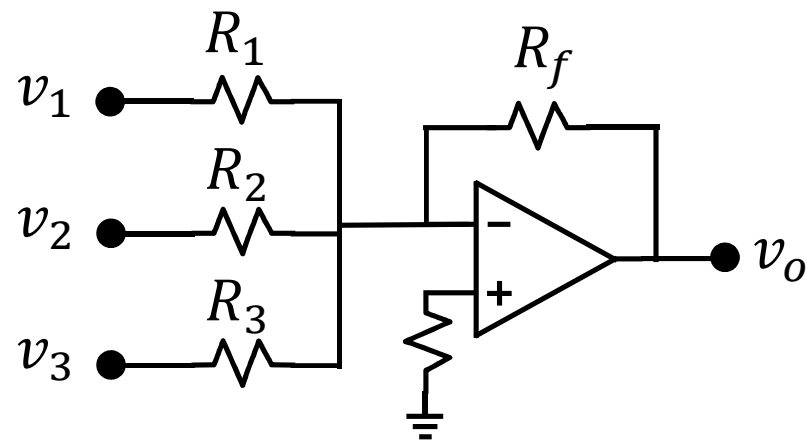
$$v_o = -R_f \left(\frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3} \right)$$




$$v_o = v^+ \left(1 + \frac{R_f}{R} \right)$$

$$\frac{v_1 - v^+}{R_1} + \frac{v_2 - v^+}{R_2} + \frac{v_3 - v^+}{R_3} = 0$$

$$v_o = (R_1 \parallel R_2 \parallel R_3) \left(1 + \frac{R_f}{R} \right) \left(\frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3} \right)$$





Differential Amplifier

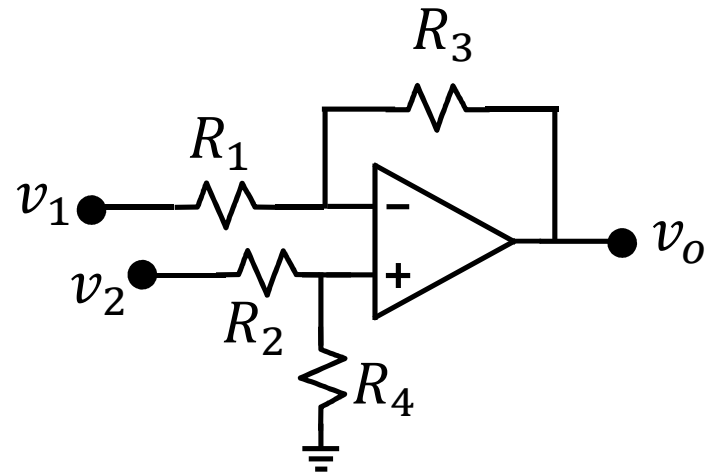

$$v_o = -\left(\frac{R_3}{R_1}\right)v_1 + \left(\frac{R_4}{R_2 + R_4}\right)\left(1 + \frac{R_3}{R_1}\right)v_2$$

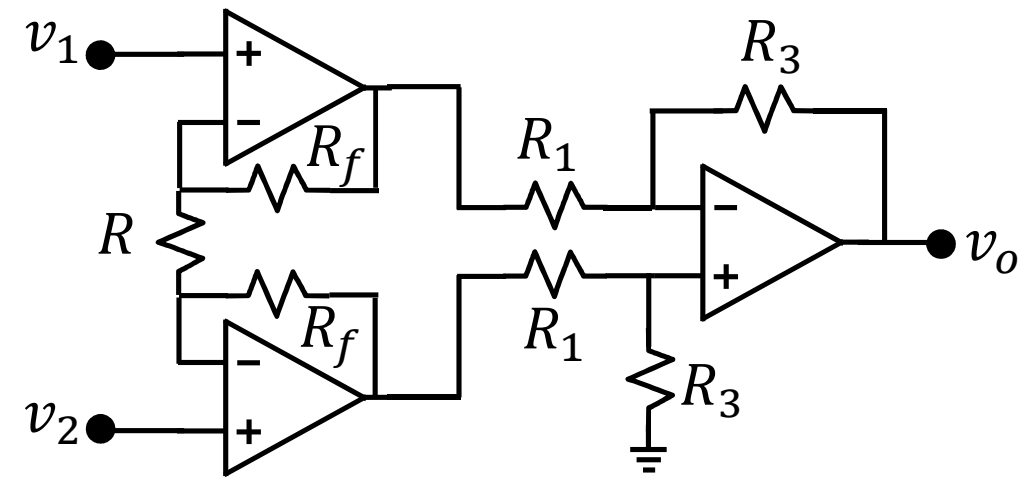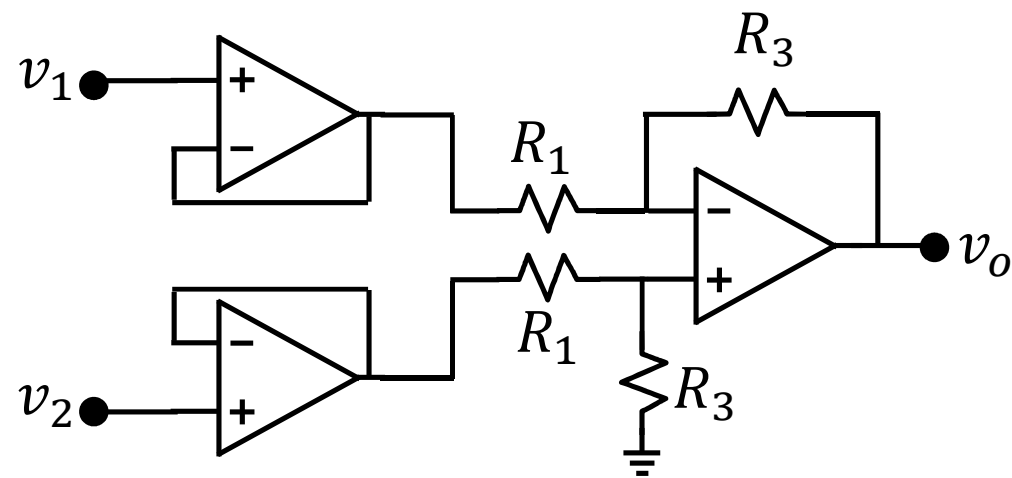
$$R_1 = R_2, R_3 = R_4 \rightarrow v_o = \left(\frac{R_3}{R_1}\right)(v_2 - v_1)$$



$$v_o = \left(\frac{R_3}{R_1}\right)\left(1 + \frac{2R_f}{R}\right)(v_2 - v_1)$$



Integrator / Differentiator Amplifier


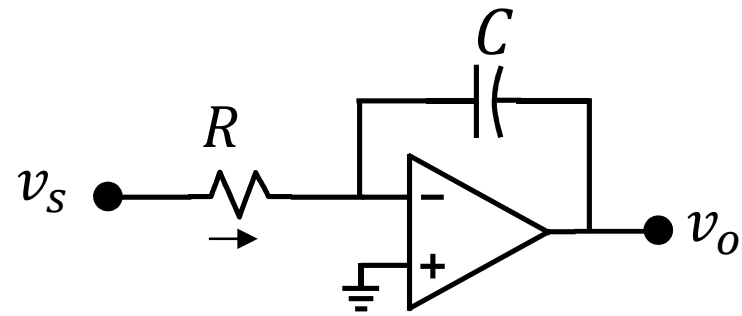


$$i = \frac{v_s}{R}$$

$$v_o = -v_c$$

$$v_c = v(0) + \frac{1}{C} \int_0^t i(\tau) d\tau$$
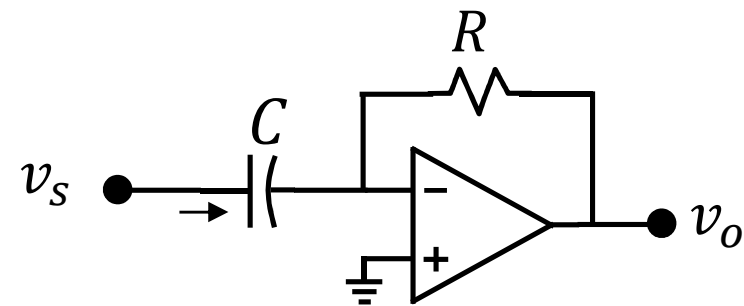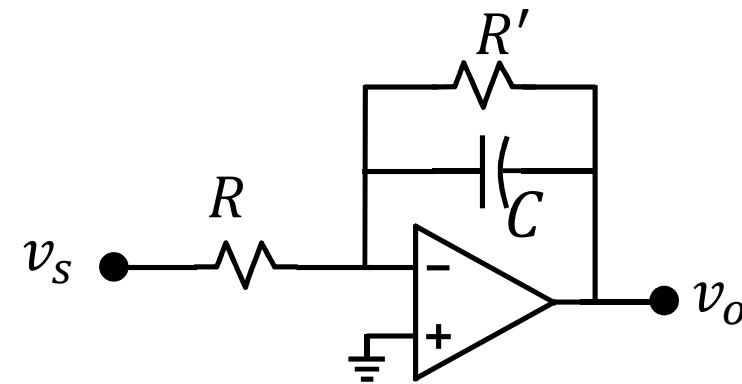
$$v_o = -v(0) - \frac{1}{RC} \int_0^t v_s(\tau) d\tau$$




$$i = C \frac{dv_s}{dt}$$

$$v_o = -RC \frac{dv_s}{dt}$$




Logarithmic / Exponential Amplifier

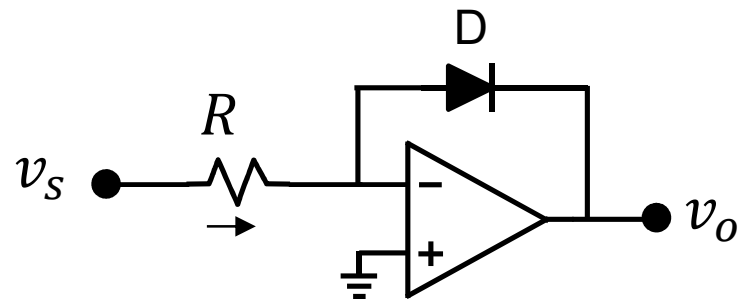

$$i = \frac{v_s}{R}$$

$$i_D = I_S (e^{v_D/V_T} - 1) \cong I_S e^{v_D/V_{Th}}$$
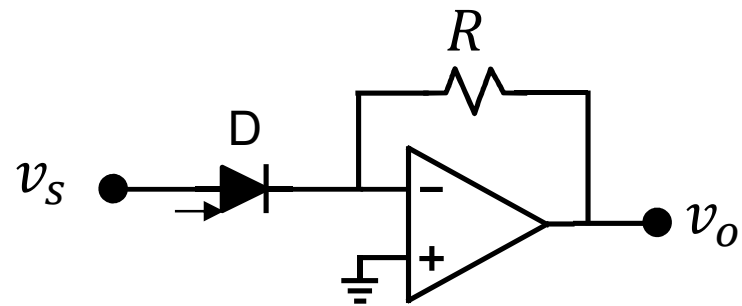
$$v_D = V_{Th} \ln \left(\frac{i_D}{I_S} \right) = V_{Th} \ln \left(\frac{v_s}{RI_S} \right)$$



$$i_D = I_S (e^{v_D/V_{Th}} - 1) \cong I_S e^{v_s/V_{Th}}$$

$$v_o = -Ri_D = -RI_S e^{v_s/V_{Th}}$$

So what?



end

