

Session6 Electronics1



Diodes




Non-Linear Circuit – Diode!






AC vs. DC

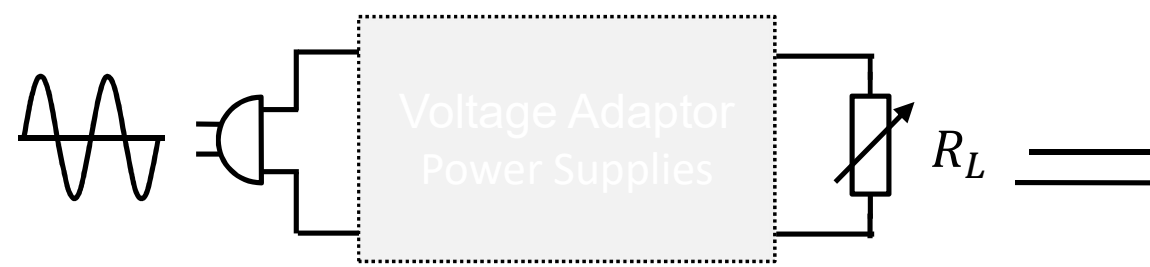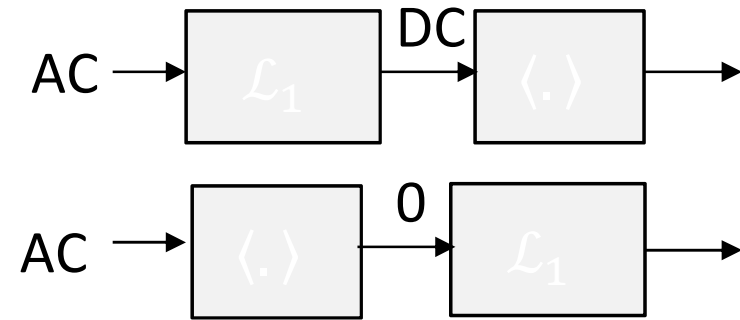


Power Supplies
(Voltage Regulators)

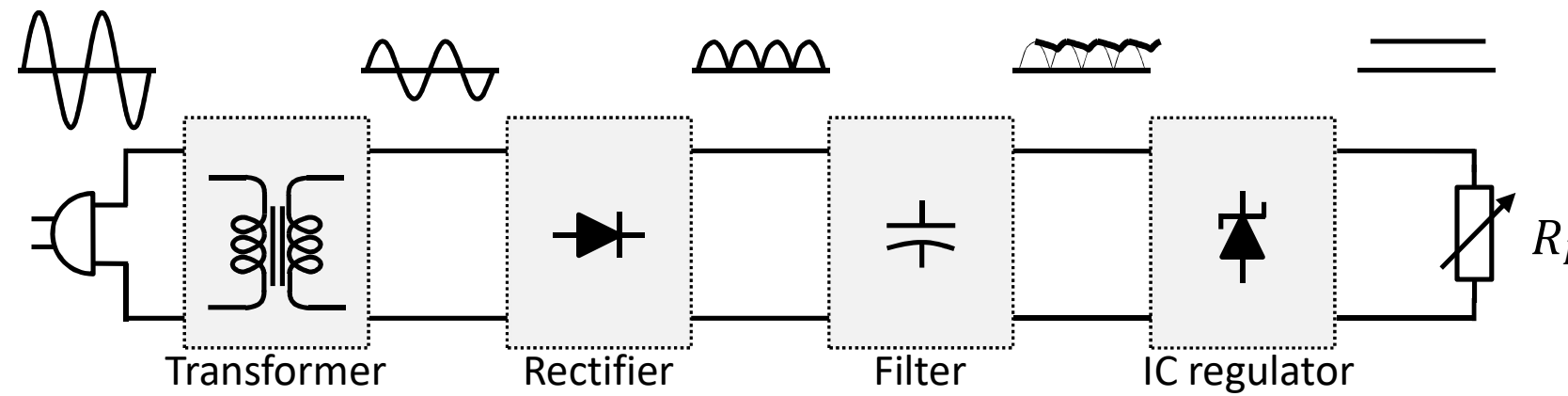


crystal radio
راديو گوشى

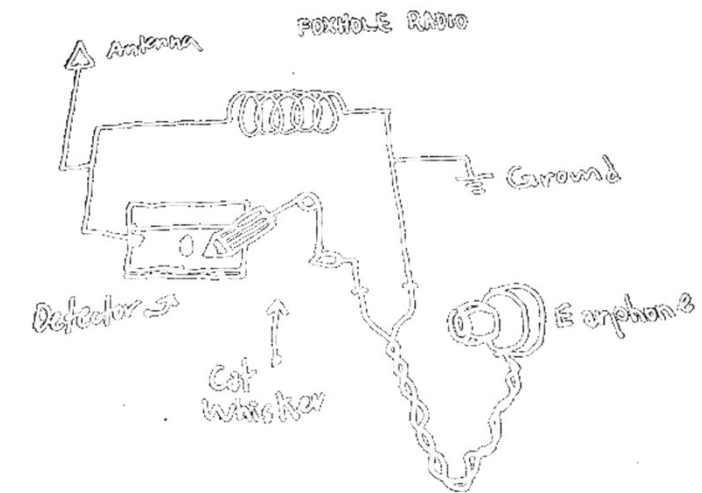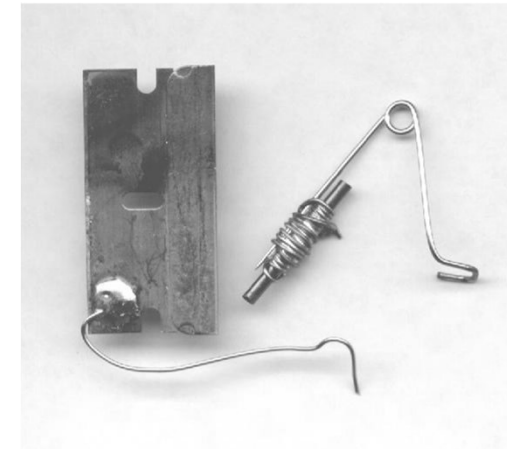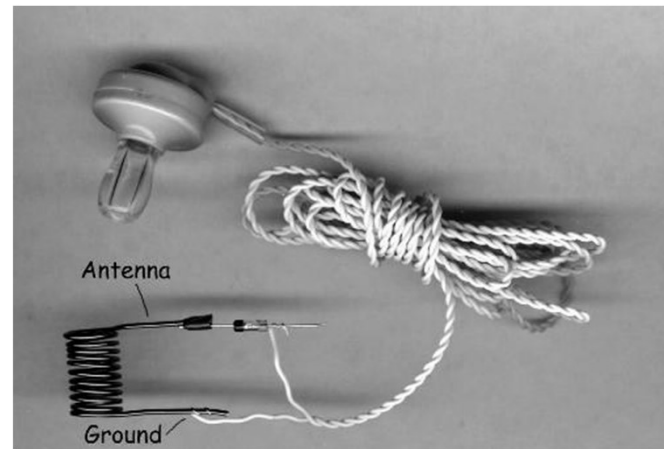

Resistance

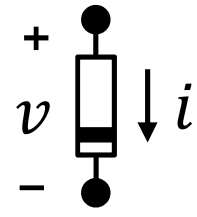

Definition:

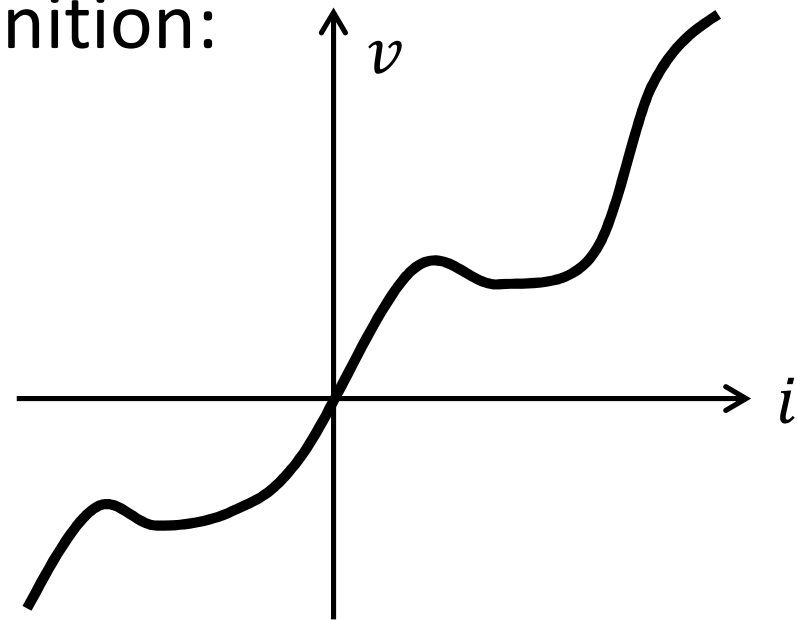

$$i(t) \equiv \hat{G}(v(t))$$

conductance


- TI: Time Independent
- TD: Time Dependent
- L: Linear
- NL: Non-linear

NLTI: Diode

$$i(t) = I_s \left(e^{qv(t)/nkT} - 1 \right)$$

$$V_T = \frac{kT}{q} \Big|_{300^\circ K} = 26mV$$

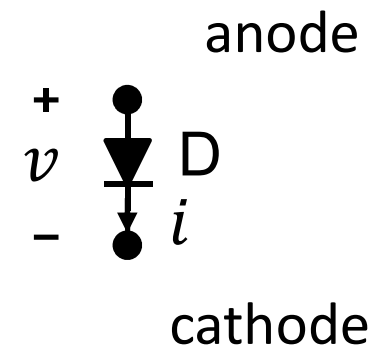
$$i(t) = I_s \left(e^{v(t)/nV_T} - 1 \right)$$



$$n = 1 \dots 2$$



Resistance - NLTI

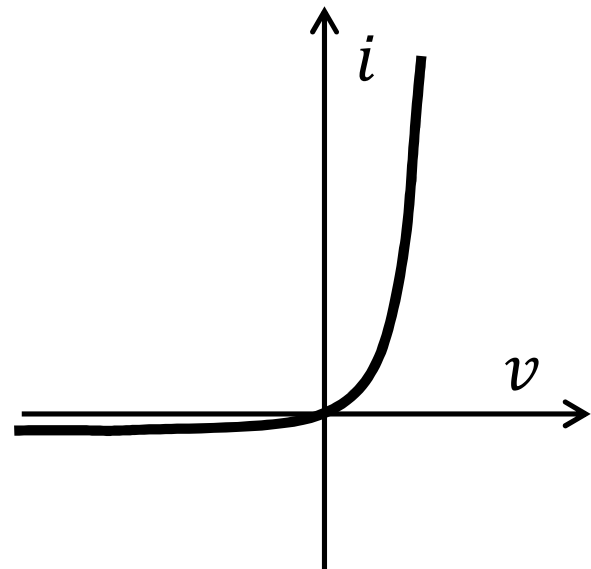


NLTI: Diode


$$i(t) = I_s \left(e^{qv(t)/nkT} - 1 \right)$$

$$V_T = \frac{kT}{q} \Big|_{300^\circ K} = 26mV$$

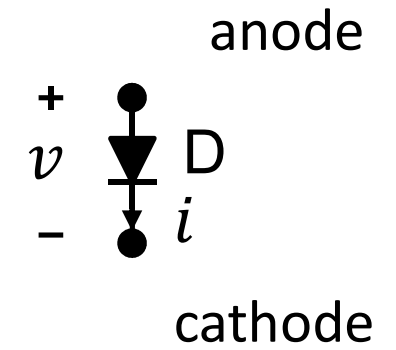
$$i(t) = I_s \left(e^{v(t)/nV_T} - 1 \right) \quad n = 1 \dots 2$$




voltage controlled

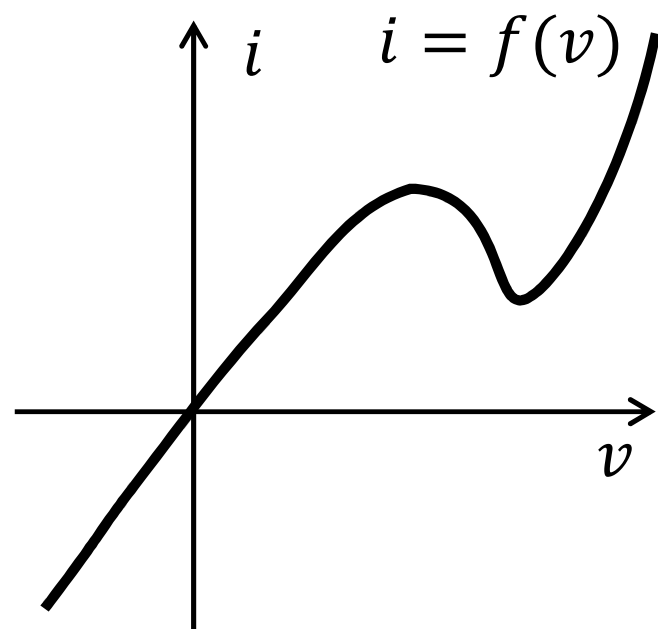


current controlled

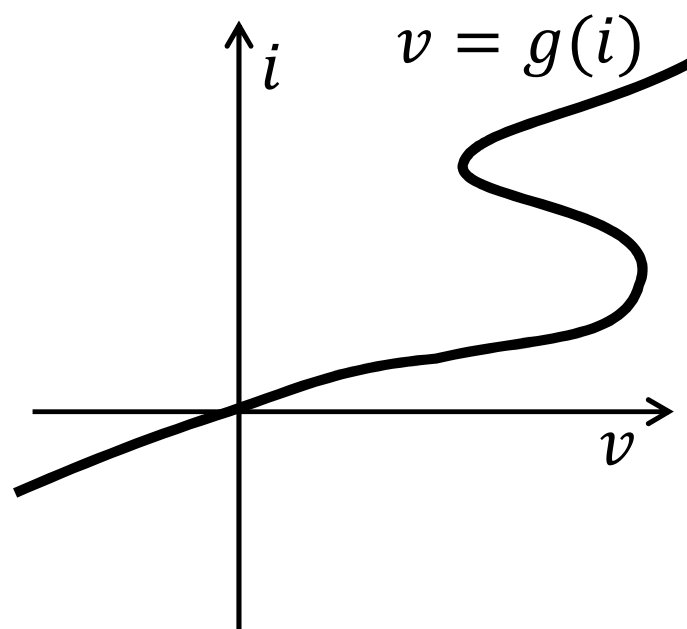

both

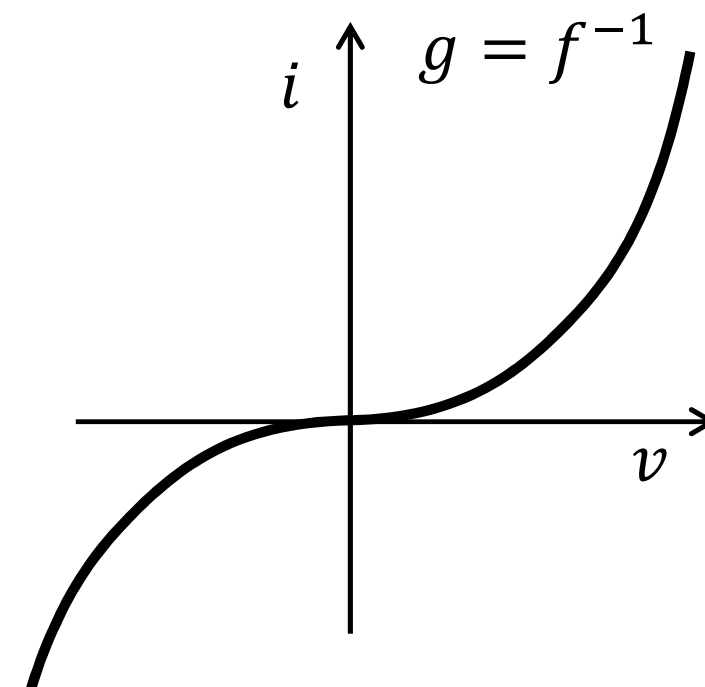


Diode – Large Signal

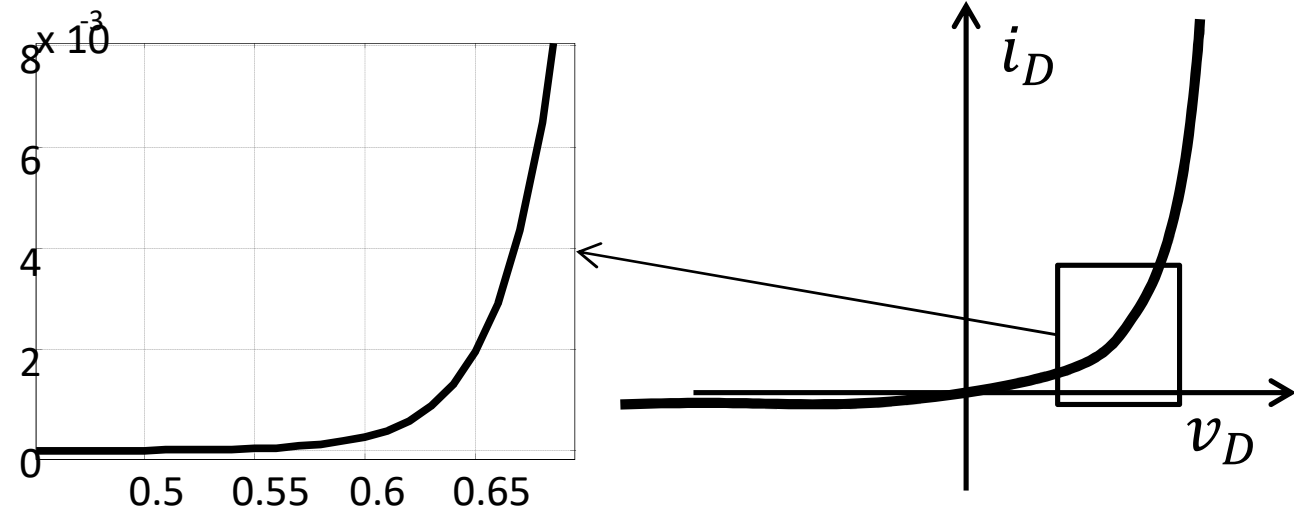



NLTI: Diode

$$i_D = I_S \left(e^{qv_D/nkT} - 1 \right)$$

$$V_T = \frac{kT}{q} \Big|_{300^\circ K} = 26mV$$

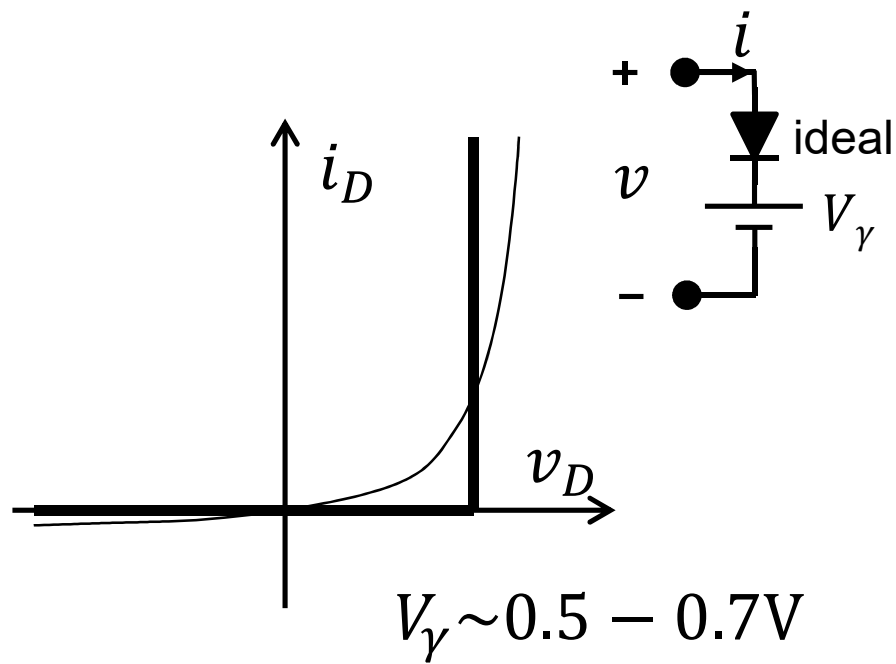

$V_{D,on}$

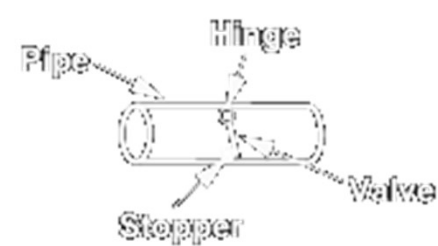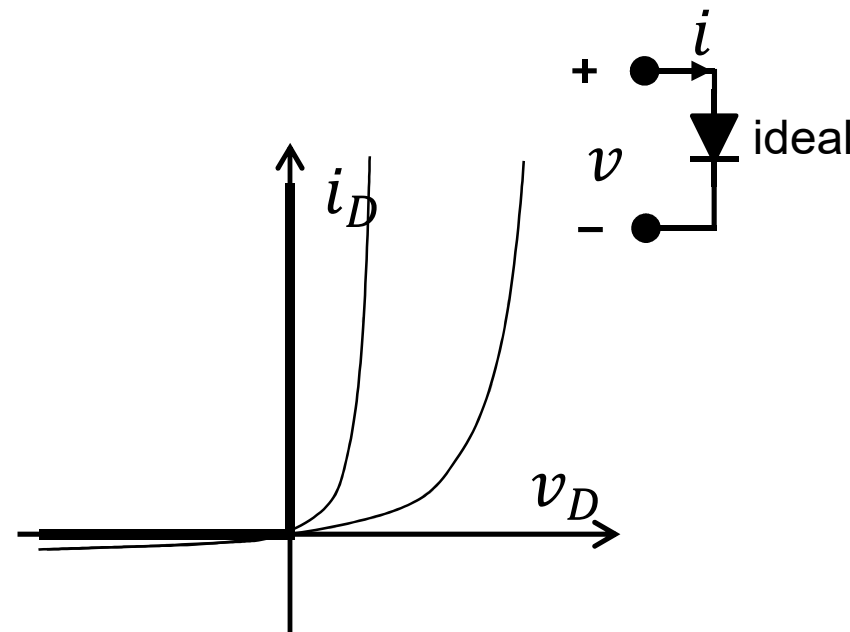

Forward Bias




Reverse Bias




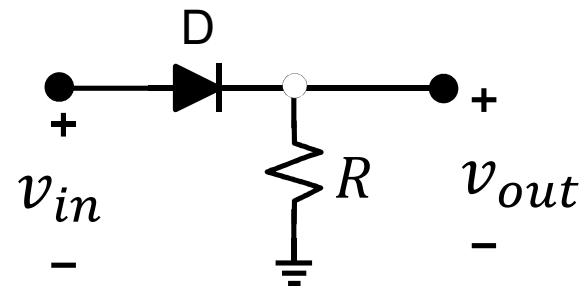Example 01

Find $v_{in} - v_{out}$ and $i_{in} - v_{in}$ assume $V_{D.on} = 0, 0.7V$



1: (F) If $i_D > 0$

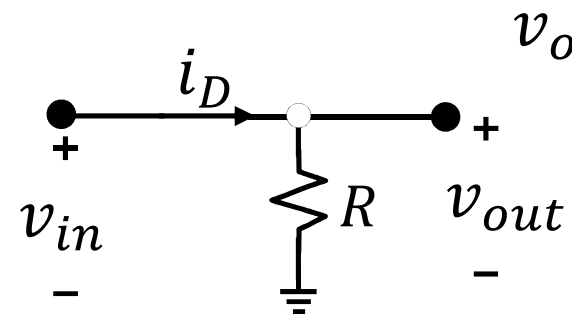

$$v_{out} = v_{in}$$


condition $i_D > 0$

$$\rightarrow i_D = v_{out}/R > 0 \rightarrow v_{out} > 0$$

$$v_{in} > 0$$

$$i_{in} = i_D = v_{in}/R$$

2: (R) If $v_D < 0$



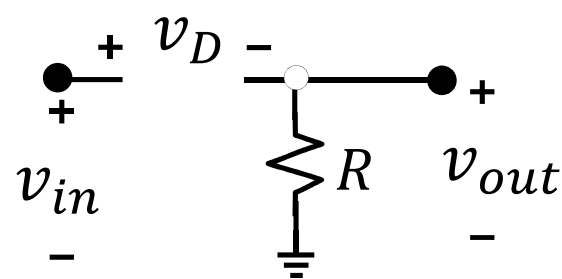


$$v_{out} = 0$$




condition $v_D < 0$

$$\rightarrow v_{in} - v_{out} < 0 \rightarrow v_{in} < 0$$

$$i_{in} = 0$$

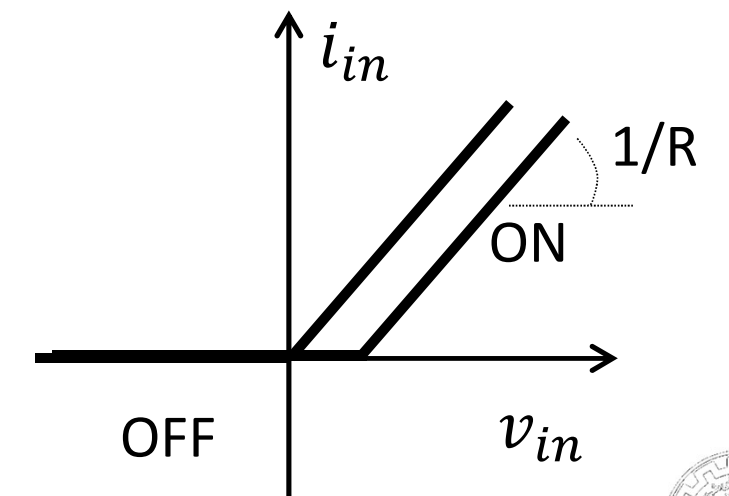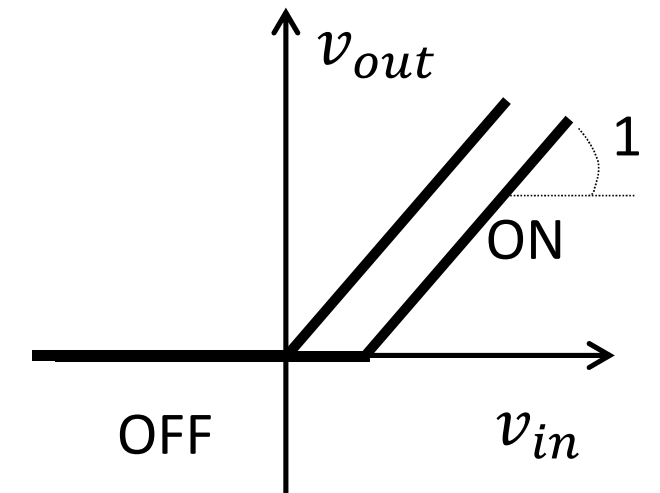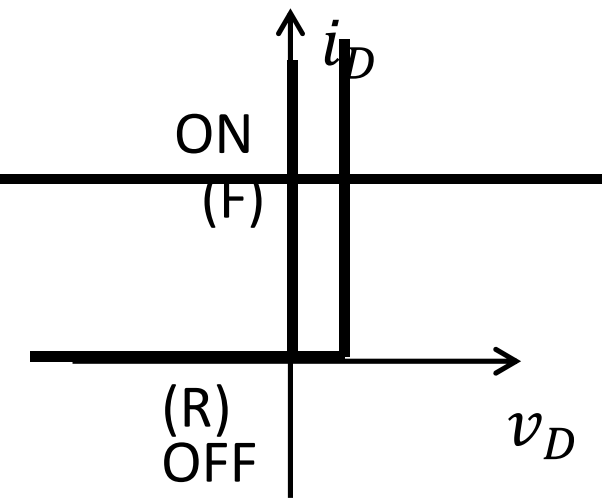




Example 01 - Rectifier

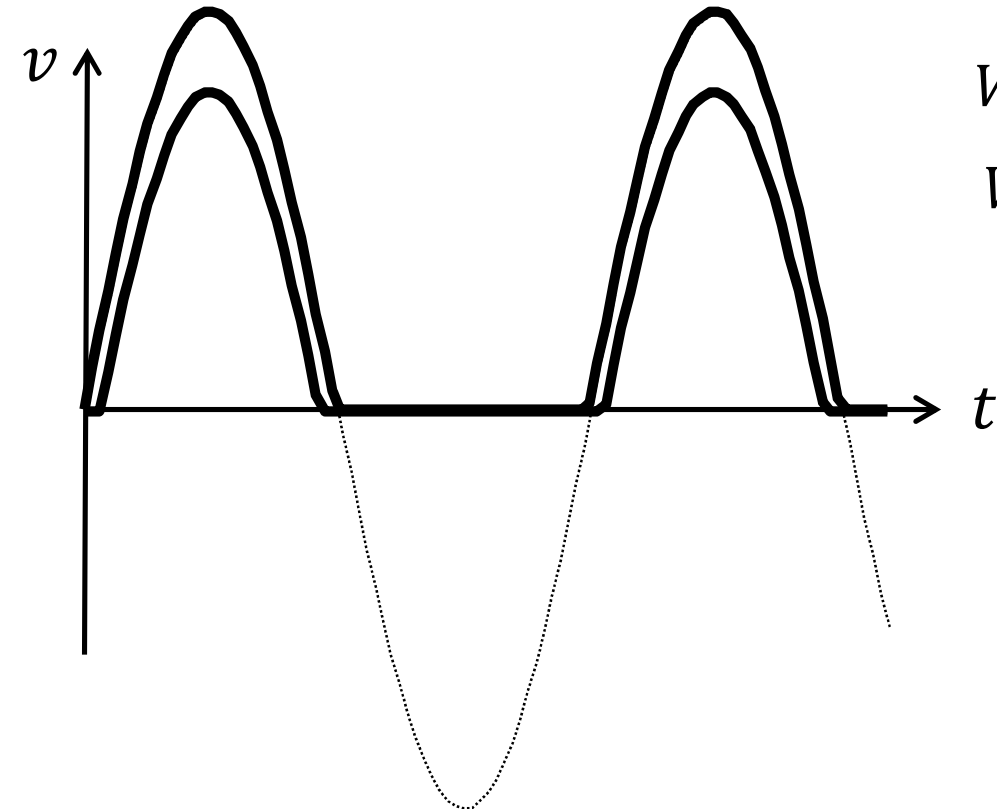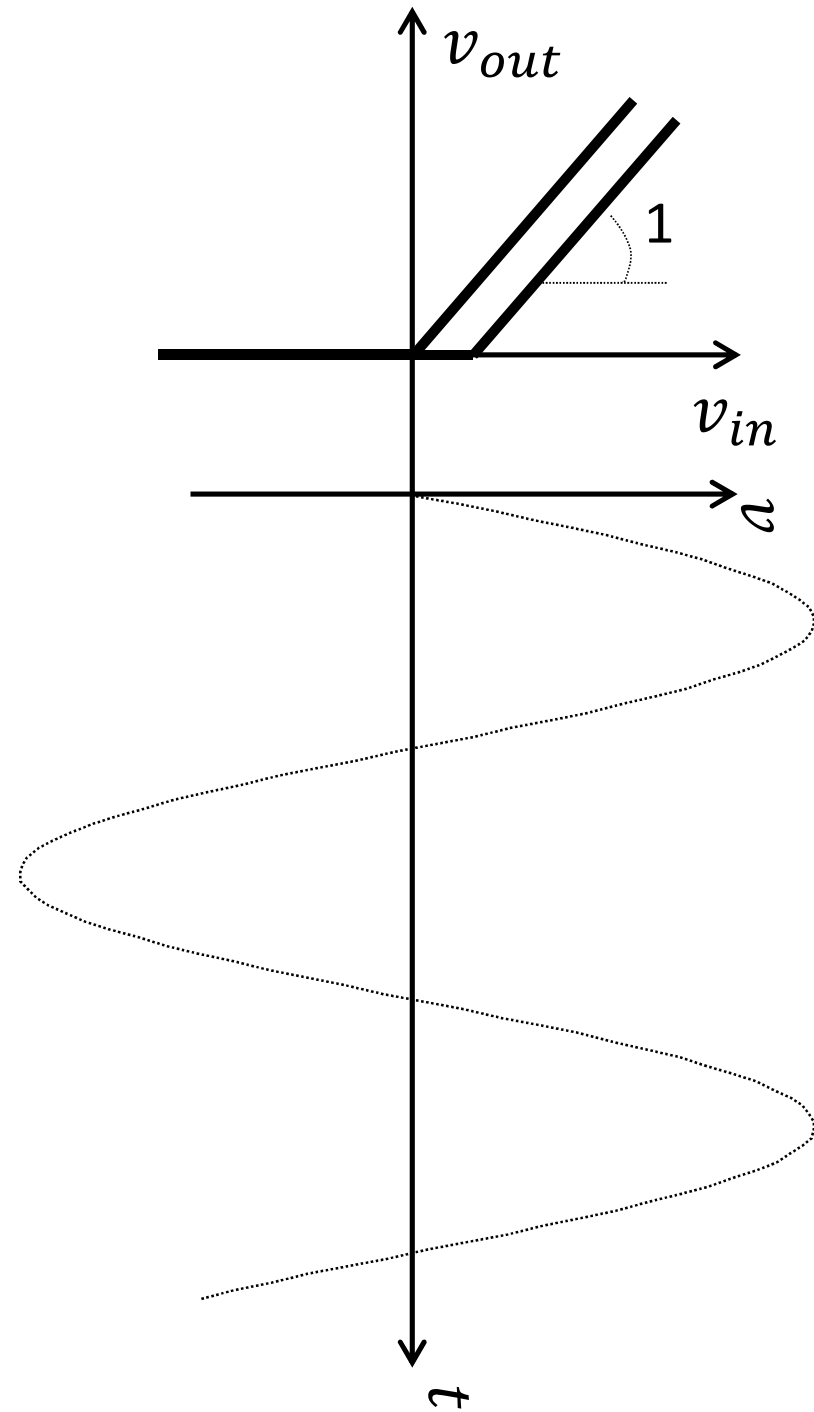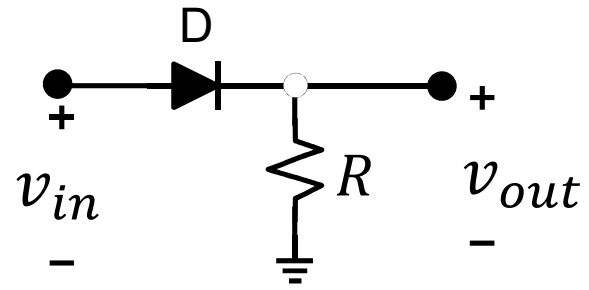





$$V_{D.on} = 0$$
$$V_{D.on} = 0.7V$$






Example 01

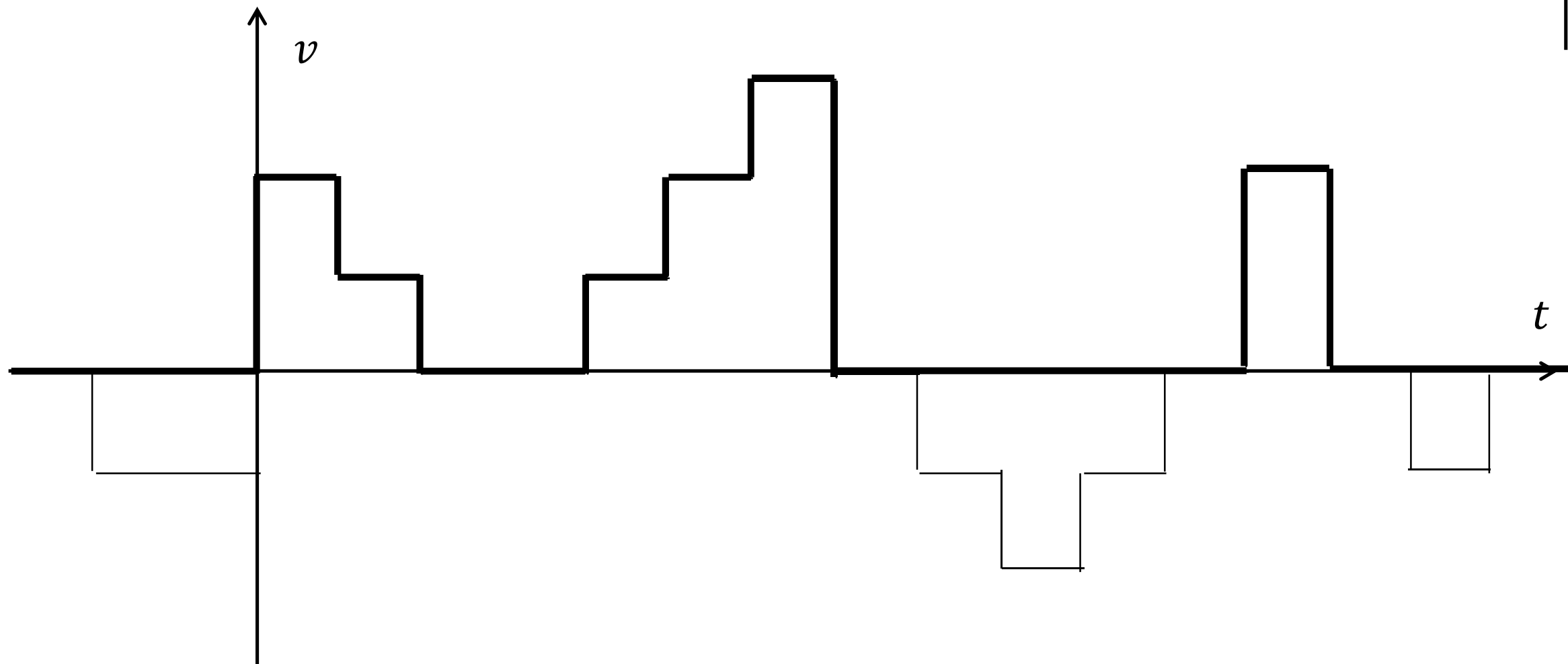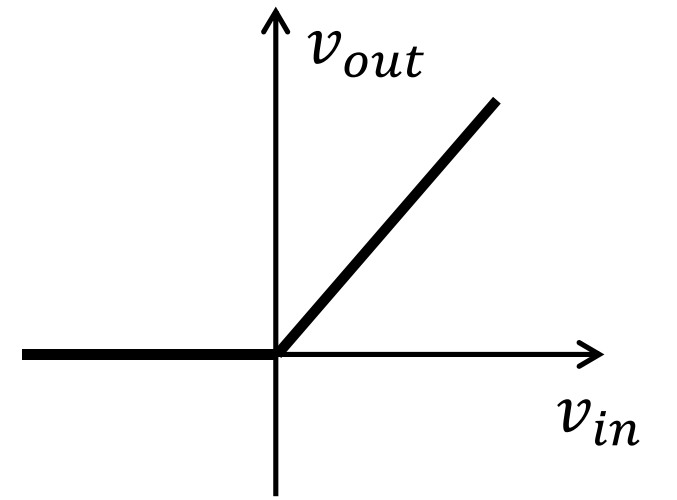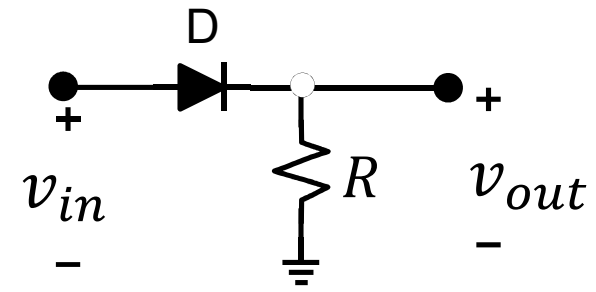



Example 01

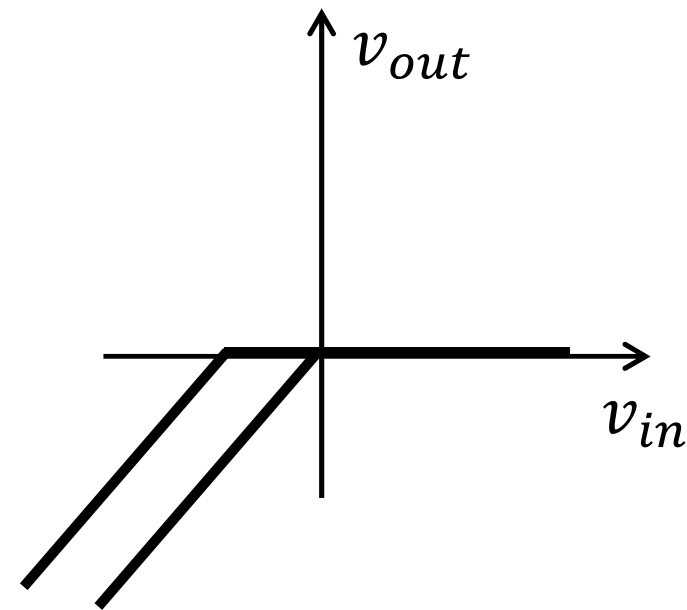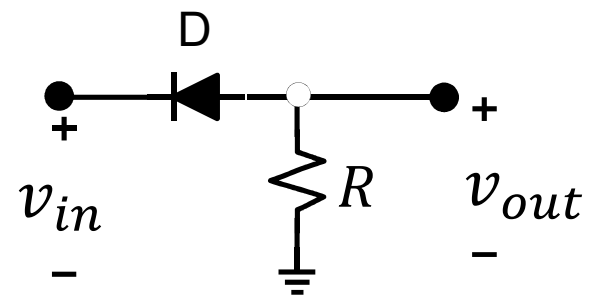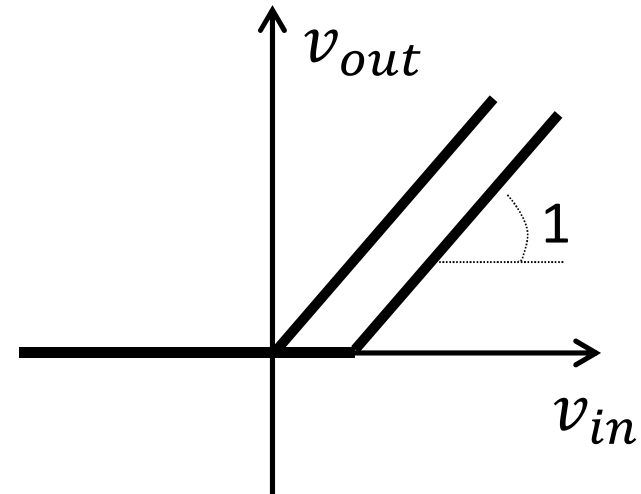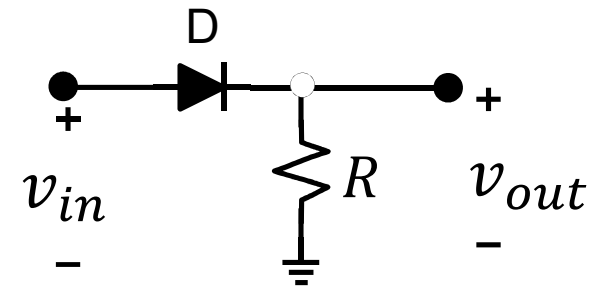


Example 02

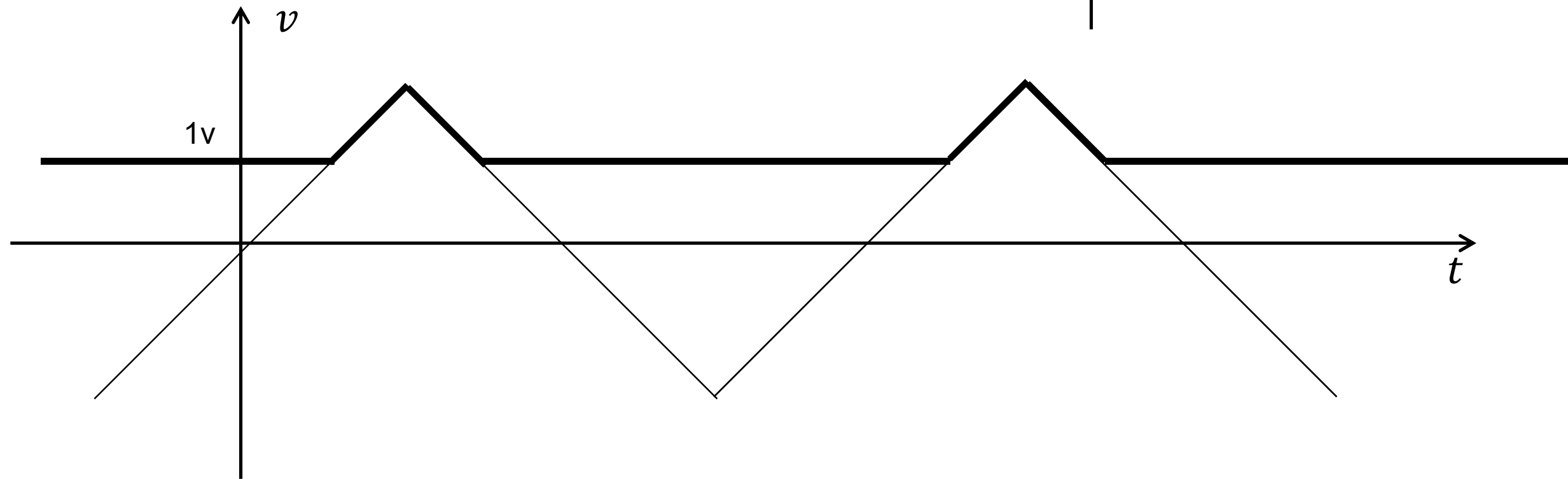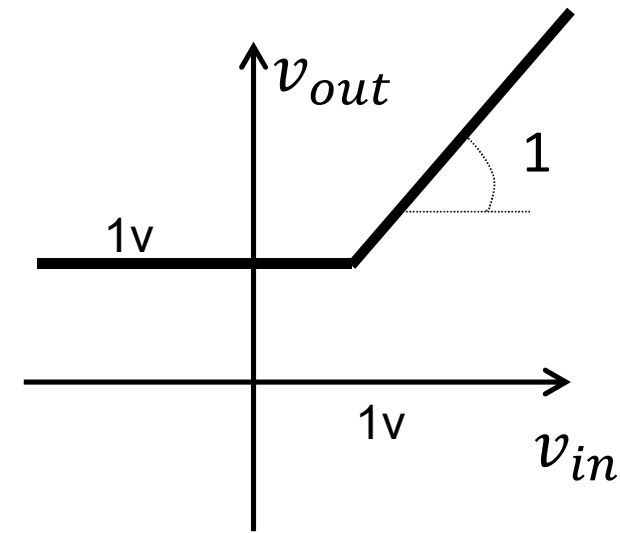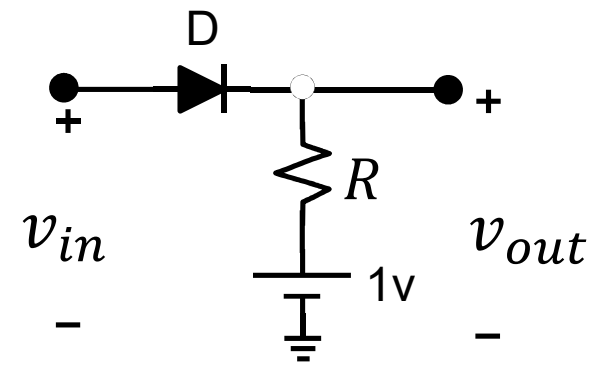


Example 03

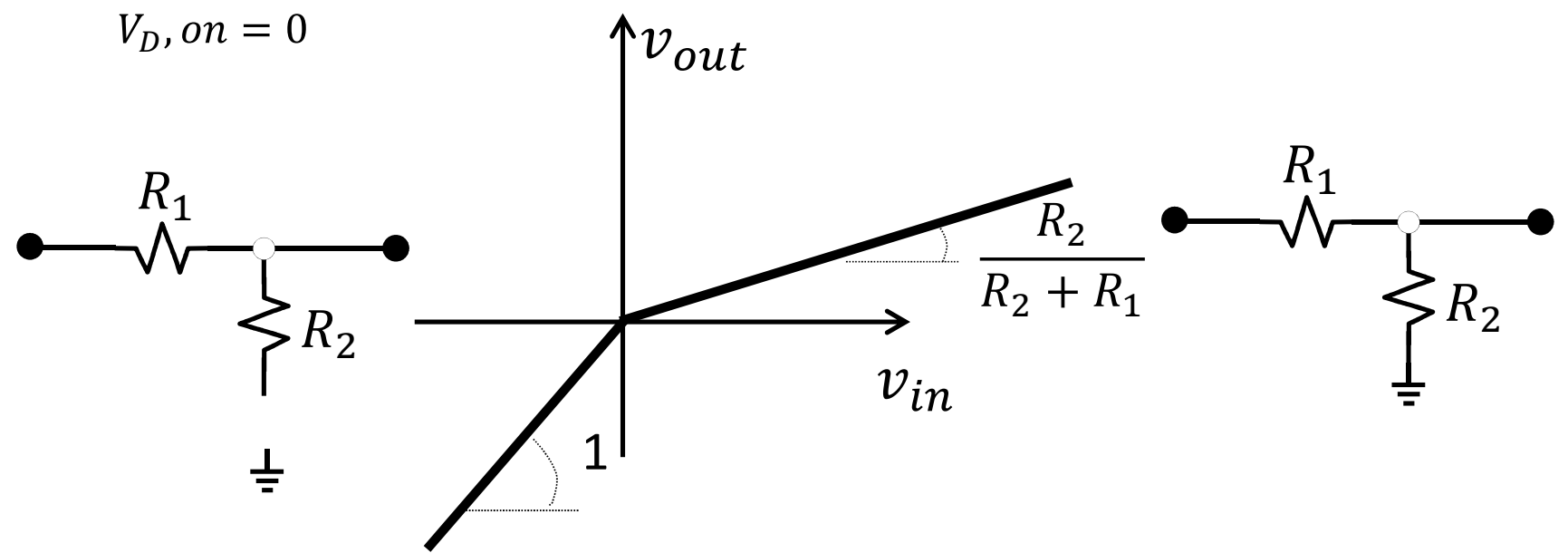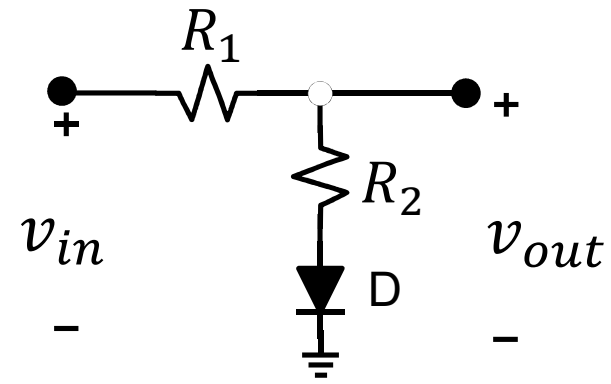


$V_{D, on} = 0.7V$

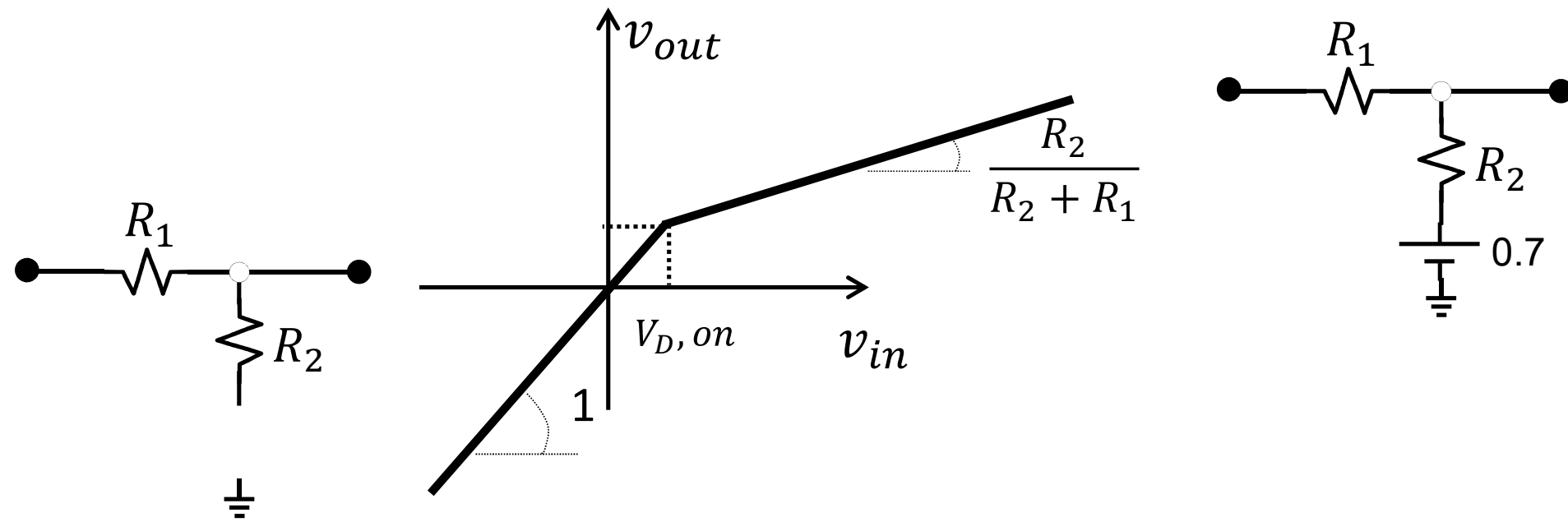

Example 04

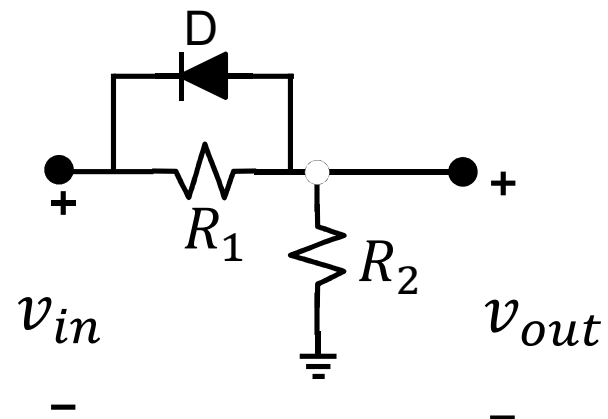



$$V_{D,on} = 0.7V$$

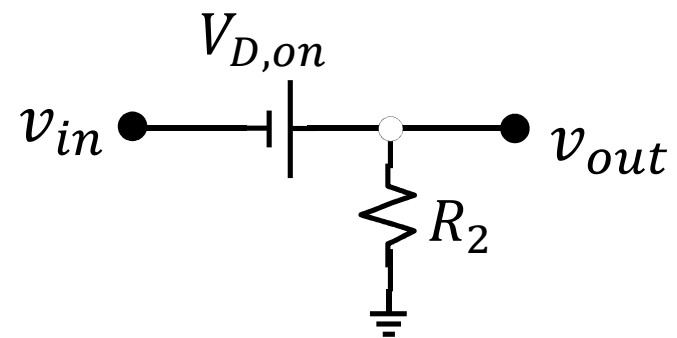


$$v_{out} = v_{in} + V_{D,on}$$

$$I_D = \frac{v_{out}}{R_2} + \frac{V_{D,on}}{R_1} > 0$$

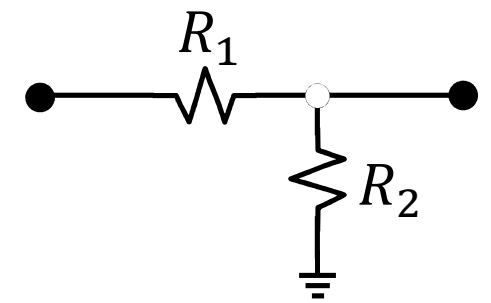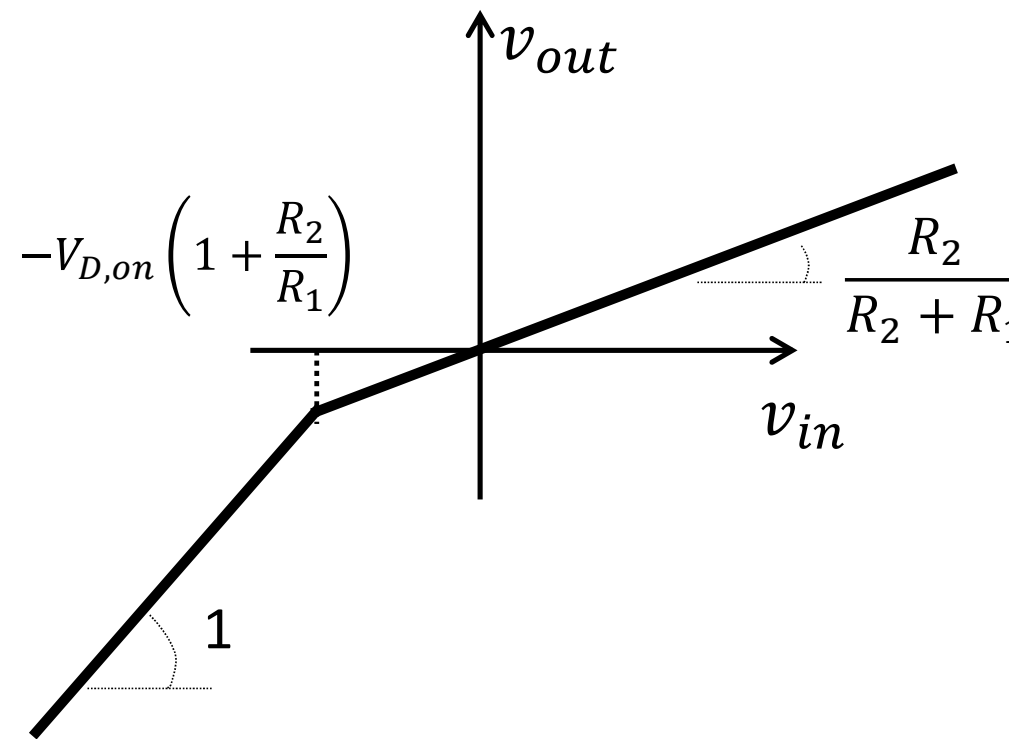
$$v_{in} < -V_{D,on} \left(1 + \frac{R_2}{R_1} \right)$$



Voltage Limiter

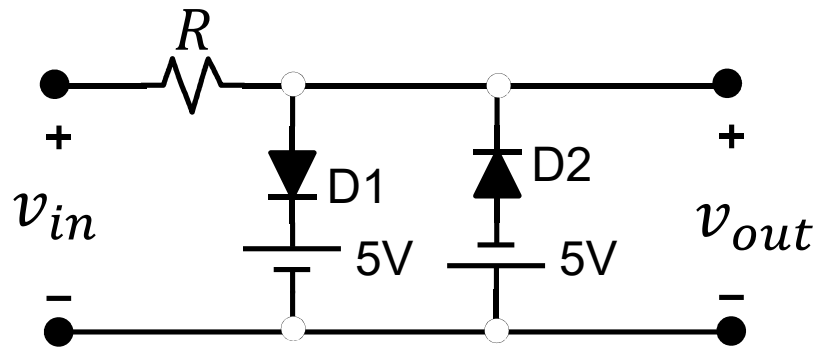


1 : D1:OFF , D2:OFF

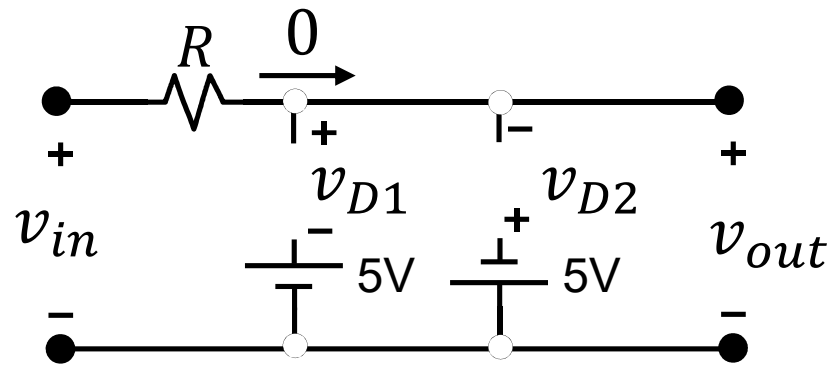


$$v_{out} = v_{in}$$

$$v_{D1} < 0 \rightarrow v_{out} - 5 < 0 \rightarrow v_{out} < 5$$

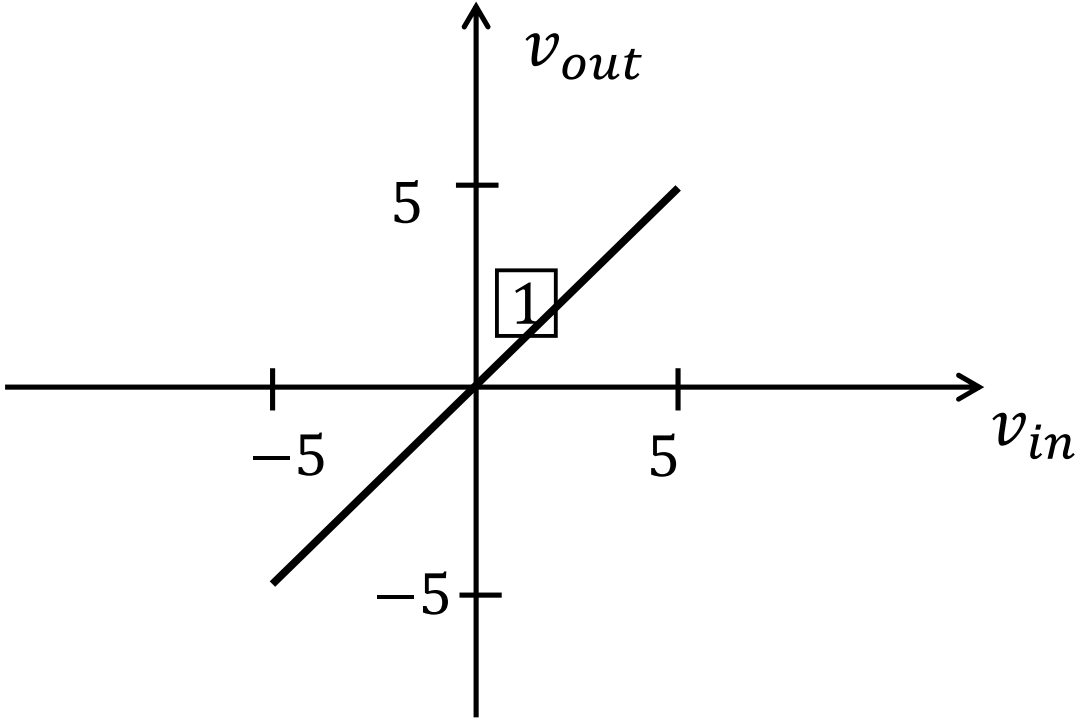
$$v_{D2} < 0 \rightarrow -v_{out} - 5 < 0 \rightarrow v_{out} > -5$$



Voltage Limiter

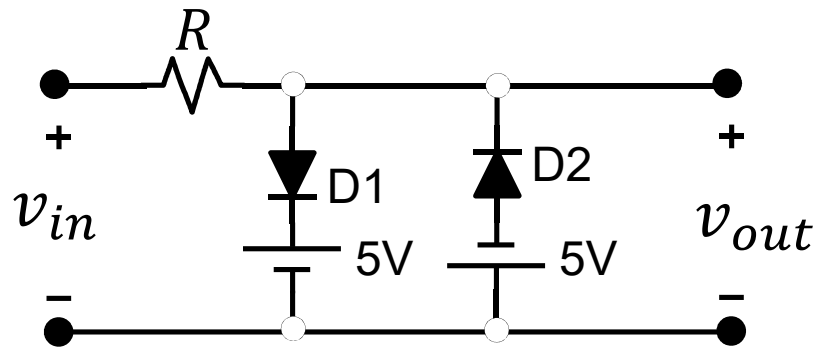


2 : D1:ON , D2:OFF

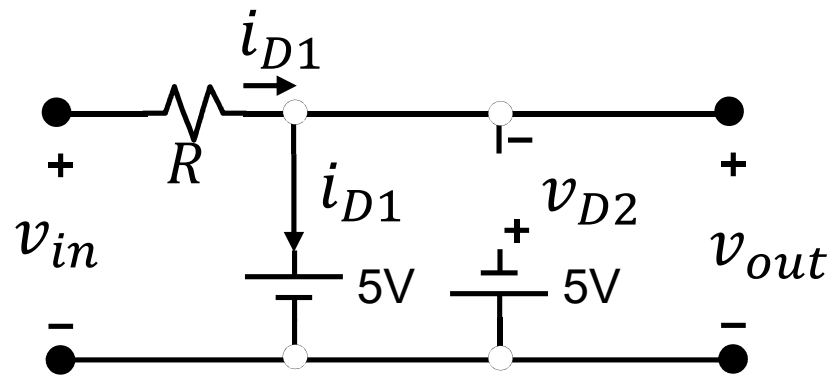


$$v_{out} = 5V$$

$$v_{D2} = -5 - v_{out} = -10 < 0 \quad \checkmark$$

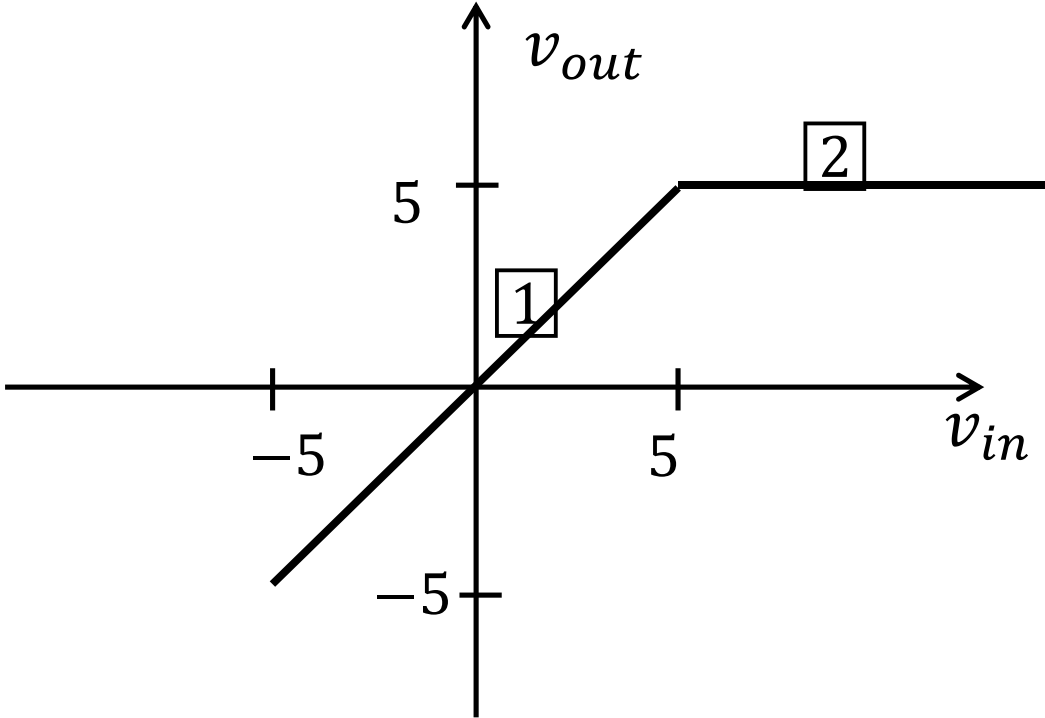
$$i_{D1} = \frac{v_{in} - 5}{R} > 0 \rightarrow v_{in} > 5$$



Voltage Limiter

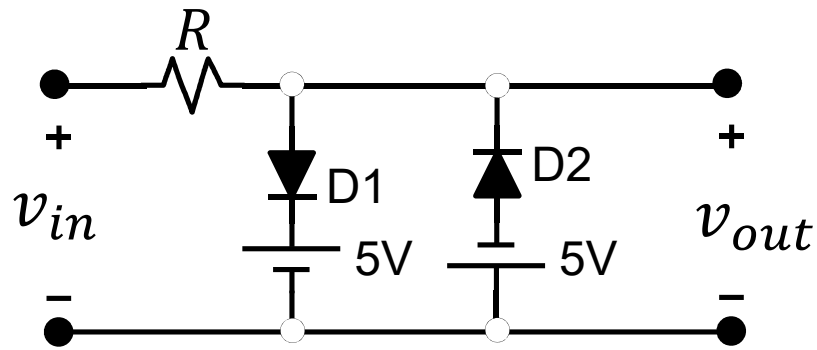


3 : D1:OFF , D2:ON

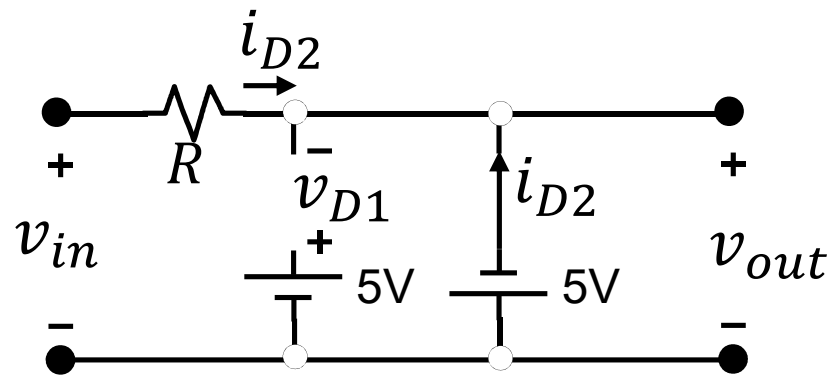



$$v_{out} = -5V$$

$$v_{D1} = v_{out} - 5 = -10 < 0 \quad \checkmark$$
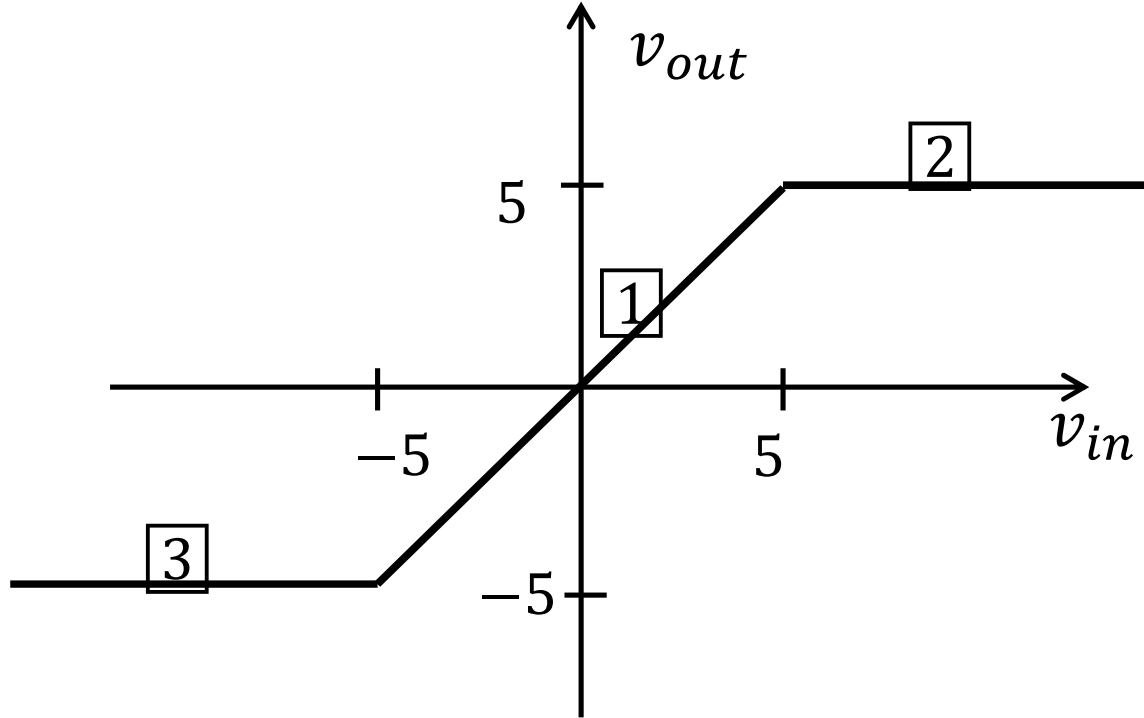
$$i_{D2} = \frac{-v_{in} - 5}{R} > 0 \rightarrow v_{in} < -5$$



Voltage Limiter

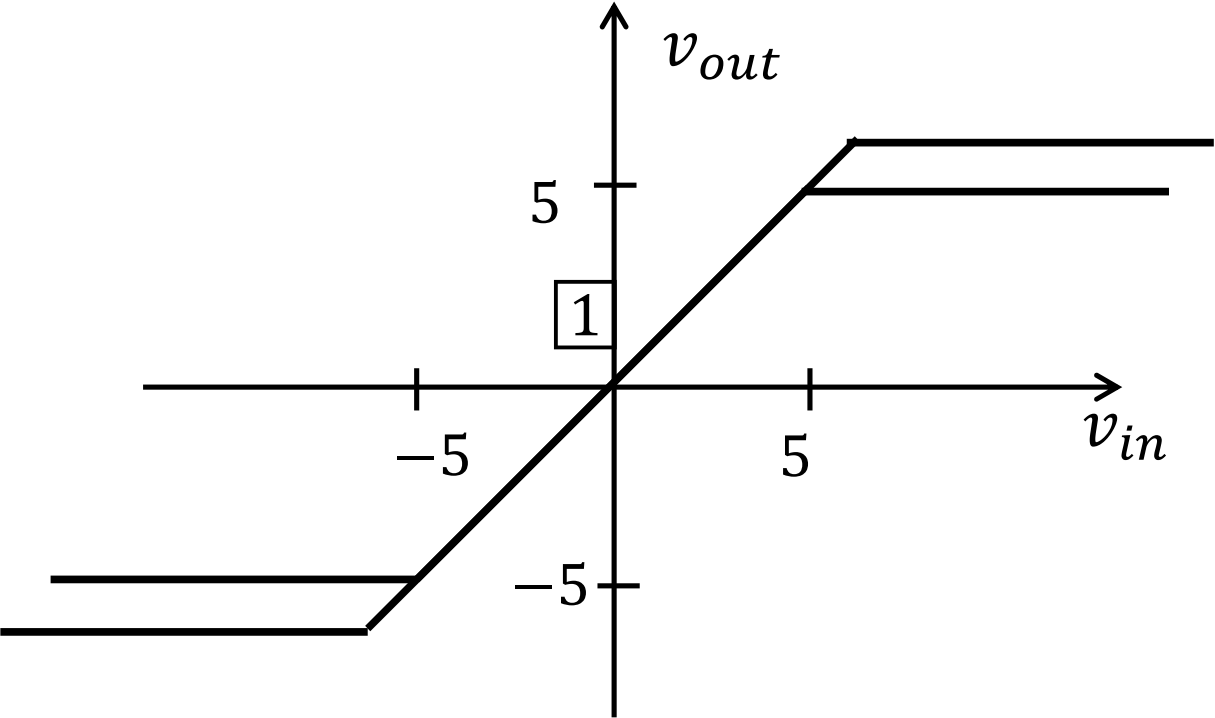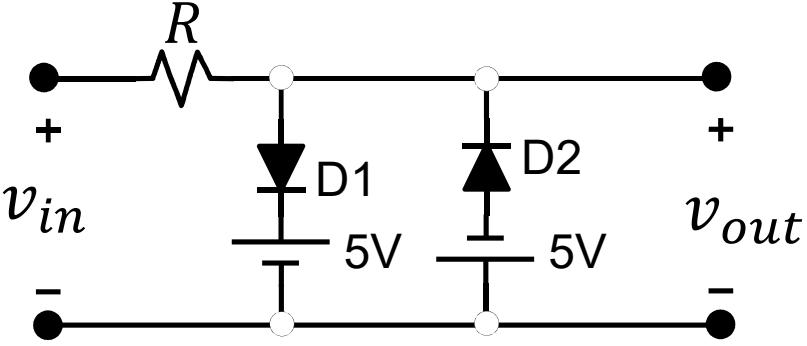

end

