

$$3 = 1^k I_c + 0.7 + 237.5^k \frac{I_c}{50}$$


$$I_c = \frac{2.3}{1^k + \frac{237.5^k}{50}} = 0.4 \text{ mA}$$

max Swing = 0.9V

$$\begin{aligned} g_m &= 16 \text{ mS} \\ r_{\pi} &= 62.5 \\ r_{re} &= 3.12^k \\ r_o &= 125^k \end{aligned}$$


$$R_{in} = 237.5^k \parallel 3.12^k = 3.1^k$$


$$R_{out} = 3.7^k$$

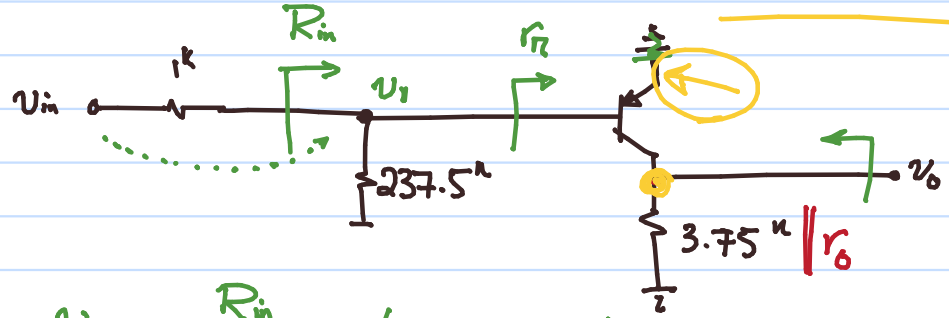



$$\frac{v_o}{v_{in}} = \frac{R_{in}}{R_{in} + 1^k} \times \left( -g_m \underbrace{(3.75^k \parallel r_o)}_{3.7^k} \right) = -45.3$$

0.75

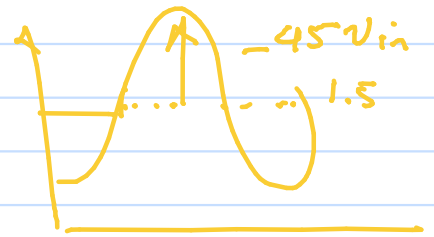

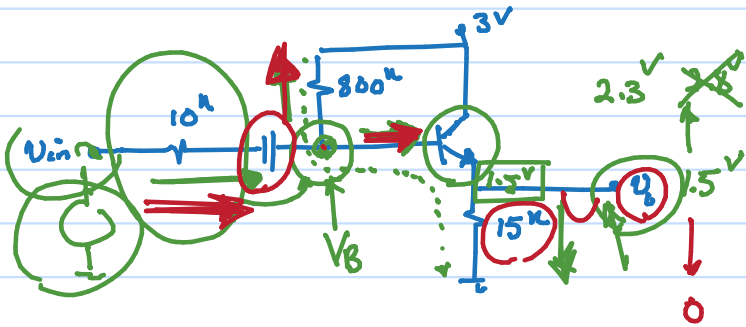


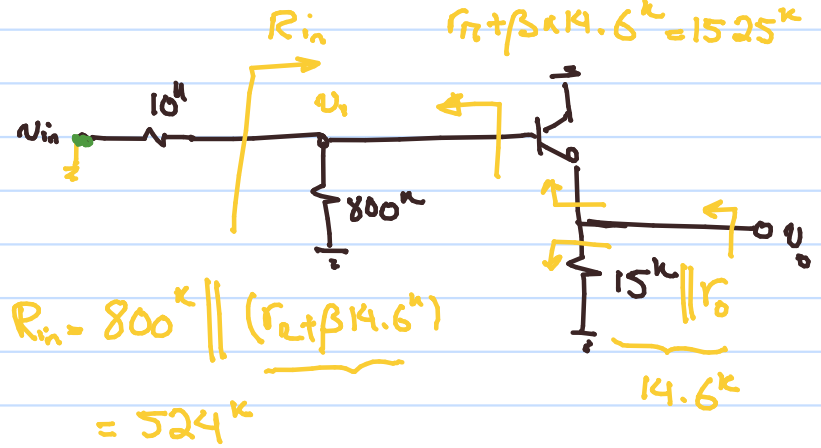
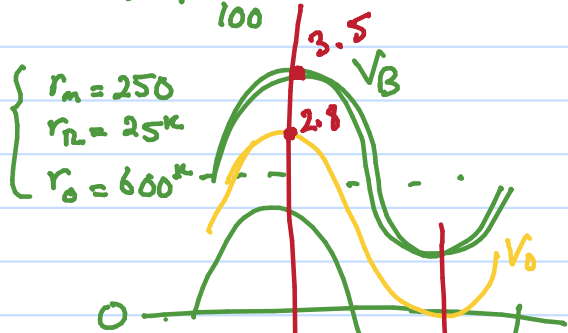
$$I_C = \frac{2.3}{15k + \frac{800k}{100}} = 0.1 \text{ mA}$$




$$\frac{V_o}{V_{in}} = \frac{R_{in}}{R_{in} + 10k} \cdot \frac{14.6k}{14.6k + r_m} = 0.98$$
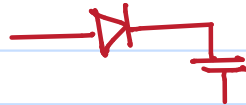
$$R_{out} = 14.6k \parallel \frac{r_o + r_{\pi}}{\beta} = 348 \Omega \quad (R_B = 10k \parallel 800k)$$




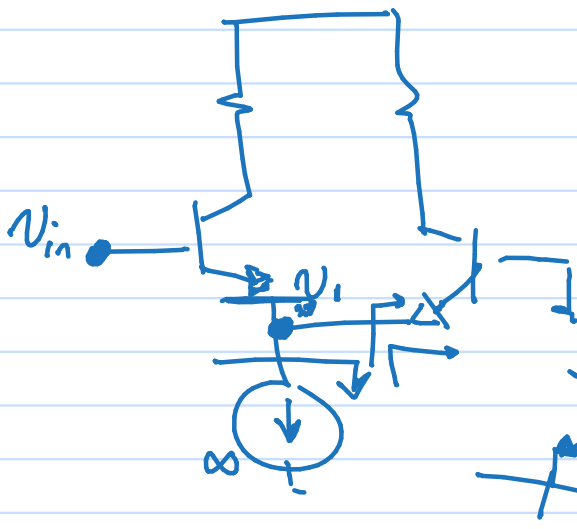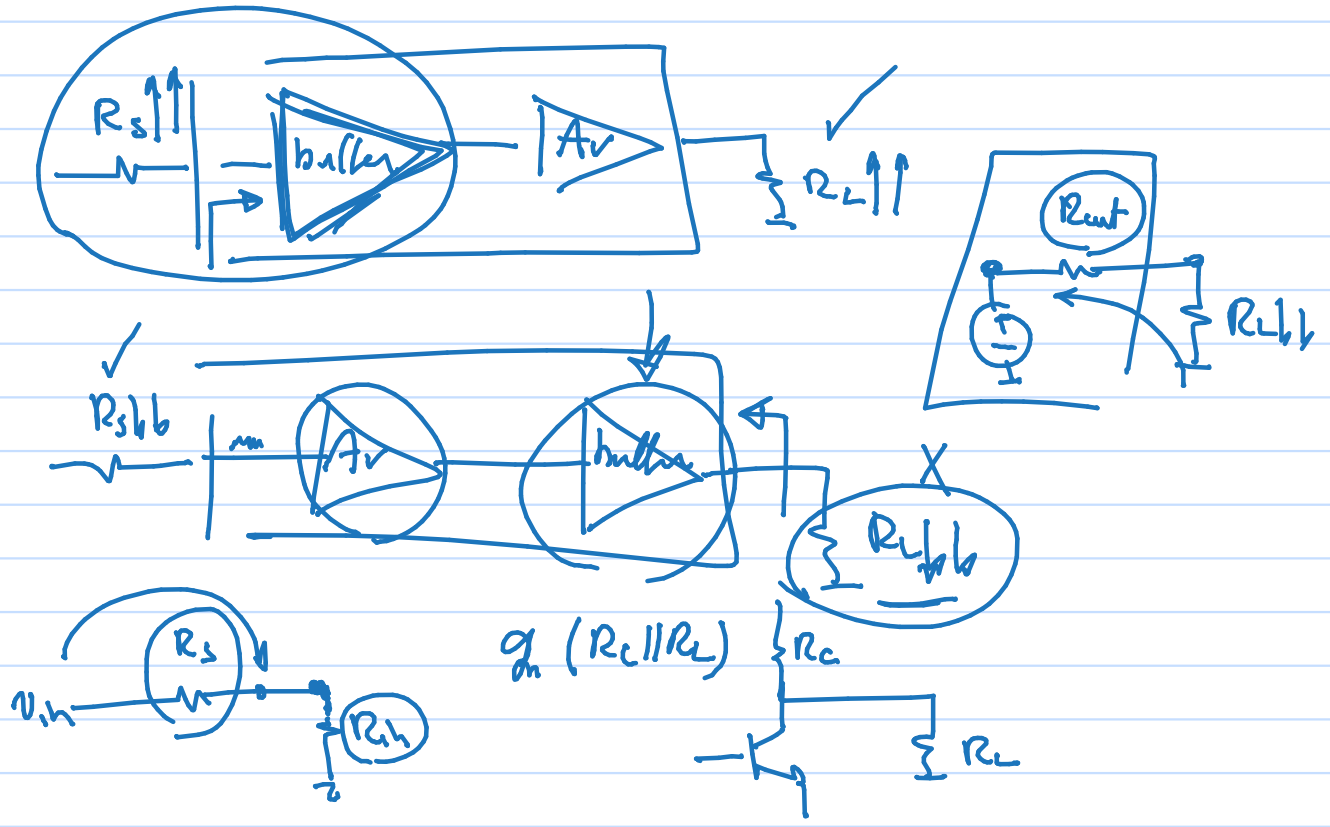

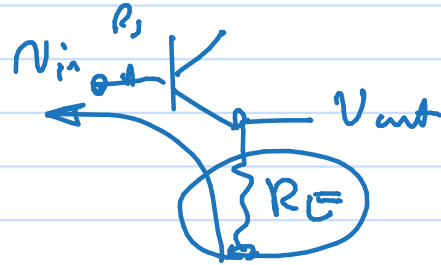
$$\frac{V_i}{V_{in}} = \frac{R_E}{R_E + r_m} = \frac{r_m}{r_m + R_E} = \frac{1}{2}$$



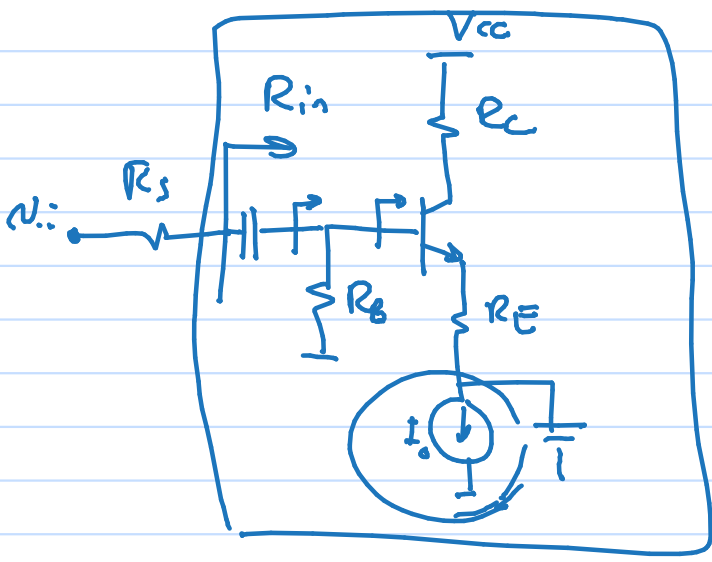
$$A_v = \frac{R_c}{R_E + \frac{r_m + R_s}{\beta}}$$




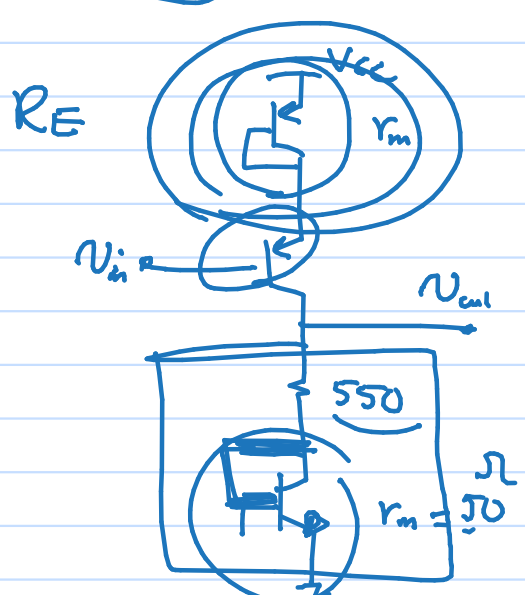
$\checkmark R_s$   
 $\checkmark V_{CC}$   
 $\checkmark R_c$



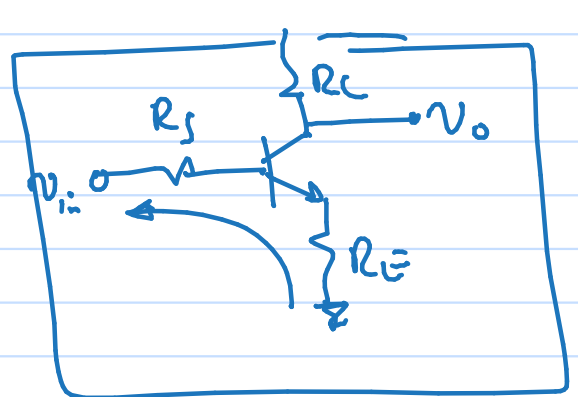
$$\frac{-R_c}{R_E + \frac{r_m}{\beta}} = \frac{-600}{50 + 50} = -6$$



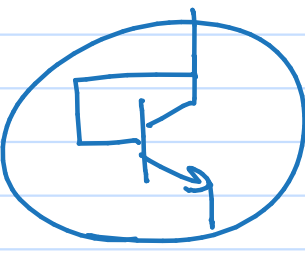
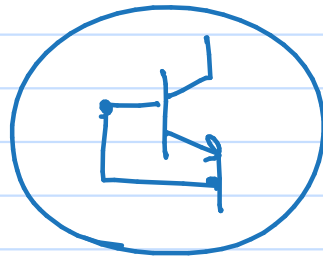
$$\frac{V_o}{V_{in}} = \frac{-R_c}{R_E + \frac{R_s + r_m}{\beta}}$$



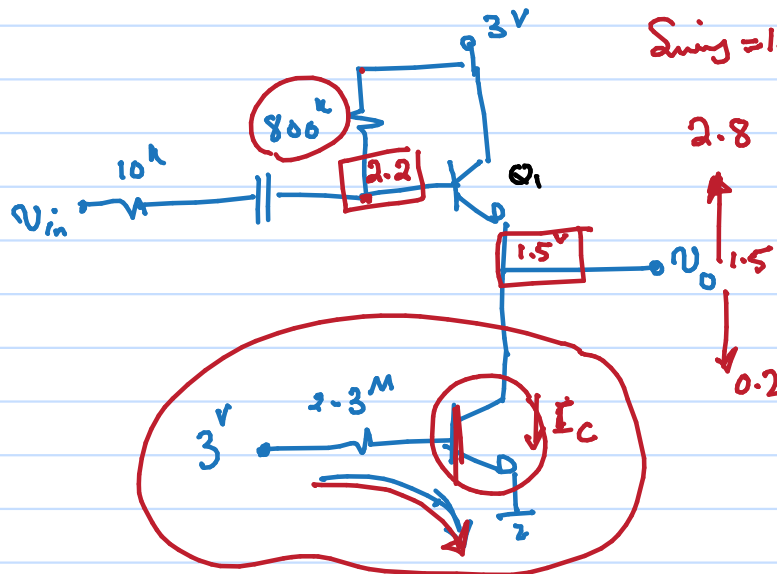

$$I_C = \frac{2.3}{\frac{2.3M}{100}} = 0.1 \text{ mA}$$





$$S_{\text{wing}} = 1.3 \text{ V}$$

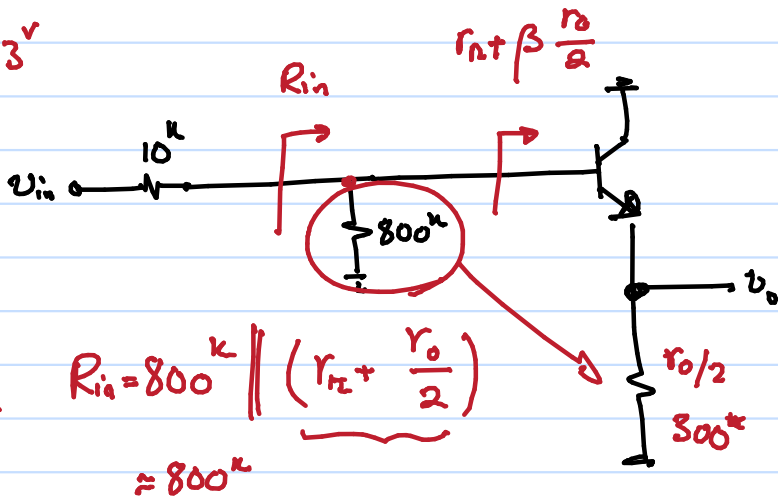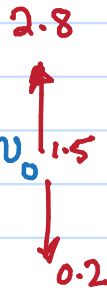

$$R_{in} = 800 \text{ k} \parallel \left( r_{\pi} + \frac{r_o}{2} \right) \approx 800 \text{ k}$$

$$\frac{v_o}{v_{in}} = \frac{R_{in}}{R_{in} + 10 \text{ k}} \times \frac{r_{o/2}}{r_{o/2} + r_m} = 0.99$$
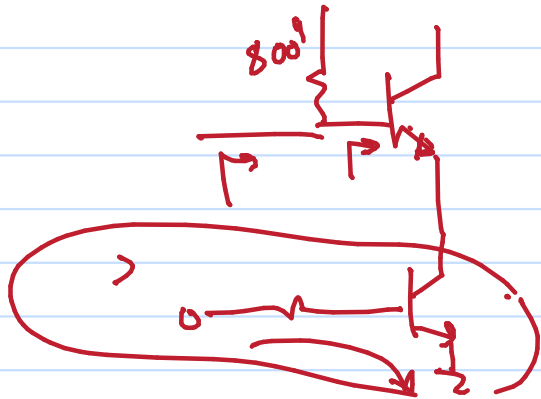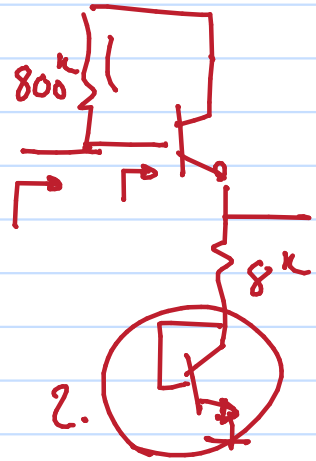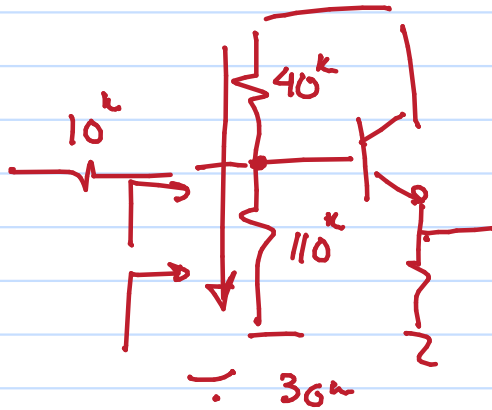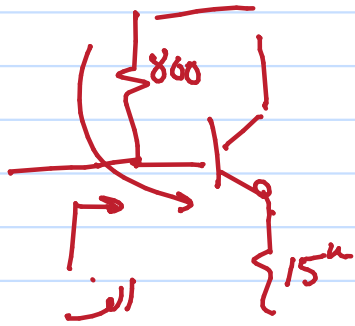
$$R_{out} = 300 \text{ k} \parallel \frac{R_B + r_m}{1} = 348 \Omega$$







مدبران  
(ب)

ببرن  
(ب)




$$r_m = \frac{1}{g_m}$$

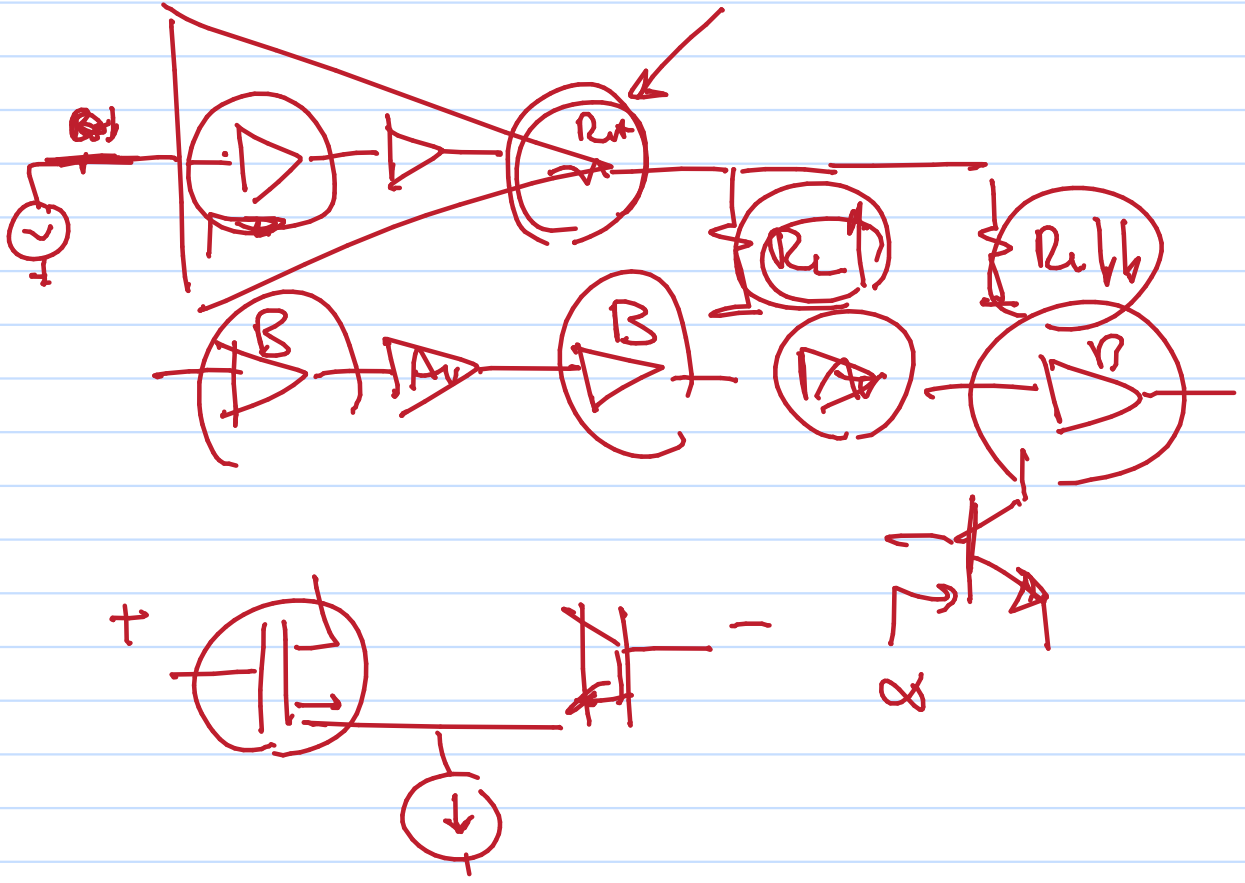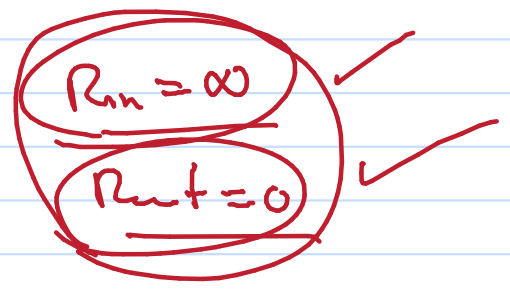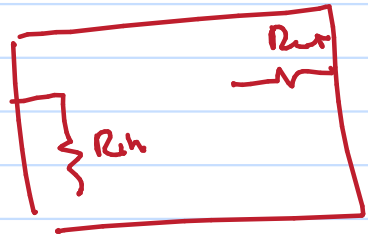

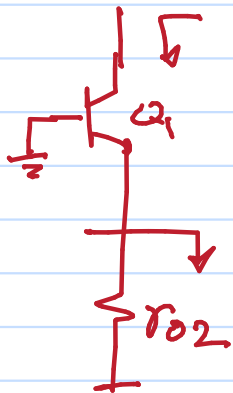
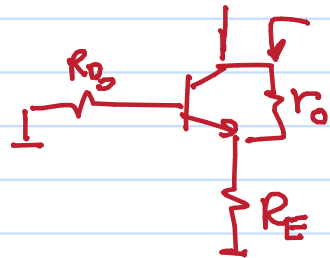
$$r_{o1} \left( 1 + \frac{\beta r_{o2}}{r_{o2} + r_{\pi}} \right) = \beta r_{o1}$$



$$r_{o1} \left( 1 + \frac{\beta R_E}{R_{B1} + R_E + r_{\pi}} \right)$$