


EE100 Fall 2008

Guest Lecture 2: Mesh and Nodal Analysis

Bharathwaj Muthuswamy
NOEL Laboratory
151M Cory Hall
Department of EECS
University of California, Berkeley
mbharat@cory.eecs.berkeley.edu
<http://nonlinear.eecs.berkeley.edu>



Today: (1) Concept of a ground.


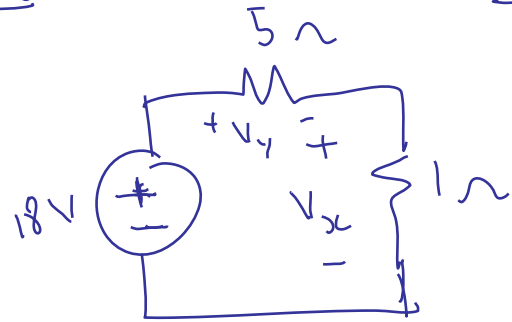


$$V_x = 3V =$$

$$\boxed{(18V) \frac{1}{(5+1)}} \rightarrow \text{Voltage Divider}$$

$$V_y = 15V = 18 - 3 = (18V) \left(\frac{5}{5+1} \right)$$

Suppose:

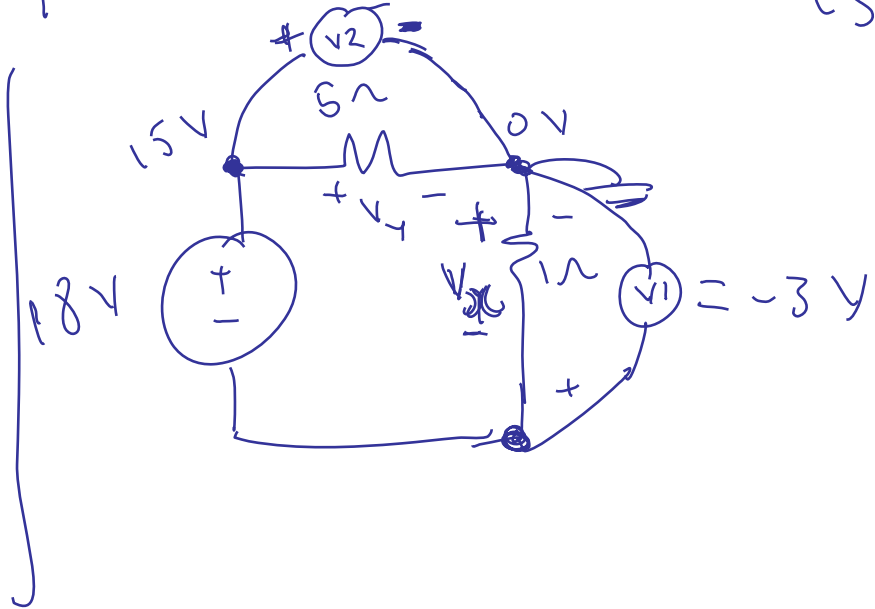
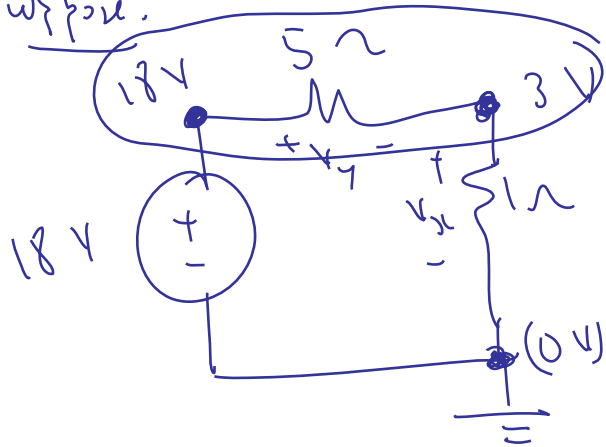


Mesh Analysis: ("Dual" of nodal analysis) [Read: sections 4.5-4.7 in your book]

Pr. 4.2 on p. 107 as Find the power delivered by the 80V

source to the circuit shown.

Need: (Sign convention)

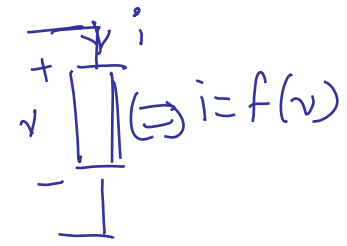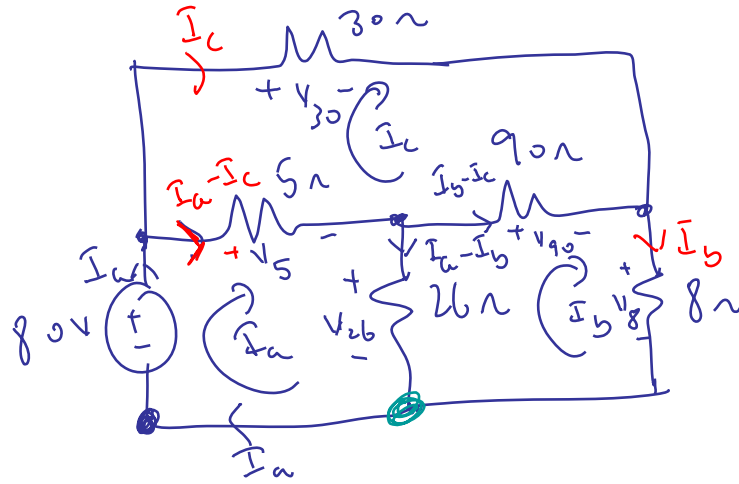

Note: (counterclockwise);
loop I_a : $V_{26} + V_5 - 80 = 0$

$$\Rightarrow + (I_a - I_b)26 + (I_a - I_c)5 - 80 = 0$$

KVL around loop I_a :

$$80 - V_5 - V_{26} = 0 \quad \checkmark \Rightarrow 80 - V_5 - V_{26} = 0$$

$$-80 + V_5 + V_{26} = 0 \Rightarrow \boxed{80 - (I_a - I_c)5 - (I_a - I_b)26 = 0} \quad (1)$$

KVL around loop I_b : $26(I_a - I_b) - 90(I_b - I_c) - 8I_b = 0 \quad (2)$

KVL around loop I_c : $90(I_b - I_c) + 5(I_a - I_c) - 30I_c = 0 \quad (3)$



I_n matrix form:

$$\begin{bmatrix} 31 & -26 & -5 \\ 26 & -124 & 90 \\ 5 & 90 & -125 \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 80 \\ 0 \\ 0 \end{bmatrix}$$



$$\Rightarrow \begin{aligned} I_a &= 5 \text{ A} \\ I_b &= 2.5 \text{ A} \\ I_c &= 2 \text{ A} \end{aligned}$$


$$P_{\text{associated}} = -(80)(5) = -400 \text{ W}$$

$$P_{\text{delivered}} = 400 \text{ W}$$



p4.17 (p.140) (a) Find v_o in the circuit below using nodal analysis.

analysis:

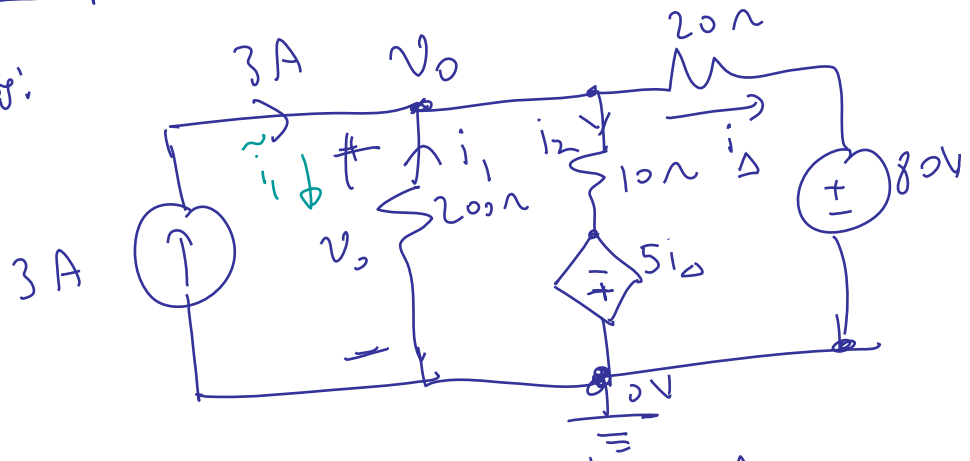

Nodal: ① Pick a ground node

② Figure out the number of unknown essential nodes. $\left[\begin{array}{l} \text{only one:} \\ v_o \end{array} \right]$

③ KCL @ v_o : $\sum i_{in} = \sum i_{out}$
 $\Rightarrow 3 + i_1 = i_2 + i_\Delta$

$\sum i_{in} = \sum i_{out}$
 $\Rightarrow 3 = i_1 + i_2 + i_\Delta$

$\left. \begin{array}{l} + \\ v_o \\ 20\Omega \\ i_1 \\ = \\ \frac{v_o}{20\Omega} \end{array} \right\}$


④ Replace unknown currents in KCL eqn. with node voltages

$i_1: \frac{v_o}{20\Omega} \Leftrightarrow i_1 = \frac{-v_o}{20\Omega}$



p4.17 (p.140) (a) Find v_o in the circuit below using nodal analysis.

analysis:

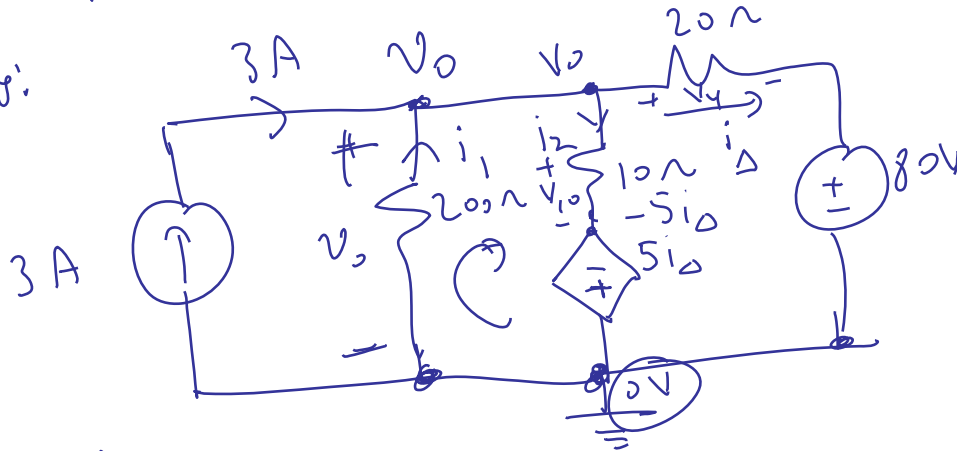


$$v_o \uparrow i_1 \left(\begin{array}{c} + \\ - \end{array} \right) \begin{array}{c} \uparrow \\ \downarrow \end{array} \Leftrightarrow i_1 = \frac{-v_o}{200}$$

Recall: KCL eqn:

$$3 + i_1 = i_2 + i_\Delta \quad (1)$$

$$i_1 = \frac{-v_o}{200}$$

$$i_2 = \frac{v_{10}}{10}$$

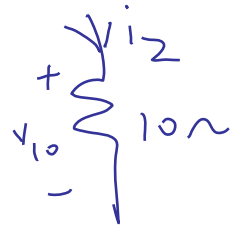

KVL: $v_o - v_{10} + 5i_\Delta = 0$

$$\Rightarrow v_{10} = v_o + 5i_\Delta$$


$$\therefore i_2 = \frac{v_o + 5i_\Delta}{10}$$

$$i. (1) \Rightarrow 3 + \left(\frac{-v_o}{200} \right) = \frac{v_o + 5i_\Delta}{10} + i_\Delta, \quad i_\Delta = \frac{v_o - 80}{20}$$

(substit eqn.)



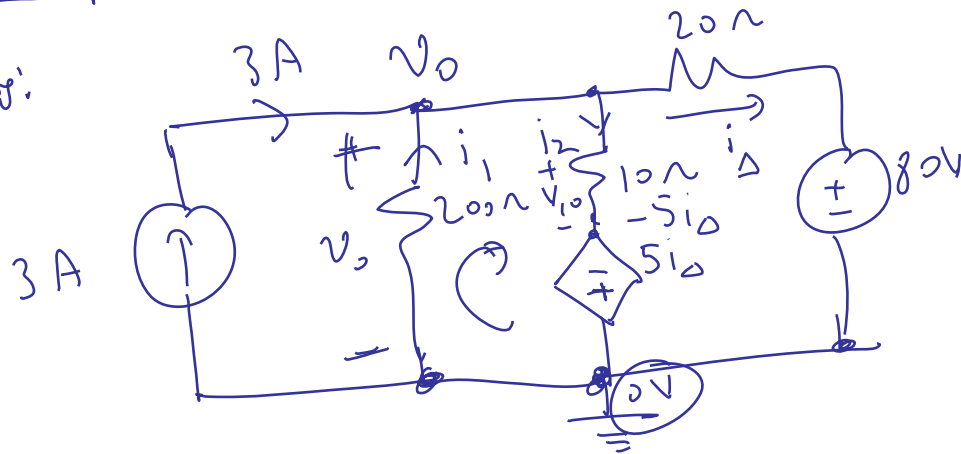p4.17 (p.140) (a) Find v_o in the circuit below using nodal analysis.



$$i. \textcircled{1} \Rightarrow 3 + \left(\frac{-v_o}{200} \right) = \frac{v_o + 5i_\Delta}{10} + i_\Delta, \quad i_\Delta = \frac{v_o - 80}{20}$$

(substit eqn.)

$$i. \quad 3 - \frac{v_o}{200} = \frac{v_o + 5 \left(\frac{v_o - 80}{20} \right)}{10} + \frac{v_o - 80}{20}$$

$$\Rightarrow \boxed{v_o = 50 \text{ V}}$$

Supernode \Rightarrow cut set!
 \downarrow
 related

